

# BME2301 - Circuit Theory

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN

[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/nakkan>

# LECTURE 1

# Course Outline

## 1. Introduction.

Lumped circuit elements, Levels of abstraction, What are the circuits?, Course objectives.

## 2. Basic Concepts.

Units, Charge, Current, Voltage, Power, Conservation of Energy, Circuit Elements, Networks vs. Circuits, Ohm's Law, .

## 3. Voltage and Current Laws.

Circuit Terminology, Kirchhoff's Current Law, Kirchhoff's Voltage Law, The Single-Loop Circuit, Conservation of Energy, The Single-Node-Pair Circuit, Series Circuits, Parallel Circuits, Voltage Division, Current Division.

## 4. Nodal and Mesh Analysis.

Nodal (or "Node-Voltage") Analysis, Nodal Analysis with Supernodes, Mesh (Current) Analysis, Mesh Analysis with Supermeshes, Equivalent Practical Sources.

## 5. Linearity & Superposition.

Linearity, Superposition, Superposition: Voltage Sources, Superposition: Current Sources, Practical Voltage Sources, Practical Current Sources.

## 6. Thevenin & Norton Equivalents.

Thevenin Equivalent, Power from a Practical Source, Maximum Power Transfer .

## 7. The Operational Amplifier.

The Operational Amplifier, Inverting Amplifier, Noninverting Amplifier, Voltage Follower, Summing Amplifier, Difference Amplifier, Op-Amp Cascades, Op-Amp Parameters, Common Mode Rejection, Saturation, An instrumentation amplifier.

# Course Outline

## 8. Capacitors and Inductors.

Capacitance, Capacitor Current & Voltage, Capacitor Characteristics, Inductance, Inductor Current & Voltage, Inductor Characteristics, Inductor Energy Storage, DC Capacitor Circuits, DC Inductor Circuits.

## 9. Basic RL and RC Circuits.

The Source-Free RL Circuit, The Source-Free RC Circuit, Unit-Step Definition, Driven RL Circuit, Driven RC Circuit.

## 10. RLC Circuits.

Parallel RLC Circuit, Series RLC Circuit, RLC Solution: Over-damped, RLC Solution: Critically Damped, RLC Solution: Under-damped, The Complete Response Of The RLC Circuit.

## 11. AC Analysis.

Complex numbers, phasors, impedance, admittance, Sinusoidal steady-state; Ohm's Law, KVL, KCL for AC circuits, Sinusoidal steady-state: Thevenin, superposition, examples.

## 12. The Frequency Response.

Frequency response: transfer function, logarithms, Bode plots.

Frequency response: resonance, passive & active filter design

## 13. Laplace Transform.

Laplace: introduction to transforms, inverse transform.

Laplace: theorems, solving differential equations

## 14. s-Domain analysis

s-Domain analysis: transfer functions, poles, zeroes.

s-Domain analysis: nodal, mesh, additional techniques


# Main course book

## Engineering Circuit Analysis

by William Hayt, Jack  
Kemmerly, Steven  
Durbin.

Published by McGraw-Hill.

Isbn: 0073529575

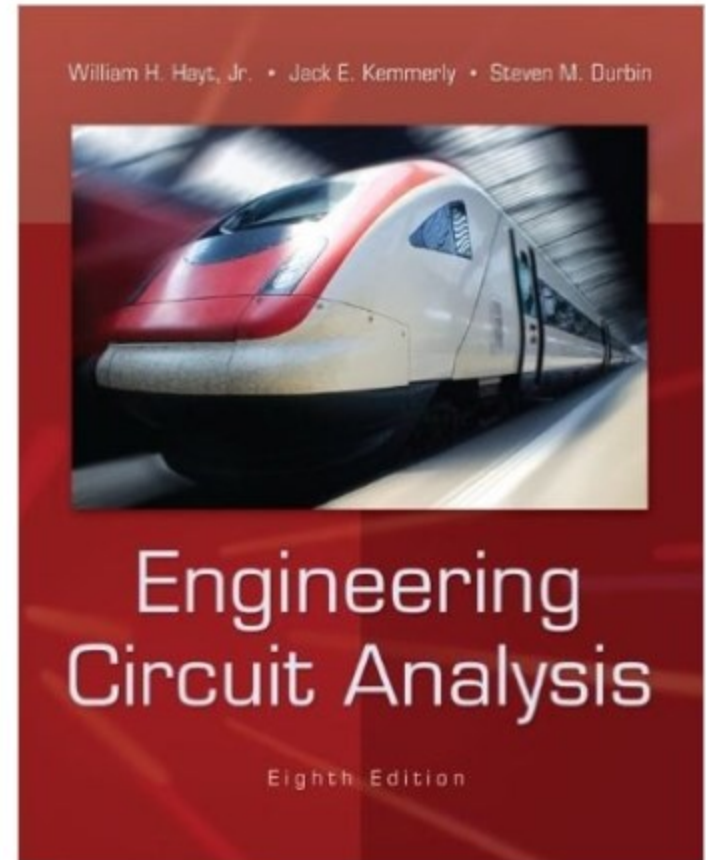

# Rules of the Conduct

- No eating /drinking in class
  - *except water*
- Cell phones must be kept outside of class or switched-off during class
  - *If your cell-phone rings during class or you use it in any way, you will be asked to leave and counted as unexcused absent.*
- No web surfing and/or unrelated use of computers,
  - *when computers are used in class or lab.*

# Rules of the Conduct

- You are responsible for checking the class web page often for announcements.
- Academic dishonesty and cheating will not be tolerated and will be dealt with according to university rules and regulations
  - *Presenting any work, or a portion thereof, that does not belong to you is considered academic dishonesty.*
- University rules and regulations:
  - <http://www.ogi.yildiz.edu.tr/category.php?id=17>
  - [https://www.yok.gov.tr/content/view/544/230/lang,tr\\_TR/](https://www.yok.gov.tr/content/view/544/230/lang,tr_TR/)



# Attendance Policy

- The requirement for attendance is **70%**.
  - *Hospital reports are not accepted to fulfill the requirement for attendance.*
  - *The students, who fail to fulfill the attendance requirement, will be excluded from the final exams and the grade of **F0** will be given.*




# Abstraction

- We have electromagnetic phenomena and this data can be expressed by using Maxwell's equations. (Scientific part)
- Electrical engineers create a new abstraction layer on top of Maxwell's equations called the **lumped circuit abstraction**.
- By using this lumped circuit abstraction electrical and computer systems can be designed.
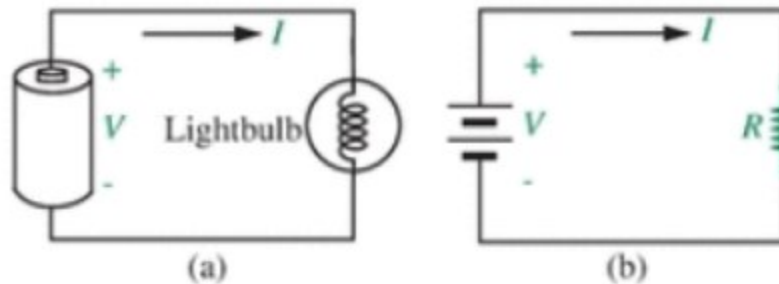
# Lumped circuit element


- A lumped circuit element is often used as an abstract representation or a model of a piece of material with complicated behaviour.



a) A simple light bulb circuit b) The lumped circuit representation


- $R$  is a lumped element abstraction for the bulb.
- A lumped element is described by its  $v$ - $i$  (voltage - current) relation.

# Levels of abstraction

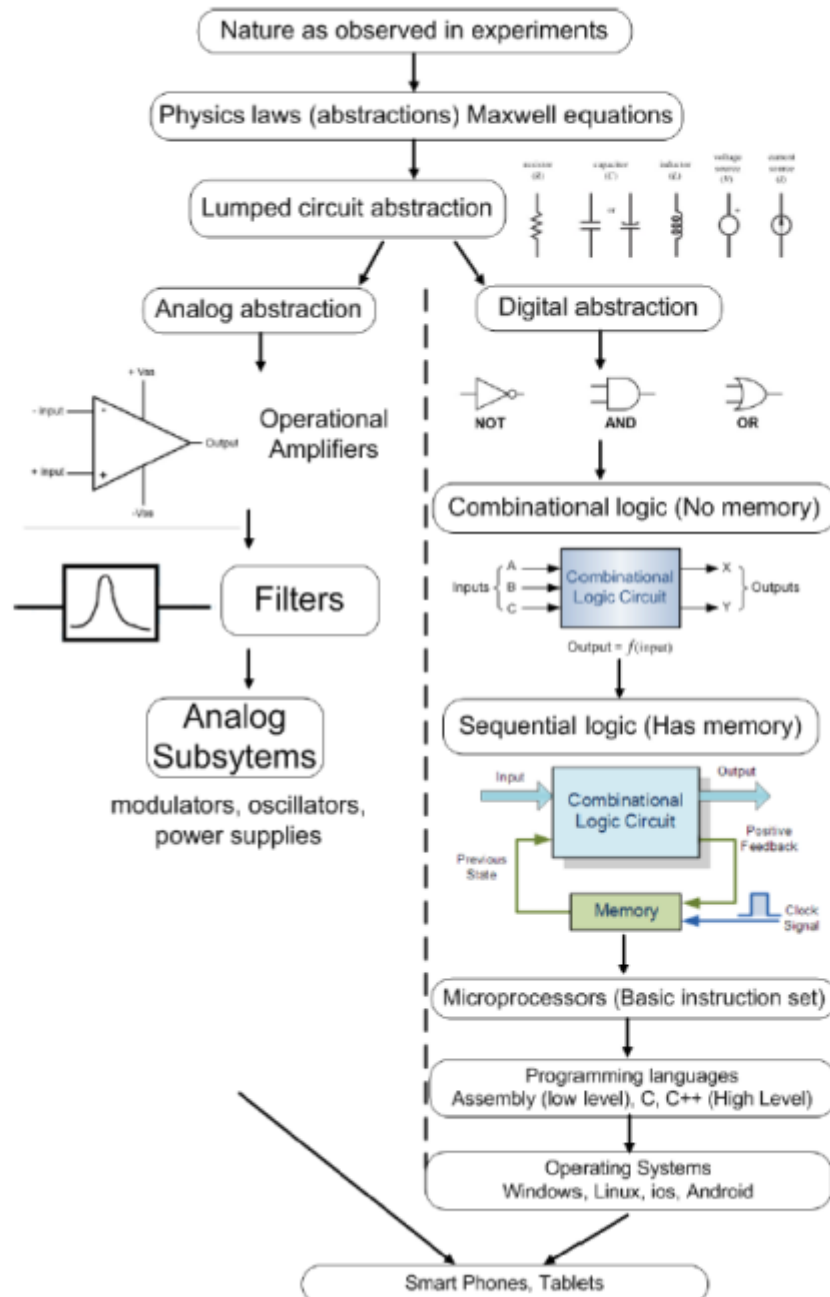

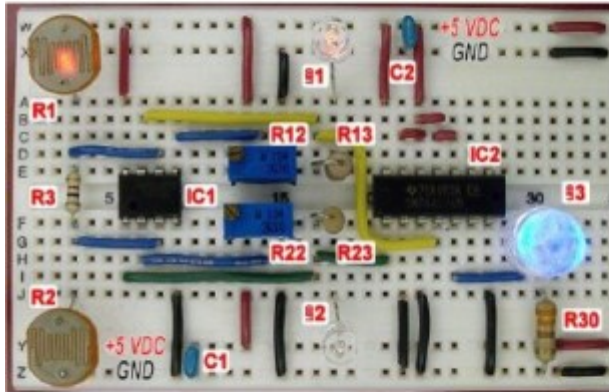
# What are the circuits?


- A *circuit* consists of electrical or electronic components interconnected with metal wires.
- Every electrical or electronic device is a circuit.



Breadboard

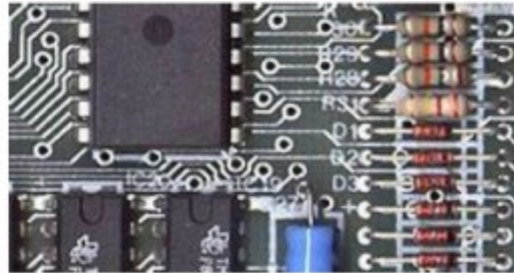

Printed Circuit Boards (PCBs)

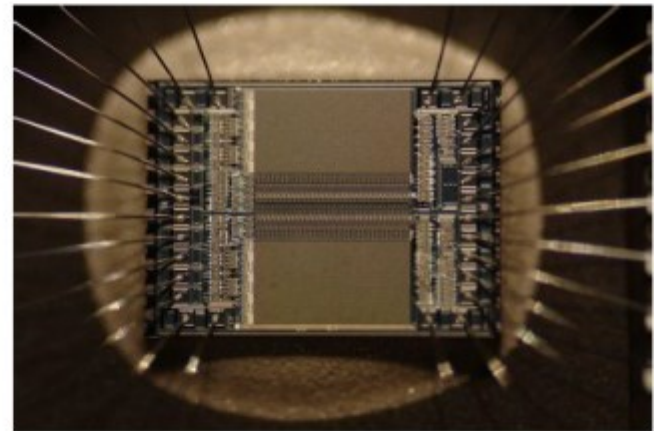

Integrated Circuits (ICs)



# Linear vs. Nonlinear

- Linear problems are inherently more easily solved than their nonlinear counterparts.
- For this reason, we often seek reasonably accurate **linear approximations** (or *models*) to physical situations.
- The linear models are more easily manipulated and understood which makes **analysis** and **design** a more straightforward process.

# Analysis and Design

- ***Analysis*** is the process through which we determine the scope of a problem, obtain the information required to understand it, and compute the parameters of interest.
- ***Design*** is the process by which we synthesize something **new** as part of the solution to a problem.
- A crucial part of design is analysis of potential solutions!

# Units of Measurement

- As engineers, we deal with measurable quantities.
- Measurement must be communicated in a standard language.
- The International System of Units (SI),
  - adopted by the General Conference on Weights and Measures in 1960.
- In SI, there are seven principal units from which the units of all other physical quantities can be derived.



# Units of Measurement

- Six basic SI units and one derived unit relevant to this text.

| Quantity                  | Basic unit | Symbol |
|---------------------------|------------|--------|
| Length                    | meter      | m      |
| Mass                      | kilogram   | kg     |
| Time                      | second     | s      |
| Electric current          | ampere     | A      |
| Thermodynamic temperature | kelvin     | K      |
| Luminous intensity        | candela    | cd     |
| Charge                    | coulomb    | C      |

# Units of Measurement

- One great advantage of the SI unit is that it uses prefixes based on the power of 10 to relate larger and smaller units to the basic unit.
- For example, the following are expressions of the same distance in meters (m):
  - 600 000 000 mm
  - 600 000 m
  - 600 km

The SI prefixes.

| Multiplier | Prefix | Symbol |
|------------|--------|--------|
| $10^{18}$  | exa    | E      |
| $10^{15}$  | peta   | P      |
| $10^{12}$  | tera   | T      |
| $10^9$     | giga   | G      |
| $10^6$     | mega   | M      |
| $10^3$     | kilo   | k      |
| $10^2$     | hecto  | h      |
| 10         | deka   | da     |
| $10^{-1}$  | deci   | d      |
| $10^{-2}$  | centi  | c      |
| $10^{-3}$  | milli  | m      |
| $10^{-6}$  | micro  | $\mu$  |
| $10^{-9}$  | nano   | n      |
| $10^{-12}$ | pico   | p      |
| $10^{-15}$ | femto  | f      |
| $10^{-18}$ | atto   | a      |

# Units of Measurement

- The numerical value substituted into an equation must have the unit of measurement specified by the equation.
- For example,
  - consider the equation for the velocity  $v = d / t$ .
    - $v$ : velocity,  $d$ : distance,  $t$ : time
  - Assume that the following data are obtained for a moving object:  $d = 4000$  m,  $t = 1$  min and  $v$  is desired in km per hour.
  - Incorrect answer:
    - $v = 4000 / 1 = 4000$  kmh
  - Correct answer:
    - $v = 4000 \times 10^{-3} / (1/60) = 240$  kmh

# Units of Measurement

- Before substituting numerical values into an equation, be absolutely sure of the following:
  - Each quantity has the proper unit of measurement as defined by the equation.
  - The proper magnitude of each quantity as determined by the defining equation is substituted.
  - Each quantity is in the same system of units (or as defined by the equation).
  - The magnitude of the result is of a reasonable nature when compared to the level of the substituted quantities.
  - The proper unit of measurement is applied to the result.


# Systems of Units

- Comparison of the English and metric systems of units.

| English   | Metric  |   | SI   |
|---|---|---|--|
|   | MKS   | CGS   |  |
| <i>Length:</i><br>Yard (yd)<br>(0.914 m)  | Meter (m)<br>(39.37 in.)<br>(100 cm)  | Centimeter (cm)<br>(2.54 cm = 1 in.)              | <b>Meter (m)</b>                                     |
| <i>Mass:</i><br><b>Slug</b><br>(14.6 kg)  | Kilogram (kg)<br>(1000 g)   | Gram (g)  | <b>Kilogram (kg)</b>                                 |
| <i>Force:</i><br><b>Pound (lb)</b><br>(4.45 N)  | Newton (N)<br>(100,000 dynes)   | Dyne  | <b>Newton (N)</b>                                    |
| <i>Temperature:</i><br>Fahrenheit (°F)<br>$\left( = \frac{9}{5}^{\circ}\text{C} + 32 \right)$ | Celsius or<br>Centigrade (°C)<br>$\left( = \frac{5}{9} (^{\circ}\text{F} - 32) \right)$ | Centigrade (°C)                                   | <b>Kelvin (K)</b><br>$K = 273.15 + ^{\circ}\text{C}$ |
| <i>Energy:</i><br>Foot-pound (ft-lb)<br>(1.356 joules)  | Newton-meter (N•m)<br>or joule (J)<br>(0.7376 ft-lb)                                    | Dyne-centimeter or erg<br>(1 joule = $10^7$ ergs) | <b>Joule (J)</b>                                     |
| <i>Time:</i><br>Second (s)  | Second (s)  | Second (s)  | <b>Second (s)</b>                                    |


# Comparison of units of the various systems of units

## Length:

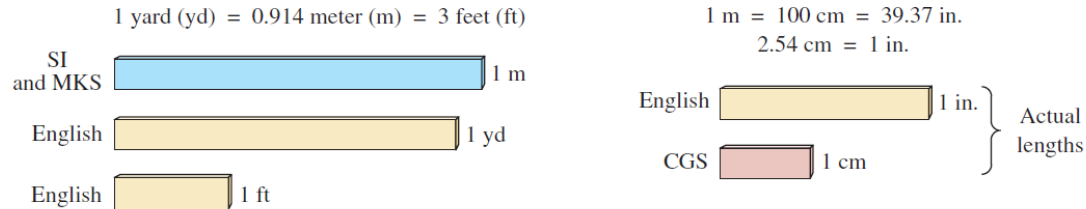


## Mass:


1 slug = 14.6 kilograms

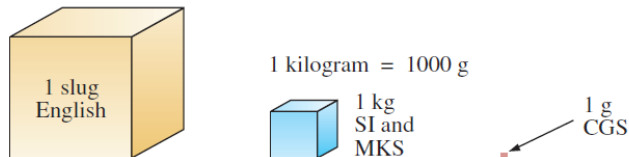


## Force:

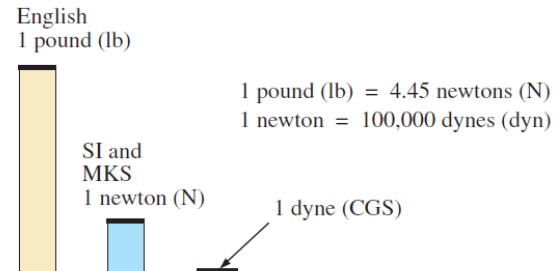

## Temperature:

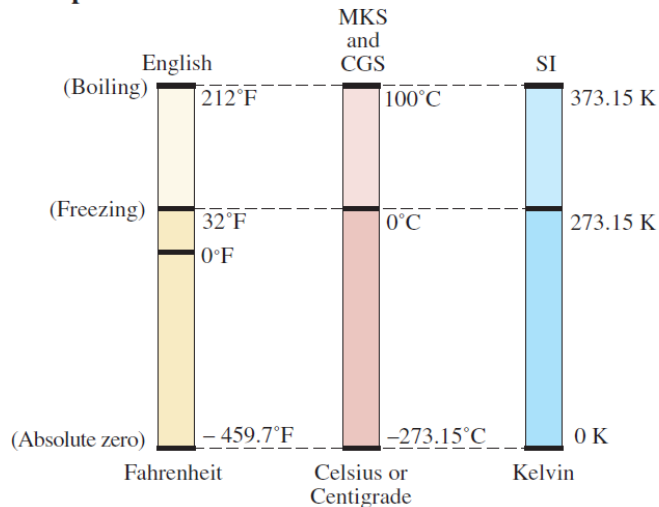

## Energy:

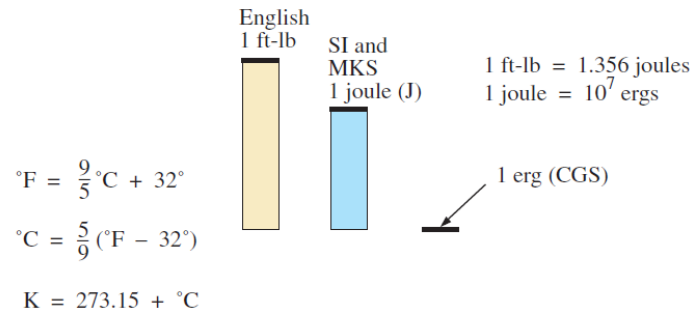

# Standards of some units

- The **meter** is defined with reference to the speed of light in a vacuum, which is **299792458** m/s.
  - It was originally defined in 1790 to be 1/**10000000** the distance between the equator and either pole at sea level, a length preserved on a platinum-iridium bar at the International Bureau of Weights and Measures at Sèvres, France.
- The **kilogram** is defined as a mass equal to 1000 times the mass of one cubic centimeter of pure water at 4°C.
  - This standard is preserved in the form of a platinum-iridium cylinder in Sèvres.



# Standards of some units

- The **second** is redefined in 1967 as 9192631770 periods of the electromagnetic radiation emitted by a particular transition of cesium atom.
  - It was originally defined as 1/86400 of the mean solar day.
  - However, Earth's rotation is slowing down by almost 1 second every 10 years.

# Significant Figures, Accuracy, Round off

- Two types of numbers:
  - Exact
    - For example 12 apples
  - Approximate
    - Any reading obtained in the laboratory should be considered approximate
- The **precision** of a reading can be determined by the number of **significant figures** (**digits**) present.
- **Accuracy** refers to the closeness of a measured value to a standard or known value
- For approximate numbers, there is often a need to **round off** the result
  - that is, you must decide on the appropriate level of accuracy and alter the result accordingly.
    - For example,  $3.186 \cong 3.19 \cong 3.2$

# Powers of ten

- To express very large and very small numbers
- The notation used to represent numbers that are integer powers of ten is as follows:

$$1 = 10^0 \qquad 1/10 = 0.1 = 10^{-1}$$

$$10 = 10^1 \qquad 1/100 = 0.01 = 10^{-2}$$

$$100 = 10^2 \qquad 1/1000 = 0.001 = 10^{-3}$$

$$1000 = 10^3 \qquad 1/10,000 = 0.0001 = 10^{-4}$$

# Powers of ten

- Some important mathematical equations and relationships pertaining to powers of ten:

$$\frac{1}{10^n} = 10^{-n} \quad \frac{1}{10^{-n}} = 10^n$$

$$(10^n)(10^m) = (10)^{(n+m)}$$

$$\frac{10^n}{10^m} = 10^{(n-m)}$$

$$(10^n)^m = 10^{nm}$$

# Powers of ten

- Addition and subtraction

$$A \times 10^n \pm B \times 10^n = (A \pm B) \times 10^n$$

- Multiplication

$$(A \times 10^n)(B \times 10^m) = (A)(B) \times 10^{n+m}$$

- Division

$$\frac{A \times 10^n}{B \times 10^m} = \frac{A}{B} \times 10^{n-m}$$

- Power

$$(A \times 10^n)^m = A^m \times 10^{nm}$$

# Scientific notation vs. Engineering notation

- Scientific notation and engineering notation make use of powers of ten, with restrictions on the mantissa (multiplier) or scale factor (power of ten).
  - Scientific notation requires that the decimal point appear directly after the first digit greater than or equal to 1 but less than 10.
  - Engineering notation specifies that all powers of ten must be multiples of 3, and the mantissa must be greater than or equal to 1 but less than 1000.

# Scientific notation vs. Engineering notation

- Scientific notation example:

$$\frac{1}{3} = 3.333333333333\text{E}-1 \quad \frac{1}{16} = 6.25\text{E}-2 \quad \frac{2300}{2} = 1.15\text{E}3$$

$$\frac{1}{3} = 3.33\text{E}-1 \quad \frac{1}{16} = 6.25\text{E}-2 \quad \frac{2300}{2} = 1.15\text{E}3$$

- Engineering notation example:

$$\frac{1}{3} = 333.3333333333\text{E}-3 \quad \frac{1}{16} = 62.5\text{E}-3 \quad \frac{2300}{2} = 1.15\text{E}3$$


$$\frac{1}{3} = 333.33\text{E}-3 \quad \frac{1}{16} = 62.50\text{E}-3 \quad \frac{2300}{2} = 1.15\text{E}3$$



# Electricity





- Electricity is a result from the flow of electrons.

● = electron

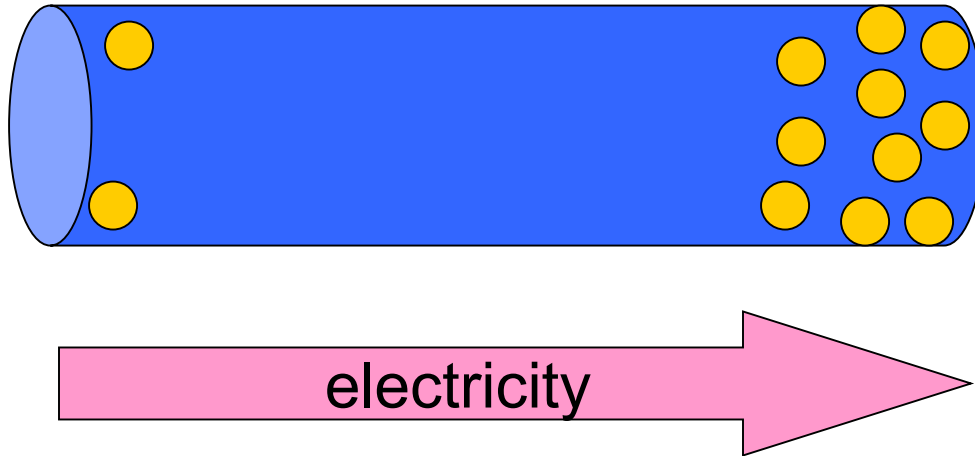

- Electricity flows in the opposite direction of electron flow.

# Electric Current vs. Electron Current

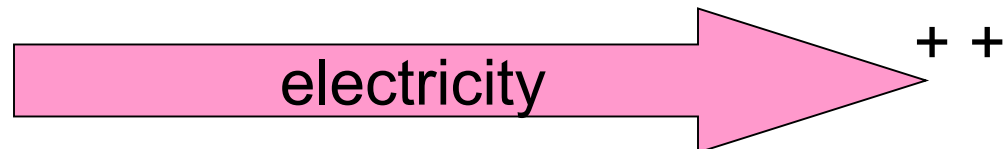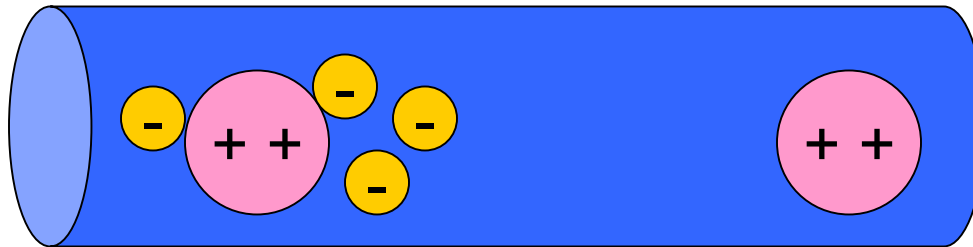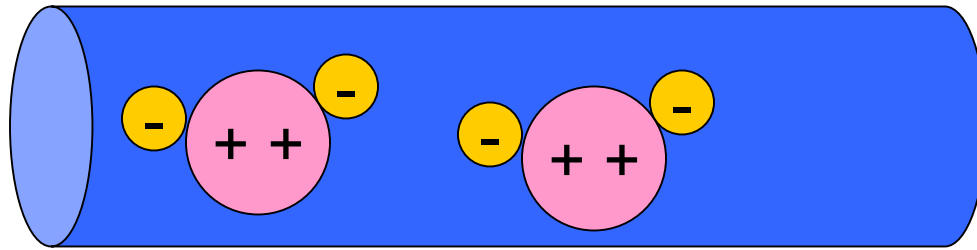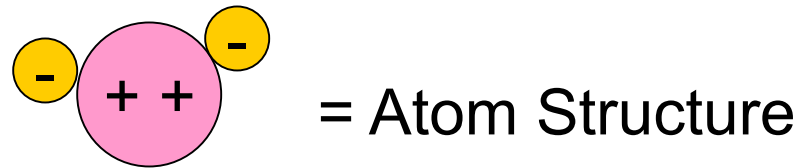

# Electric current



- We cannot see electric current.
- We need a metaphor.
- Which thing has similar property with electricity??



Water

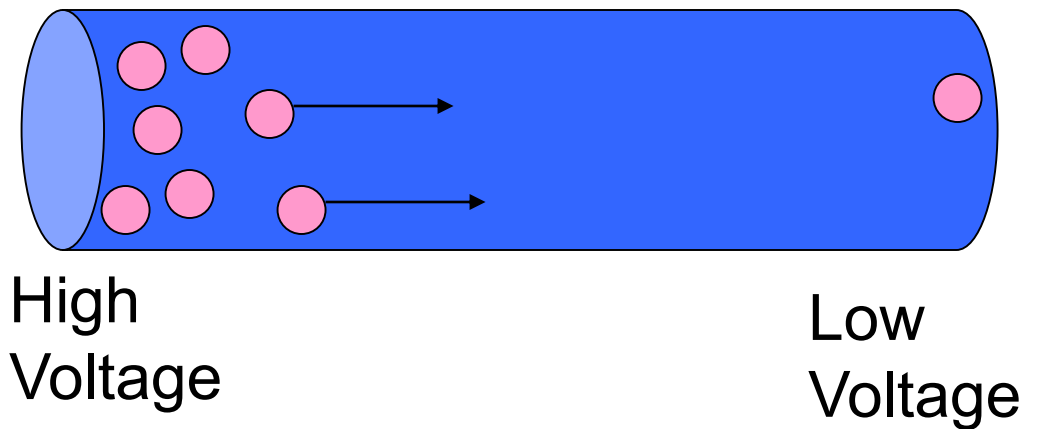
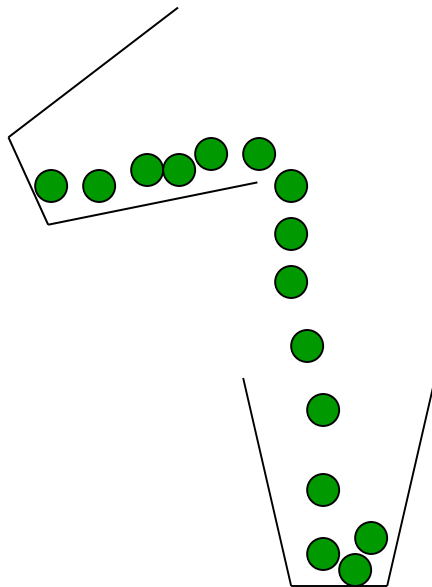
# Electric current

- Electricity is similar to water flow.
  - Water flows from high level to low level.
  - Electricity flows from high voltage to low voltage.


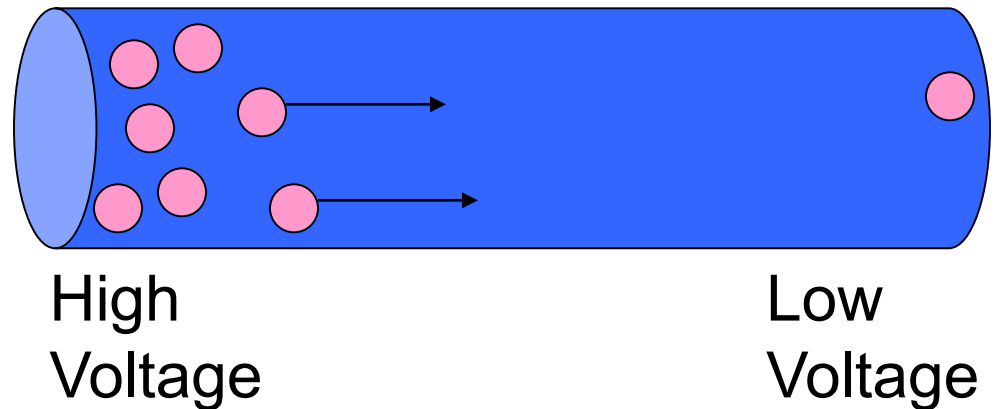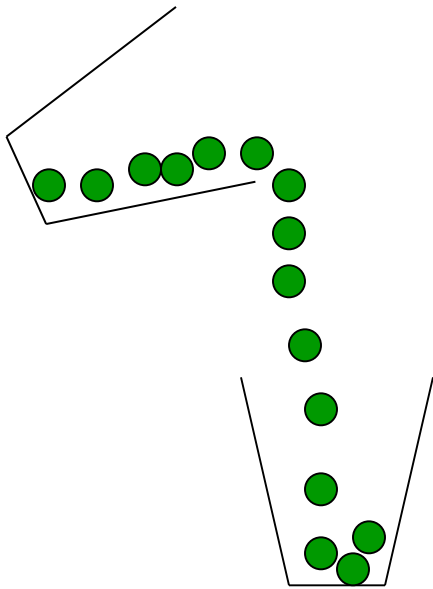
# Measurement of Electricity

- Since we use electricity to do work for us, how can we measure its energy?
- How can we measure the water power?
  - Think about a water gun.



- strong (fast, high kinetic energy)
- amount of water

Voltage  
Current


# Measurement of Electricity

- Imagine the water power at the outlet



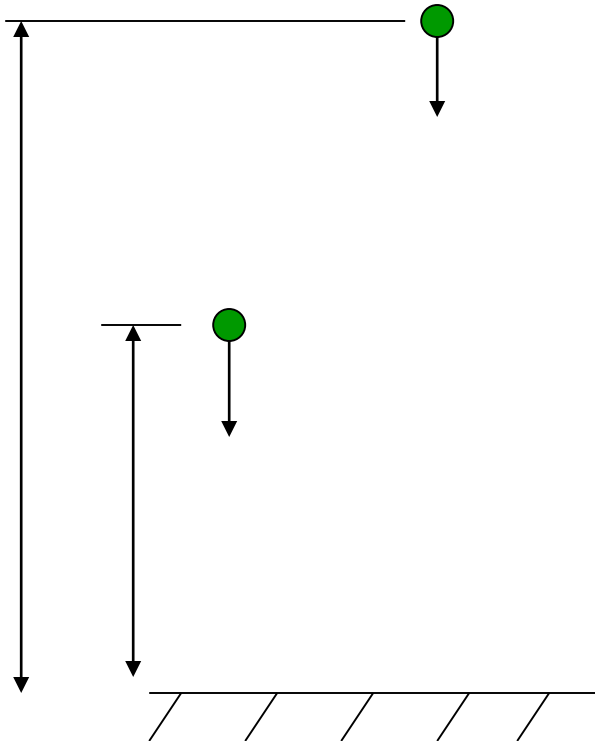
# Electric Potential

- Which water drop has more impact force at the ground?



- Potential Energy-Height

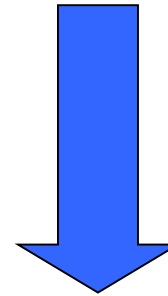

transform

- Kinetic Energy-Velocity

– Electric potential can be compared with the height of the water drop from the reference ground


# Ground: Reference Point

- Normally, we measure height compared to the sea level.
- Also, electric potential at a point can be measured compared to the electric potential at the **ground**.
- Electric potential, or voltage has a unit **volt(V)**.
- Ground always has **0** volts.


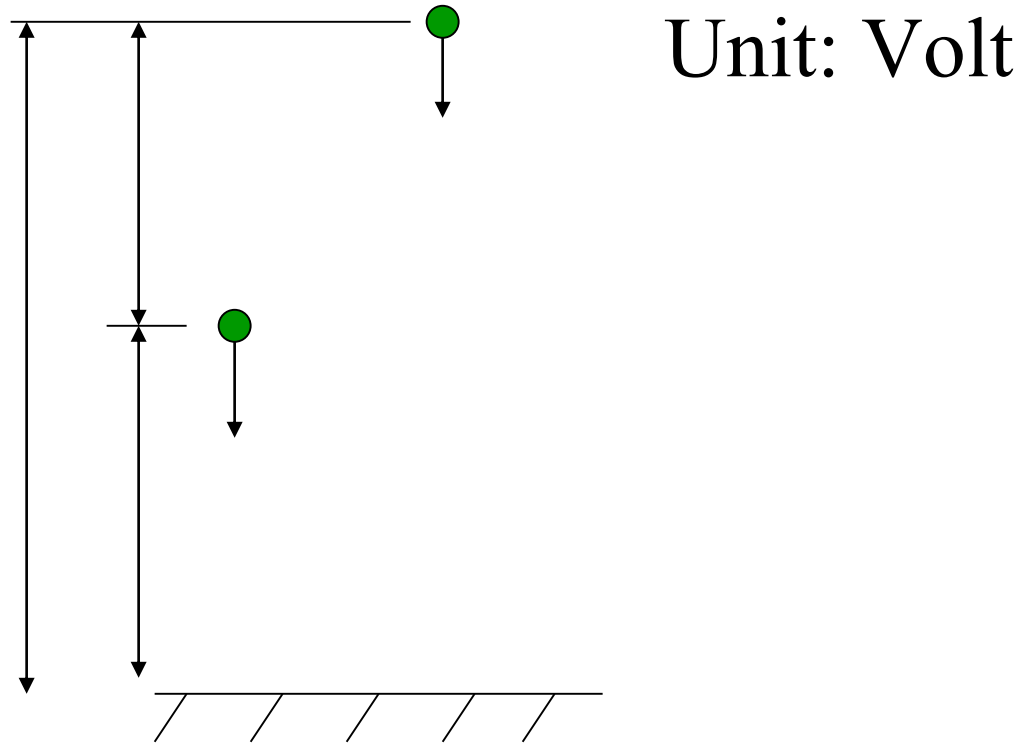
# Voltage


- Voltage is a difference of electric potential between 2 points




- Compare to the height of 2 water drops

# Electric Current



Unit: Ampere,  
Amp (A)

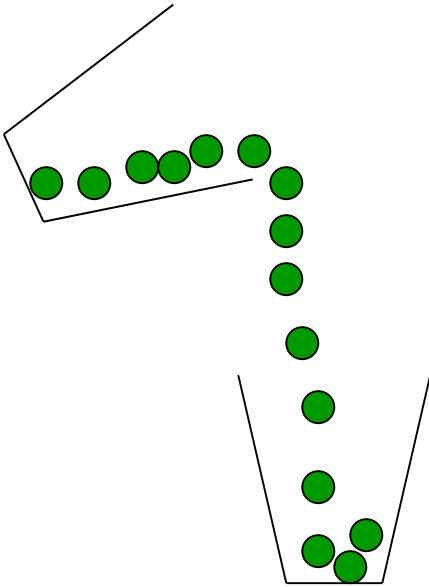

Low current

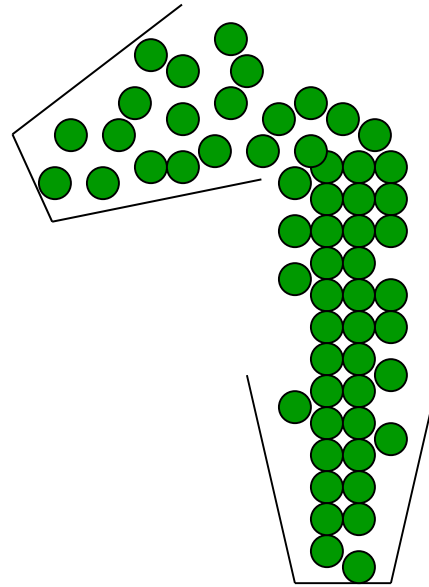


High current

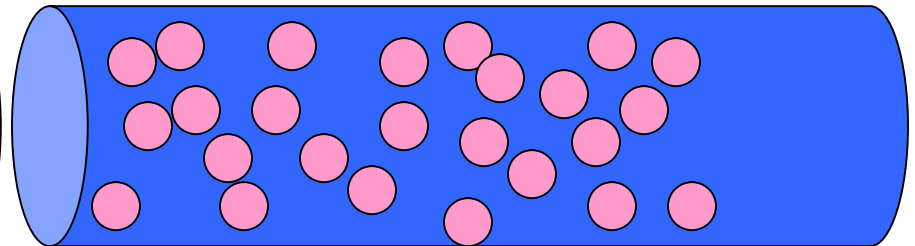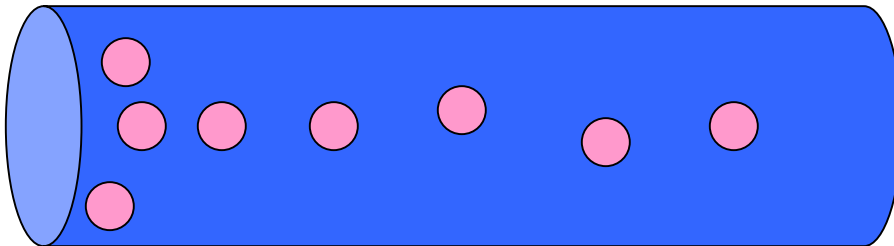


# Charge

| Charge   |             |
|----------|-------------|
| Units    | coulomb (C) |
| Variable | $q, Q$      |

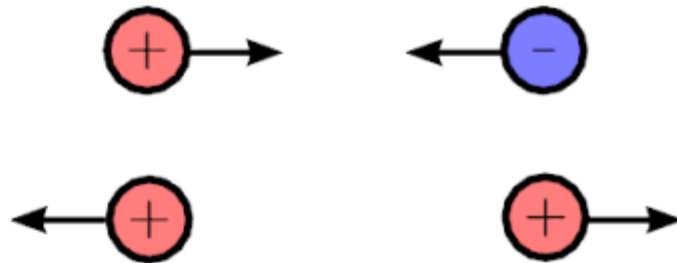- is the fundamental property of matter that causes it to experience a force when placed in electro magnetic field and refers to electrons & protons
  - particles that attract each other (opposite “charge”) or repel each other (same “charge”)



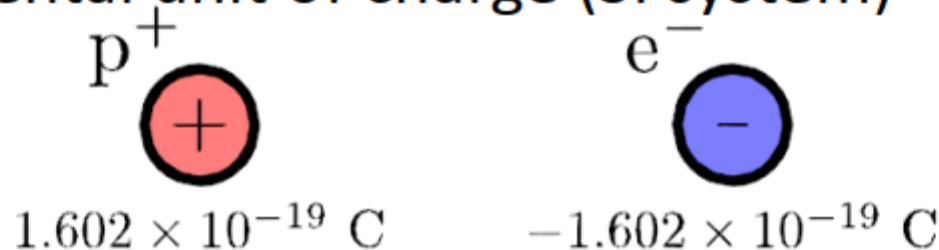- fundamental unit of charge (SI system) = coulomb




# Current

| Current  |                              |
|----------|------------------------------|
| Units    | ampere ( $A = \frac{C}{s}$ ) |
| Variable | $i$                          |

- The movement of charge is called a current
- Historically the moving charges were thought to be positive

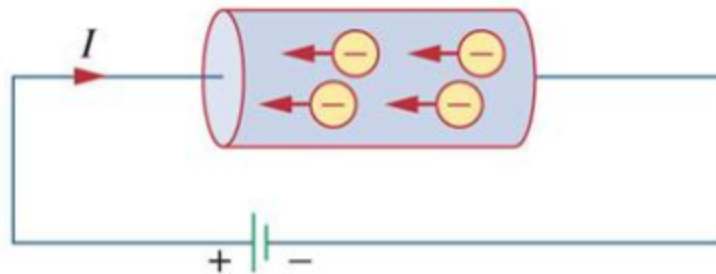Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The mechanism by which electrical energy is transferred
  - Send power from generation point to consumption point
  - Send signals from source to sink



# Current

- Current,  $i$ , is measured as charge moved per unit time through an element.

$$i = \frac{dq}{dt}$$

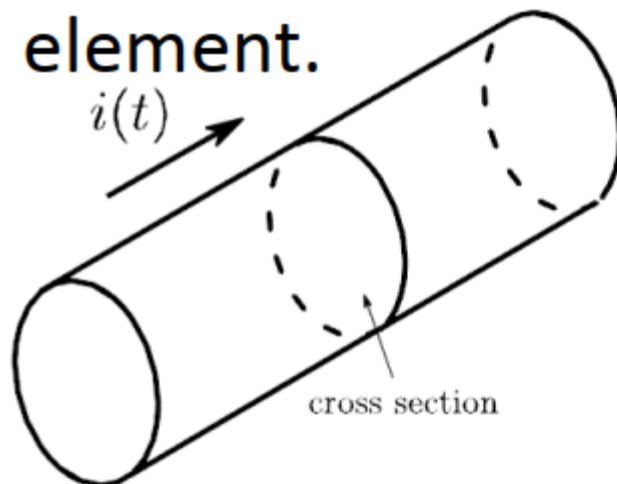


- Amount of charge that has passed a given point:

$$q(t) = \int_{t_0}^t i(\tau) d\tau + q(t_0)$$

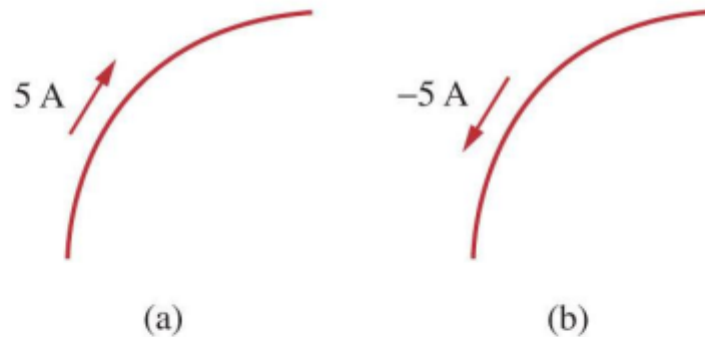
# Direction of Current

- defined as the flow of *positive* charge in a conductor (i.e. in reality, a positive forward current means the electrons are flowing backwards)
- when written, current must be labeled with **direction** & **value**:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



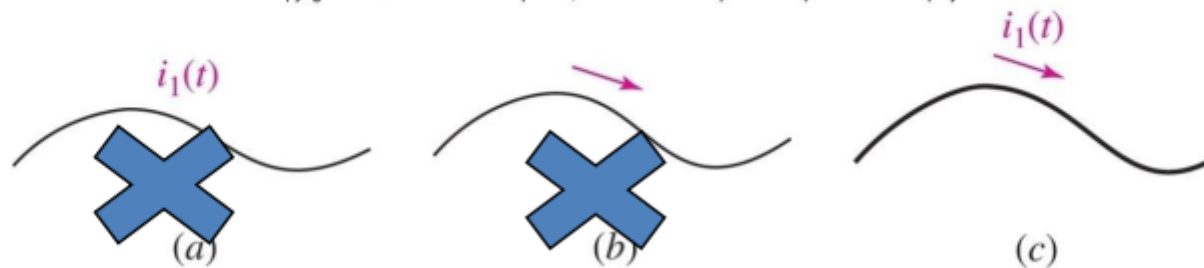
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Examples

- The charge entering a certain element is shown in below Figure. Find the current at:

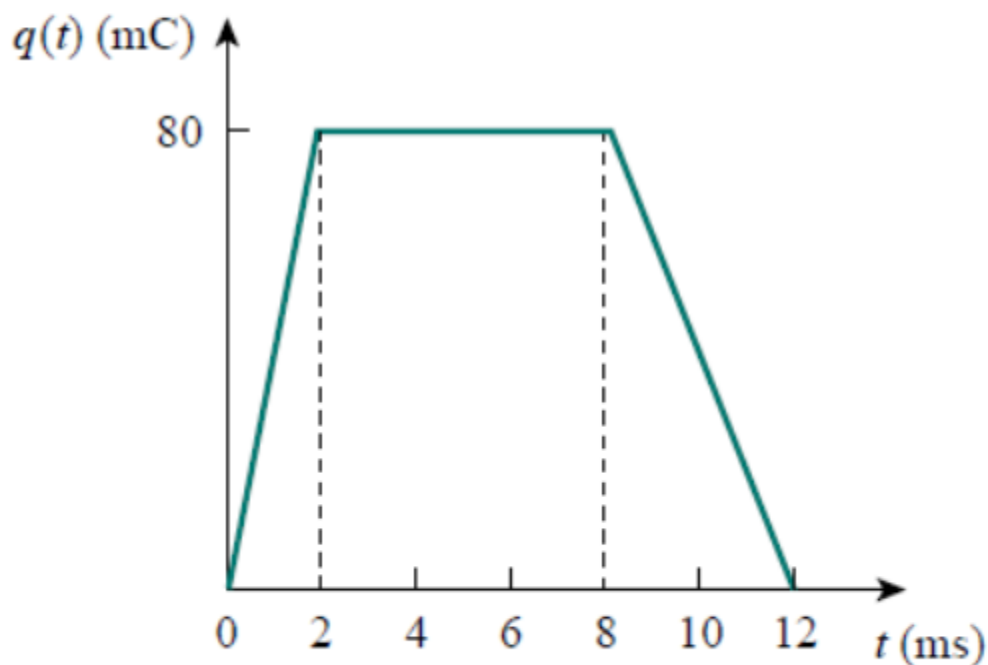
(a)  $t = 1 \text{ ms}$       (b)  $t = 6 \text{ ms}$       (c)  $t = 10 \text{ ms}$



- The slope is defined as the ratio of the vertical change between two points, to the horizontal change between the same two points.
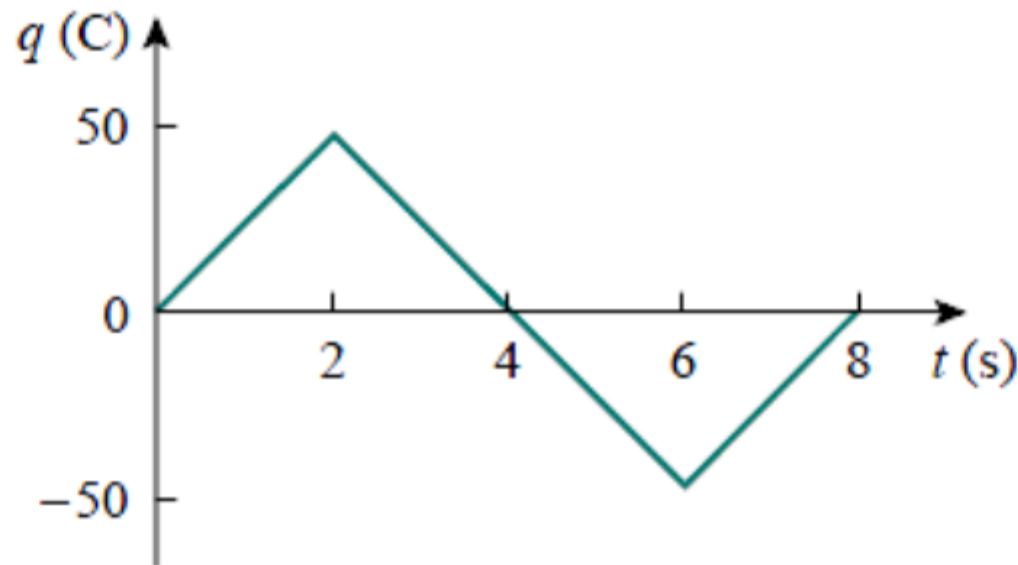
# Examples

- The charge flowing in a wire is plotted in below Figure. Sketch the corresponding current.






# Voltage


| Voltage  |                            |
|----------|----------------------------|
| Units    | volt ( $V = \frac{J}{C}$ ) |
| Variable | $v$                        |

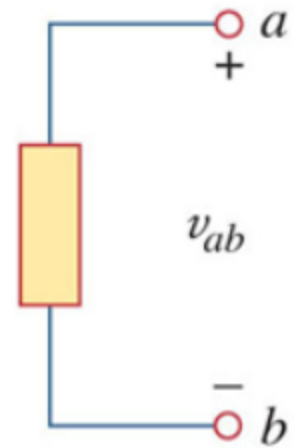- Electrons move when there is a difference in charge between two locations.
- Voltage (or potential difference) is the energy required to move a unit charge through an element, measured in **volts** (V) (from  $a$  to  $b$ ).



- $V_{ab}$ 
  - point  $a$  is at a potential of  $V_{ab}$  volts higher than point  $b$

$$V_{ab} = -V_{ba}.$$

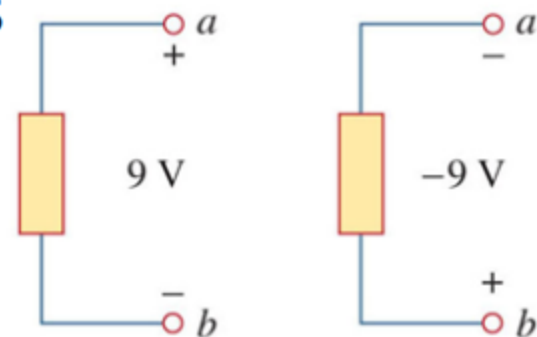


# Power

| Power    |                            |
|----------|----------------------------|
| Units    | watt ( $W = \frac{J}{s}$ ) |
| Variable | $p$                        |

- Power is the product of voltage and current


$$p = vi$$

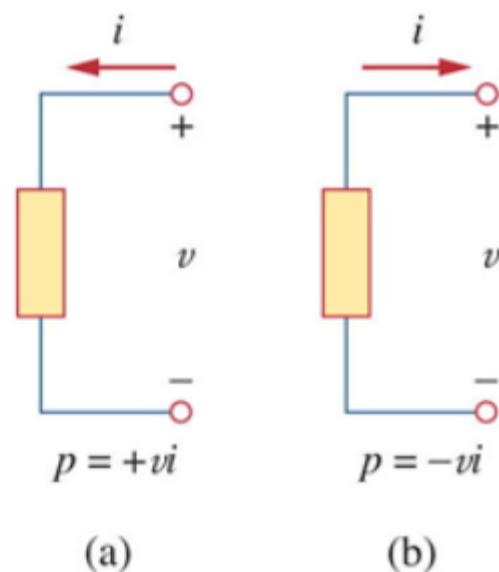- It is equal to the rate of energy provided or consumed per unit time.
- It is measured in Watts (W)
- Passive sign convention
  - current into positive terminal
  - positive for power *absorbed*
  - negative for power *supplied*



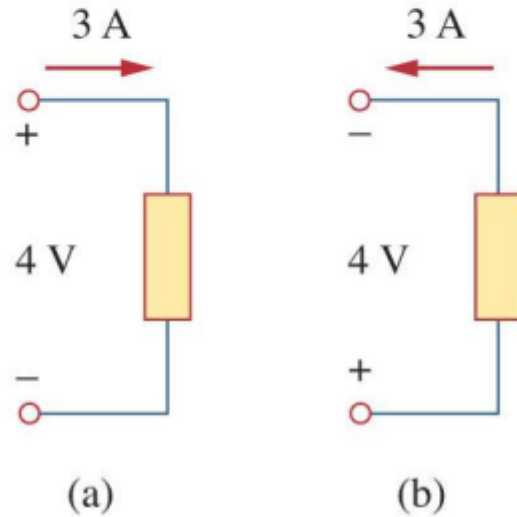
# Power

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Two cases of an element  
with an absorbing power of  
12 W

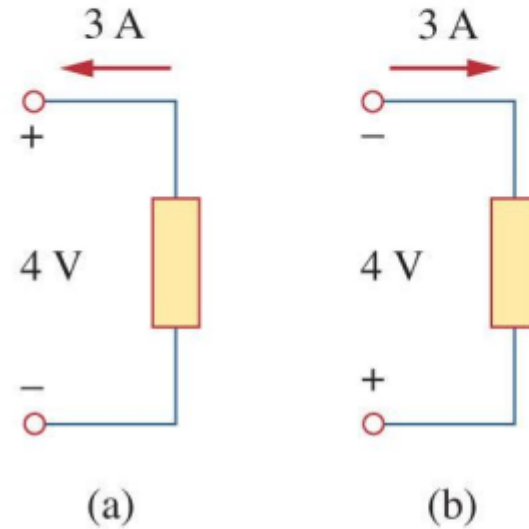Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Two cases of an element  
with an supplying power of  
12 W

# Conservation of Energy (Tellegen's Theorem )

- The sum of all power supplied must be absorbed by the other elements.
- For this reason, the algebraic sum of power in a circuit, at any instant of time, must be zero

$$\sum p = 0$$

- The energy absorbed or supplied by an element from time  $t_0$  to time  $t$  is



$$w = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt$$

# Circuit Components


- Active elements
  - Independent power sources
    - voltage, current
  - Dependent power sources
    - voltage, current
- Passive Elements
  - Resistors
  - Capacitors
  - Inductors
- Measurement Devices
  - Ampermeters:
    - measure current
  - Voltmeters:
    - measure voltage
- Ground
  - reference point
- Electric Wire
- Switches
- Protective devices
  - Fuse
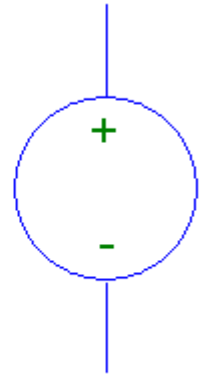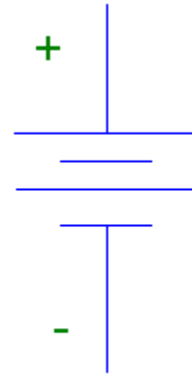
# Independent Power Sources

- Independent voltage source outputs a voltage, either dc or time varying, to the circuit no matter how much current is required.



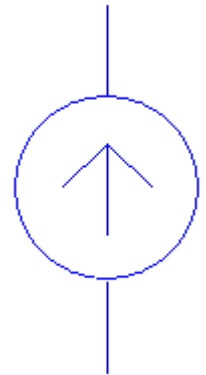- Independent current source outputs a dc or ac current to the circuit no matter how much voltage is required.




# Independent Power Sources

- Current can flow in and out of an independent voltage source, but the polarity of the voltage is determined by the voltage source.
- There is always a voltage drop across the independent current source and the direction of positive current is determined by the current source.
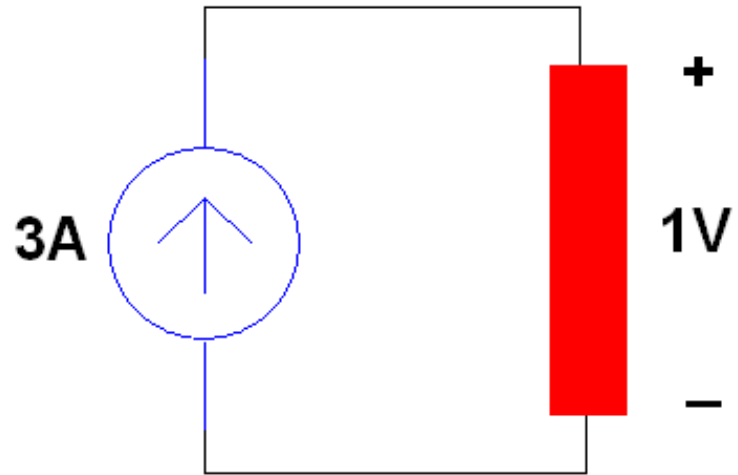
# Example 1

- 1 V is dropped across some element (in red) and the wires to that element are connected directly to the independent current source.






# Example 1


- This means that 1 V is also dropped across the independent current source. Therefore, the current source is generated  $1 \text{ V}(3 \text{ A}) = 3 \text{ W}$  of power.

- Passive sign convention: When current leaves the + side of a voltage drop across the independent current source, the power associated with the current source is:
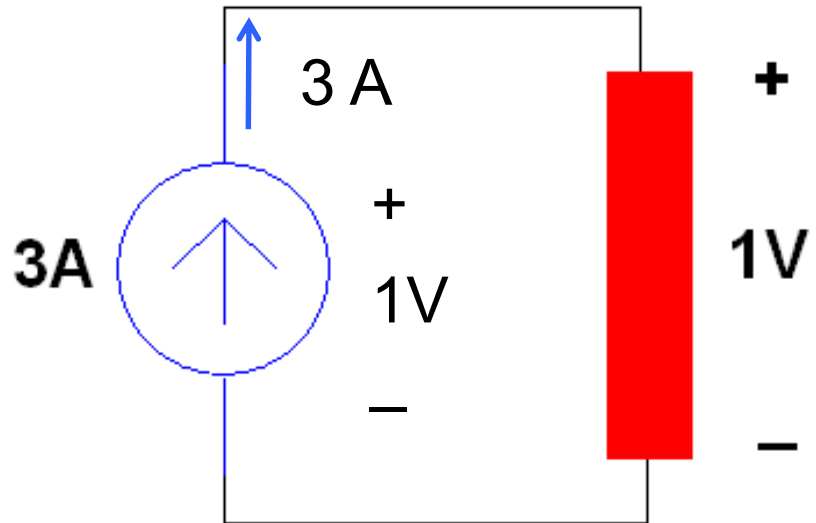
$$p = -3 \text{ A}(1 \text{ V}) = -3 \text{ W}$$



# Example 1

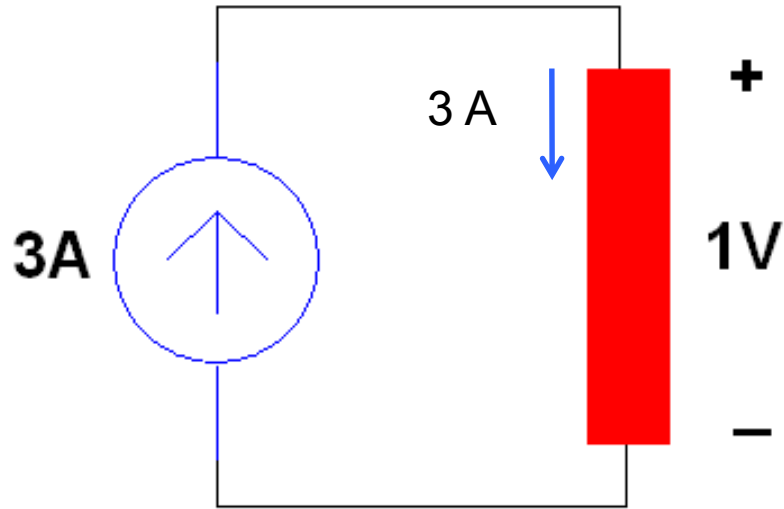

- Conservation of energy means that the other element in red must be dissipating 3 W of power.


$$\sum p = p_{\text{current source}} + p_{\text{red element}} = 0$$

$$p_{\text{current source}} = -3 \text{ W}; \text{ therefore, } p_{\text{red element}} = 3 \text{ W}$$

- Passive sign convention: When current enters the + side of a voltage drop across the element in red, the power associated with this element is:

$$p = 3 \text{ A}(1 \text{ V}) = 3 \text{ W}$$



# Example 1

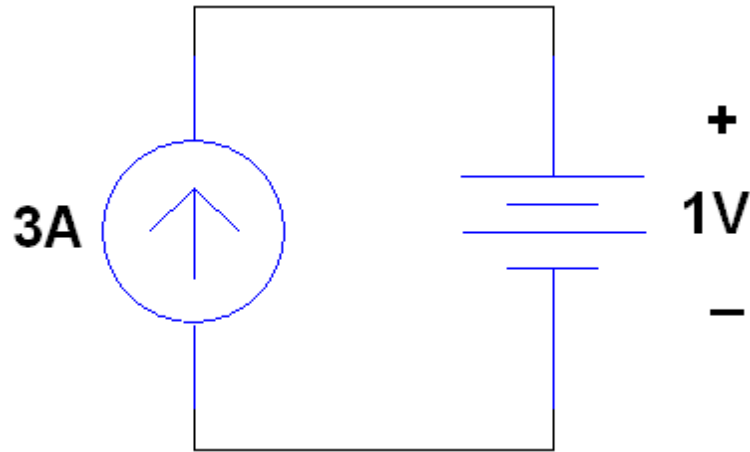

- Suppose the red element was an independent voltage source.
- This means is that the independent current source happens to be supplying power to the independent voltage source, which is dissipating power.
- This happens when you are charging a battery, which is considered to be an independent voltage source.

# Dependent Power Sources



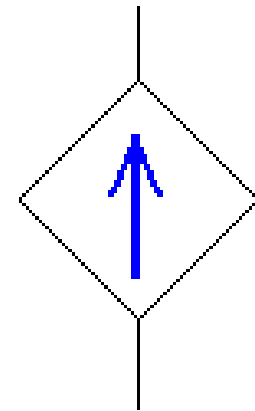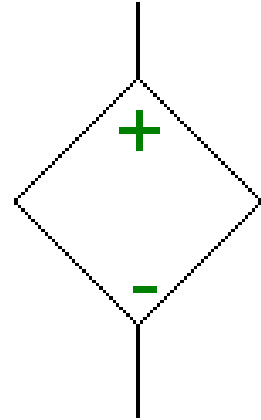



- Voltage controlled voltage source
  - (VCVS)
- Current controlled voltage source
  - (CCVS)
- Voltage controlled current source
  - (VCCS)
- Current controlled current source
  - (CCCS)



# Passive Elements

- The magnitude of the voltage drop and current flowing through passive devices depends on the voltage and current sources that are present and/or recently attached to the circuit.
  - These components can dissipate power immediately or store power temporarily and later release the stored power back into the circuit.

# Passive Components

| Component  | Symbol   | Basic Measure (Unit) |
|--|--|----------------------|
| Resistor<br>    |    | Ohm ( $\Omega$ )     |
| Inductor<br>    |    | Henry (H)            |
| Capacitor<br> |  | Farad (F)            |

# Other Basic Circuit Elements

- Electric wire



Symbol

---

- Ground



earth



chassis



ground



ground




analog  
ground



digital  
ground

- Switch

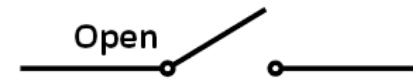

Open



Closed

- Fuse



IEEE/ANSI Standard



IEC Standard



IEEE/ANSI Standard



Old Symbol

# Switches

- Switches are used to control whether a complete path is formed from an end of at least one power supply to the other end of the same power supply (closed circuit).
  - Current will only flow when there is a closed circuit.
- Switches can be mechanical, as are used on light switches in your home, or are electronic switches, which are semiconductor based.
- Electronic switches are used in TV sets, for example, to turn on the TV when an infrared optical signal from the remote control is detected.



# Protective Devices

- Circuits that have carry dangerous levels of current and voltages are required to include fuses, circuit breakers, or ground fault detectors by federal and state electrical safety codes.
  - These protective devices are designed to create an open circuit, or a break in the round trip path in the circuit, when a malfunction of a component or other abnormal condition occurs.
  - The speed of response of the protective device, fast-acting or time-delay (slow-blow) is determine by the engineer, based upon the expected type of malfunction.

# Wires

- Wires are assumed to have zero resistance; i.e., they are ideal conductors or short circuits.
  - The current carrying capability of a wire is determined by its diameter or cross-sectional area.
  - AWG, American wire gauge, is the standard followed in the US and is used to rate how much current a wire can safely carry.
  - The larger the gauge wire, the smaller its current carrying capability is.
    - The AWG standard includes copper, aluminum and other wire materials.
    - Typical household copper wiring is AWG number 12 or 14.
    - Telephone wire is usually 22, 24, or 26.
    - The higher the gauge number, the smaller the diameter and the thinner the wire.

# AWG to square mm cross sectional area

| American Wire Gauge (#AWG) | Diameter (inches) | Diameter (mm) | Cross Sectional Area (mm <sup>2</sup> ) |
|----------------------------|-------------------|---------------|---|
| 0000 (4/0)                 | 0.460             | 11.7          | 107                                     |
| 000 (3/0)                  | 0.410             | 10.4          | 85.0                                    |
| 00 (2/0)                   | 0.365             | 9.27          | 67.4                                    |
| 0 (1/0)                    | 0.325             | 8.25          | 53.5                                    |
| 1                          | 0.289             | 7.35          | 42.4                                    |
| 2                          | 0.258             | 6.54          | 33.6                                    |
| 3                          | 0.229             | 5.83          | 26.7                                    |
| 4                          | 0.204             | 5.19          | 21.1                                    |
| 5                          | 0.182             | 4.62          | 16.8                                    |
| 6                          | 0.162             | 4.11          | 13.3                                    |
| 7                          | 0.144             | 3.67          | 10.6                                    |
| 8                          | 0.129             | 3.26          | 8.36                                    |
| 9                          | 0.114             | 2.91          | 6.63                                    |
| 10                         | 0.102             | 2.59          | 5.26                                    |

| American Wire Gauge (#AWG) | Diameter (inches) | Diameter (mm) | Cross Sectional Area (mm <sup>2</sup> ) |
|----------------------------|-------------------|---------------|---|
| 11                         | 0.0907            | 2.30          | 4.17                                    |
| 12                         | 0.0808            | 2.05          | 3.31                                    |
| 13                         | 0.0720            | 1.83          | 2.63                                    |
| 14                         | 0.0641            | 1.63          | 2.08                                    |
| 15                         | 0.0571            | 1.45          | 1.65                                    |
| 16                         | 0.0508            | 1.29          | 1.31                                    |
| 17                         | 0.0453            | 1.15          | 1.04                                    |
| 18                         | 0.0403            | 1.02          | 0.82                                    |
| 19                         | 0.0359            | 0.91          | 0.65                                    |
| 20                         | 0.0320            | 0.81          | 0.52                                    |
| 21                         | 0.0285            | 0.72          | 0.41                                    |
| 22                         | 0.0254            | 0.65          | 0.33                                    |
| 23                         | 0.0226            | 0.57          | 0.26                                    |
| 24                         | 0.0201            | 0.51          | 0.20                                    |
| 25                         | 0.0179            | 0.45          | 0.16                                    |
| 26                         | 0.0159            | 0.40          | 0.13                                    |


# AWG to ohm/meter

Approximate resistance of copper wire<sup>[6]:27</sup>

| AWG | mΩ/ft | mΩ/m | AWG | mΩ/ft | mΩ/m | AWG | mΩ/ft | mΩ/m | AWG | mΩ/ft | mΩ/m |
|-----|-------|------|-----|-------|------|-----|-------|------|-----|-------|------|
| 0   | 0.1   | 0.32 | 10  | 1     | 3.2  | 20  | 10    | 32   | 30  | 100   | 320  |
| 1   | 0.125 | 0.4  | 11  | 1.25  | 4    | 21  | 12.5  | 40   | 31  | 125   | 400  |
| 2   | 0.16  | 0.5  | 12  | 1.6   | 5    | 22  | 16    | 50   | 32  | 160   | 500  |
| 3   | 0.2   | 0.64 | 13  | 2     | 6.4  | 23  | 20    | 64   | 33  | 200   | 640  |
| 4   | 0.25  | 0.8  | 14  | 2.5   | 8    | 24  | 25    | 80   | 34  | 250   | 800  |
| 5   | 0.32  | 1    | 15  | 3.2   | 10   | 25  | 32    | 100  | 35  | 320   | 1000 |
| 6   | 0.4   | 1.25 | 16  | 4     | 12.5 | 26  | 40    | 125  | 36  | 400   | 1250 |
| 7   | 0.5   | 1.6  | 17  | 5     | 16   | 27  | 50    | 160  | 37  | 500   | 1600 |
| 8   | 0.64  | 2    | 18  | 6.4   | 20   | 28  | 64    | 200  | 38  | 640   | 2000 |
| 9   | 0.8   | 2.5  | 19  | 8     | 25   | 29  | 80    | 250  | 39  | 800   | 2500 |
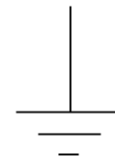
# Ground

- Earth ground is a ground that is physically connected to the earth, itself.
  - All homes have an earth ground
    - a wire connected to a metal pipe that is driven into the ground immediately next to the house.
    - Wires that have a green jacket or are bare copper are connected to this pipe.
- Reference ground or common is used in a circuit to indicate a point where the voltage in the circuit is equal to zero.



# General Rules

- All points on a same electric wire have the same voltage.
- A voltage source always have voltage difference of its pins equal to its value.
- A current source always have current pass through it equal to its value.
- Ground always has zero voltage. (0 volts)

# Electric Flow Rule

- Electric current flows from high voltage to low voltage when there is a path.
- Electric current can freely pass through electric wire.
- Electric current can flow through a resistor with the amount according to Ohm's law.
- Electric current can flow through a voltage source with the amount depended on other components in the circuit.
- Electric current can flow pass a current source according to its value.

# Charge

- Electrical property of atomic particles
  - Electrons are negatively charged
  - Protons are positivity charged
- The absolute value of the charge on an electron is  $1.6 \times 10^{-19}$  C
- The symbol used is  $Q$  or  $q$ 
  - Uppercase is used to denote a steady-state or constant value
  - Lowercase is used to denote an instantaneous value or time-varying quantity



# Current

- The flow of charge through a cross-sectional area as a function of time or the time rate of change of charge
- Symbol used is  $I$  or  $i$

$$i = \frac{dq}{dt}$$

$$Q = \int_{t_1}^{t_2} i \, dt$$

# DC vs. AC

- DC (or dc) is the acronym for direct current.
  - The current remains constant with time.
    - Uppercase variables are used when calculating dc values.
- AC (or ac) is the acronym for alternating current.
  - Specifically, AC current varies sinusoidally with time and the average value of the current over one period of the sinusoid is zero.
    - Lowercase variables are used when calculating ac values.
  - Other time-varying currents exist, but there isn't an acronym defined for them.

# Voltage (Potential Difference)

- The **electromotive force (emf)** that causes charge to move.
- 1 Volt = 1 Joule/1 Coulomb

$$V = \frac{dw}{dq}$$

# Power

- The change in energy as a function of time is power, which is measured in **watts (W)**.

$$p = \frac{dw}{dt} = \left[ \frac{dw}{dq} \right] \left[ \frac{dq}{dt} \right] = vi$$

# Energy

- Energy is the capacity to do work.

$$w = \int_{t_1}^{t_2} p \, dt = \int_{t_1}^{t_2} v \, i \, dt$$


- Units for energy are kW-hr, which is what the electric company measures on your electric meter.

$$1 \text{ kW-hr} = 3.6 \text{ MJ.}$$

# Positive vs. Negative Power

- Power consumed/dissipated by a component is positive power


$$P = +1\text{W}$$

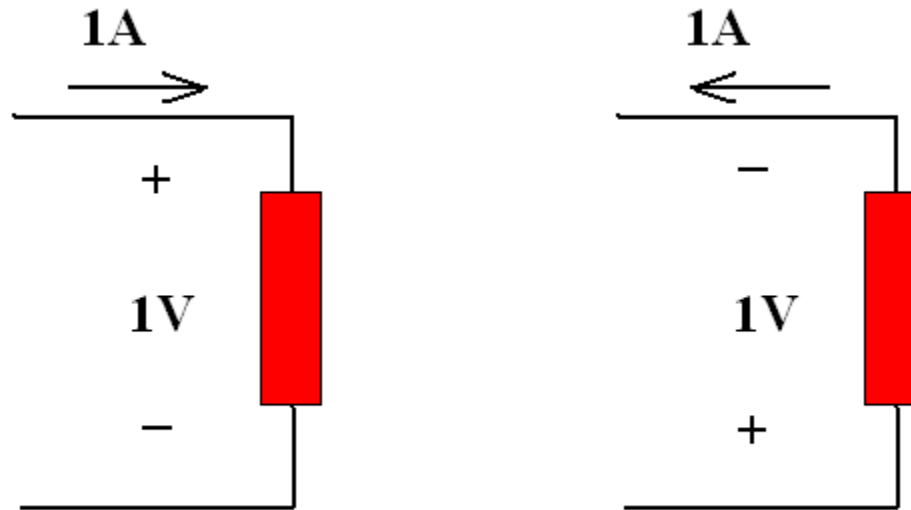

# Positive vs. Negative Power

- Generated power has a negative sign

$$P = -1\text{ W}$$

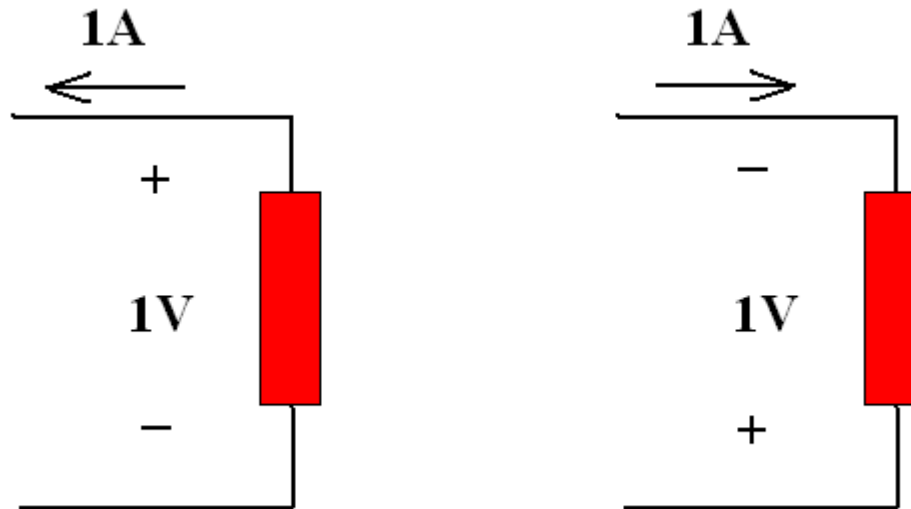

# Conservation of Energy


- All power instantaneously consumed by components must be instantly generated by other components within the circuit.

$$\sum p = 0$$


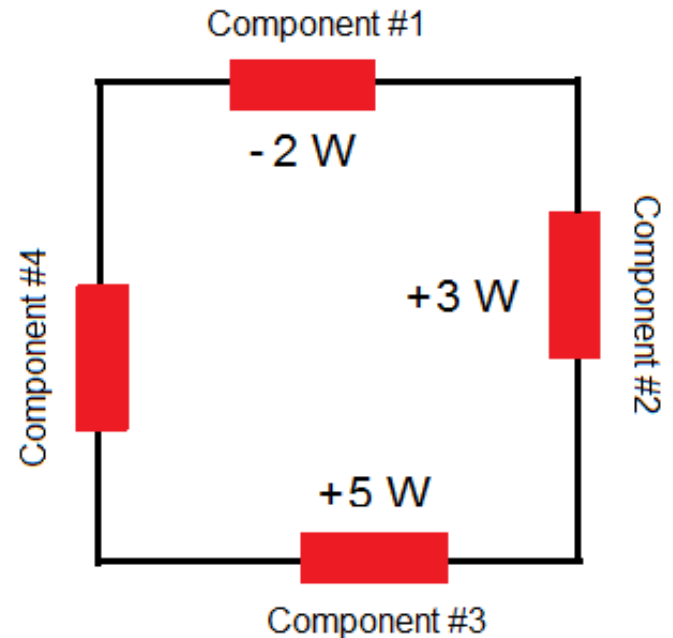
# Example


- There are 4 electrical components in the circuit shown to the right.
- Component #1 is generating 2 W of power and supplying this power to the circuit.
- Components #2 and #3 are consuming power.
- Component #2 is dissipating 3 W of power while Component #3 is dissipating 5 W of power.
- Component #4 must be generating 6 W of power in order to maintain the Conservation of Energy.




$$\sum p = p_{\text{Component\#1}} + p_{\text{Component\#2}} + p_{\text{Component\#3}} + p_{\text{Component\#4}} = 0$$

$$p_{\text{Component\#4}} = -(p_{\text{Component\#1}} + p_{\text{Component\#2}} + p_{\text{Component\#3}}) = -(-2 \text{ W} + 3 \text{ W} + 5 \text{ W}) = -6 \text{ W}$$


# Simple DC Circuit

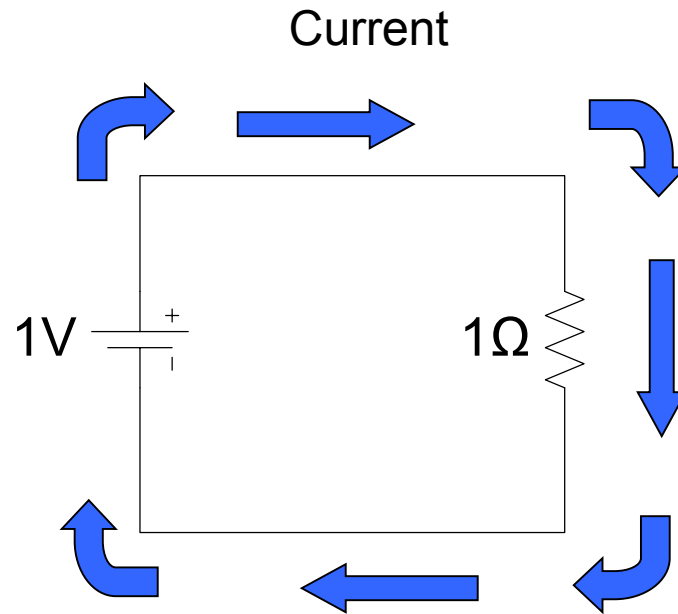

# Metaphor

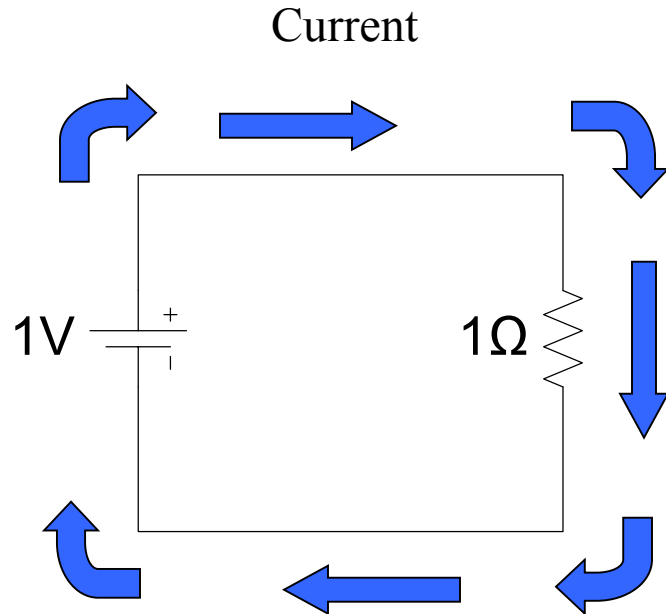

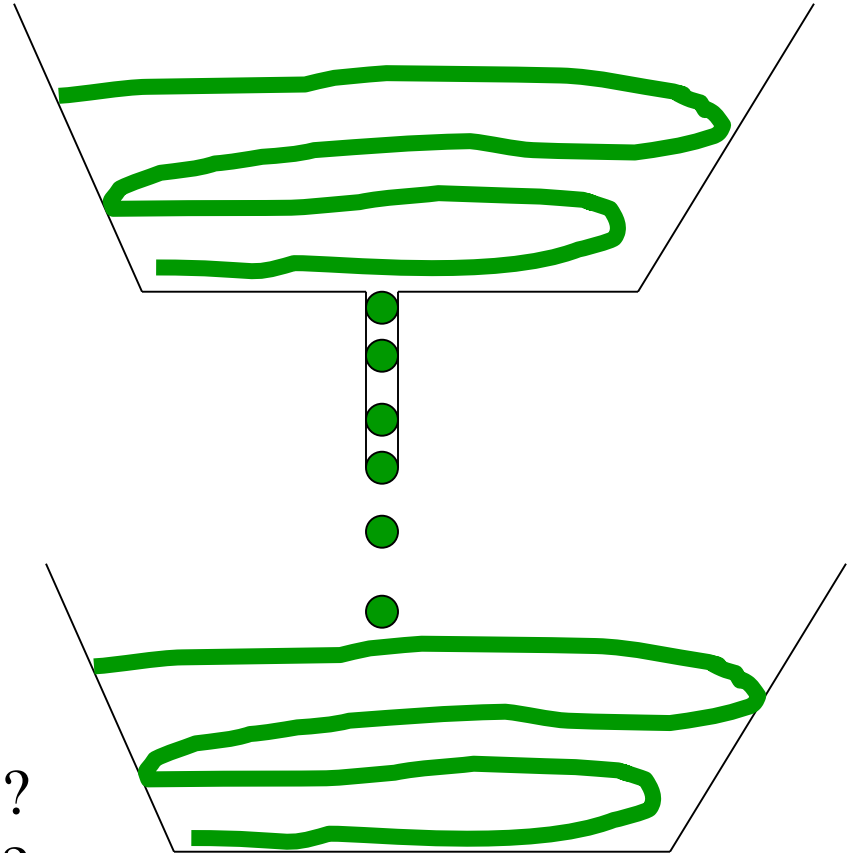- Increasing  $V$  is compared to ?
- Increasing  $R$  is compared to ?




# Ohm's Law

$$V = IR$$


for using with a resistor only

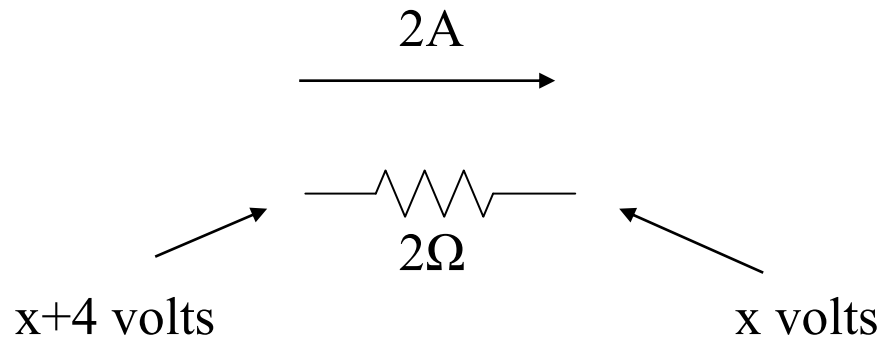Voltage (Volts) =  
current (Amperes) x resistance (Ohms)




Note: (Theoretically) Electric wire has a resistance of 0 ohms

# Electric Current

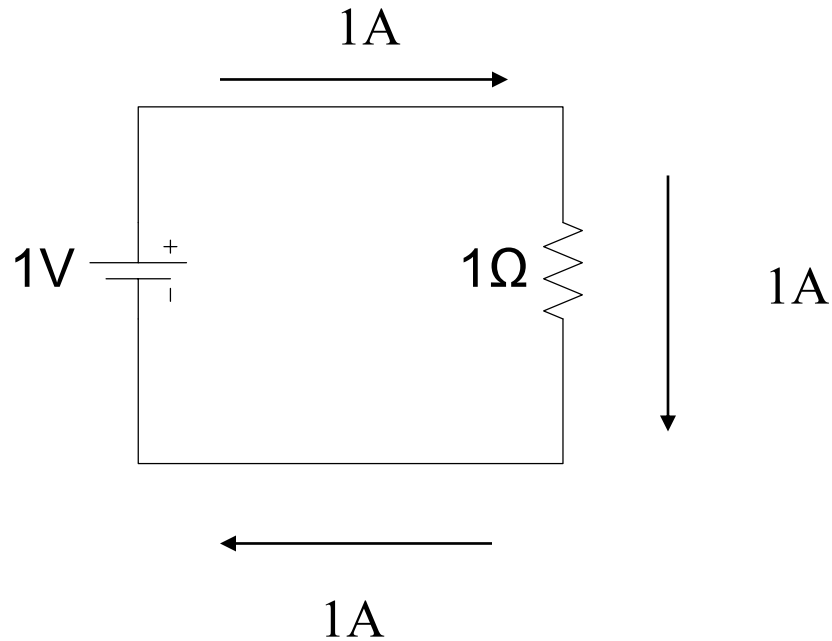


Every point in the circuit has current =  $1A$

# Electric Voltage

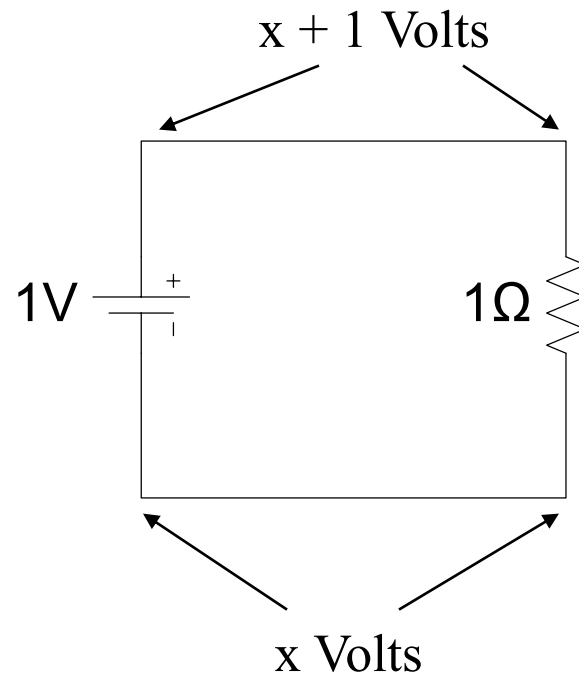
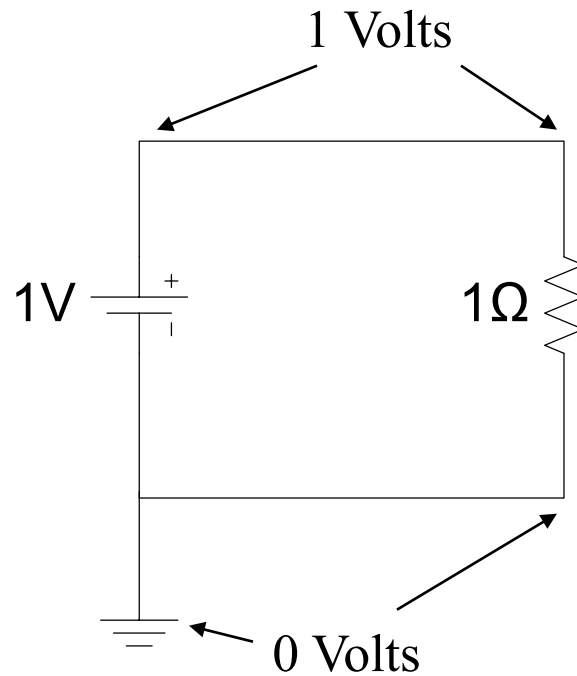
# Ground


Ground = reference point always have voltage = 0 volts



# Electric Voltage (2)

1 Volts


0 Volts

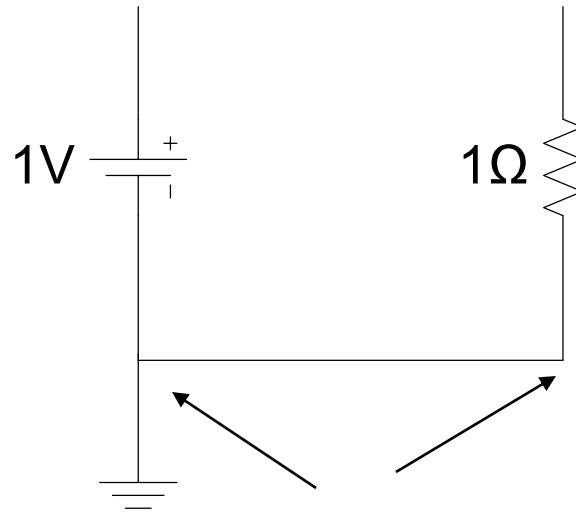


0 Volts





# Electric Voltage (3)

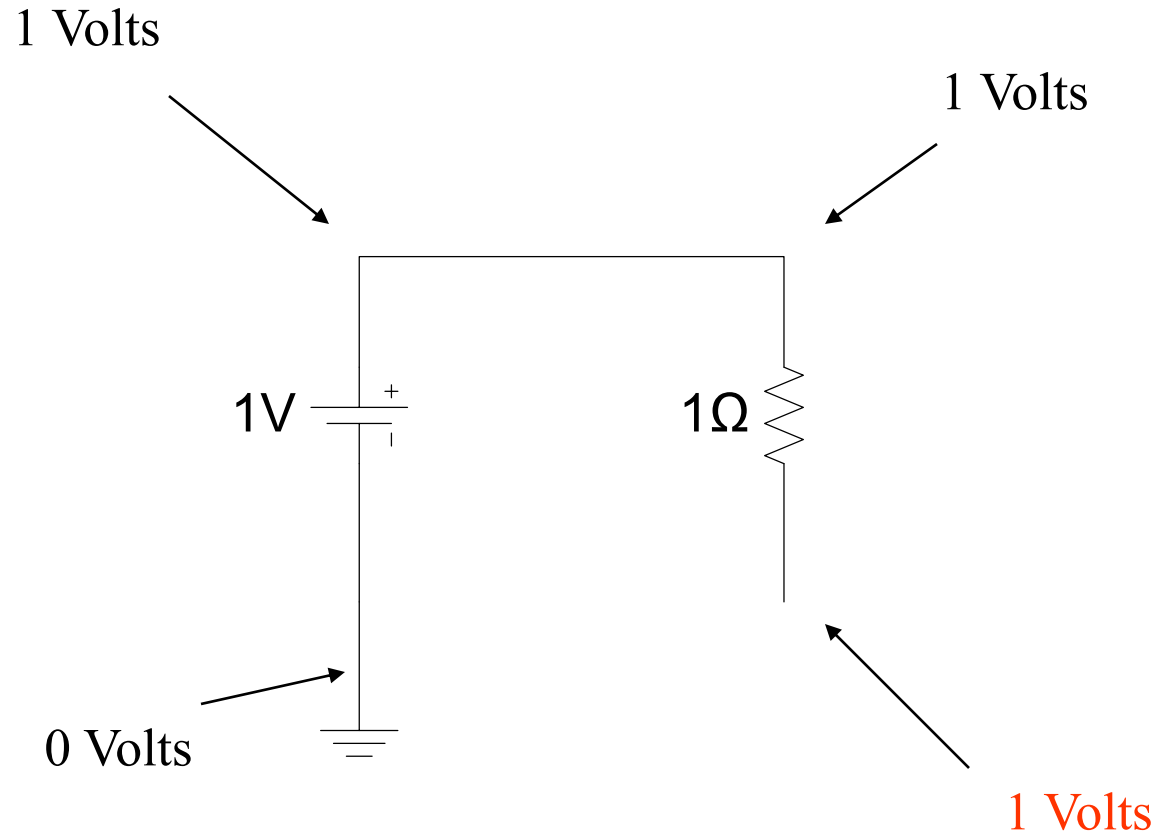


# Negative Voltage and Current

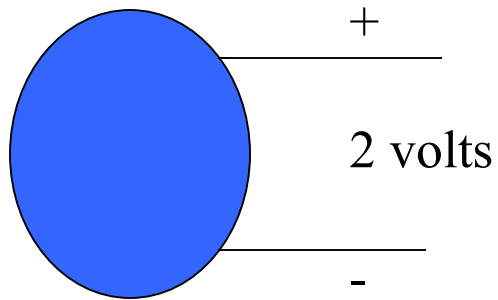

Same as

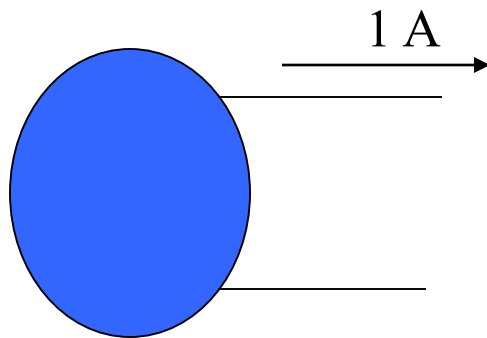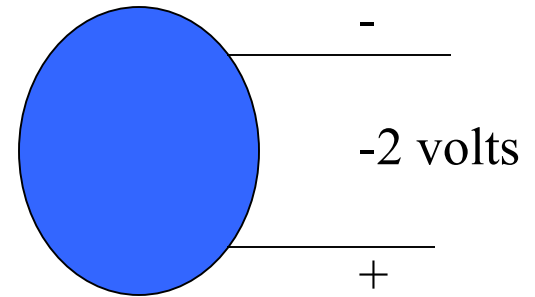


Same as

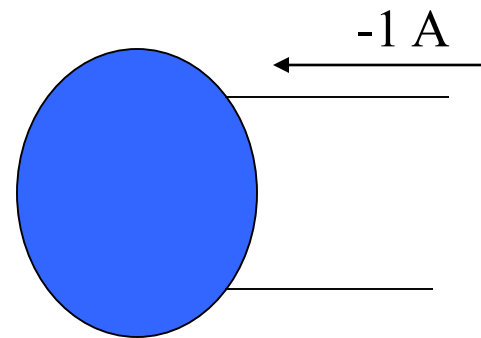


# Power

Symbol  $P$  has a unit of Watt

$$P = VI$$

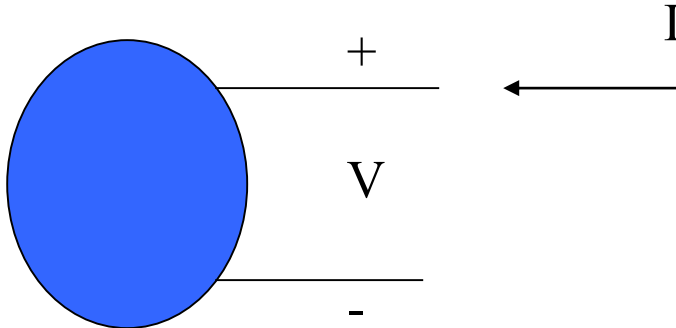

Absorb power

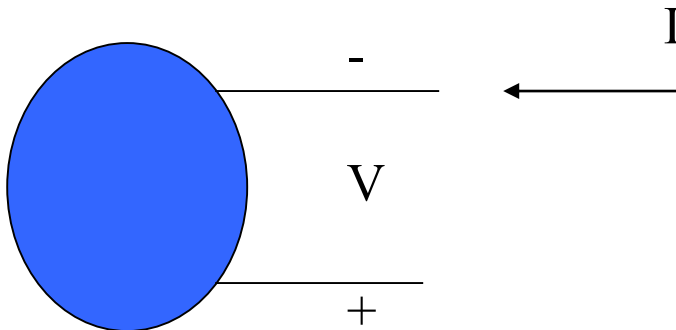


Generate power

# Passive Sign Convention

Absorb power: Power has a sign +

Generate power: Power has a sign -

# Example

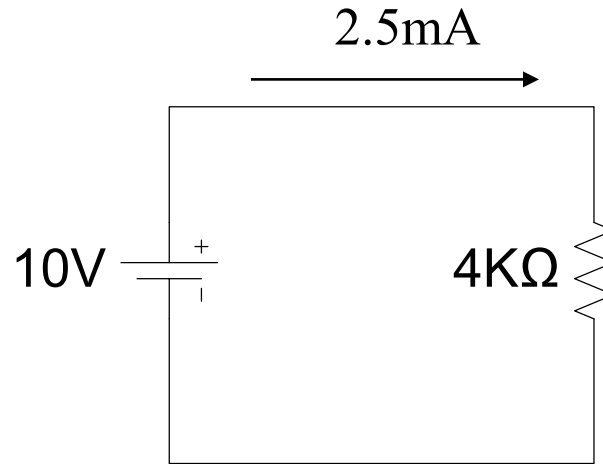


DC source generates power =  $10\text{V} * -2.5\text{mA} = -25\text{mW}$

Resistor absorbs power =  $10\text{V} * 2.5\text{mA} = 25\text{mW}$

Note: Resistors always absorb power but DC source can either generate or absorb power
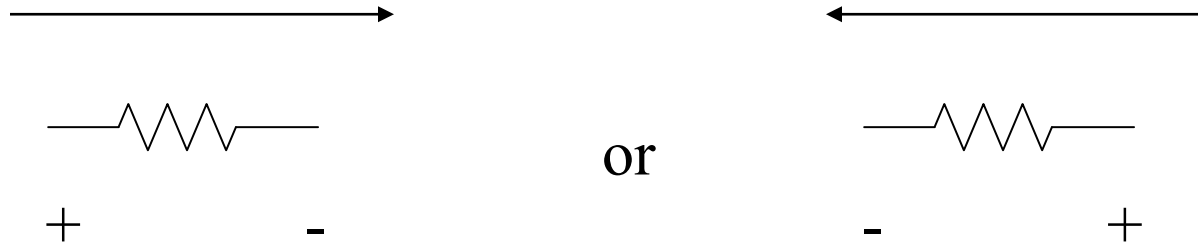
# Direction of Voltage & Current on Resistors



- Resistor always absorb power.
- Therefore, it always have current flow through it from high voltage pin to low voltage pin.