

# BME2322 – Logic Design

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN


[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/nakkan>

# LECTURE 3


# Inside the Digital Gates

Inside the Digital Gate

 
 
# The Digital Abstraction

- Discretize value: 0, 1
- Static discipline -- digital devices meet voltage thresholds




Specifies how gates must be designed

# Combinational Elements

 
## Combinational gate abstraction

- outputs function of input alone
- satisfies static discipline



A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


## A digital circuit

 

3 gates here

If we use combination of simple gates

# How to build a digital gate

 


(a) The lightbulb circuit with a switch; (b) the lumped circuit representation.

The switch is normally off and behaves like an open circuit. When pressure is applied to the switch, it closes and behaves like a wire and conducts current.



Accordingly, the switch can be modeled as the three-terminal device
 
# How to build a digital gate

When the control terminal has a TRUE or a logical 1 signal on it, the input is connected to the output through a short circuit.



  Otherwise, there is an open circuit between the input and the output.




# $v$ - $i$ Characteristics of the Switch

The  $v$ - $i$  characteristics of a switch can also be expressed in algebraic form as:

for Control = "0,"  $i = 0$

and

for Control = "1,"  $v = 0$ .


 


$v$ - $i$  characteristics of a switch.  $v$  is the voltage across the input and the output terminals of the switch and  $i$  is the current through the same pair of terminals.




# Logic Functions using Switches

  
(a) The lightbulb circuit with switch in an *AND* configuration; (b) the lightbulb circuit with switches in an *OR* configuration.



# Using Three Terminal Switch Device

 

# Behavior of this Basic Circuit

 


NOT Gate



egot.

$C$	$z$
0	1
1	0

# NAND Gate

 


$c_1$	$c_2$	$z$
0	0	1
0	1	1
1	0	1
1	1	0

Truth table for



# NOR Gate

 

$C_1$	$C_2$	$Z$
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table for ?


 
# The MOSFET Device


Metal-Oxide Semiconductor  
Field-Effect Transistor

3 terminal lumped element  
behaves like a switch



Port representation  
of a MOSFET.


Similar to switch

 


$G$ : control terminal

$D, S$ : behave in a symmetric  
manner (for our needs)


# The MOSFET Device (S model)

 

$v_{GS} < V_T$

 


$v_{GS} \geq V_T$

 


$V_T \sim 1V$   
for example

# MOSFET Device on Scope

 







# A MOSFET Inverter

 


Note the power of abstraction:

The abstract inverter gate representation hides internal details such as power supply connections,  $R_L$ ,  $GND$ , etc. When we build digital circuits, the  $\uparrow$  and  $\perp$  are common across all gates!

# Input – Output Voltage Relation

    


Called voltage transfer characteristic

 

# An Inverter Design (Consider Static Discipline)

 Question: The T1000 model laptop needs gates that satisfy a static discipline with voltage thresholds given below. Does our inverter qualify?




$$V_{OL} = 0.5V \quad V_{IL} = 0.9V$$


$$V_{OH} = 4.5V \quad V_{IH} = 4.1V$$

1:

sender

 

0:

 



1

receiver


0
  
# An Inverter Design (Consider Static Discipline)

Does our inverter satisfy the voltage thresholds for this static discipline?




 
$$\begin{array}{ll} V_{OL} = 0.5V & V_{IL} = 0.9V \\ V_{OH} = 4.5V & V_{IH} = 4.1V \end{array}$$


  
# An Inverter Design (Consider Static Discipline)

Does our inverter satisfy the static discipline for these different thresholds?





$V_{OL} = 0.2V$	$V_{IL} = 0.5V$
$V_{OH} = 5.1V$	$V_{IH} = 4.5V$

$V_{OL} = 0.2V$	$V_{IL} = 0.5V$
$V_{OH} = 5.1V$	$V_{IH} = 4.5V$

# An Inverter Design (Consider Static Discipline)

How about these thresholds?


 
 


$V_{OL} = 0.5V$	$V_{IL} = 1.5V$
$V_{OH} = 4.5V$	$V_{IH} = 3.5V$

$$V_{OL} = 0.5V \quad V_{IL} = 1.5V$$





$$V_{OH} = 4.5V \quad V_{IH} = 3.5V$$
   
# Switch-Resistor (SR) Model – More Accurate




e.g.  $R_{ON} = 5k\Omega$

# SR Model of MOSFET

    




# Using SR Model - Inverter

 

 when the input  $v_{IN}$  is high (and above the threshold  $V_T$ ), the MOSFET is on and displays a resistance  $R_{ON}$  between its D and S terminals, thereby pulling the output voltage lower




when the input is low, the MOSFET is off, and the output is raised to a high value

$$v_{OUT} = V_S \frac{R_{ON}}{R_{ON} + R_L}.$$
 
# Using SR Model - Inverter

The resulting inverter transfer characteristics, assuming  $V_S = 5\text{ V}$ ,  $V_T = 1\text{ V}$ ,  $R_{ON} = 1\text{ k}\Omega$ , and  $R_L = 14\text{ k}\Omega$ , are shown in Figure. Notice that the lowest output voltage of the inverter is no longer  $0\text{ V}$ , rather it is

$$V_S \frac{R_{ON}}{R_{ON} + R_L} = 0.33\text{ V}.$$





Inverter transfer characteristics using the SR model.

 
 
# Static Discipline Criteria

When the  $R_L/R_{ON}$  ratio is 10.

Does our inverter satisfy the voltage thresholds for this static discipline?




$V_{OL} = 0.5V$	$V_{IL} = 0.9V$
$V_{OH} = 4.5V$	$V_{IH} = 4.1V$

  
 
# Static Power – NAND Gate Example

In this case, the output voltage when both inputs are high is given by

$$v_{\text{OUT}} = V_S \frac{2R_{\text{ON}}}{2R_{\text{ON}} + R_L}.$$



SR circuit model for NAND gate.