

# Circuit Theory


Asst. Prof. Görkem SERBES

## AC Sample Questions

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

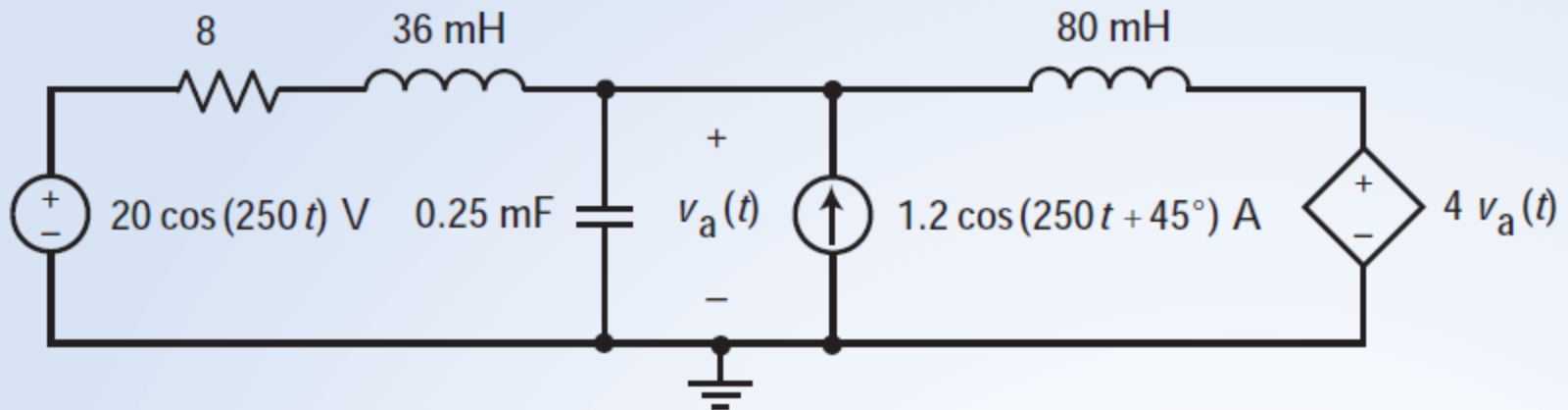
# Sample 1

Determine the voltage  $v_a(t)$  for the circuit shown in Figure 10.6-2.



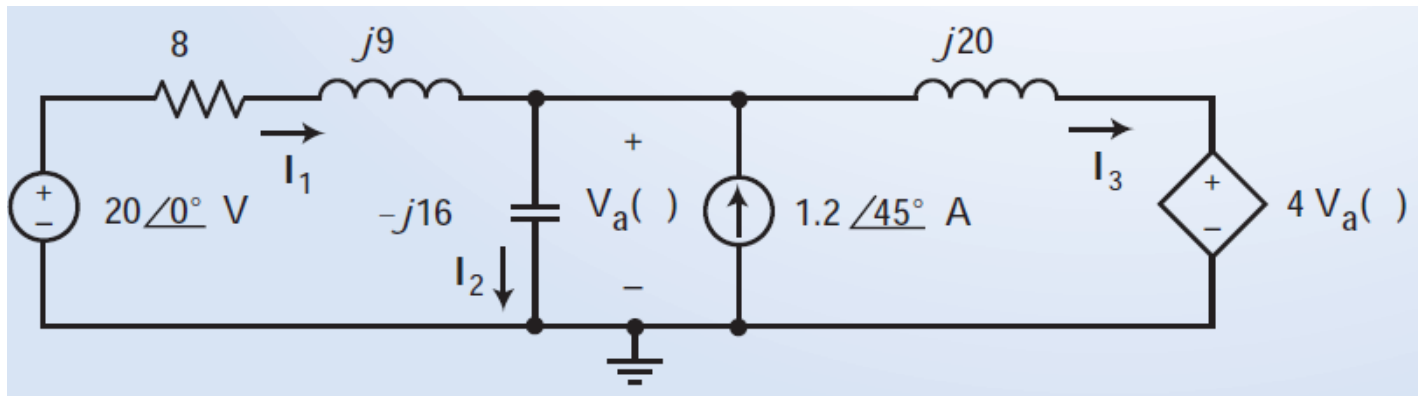
# Solution 1


Represent the circuit in Frequency Domain



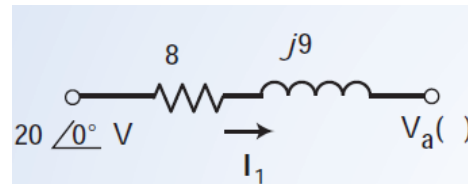
$$\mathbf{I}_1 = \frac{20 \angle 0^\circ - \mathbf{V}_a(\omega)}{8 + j9}$$


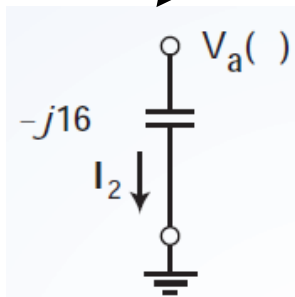
$$\mathbf{I}_2 = \frac{\mathbf{V}_a(\omega) - 0}{-j16} = \frac{\mathbf{V}_a(\omega)}{-j16}$$


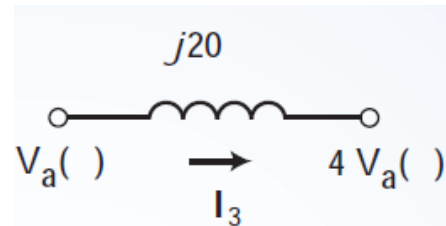
$$\mathbf{I}_3 = \frac{\mathbf{V}_a(\omega) - 4\mathbf{V}_a(\omega)}{j20} = -\frac{3\mathbf{V}_a(\omega)}{j20}$$



# Solution 1

Applying KCL at the top node of the capacitor gives

$$\mathbf{I}_1 + 1.2 \angle 45^\circ = \mathbf{I}_2 + \mathbf{I}_3$$

Substituting for  $\mathbf{I}_1$ ,  $\mathbf{I}_2$ , and  $\mathbf{I}_3$  gives

$$\frac{20 \angle 0^\circ - \mathbf{V}_a(\omega)}{8 + j9} + 1.2 \angle 45^\circ = \frac{\mathbf{V}_a(\omega)}{-j16} + \left( -\frac{3\mathbf{V}_a(\omega)}{j20} \right)$$

Collecting the terms involving  $\mathbf{V}_a(\omega)$  gives

$$\frac{20 \angle 0^\circ}{8 + j9} + 1.2 \angle 45^\circ = \left( \frac{1}{8 + j9} + \frac{1}{-j16} - \frac{3}{j20} \right) \mathbf{V}_a(\omega)$$

Solving for  $\mathbf{V}_a(\omega)$ , perhaps using MATLAB (see Figure 10.6-5), gives

$$\mathbf{V}_a(\omega) = 12.43 \angle -81.2^\circ \text{ V}$$

The corresponding sinusoid is

$$v_a(t) = 12.43 \cos(250t - 81.2^\circ) \text{ V}$$

```
>> Vs = 20;
```

```
>> Is = 1.2*exp(j*45*pi/180);
```

```
>> Va = (Vs/(8+9j) + Is) / (1/(8+9j) + 1/-16j + -3/20j)
```

```
Va =
```

```
1.8929 -12.2816i
```

```
>> abs(Va)
```

```
ans =
```

```
12.4267
```

```
>> angle(Va)*180/pi
```

```
ans =
```


```
-81.2381
```

## Sample 2

The input to the circuit shown in Figure 10.6-10 is the voltage source voltage

$$v_s(t) = 10 \cos(10t) \text{ V}$$

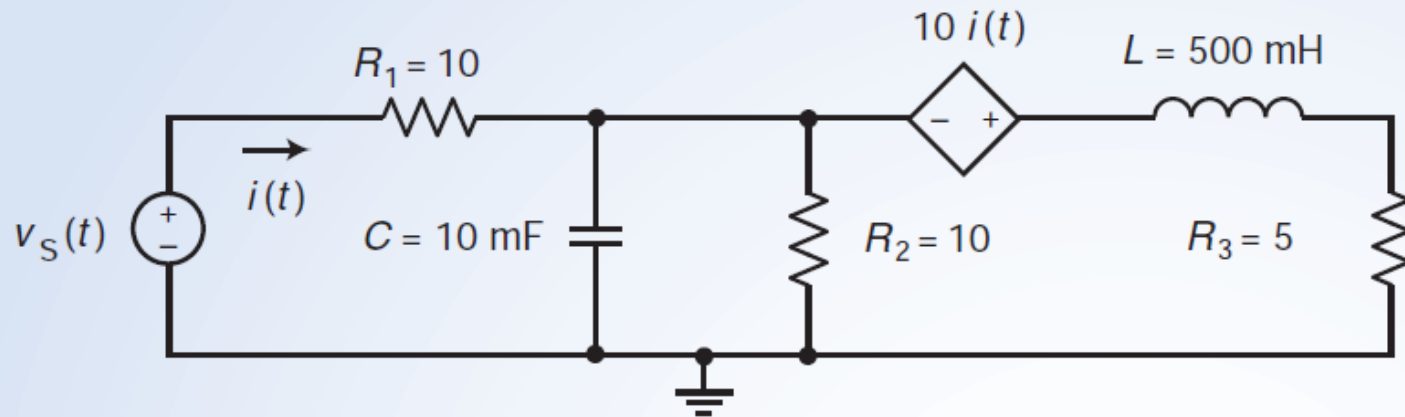The output is the current  $i(t)$  in resistor  $R_1$ . Determine  $i(t)$ .




# Solution 2

First, we will represent the circuit in the frequency domain using phasors and impedances. The impedances of the capacitor and inductor are


$$\mathbf{Z}_C = -j \frac{1}{10(0.010)} = -j10 \, \Omega \text{ and } \mathbf{Z}_L = j10(0.5) = j5 \, \Omega$$

The frequency domain representation of the circuit is shown in Figure 10.6-11. We can analyze this circuit by writing and solving node equations. To simplify this process, we can first replace series and parallel impedances by equivalent impedances as shown in Figure 10.6-12. Impedances  $\mathbf{Z}_1$  and  $\mathbf{Z}_2$  in Figure 10.6-12 are given by
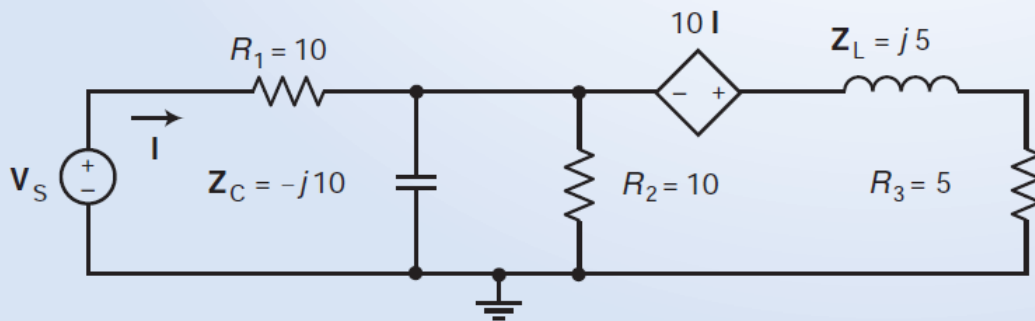
$$\mathbf{Z}_1 = 10 \parallel (-j10) = \frac{10(-j10)}{10 - j10} = 5 - j5 \, \Omega \text{ and } \mathbf{Z}_2 = 5 + j5 \, \Omega$$



# Solution 2

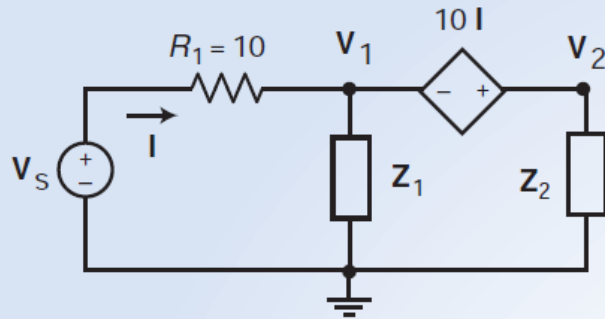

Next, consider the dependent source in Figure 10.6-12. We can use Ohm's law to express the controlling current  $\mathbf{I}$  as

$$\mathbf{I} = \frac{\mathbf{V}_s - \mathbf{V}_1}{R_1} \quad (10.6-7)$$

Using KVL, we can express the dependent source voltage as

$$10\mathbf{I} = \mathbf{V}_2 - \mathbf{V}_1$$

Apply KCL to the supernode identified in Figure 10.6-12 to get

$$\mathbf{I} = \frac{\mathbf{V}_1}{\mathbf{Z}_2} + \frac{\mathbf{V}_2}{\mathbf{Z}_3} = \frac{\mathbf{V}_1}{\mathbf{Z}_2} + \frac{\mathbf{V}_1 + 10\mathbf{I}}{\mathbf{Z}_3} \Rightarrow (\mathbf{Z}_2 + \mathbf{Z}_3)\mathbf{V}_1 + \mathbf{Z}_2(10 - \mathbf{Z}_3)\mathbf{I} = 0 \quad (10.6-8)$$

Organizing Eqs. 10.6-7 and 10.6-8 into matrix form, we get

$$\begin{bmatrix} 1 & R_1 \\ \mathbf{Z}_2 + \mathbf{Z}_3 & \mathbf{Z}_2(10 - \mathbf{Z}_3) \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_s \\ 0 \end{bmatrix}$$

Solving these equations, perhaps using MATLAB, gives

$$\mathbf{V}_1 = 4.4721 \angle 63.4^\circ \text{ V and } \mathbf{I} = 0.89443 \angle -26.6^\circ \text{ A}$$

Back in the time domain, the output current is

$$i(t) = 0.89443 \cos(10t - 26.6^\circ) \text{ A}$$


# Sample 3/Solution 3

The input to the ac circuit shown in Figure 10.6-13 is the voltage source voltage

$$v_s(t) = 125 \cos(500t + 15^\circ) \text{ mV}$$

Determine the output voltage  $v_o(t)$ .

The impedances of the capacitor and inductor are

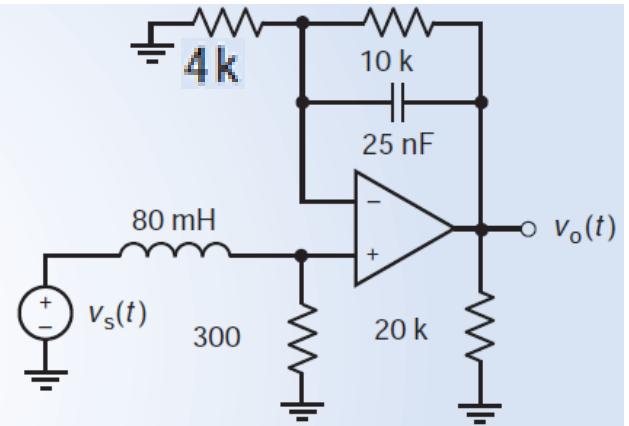

**FIGURE 10.6-13** The circuit considered in Example 10.6-4.

## Solution


The impedances of the capacitor and inductor are

$$\mathbf{Z}_C = -j \frac{1}{5000(25 \times 10^{-9})} = -j8000 \text{ } \Omega \text{ and } \mathbf{Z}_L = j5000(80 \times 10^{-3}) = j400 \text{ } \Omega$$

Figure 10.6-14 show the circuit represented in the frequency domain using phasors and impedances.



# Solution 3

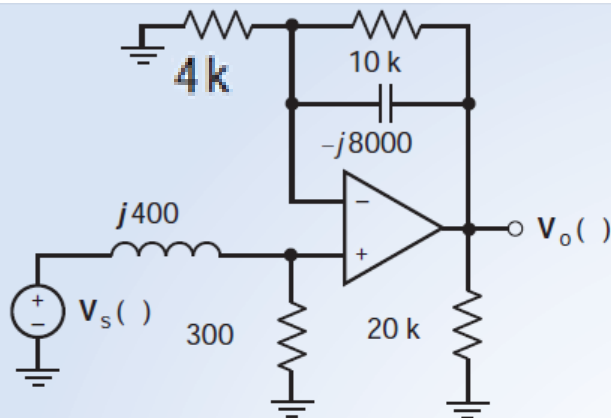

**FIGURE 10.6-14** The frequency domain representation of the circuit from Figure 10.6-13.

Applying KCL at the noninverting node of the op amp, we get

$$\frac{\mathbf{V}_s - \mathbf{V}_a}{j400} = \frac{\mathbf{V}_a}{300} + 0 \Rightarrow \mathbf{V}_s = \mathbf{V}_a \left( 1 + \frac{j400}{300} \right)$$

Solving for  $\mathbf{V}_a$  gives

$$\mathbf{V}_a = \left( \frac{300}{300 + j400} \right) \mathbf{V}_s = \left( 0.6 \angle -53.1^\circ \right) \left( 0.125 \angle 15^\circ \right) = 0.075 \angle -38.1^\circ \text{ V}$$

Next, apply KCL at the inverting node of the op amp to get

$$\frac{\mathbf{V}_a}{4000} + \frac{\mathbf{V}_a - \mathbf{V}_o}{10,000} + \frac{\mathbf{V}_a - \mathbf{V}_o}{-j8000} = 0$$

Multiplying by 80,000 gives

$$0 = 20\mathbf{V}_a + 8(\mathbf{V}_a - \mathbf{V}_o) + j10(\mathbf{V}_a - \mathbf{V}_o)$$

Solving for  $\mathbf{V}_o$  gives


$$\mathbf{V}_o = \frac{28 + j10}{8 + j10} \mathbf{V}_a = \frac{29.73 \angle 19.65^\circ}{12.81 \angle 51.34^\circ} \left( 0.075 \angle -38.1^\circ \right) = 0.174 \angle -69.79^\circ$$

In the time domain, the output voltage is

$$v_o(t) = 174 \cos(500t - 69.79^\circ) \text{ mV}$$
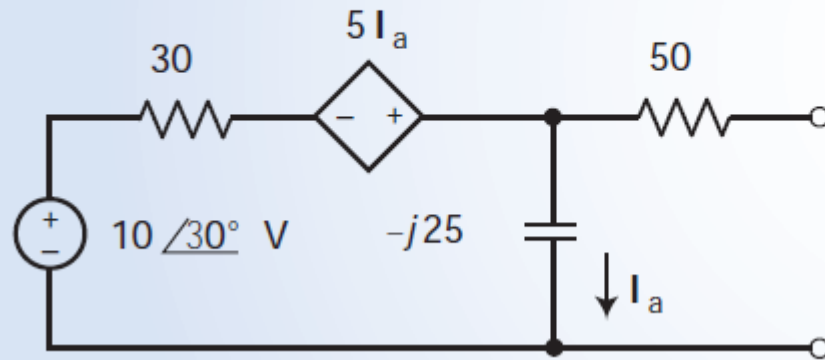
# Sample 4

Find the Norton equivalent circuit of the ac circuit in Figure 10.7-7.



# Solution 4

In Figure 10.7-8, an open circuit is connected across the terminals of circuit. The voltage across that open circuit is the open-circuit voltage  $V_{oc}$ . (Notice that there is no current in the  $50\text{-}\Omega$  impedance due to the open circuit.) Apply KVL to the left mesh to get


$$30\mathbf{I}_a - 5\mathbf{I}_a + (-j25)\mathbf{I}_a = 10\angle 30^\circ$$

Solving for  $\mathbf{I}_a$ , we get

$$\mathbf{I}_a = \frac{10\angle 30^\circ}{25 - j25} = 0.2828\angle 75^\circ \text{ A}$$

Apply KVL to the right mesh to get

$$\mathbf{V}_{oc} = -j25\mathbf{I}_a = (25\angle -90^\circ)0.2828\angle 75^\circ = 7.071\angle -15^\circ \text{ V}$$

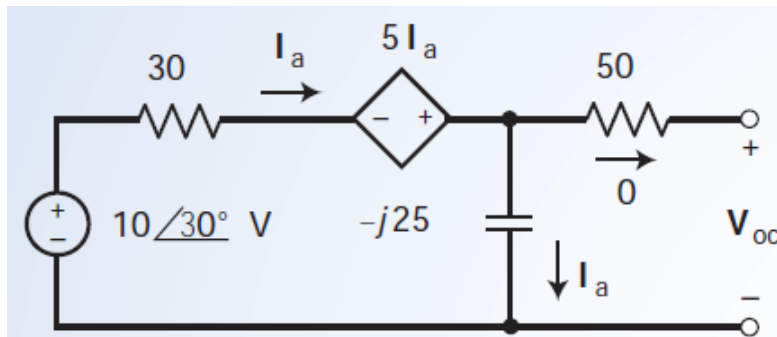

**FIGURE 10.7-8** The circuit used to determine the open circuit voltage of the circuit in Figure 10.7-7.

# Solution 4

Next, we determine the short-circuit current using the circuit shown in Figure 10.7-9. In Figure 10.7-9, a short circuit is connected across the terminals of circuit. The current in that open circuit is the short-circuit current  $\mathbf{I}_{sc}$ . In Figure 10.7-9, the controlling current of the dependent source is related to the mesh currents by

$$\mathbf{I}_a = \mathbf{I}_1 - \mathbf{I}_{sc}$$

Apply KVL to the left mesh to get

$$30\mathbf{I}_1 - 5(\mathbf{I}_1 - \mathbf{I}_{sc}) - j25(\mathbf{I}_1 - \mathbf{I}_{sc}) = 10 \angle 30^\circ$$

Apply KVL to the right mesh to get


$$50\mathbf{I}_{sc} - (-j25)(\mathbf{I}_1 - \mathbf{I}_{sc}) = 0$$

Organize these equations in matrix form to get

$$\begin{bmatrix} 25 - j25 & 5 + j25 \\ j25 & 50 - j25 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_{sc} \end{bmatrix} = \begin{bmatrix} 10 \angle 30^\circ \\ 0 \end{bmatrix}$$

Solving using MATLAB gives

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_{sc} \end{bmatrix} = \begin{bmatrix} 0.2370 \angle 61.4^\circ \\ 0.1060 \angle -2^\circ \end{bmatrix}$$

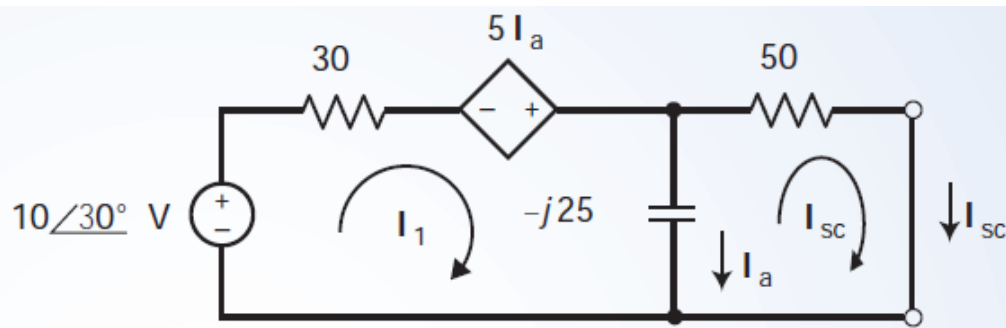


**FIGURE 10.7-9** The circuit used to determine the short circuit current of the circuit in Figure 10.7-7.

# Solution 4

The Thévenin impedance is

$$\mathbf{Z}_t = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{7.071 \angle -15^\circ}{0.1060 \angle -2^\circ} = 66.71 \angle -13^\circ \Omega$$

Finally, Figure 10.7.10 shows the Norton equivalent circuit, which consists of a current source in parallel with an impedance. The current source current is the short-circuit voltage  $\mathbf{I}_{sc}$ . The impedance is the Thévenin impedance  $\mathbf{Z}_t$ .

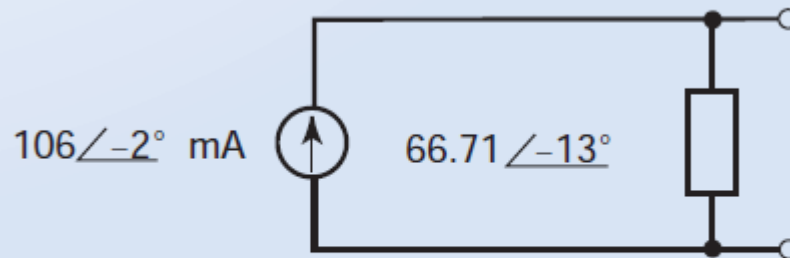

**FIGURE 10.7-10** The Norton equivalent circuit of the circuit in Figure 10.7-7.