

27.10.2023

4. Hafta

①

ELEKTRİKEL ELEMANLARIN MODELLENMESİ

DİRENÇLER (RESISTORS)



$$e_R(t) = i(t) \cdot R$$


$$i(t) = \frac{e_R(t)}{R}$$

$$\frac{e_R(t)}{i_R(t)} = R$$

$$\frac{E_R(s)}{I_R(s)} = R \rightarrow \text{impedance}$$

BOBIN (INDUCTOR)
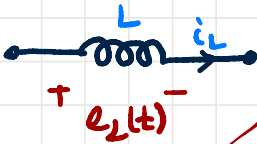
$$\phi = L \cdot i \rightarrow \frac{d\phi}{dt} = L \frac{di}{dt} \rightarrow e = L \frac{di}{dt}$$



$$e_L(t) = L \cdot \frac{di_L(t)}{dt}$$


$$i_L(t) = \frac{1}{L} \int_0^t e_L(t) dt + i_L(0)$$

$$E_L(s) = L s I_L(s)$$

$$\frac{E_L(s)}{I_L(s)} = L s \rightarrow \text{impedance}$$

KAPASİTÖR (CAPACITOR)
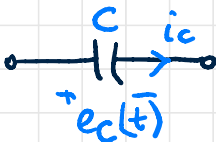
$$q = C \cdot e \rightarrow \frac{dq}{dt} = C \cdot \frac{de}{dt}$$




$$i_C(t) = C \cdot \frac{de_C(t)}{dt}$$

$$e_C(t) = \frac{1}{C} \int_0^t i_C(t) dt + e_C(0)$$

$$I_C(s) = C s E_C(s) \rightarrow$$

$$\frac{E_C(s)}{I_C(s)} = \frac{1}{C s} \rightarrow \text{impedance}$$


KIRCHHOFF'UN AKIM KANUNU

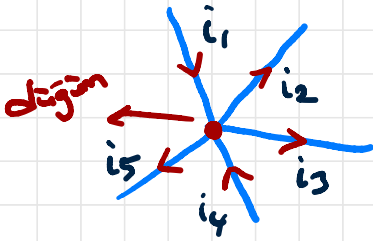

$$-i_1 + i_2 + i_3 - i_4 + i_5 = 0$$


$$i_1 + i_4 = i_2 + i_3 + i_5$$

KIRCHHOFF'UN GERİLİM KANUNU

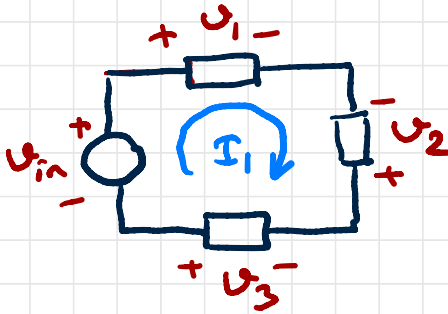

$$-v_{in} + v_1 - v_2 - v_3 = 0$$

KAYNAKLAR

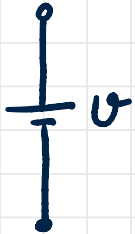


zamanla bağılı değil
(DC)
 $\int \frac{v}{s}$



zamanla bağılı
 $\int v(s)$




zamanla bağılı değil
 $\int \frac{i}{s}$

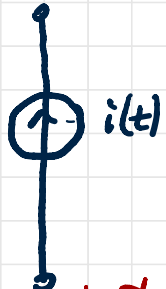

zamanla bağılı
 $\int i(s)$

Örnek:

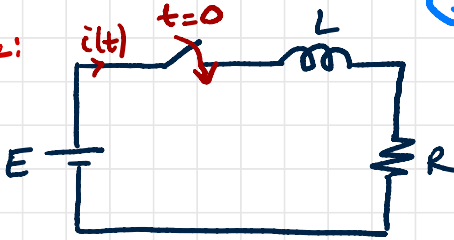


③

$$i(0) = 0$$

Anahtar $t=0$ anında
kapatılırsa $i(t) = ?$

Çözüm:

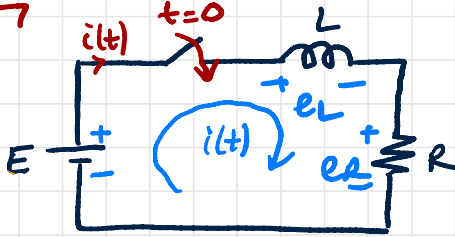

$$-E + e_L(t) + e_R(t) = 0$$

$$-E + L \frac{di(t)}{dt} + i(t) \cdot R = 0$$

$\mathcal{L} \downarrow$

$$-\frac{E}{s} + L \left[sI(s) - \cancel{i(0)} \right] + I(s) \cdot R = 0$$

$$LsI(s) + RI(s) = \frac{E}{s} \Rightarrow I(s) = \frac{E}{s} \cdot \frac{1}{Ls + R}$$

$$\mathcal{L}^{-1}\{I(s)\} = \mathcal{L}^{-1}\left\{ \frac{E}{s} \cdot \frac{1}{Ls + R} \right\}$$

$$\frac{E}{s} \cdot \frac{1}{Ls + R} = \frac{A}{s} + \frac{B}{Ls + R}$$

$$A(Ls + R) + Bs = E \quad \begin{array}{l} \nearrow s=0 \Rightarrow A = \frac{E}{R} \\ \searrow s = -\frac{R}{L} \Rightarrow B = -\frac{EL}{R} \end{array}$$


$$\mathcal{L}^{-1} \left\{ \frac{E}{s} \frac{1}{Ls+R} = \frac{A}{s} + \frac{B}{Ls+R} \right\} = \mathcal{L}^{-1} \left\{ \frac{E}{Rs} + \frac{-EL/R}{Ls+R} \right\}$$

$$\mathcal{L}^{-1} \left\{ \frac{E}{Rs} \right\} = \frac{E}{R}$$

$$\mathcal{L}^{-1} \left\{ \frac{-EL/R}{Ls+R} \right\} = \mathcal{L}^{-1} \left\{ -\frac{E}{R} \frac{L}{Ls+R} = -\frac{E}{R} \frac{1}{s+R/L} \right\} = -\frac{E}{R} e^{-Rt/L}$$

$$\mathcal{L}^{-1} \{ I(s) \} = i(t) = \frac{E}{R} - \frac{E}{R} e^{-Rt/L}$$

Or:

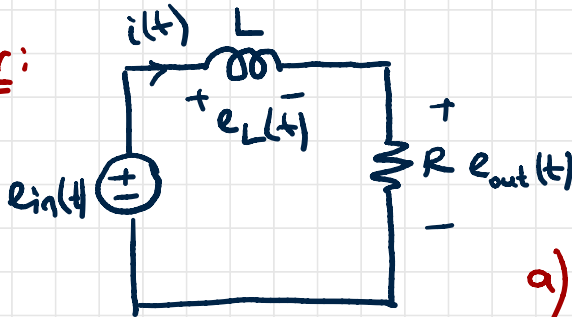


Transfer funk.

bulunur:

a) $\frac{E_{out}(s)}{E_{in}(s)} = ?$

b) $\frac{E_{in}(s)}{I(s)} = ?$


Çözüm:

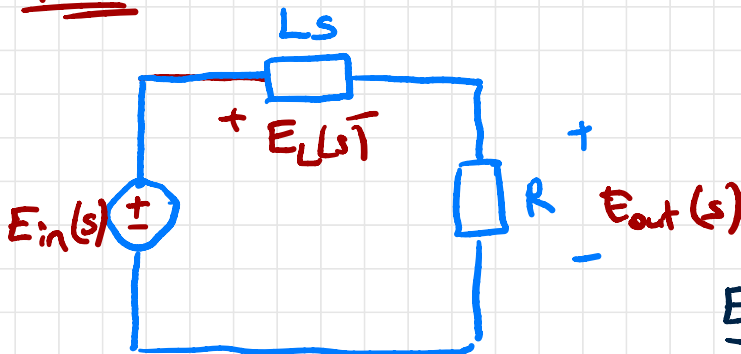

$$\frac{E_{out}(s)}{E_{in}(s)} = \frac{R}{Ls+R}$$

$$\frac{E_L(s)}{E_{in}(s)} = \frac{Ls}{Ls+R}$$

⑤

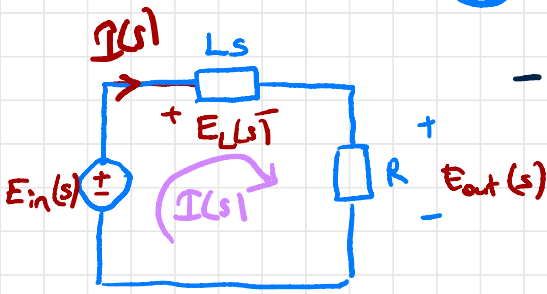

$$-E_{in}(s) + I(s) \cdot Ls + R \cdot I(s) = 0$$

$$E_{in}(s) = I(s) \cdot Ls + R \cdot I(s)$$

$$E_{out}(s) = R \cdot I(s)$$

$$\frac{E_{out}(s)}{E_{in}(s)} = \frac{R \cdot \cancel{I(s)}}{\cancel{I(s)}(Ls + R)} = \frac{R}{Ls + R}$$


$$b) \frac{E_{in}(s)}{I(s)} = Ls + R$$

$$b) -E_{in}(s) + I(s)Ls + R \cdot I(s) = 0$$

$$E_{in}(s) = Ls I(s) + R I(s)$$


$$\frac{E_{in}(s)}{I(s)} = Ls + R$$

Örnek:

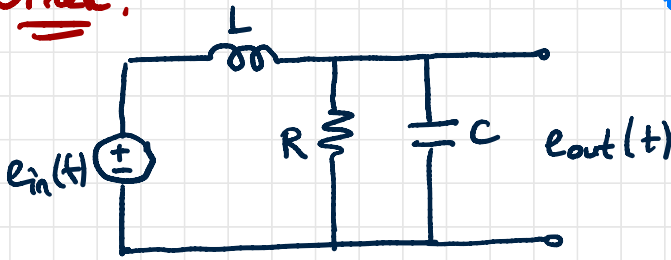

$$\begin{aligned} i(0) &= 0 \\ e(0) &= 0 \end{aligned}$$


$$\frac{E_{out}(s)}{E_{in}(s)} = ?$$

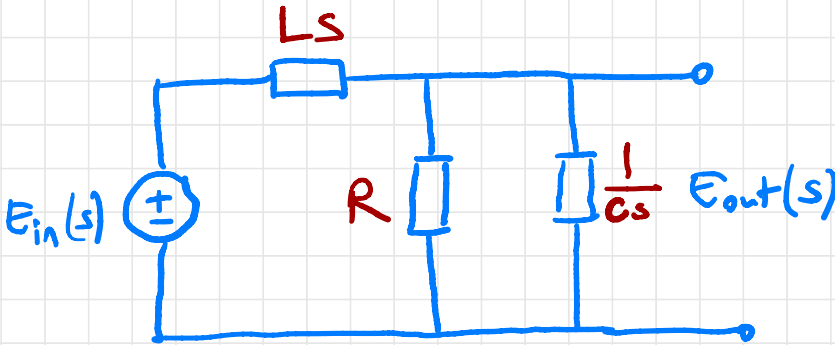


$$\frac{E_{out}(s)}{E_{in}(s)} = \frac{\frac{1}{Cs} \parallel R}{Ls + \left(R \parallel \frac{1}{Cs} \right)} = \frac{\frac{\frac{1}{Cs} \cdot R}{\frac{1}{Cs} + R}}{Ls + \left(\frac{\frac{1}{Cs} \cdot R}{\frac{1}{Cs} + R} \right)}$$

$$\frac{\frac{1}{Cs} \cdot R}{\frac{1}{Cs} + R} = \frac{R/Cs}{(1+RCs)/Cs} = \frac{R}{1+RCs}$$
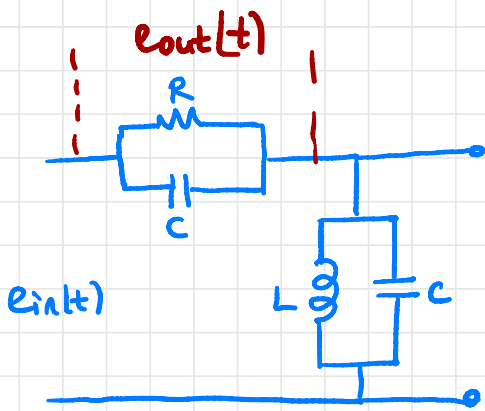
$$= \frac{\frac{R}{1+RCs}}{Ls + \frac{R}{1+RCs}} = \frac{R}{Ls + LRCs^2 + R}$$



$$\frac{E_{out}(s)}{E_{in}(s)} = ?$$

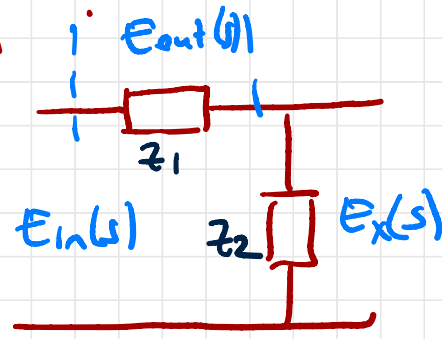

$$z_1 = R \parallel \frac{1}{Cs}$$

$$z_2 = Ls \parallel \frac{1}{Cs}$$

$$\frac{E_{out}(s)}{E_{in}(s)} = \frac{z_1}{z_1 + z_2}$$

03.11.2023


5. HAFTA

* Op-Amp T.F

* Blok Diyagram İntegrasyonu


İK - (OP-Amp)

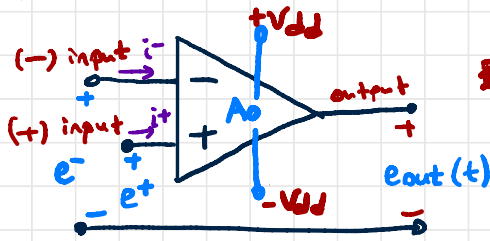İŞLEMSEL KUVVETLENDİRİCİLERİN TRANSFER FON



$$e_{out} = A_o(e^+ - e^-)$$

Kazanç
idealde $A_o \rightarrow \infty$

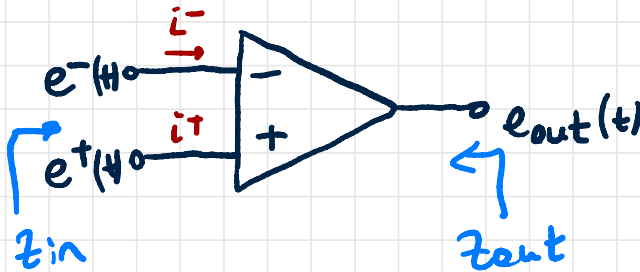

(+) ve (-) (inputs) girişlere
ler atılır sıfırdır.

(idealde) $i^- = i^+ = 0$
 $A_o \rightarrow \infty$

z_{in} : Giriş Empedansı $(z = R \pm jX)$
Empedans Reaktans
Resistans

Op-Amp'in Giriş Empedansı $z_{in} = \infty$

Op-Amp'in Çıkış Empedansı $z_{out} = 0$


$$\frac{E_{out}(s)}{E_{in}(s)} = \text{Kazanç (Gain)} \quad \left. \vphantom{\frac{E_{out}(s)}{E_{in}(s)}} \right\} \text{Transfer Fonksiyonu}$$

$$\frac{e_{in}(t)}{e_{out}(t)} = ? \quad \text{TF} \quad \frac{E_{in}(s)}{E_{out}(s)}$$

TF


TF

Ün:

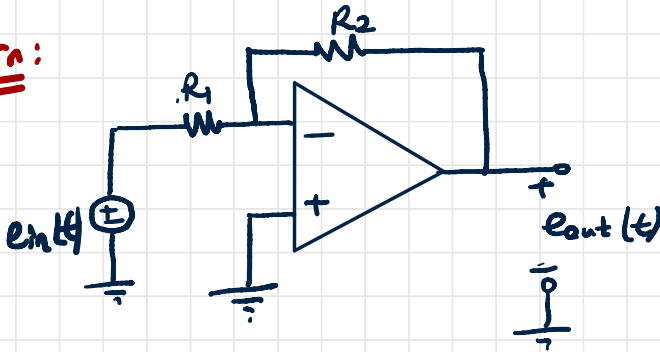

Korrektur?

$$\frac{E_{out}(s)}{E_{in}(s)} = ?$$

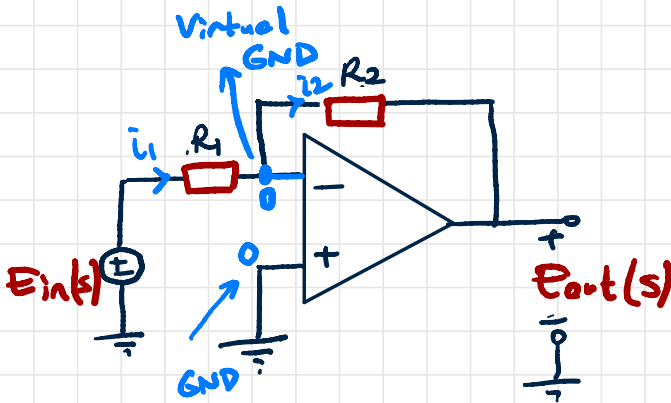


$$Z_1 = R_1$$

$$Z_2 = R_2$$

$$i_1 - i_2 = 0$$



$$\frac{E_{in} - 0}{R_1} - \frac{0 - E_{out}}{R_2} = 0 \rightarrow \frac{E_{in}}{R_1} + \frac{E_{out}}{R_2} = 0 \rightarrow \frac{E_{out}(s)}{E_{in}(s)} = -\frac{R_2}{R_1}$$

$\hat{U}_{21}$:

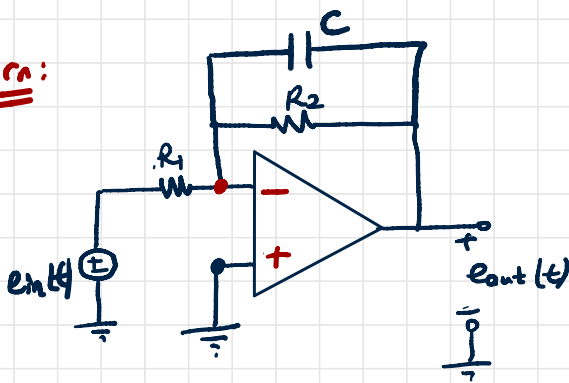

Kernsch?

$$\frac{E_{out}(s)}{E_{in}(s)} = ?$$

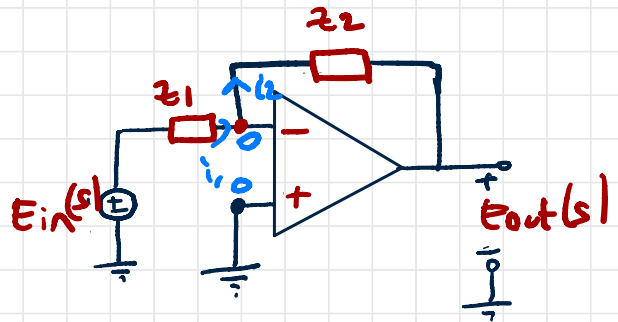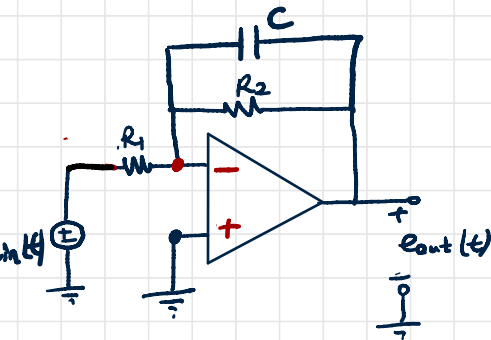



$$z_1 = R_1$$

$$z_2 = R_2 \parallel \frac{1}{sC} = \frac{R_2 \cdot \frac{1}{sC}}{R_2 + \frac{1}{sC}} = \frac{R_2/sC}{(R_2 sC + 1)/sC} = \frac{R_2}{R_2 sC + 1}$$

$$\hat{i}_1 - \hat{i}_2 = 0 \Rightarrow \frac{E_{in} - 0}{z_1} - \frac{0 - E_{out}}{z_2} = 0$$


$$\frac{E_{in}}{z_1} = \frac{-E_{out}}{z_2} \Rightarrow \frac{E_{out}}{E_{in}} = \frac{-z_2}{z_1} = \frac{-\frac{R_2}{R_2 sC + 1}}{R_1} = \underline{\underline{-\frac{R_2}{R_1} \frac{1}{R_2 sC + 1}}}$$

110°

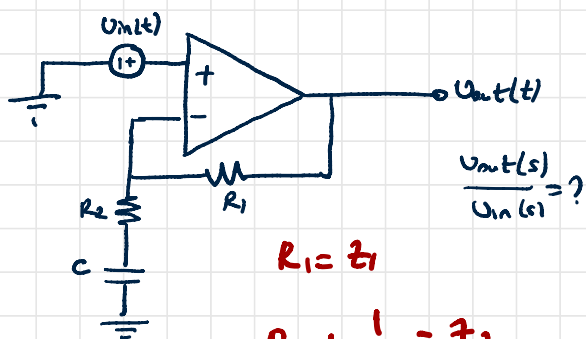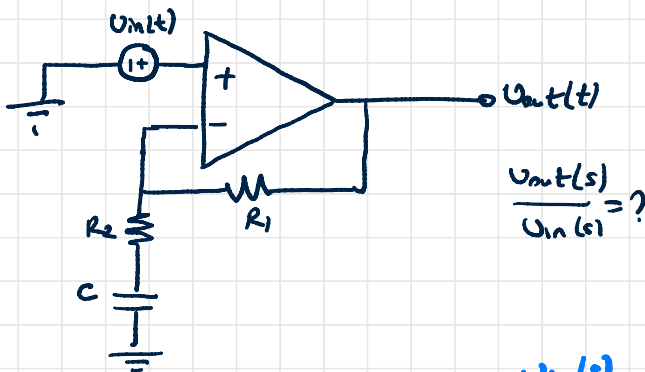

$$R_1 = z_1$$


$$R_2 + \frac{1}{sC} = z_2$$

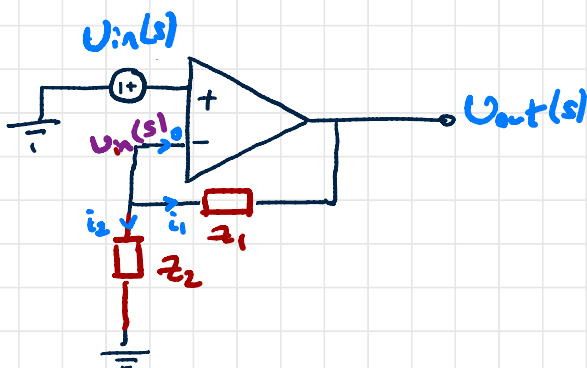

$$\left. \begin{aligned} i_2 + i_1 &= 0 \\ \frac{U_{in}}{z_2} + \frac{U_{in} - U_{out}}{z_1} &= 0 \end{aligned} \right\} \frac{U_{in}}{(R_2 sC + 1)/sC} + \frac{U_{in}}{R_1} = \frac{U_{out}}{R_1}$$

$$\left. \begin{aligned} \frac{sC U_{in} \cdot R_1}{(R_2 sC + 1) \cancel{R_1}} + \frac{(R_2 sC + 1) U_{in}}{(R_2 sC + 1) \cancel{R_1}} &= \frac{U_{out}}{\cancel{R_1}} \end{aligned} \right\} \frac{U_{out}}{U_{in}} = \frac{R_2 sC + 1 + R_1 sC}{R_2 sC + 1}$$

BLOK DİYAGRAMLARI (BLOCK DIAGRAMS)

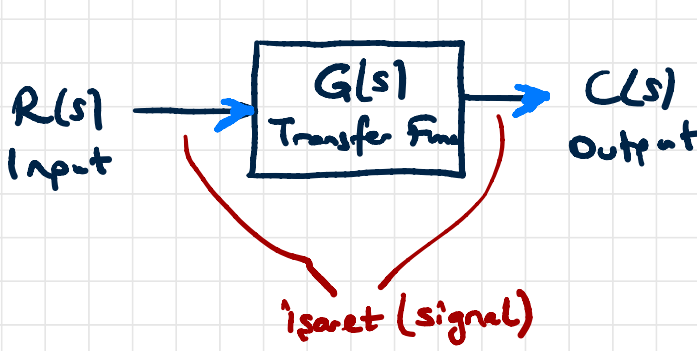

$$C(s) = R(s) \cdot G(s)$$

$G(s) \rightarrow$ Transfer fonk


$$G(s) = \frac{C(s)}{R(s)}$$

Blok Diyagramlar aşağıdaki elementlerden oluşur ?


1) Bloklardan

2) Oklardan

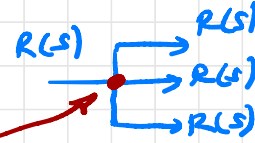3) Ayrım Noktası (Take off points / Pick off points)




4) Toplam Noktası (summing point)

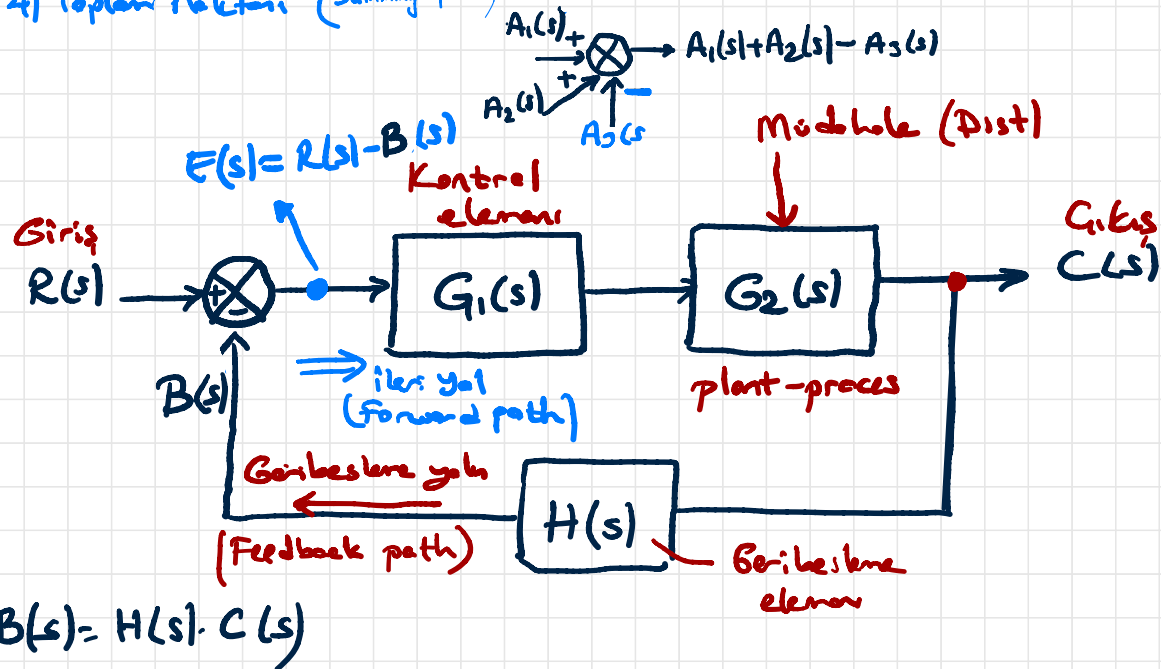

$$B(s) = H(s) \cdot C(s)$$

Kapalı Çevrim Negatif Geri Besleme

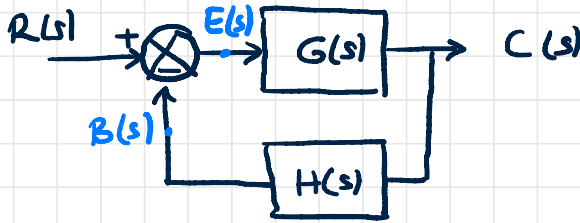


$G(s)$: Transfer Fonksiyonu = İleri Yol Transfer Fonk.

$H(s)$: Geri besleme Transfer Fonksiyonu

$G(s) \cdot H(s)$: Açık-Çevrim Transfer Fonk.

$\frac{C(s)}{R(s)}$ = Kapalı-Çevrim Transfer Fonksiyonu

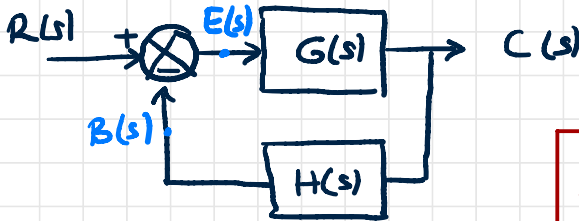$\frac{C(s)}{E(s)}$ = İleri-Yol Transfer fonksiyonu = $G(s)$



$$\frac{C(s)}{R(s)} = ?$$

$$\frac{C(s)}{R(s)} = \frac{G(s)}{1 + G(s) \cdot H(s)}$$

$$C(s) = G(s) \cdot E(s) \quad \& \quad B(s) = C(s) \cdot H(s)$$

$$E(s) = R(s) - B(s) = R(s) - C(s) \cdot H(s)$$

$$C(s) = G(s) \cdot [R(s) - C(s) \cdot H(s)]$$

$$C(s) = G(s) \cdot R(s) - G(s) \cdot C(s) \cdot H(s)$$

$$C(s) + G(s) \cdot C(s) \cdot H(s) = G(s) \cdot R(s)$$

$$C(s) (1 + G(s) H(s)) = G(s) R(s) \quad \left. \begin{array}{l} \frac{C(s)}{R(s)} = \frac{G(s)}{1 + G(s) H(s)} \\ \text{Karakteristik Denklemin} \\ \text{(Characteristic Equation)} \end{array} \right\}$$



Blak Diyagramların Sadeleştirilmesi:

► Seri Bağlı




$$C(s) = R(s) \cdot G_1(s) \cdot G_2(s) \cdot G_3(s)$$

► Paralel Bağlı

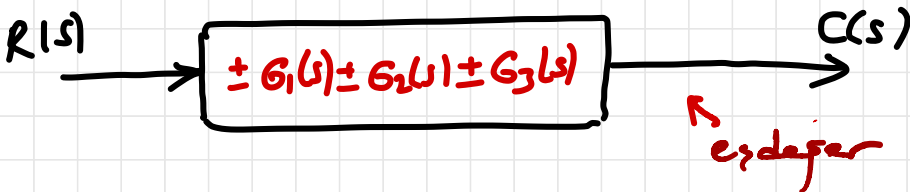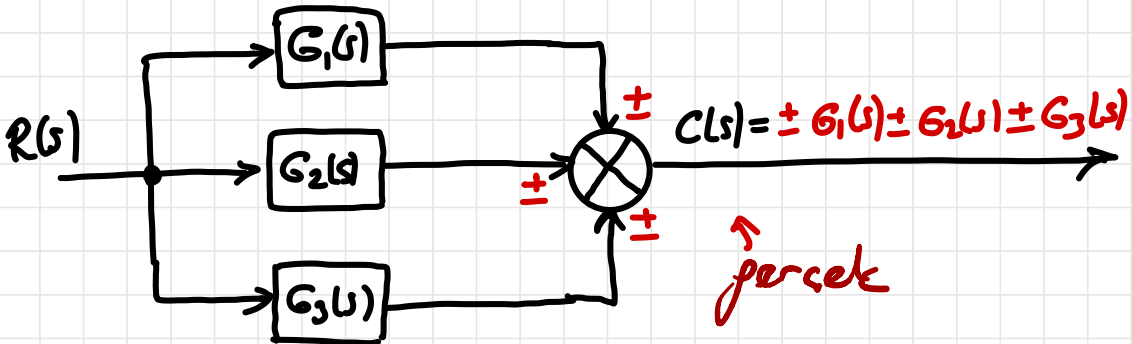

Toplama Noktası Arithmetiği


Aşağıdaki ifadeler eşdeğerler:

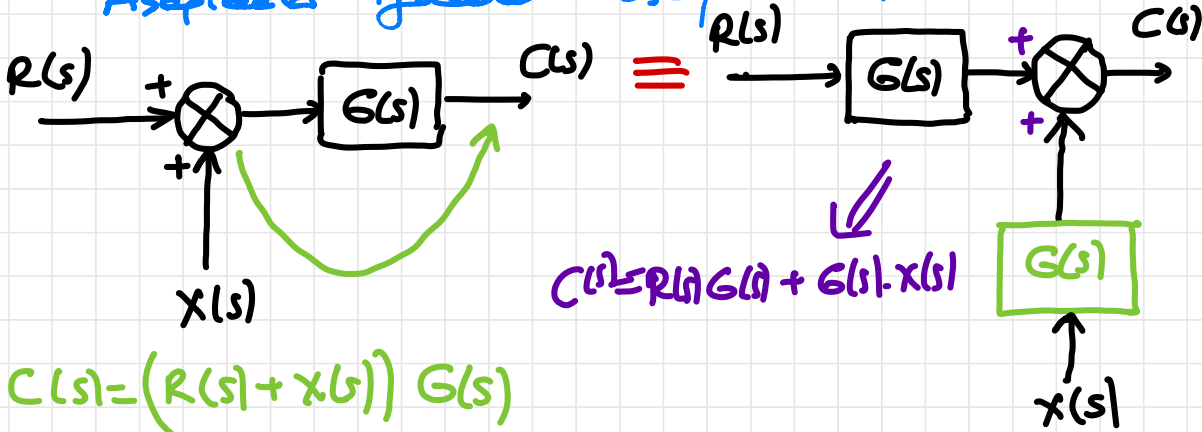

$$C(s) = R(s)G(s) + G(s) \cdot X(s)$$

$$C(s) = (R(s) + X(s)) G(s)$$

$$= R(s) \cdot G(s) + X(s) \cdot G(s)$$




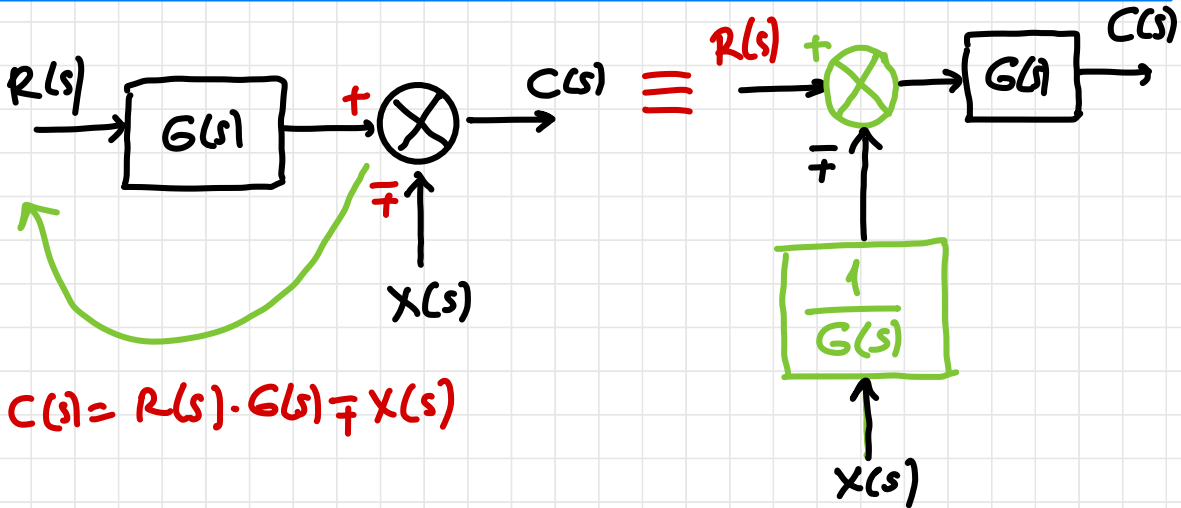


$$C(s) = R(s) \cdot G(s) \mp X(s)$$

$$\left[R(s) \mp \frac{X(s)}{G(s)} \right] G(s) = C(s)$$

$$R(s) \cdot G(s) \mp X(s) = C(s)$$

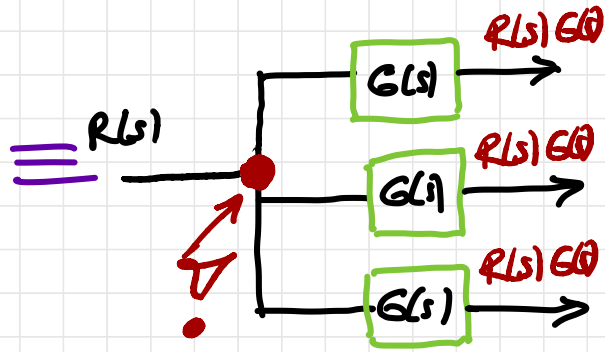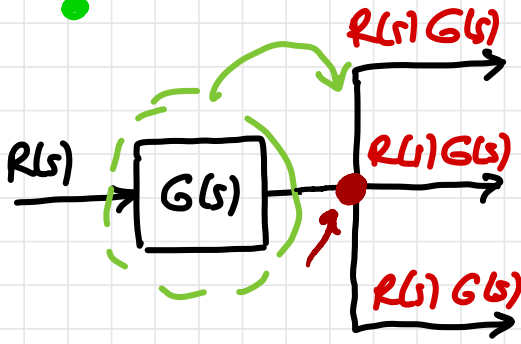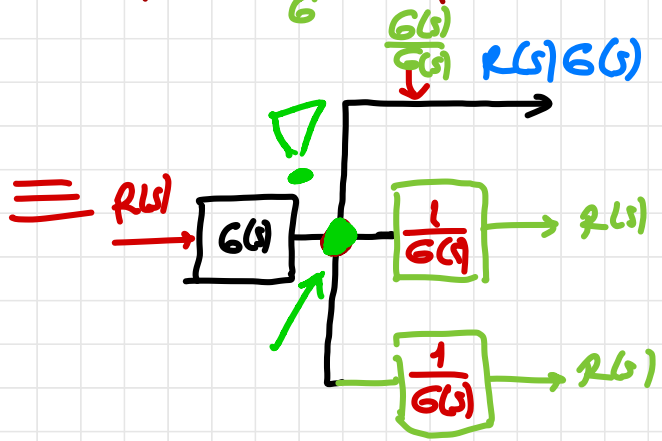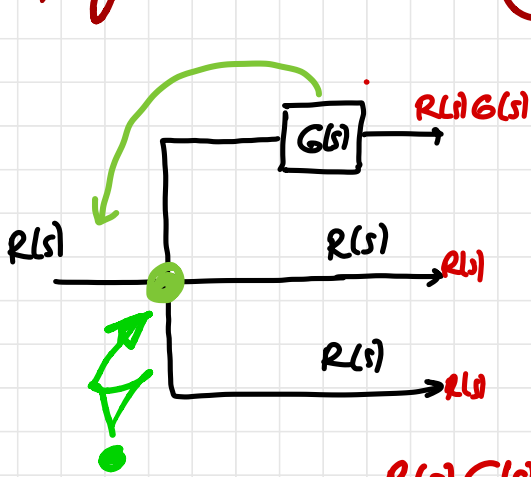Ayrım Noktaları (Pick-off Points) işlemleri




Görüldüğü gibi $G(s)$ bloğu ayrım noktasının sağına gelince her bir işarete $G(s)$ eklenir.

Block diagram

Transfer Function


Consists of Blocks

Can be reduced

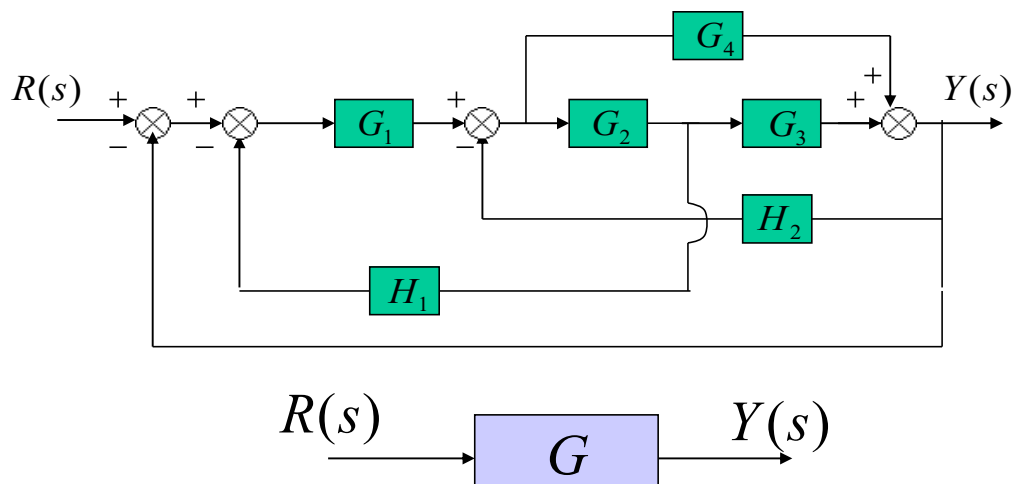


Reduction techniques

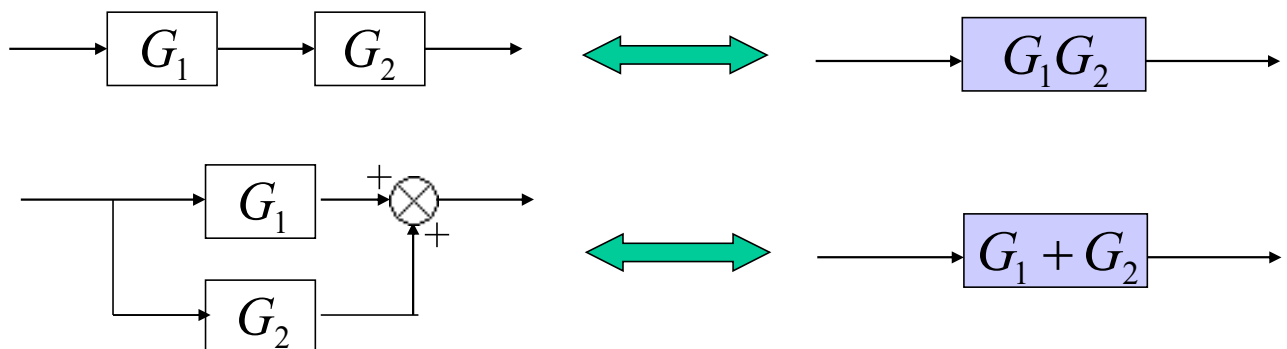
1. Combining blocks in cascade or in parallel




2. Moving a summing point behind a block

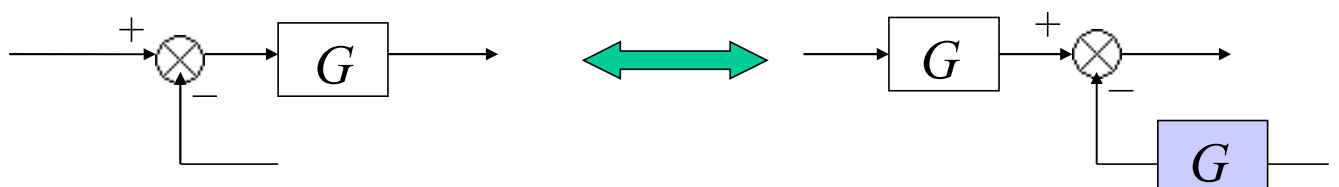

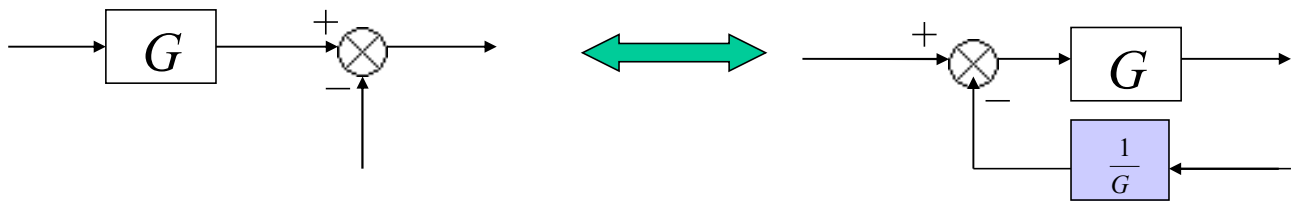
3. Moving a summing point ahead of a block





4. Moving a pickoff point behind a block

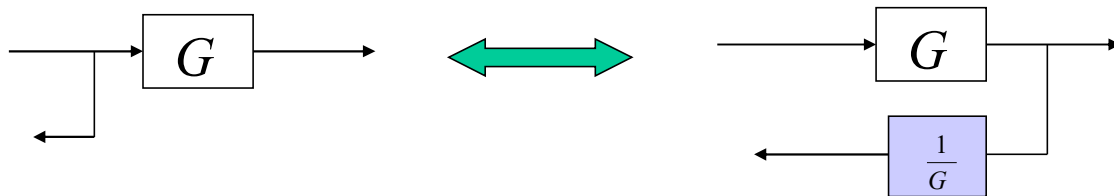

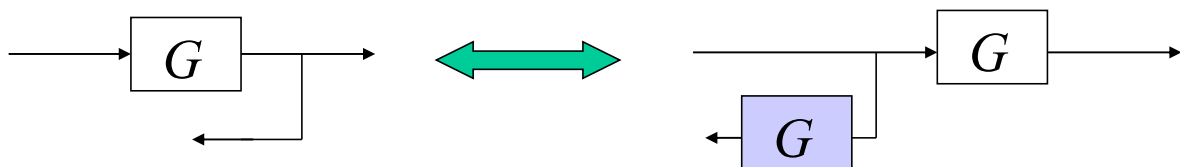
5. Moving a pickoff point ahead of a block



6. Eliminating a feedback loop

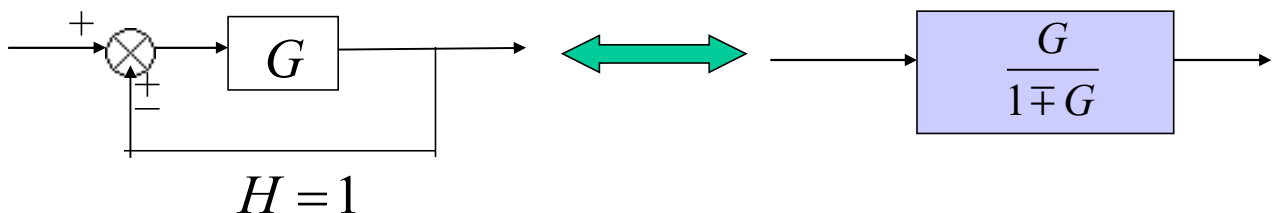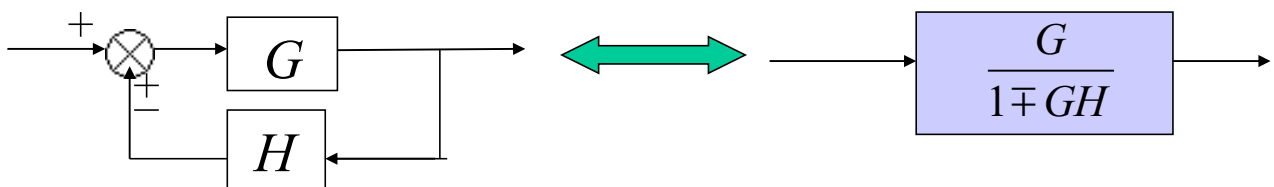



7. Swap with two neighboring summing points

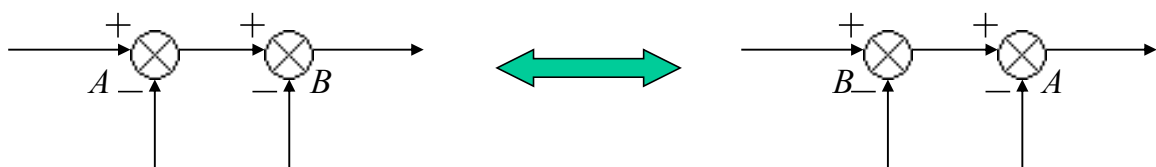

Example 1


Find the transfer function of the following block diagrams


(a)

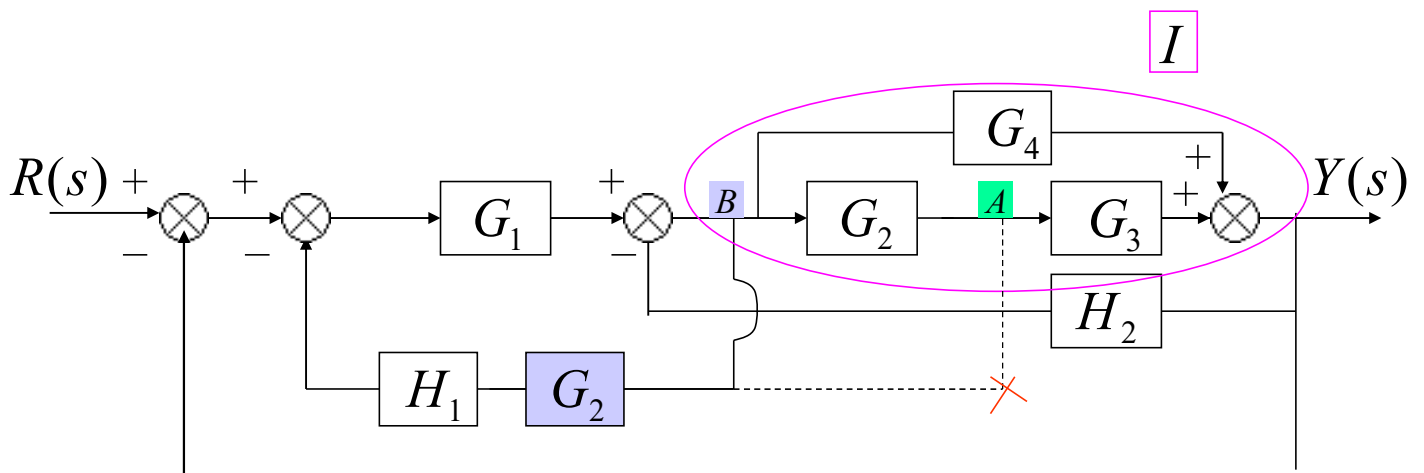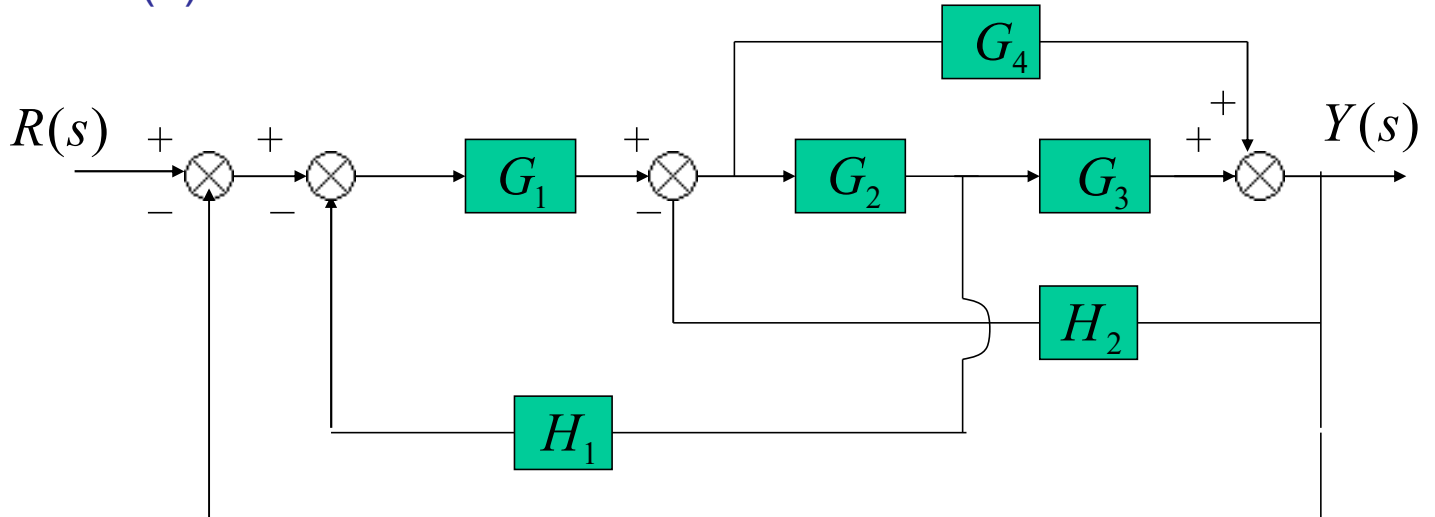


Solution:

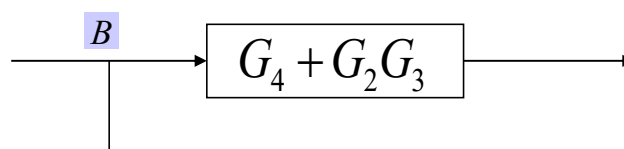1. Moving pickoff point A ahead of block G_2
2. Eliminate loop I & simplify




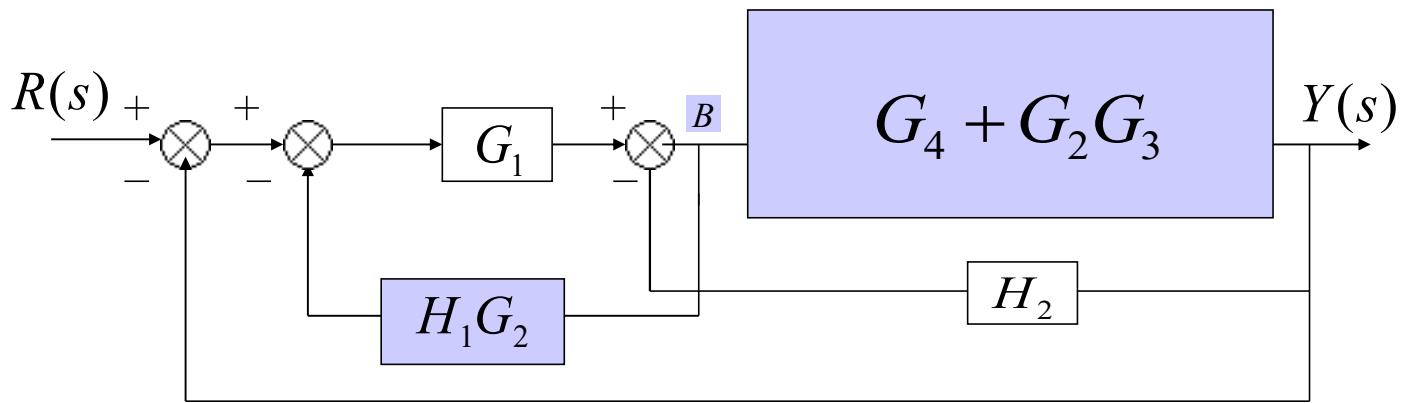

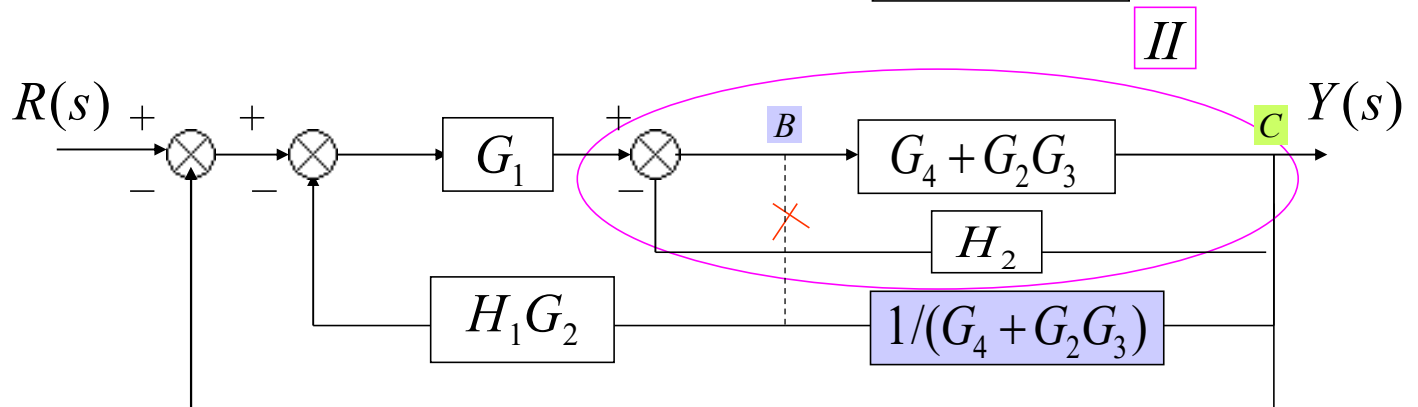
3. Moving pickoff point B behind block $G_4 + G_2G_3$



4. Eliminate loop III

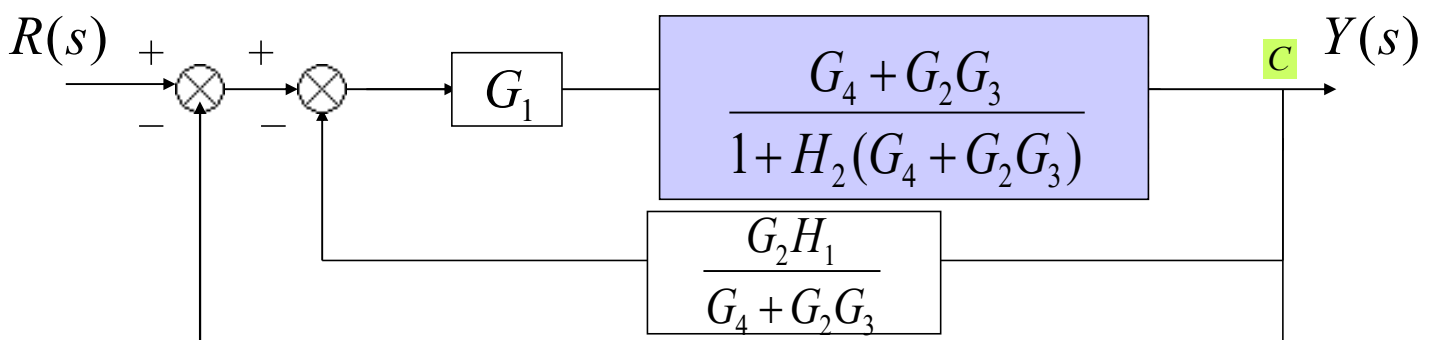


Using rule 6

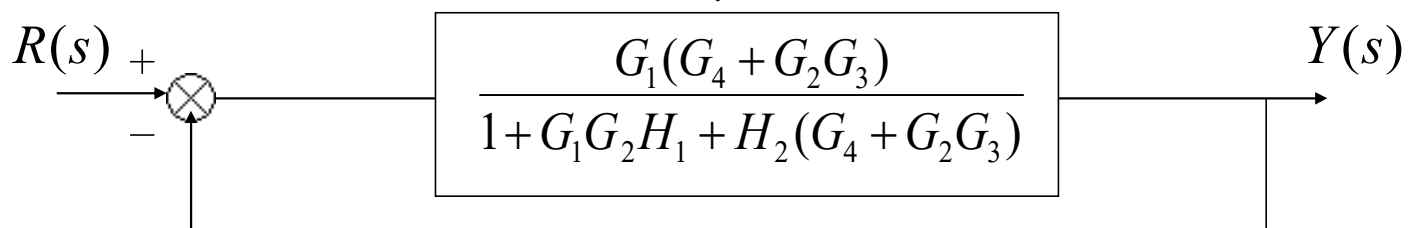


$$T(s) = \frac{Y(s)}{R(s)} = \frac{G_1(G_4 + G_2G_3)}{1 + G_1G_2H_1 + H_2(G_4 + G_2G_3) + G_1(G_4 + G_2G_3)}$$

(b)

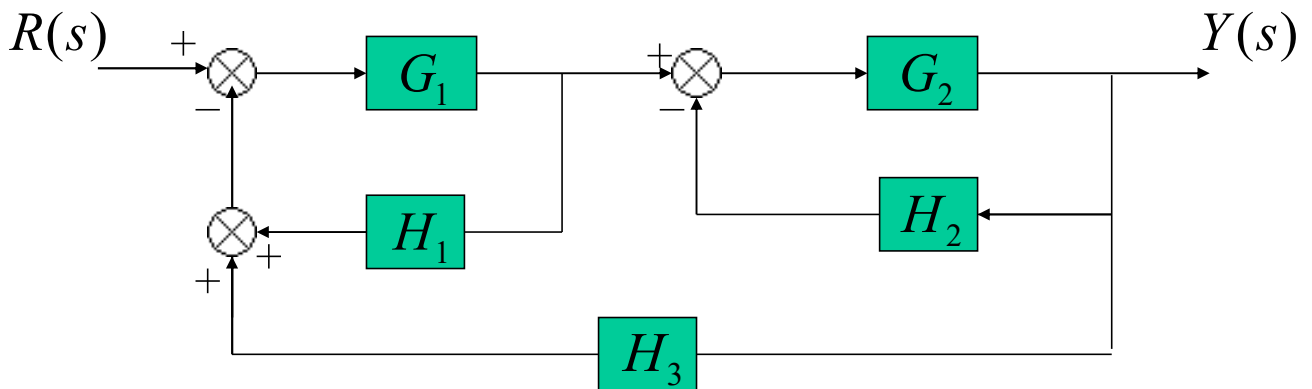


Solution:


1. Eliminate loop I

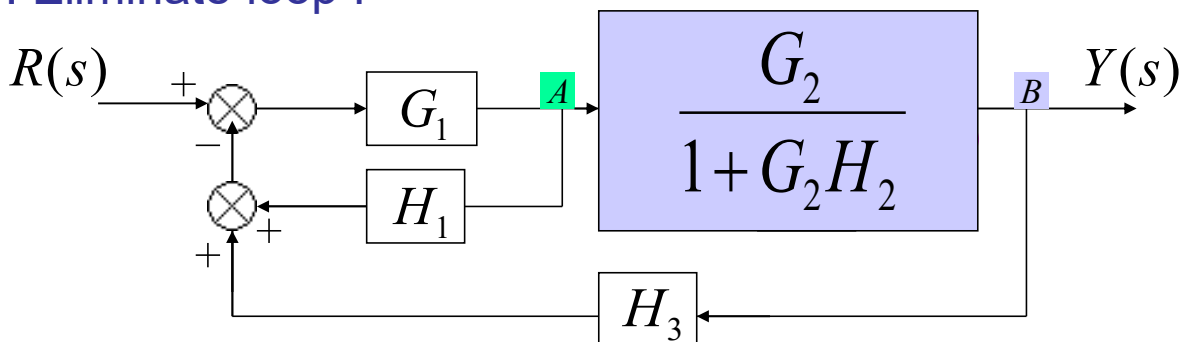

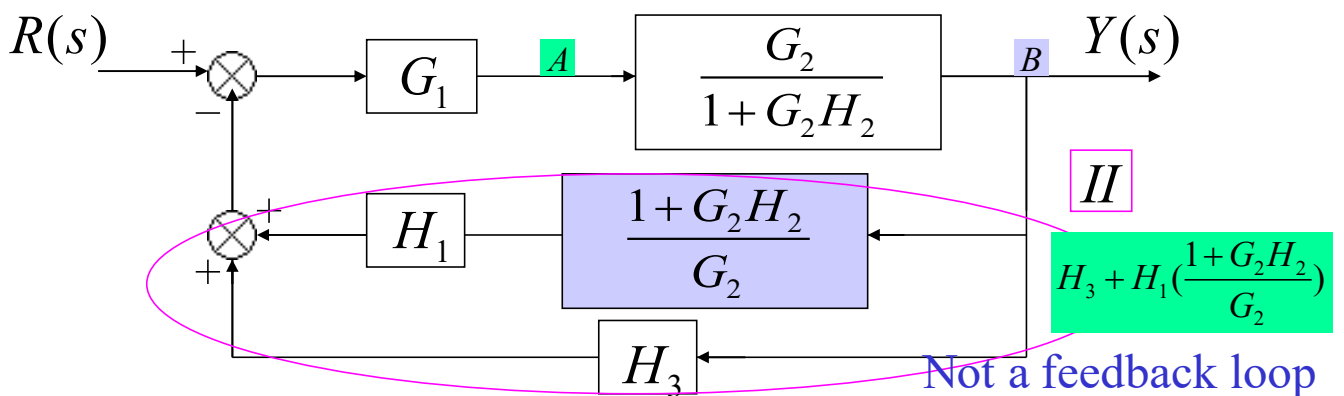2. Moving pickoff point A behind block $\frac{G_2}{1 + G_2H_2}$




3. Eliminate loop II

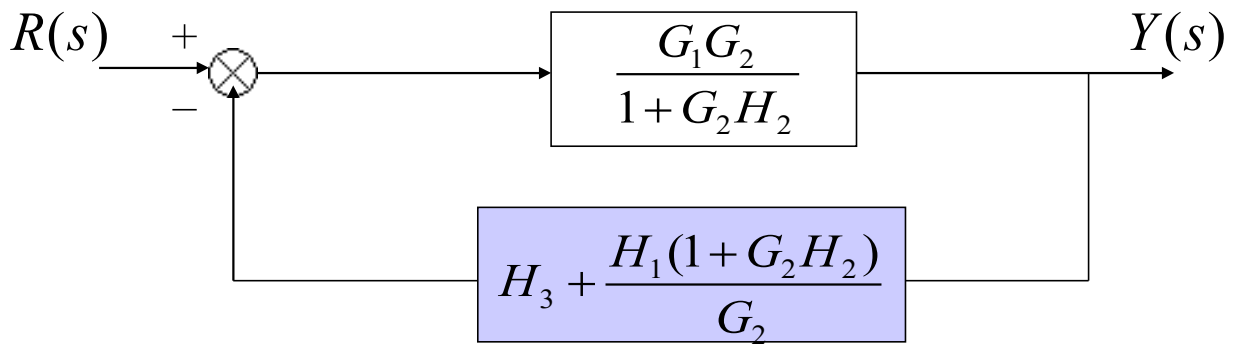

↓ Using rule 6


$$T(s) = \frac{Y(s)}{R(s)} = \frac{G_1 G_2}{1 + G_2 H_2 + G_1 G_2 H_3 + G_1 H_1 + G_1 G_2 H_1 H_2}$$

(c)

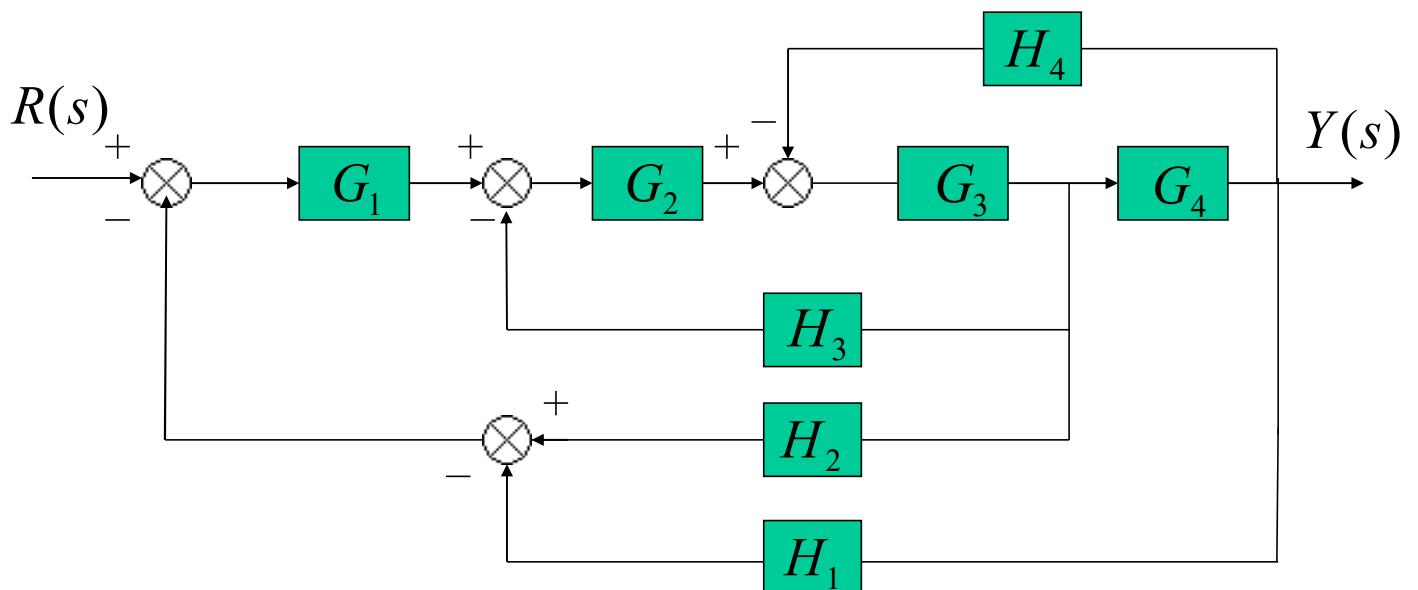


Solution:

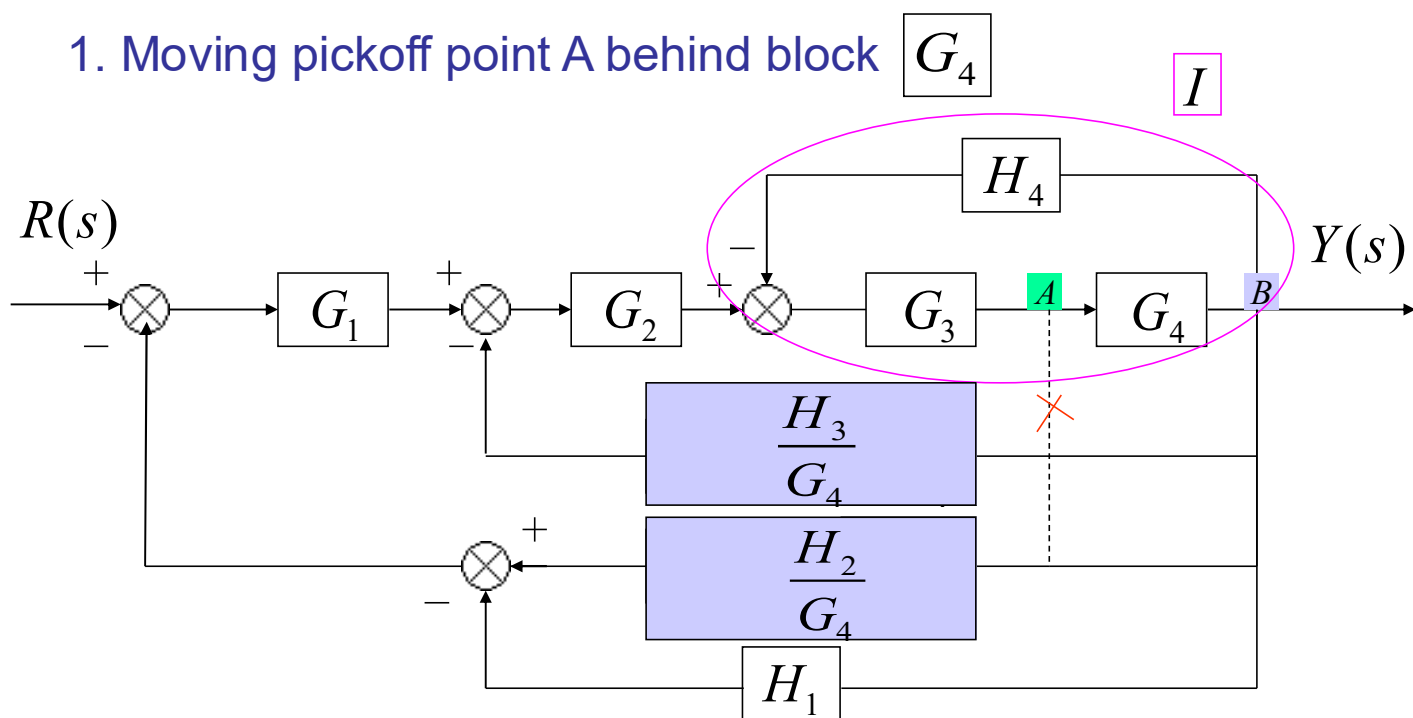1. Moving pickoff point A behind block G_4



2. Eliminate loop I and Simplify

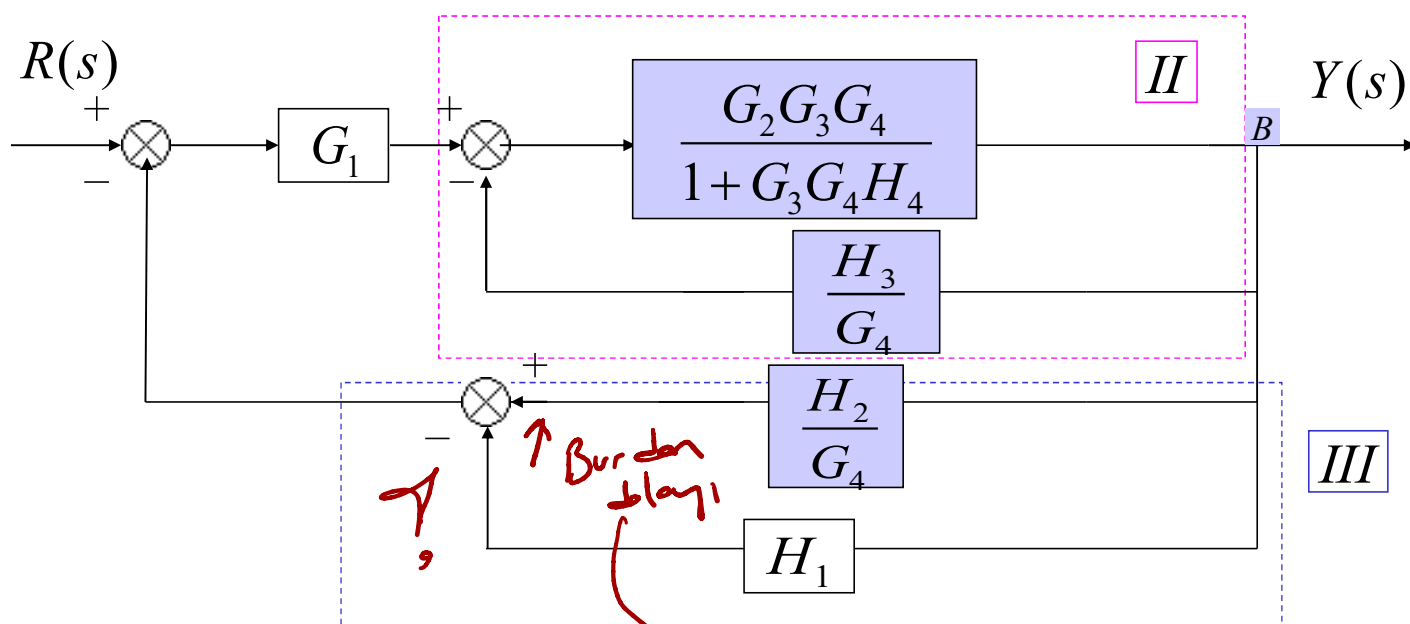


II feedback

$$\frac{G_2 G_3 G_4}{1 + G_3 G_4 H_4 + G_2 G_3 H_3}$$

III Not feedback

$$\frac{H_2 - G_4 H_1}{G_4}$$


3. Eliminate loop II & III

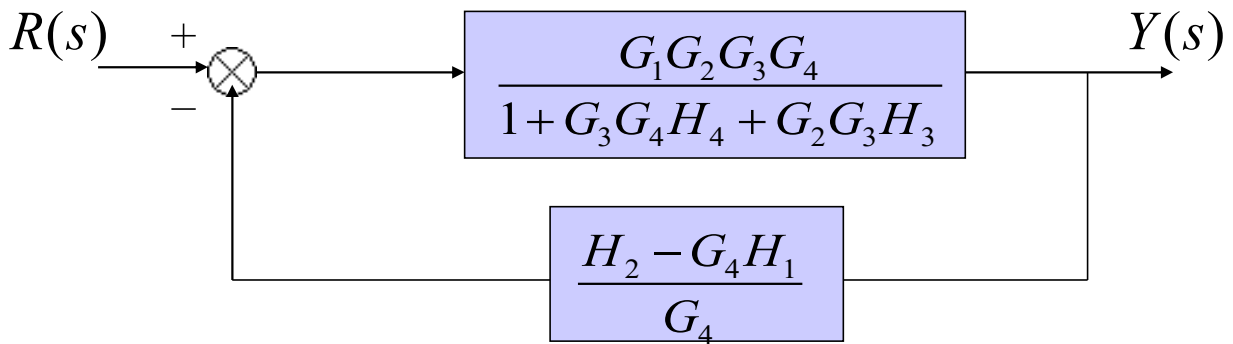

↓ Using rule 6 (Gerbeslane!)


$$T(s) = \frac{Y(s)}{R(s)} = \frac{G_1 G_2 G_3 G_4}{1 + G_2 G_3 H_3 + G_3 G_4 H_4 + G_1 G_2 G_3 H_2 - G_1 G_2 G_3 G_4 H_1}$$

(d)

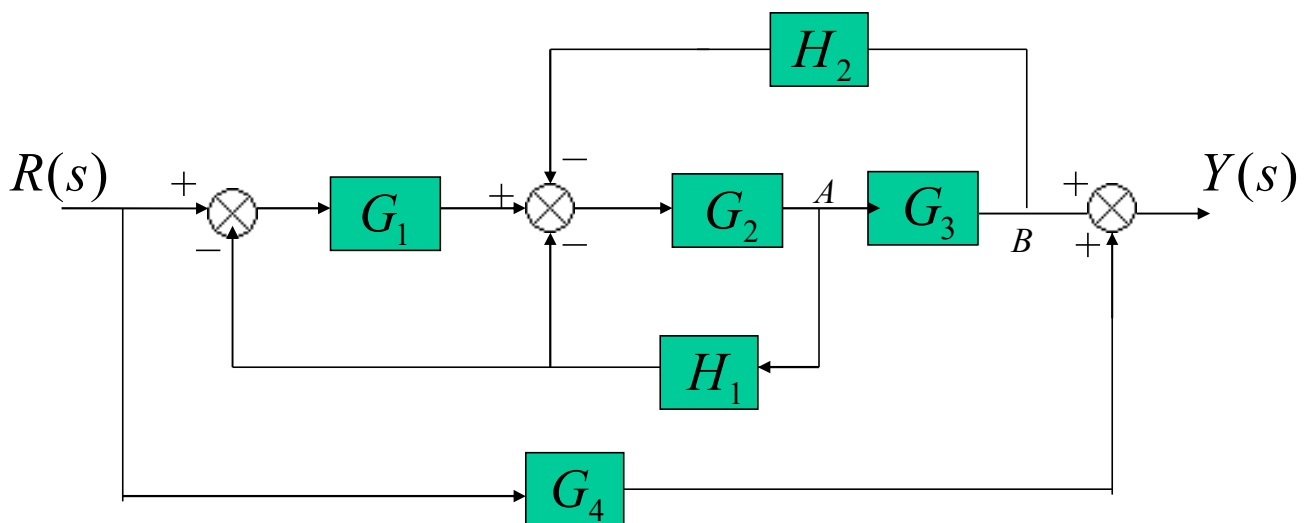


Solution:

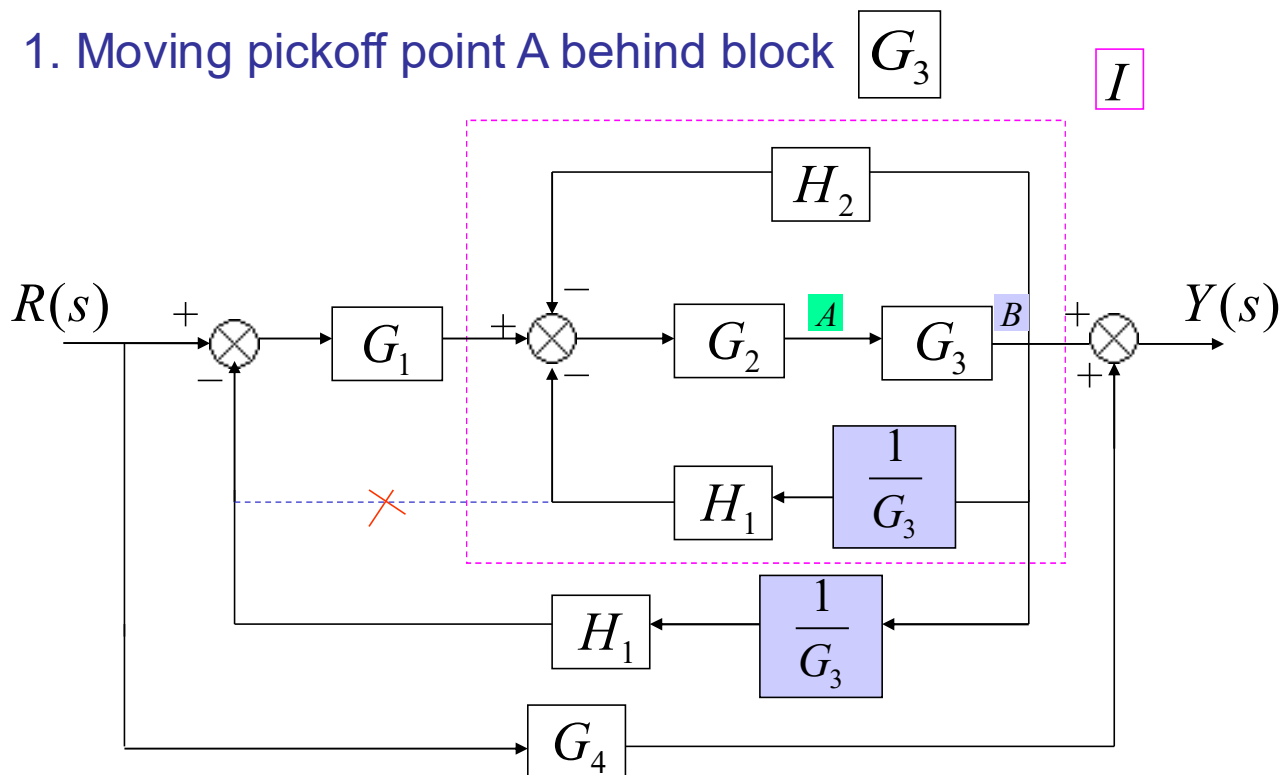
1. Moving pickoff point A behind block G_3



2. Eliminate loop I & Simplify

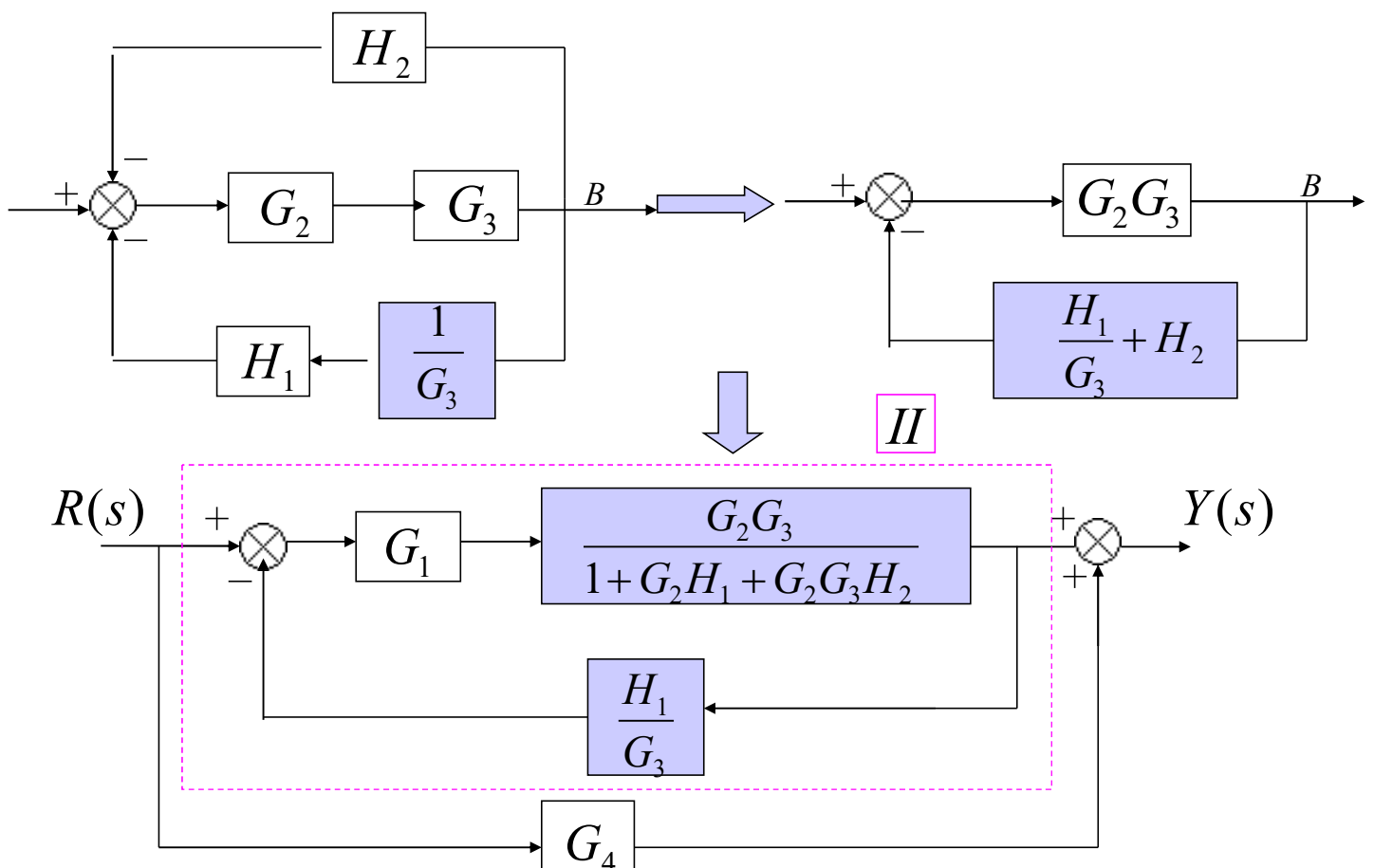


3. Eliminate loop II

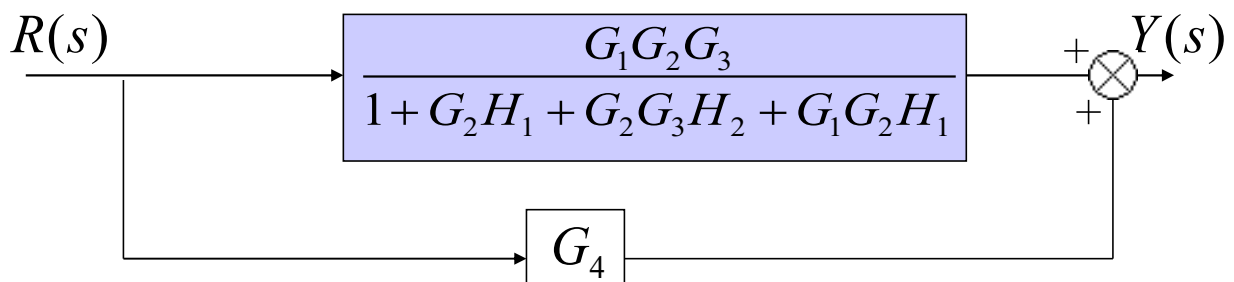

$$T(s) = \frac{Y(s)}{R(s)} = G_4 + \frac{G_1 G_2 G_3}{1 + G_2 H_1 + G_2 G_3 H_2 + G_1 G_2 H_1}$$

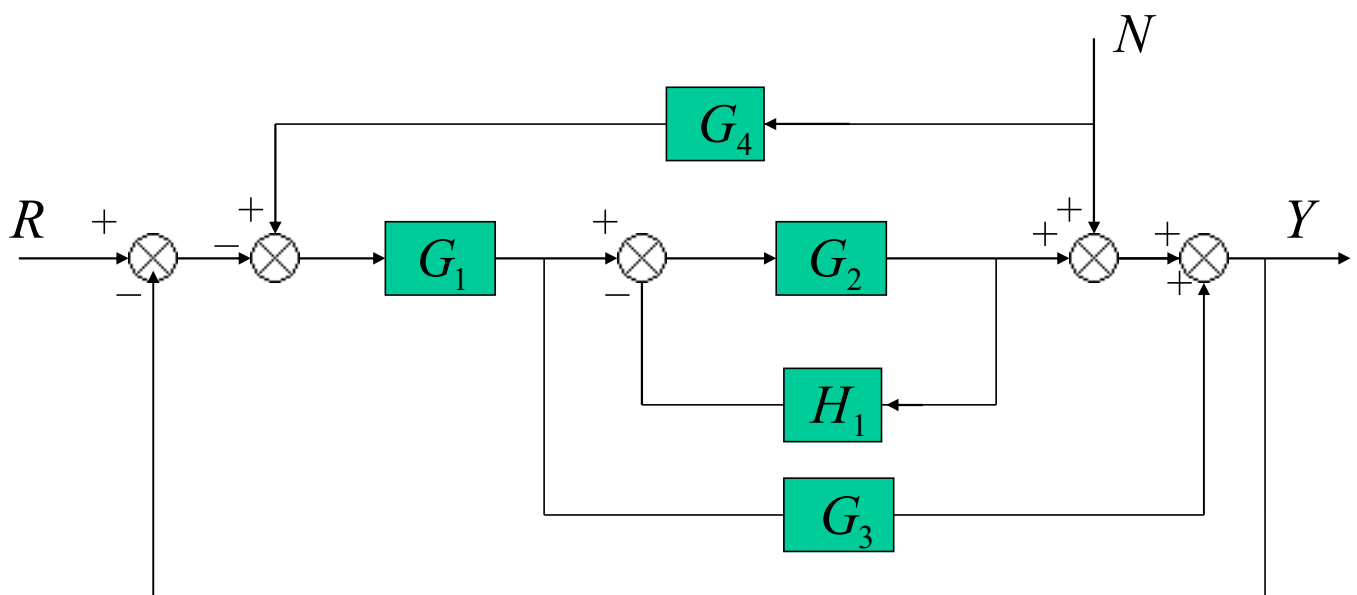Example 2

Determine the effect of R and N on Y in the following diagram



In this linear system, the output Y contains two parts, one part is related to R and the other is caused by N :

$$Y = Y_1 + Y_2 = T_1 R + T_2 N$$

If we set $N=0$, then we can get Y_1 :

$$Y_1 = Y_{N=0} = T_1 R$$

The same, we set $R=0$ and Y_2 is also obtained:


$$Y_2 = Y_{R=0} = T_2 N$$

Thus, the output Y is given as follows:


$$Y = Y_1 + Y_2 = Y_{N=0} + Y_{R=0}$$

Solution:


1. Swap the summing points A and B

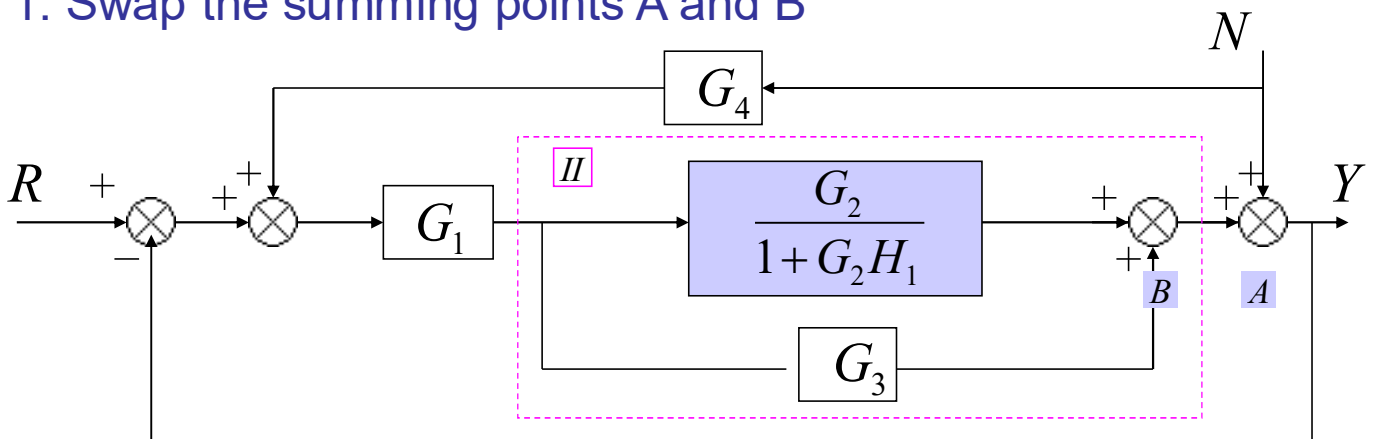


2. Eliminate loop II & simplify

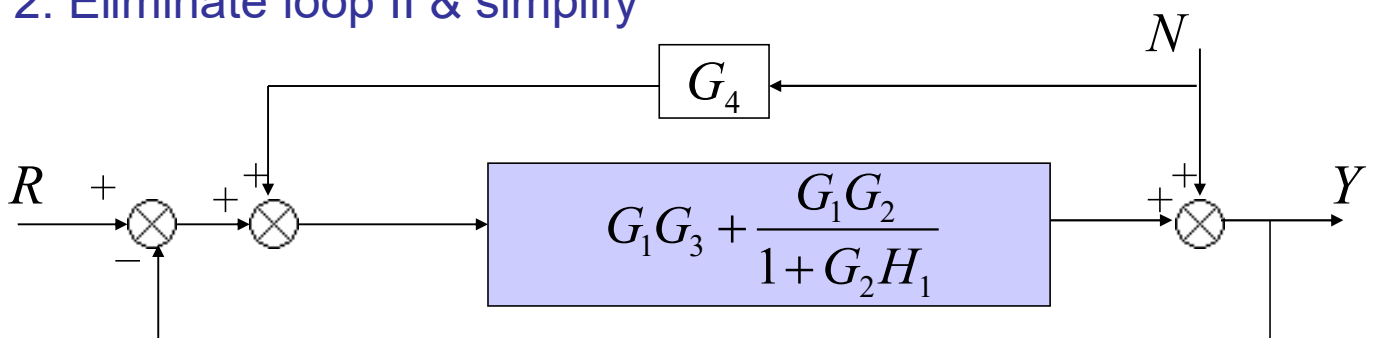

Rewrite the diagram:

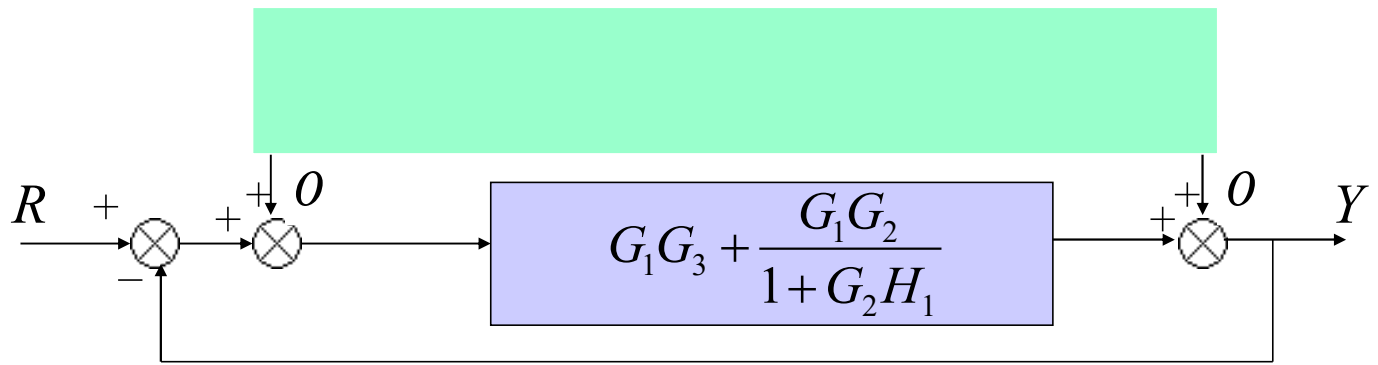


3. Let $N=0$

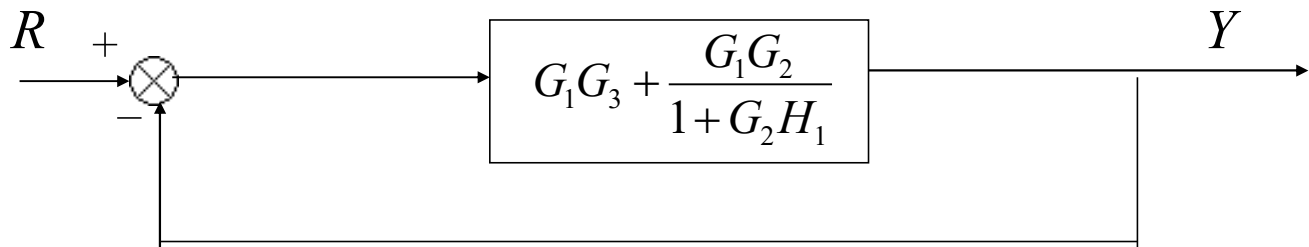


We can easily get Y_1

$$Y_1 = \frac{G_1 G_2 + G_1 G_3 + G_1 G_2 G_3 H_1}{1 + G_2 H_1 + G_1 G_2 + G_1 G_3 + G_1 G_2 G_3 H_1} R$$


4. Let $R=0$, we can get:

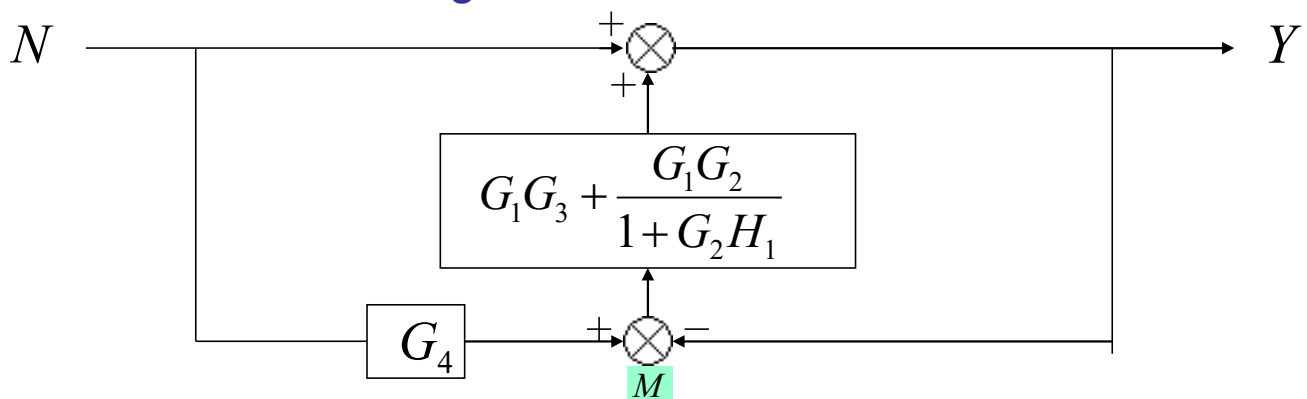

5. Break down the summing point M:

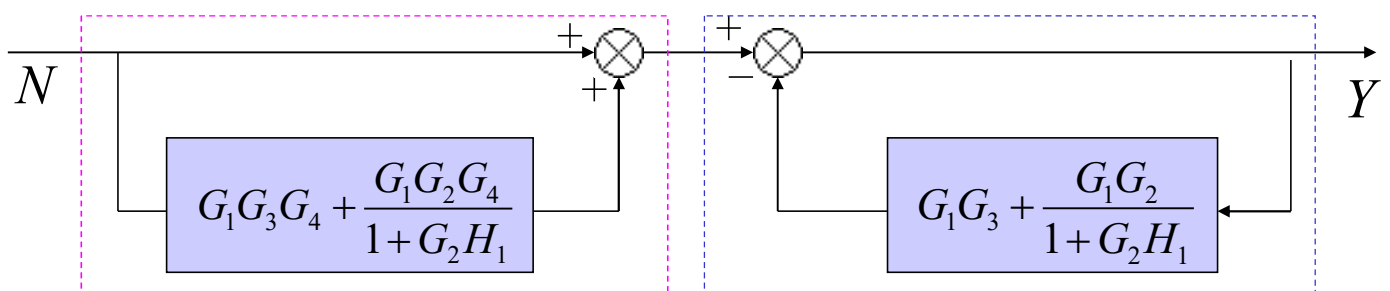

6. Eliminate above loops:

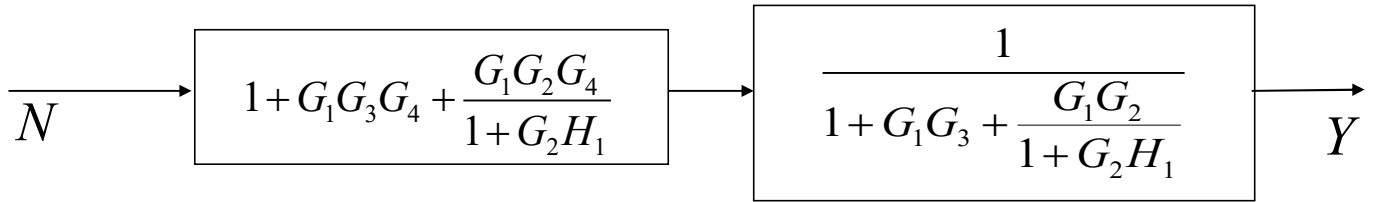

$$Y_2 = \frac{1 + G_2H_1 + G_1G_2G_4 + G_1G_3G_4 + G_1G_2G_3G_4H_1}{1 + G_2H_1 + G_1G_2 + G_1G_3 + G_1G_2G_3H_1} N$$

7. According to the principle of superposition, Y_1 and Y_2 can be combined together, So:

$$Y = Y_1 + Y_2$$

$$= \frac{1}{1 + G_2H_1 + G_1G_2 + G_1G_3 + G_1G_2G_3H_1} [(G_1G_2 + G_1G_3 + G_1G_2G_3H_1)R + (1 + G_2H_1 + G_1G_2G_4 + G_1G_3G_4 + G_1G_2G_3G_4H_1)N]$$