

Electronic Devices and Circuit Theory

Boylestad

BJT AC Analysis

Chapter 5

BJT Transistor Modeling

A model is an equivalent circuit that represents the AC characteristics of the transistor.

A model uses circuit elements that approximate the behavior of the transistor.

There are two models commonly used in small signal AC analysis of a transistor:

r_e model



Hybrid equivalent model

Ch.5 Summary

The r_e Transistor Model

BJTs are basically current-controlled devices; therefore the r_e model uses a diode and a current source to duplicate the behavior of the transistor.

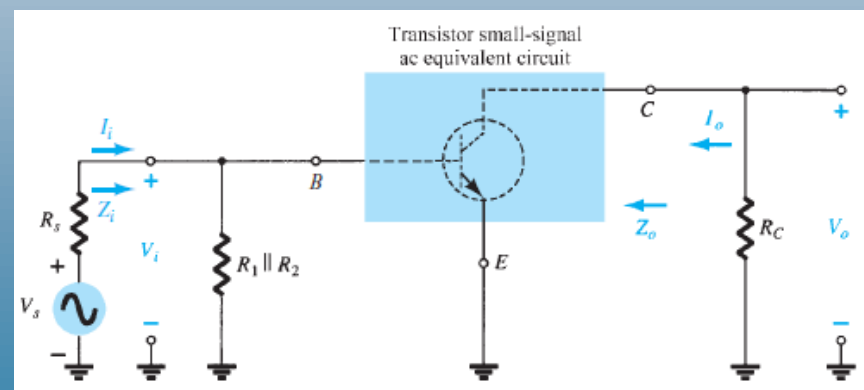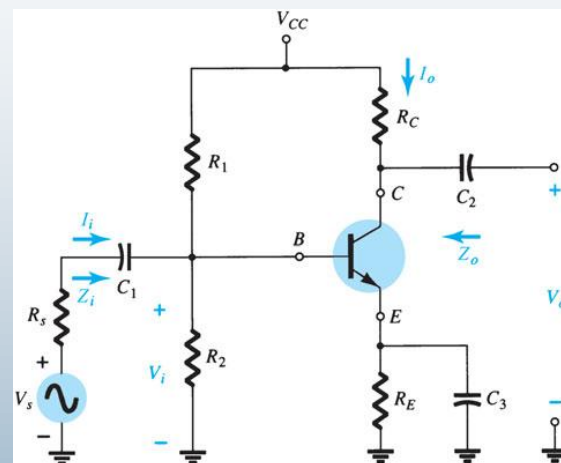One disadvantage to this model is its sensitivity to the DC level. This model is designed for specific circuit conditions.





Ch.5 Summary

Common-Emitter Configuration

The diode r_e model can be replaced by the resistor r_e .

$$I_e = (\beta + 1) I_b \cong \beta I_b$$

$$r_e = \frac{26 \text{ mV}}{I_e}$$

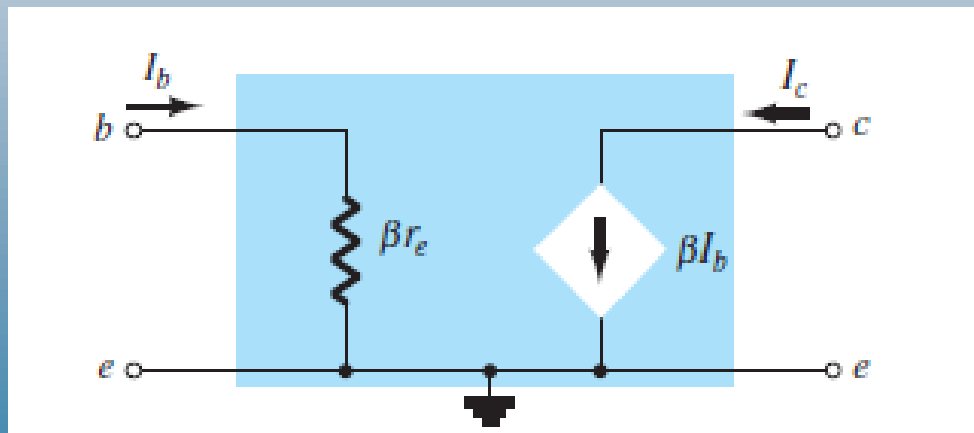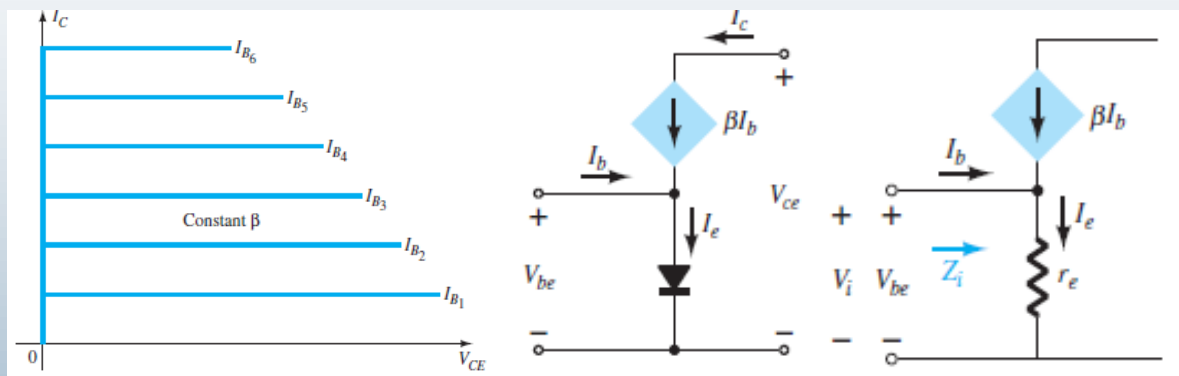

Ch.5 Summary

Common-Emitter Configuration

Input impedance: $Z_i = \beta r_e$

Output impedance:

$$Z_o = r_o \cong \infty \Omega$$



Voltage gain:

$$A_v = -\frac{R_L}{r_e}$$

Current gain:

$$A_i = \beta \Big|_{r_o = \infty}$$
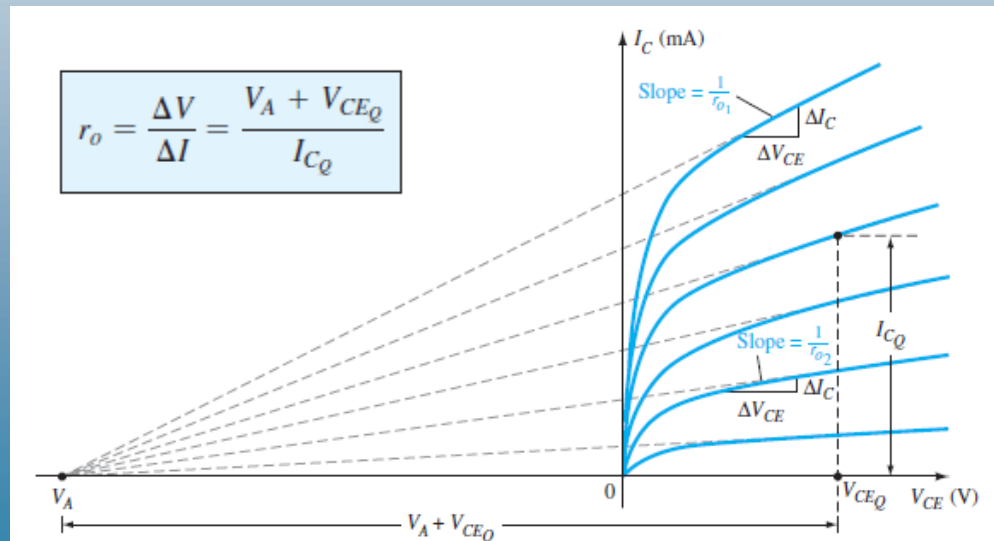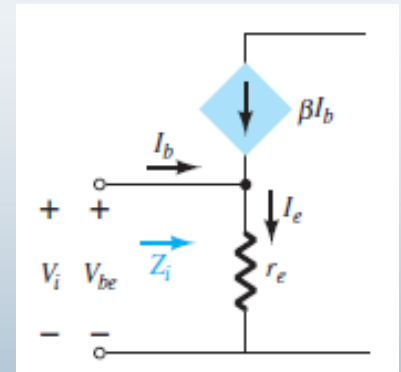
$$\begin{aligned} Z_i &= \frac{V_i}{I_b} = \frac{V_{be}}{I_b} \\ V_{be} &= I_e r_e = (I_c + I_b) r_e = (\beta I_b + I_b) r_e \\ &= (\beta + 1) I_b r_e \\ Z_i &= \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I_b} \end{aligned}$$



Ch.5 Summary

Common-Base Configuration

Input impedance:

$$r_e = \frac{26 \text{ mV}}{I_e} \quad Z_i = r_e$$

Output impedance:




$$Z_o \cong \infty \Omega$$

Voltage gain:

$$A_v = \frac{\alpha R_L}{r_e} \cong \frac{R_L}{r_e}$$

Current gain:

$$A_i = -\alpha \cong -1$$

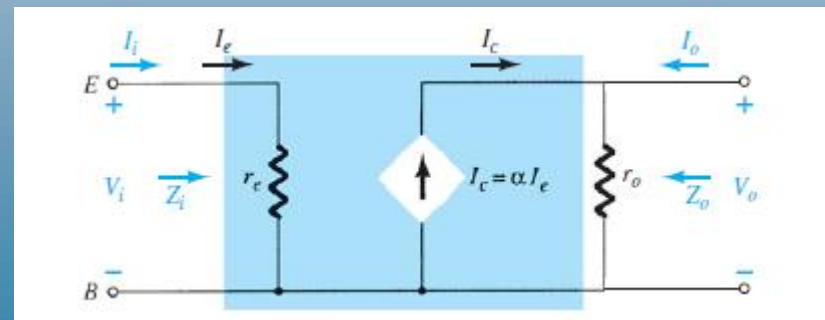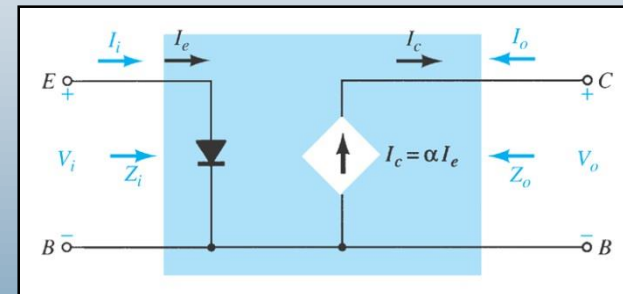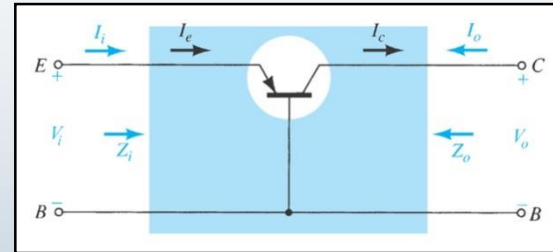

Ch.5 Summary

The Hybrid Equivalent Model


Hybrid parameters are developed and used for modeling the transistor. These parameters can be found on a transistor's specification sheet:

h_i = input resistance

h_r = reverse transfer voltage ratio (V_i/V_o) $\cong 0$


h_f = forward transfer current ratio (I_o/I_i)

h_o = output conductance

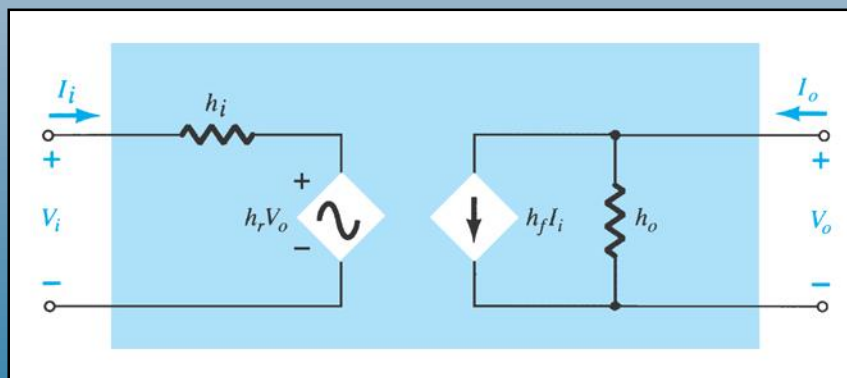

Ch.5 Summary

Simplified General h-Parameter Model

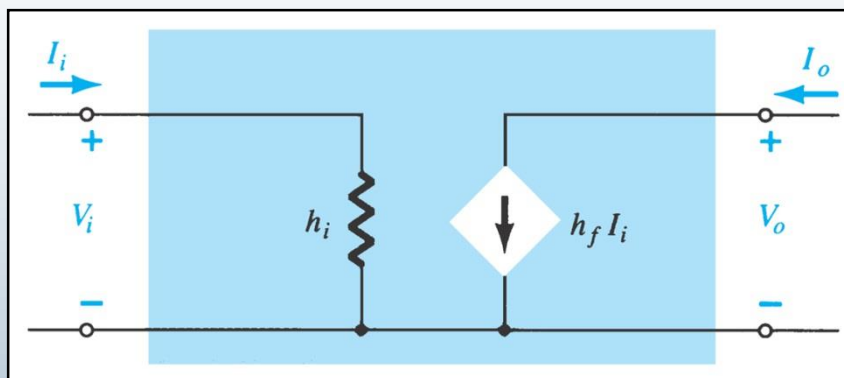

		Min.	Max.	
Input impedance ($I_C = 1 \text{ mA dc}$, $V_{CE} = 10 \text{ V dc}$, $f = 1 \text{ kHz}$) 2N4400	h_{ie}	0.5	7.5	$\text{k}\Omega$
Voltage feedback ratio ($I_C = 1 \text{ mA dc}$, $V_{CE} = 10 \text{ V dc}$, $f = 1 \text{ kHz}$)	h_{re}	0.1	8.0	$\times 10^{-4}$
Small-signal current gain ($I_C = 1 \text{ mA dc}$, $V_{CE} = 10 \text{ V dc}$, $f = 1 \text{ kHz}$) 2N4400	h_{fe}	20	250	—
Output admittance ($I_C = 1 \text{ mA dc}$, $V_{CE} = 10 \text{ V dc}$, $f = 1 \text{ kHz}$)	h_{oe}	1.0	30	$1\mu\text{S}$

h_i = input resistance

h_f = forward transfer current ratio (I_o/I_i)


Ch.5 Summary

h-Parameter vs. r_e Model

Common-Emitter

$$h_{ie} = \beta r_e$$


$$h_{fe} = \beta_{ac}$$

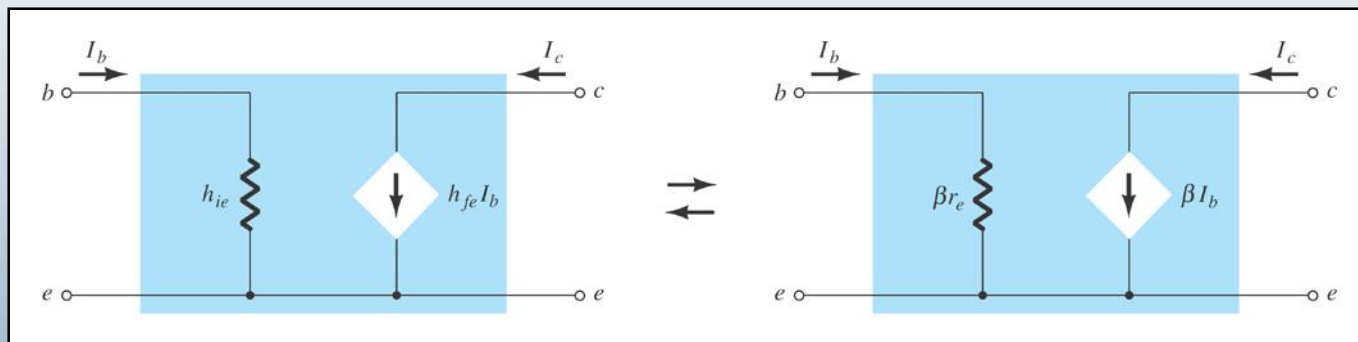

Common-Base

$$h_{ib} = r_e$$

$$h_{fb} = -\alpha \cong -1$$

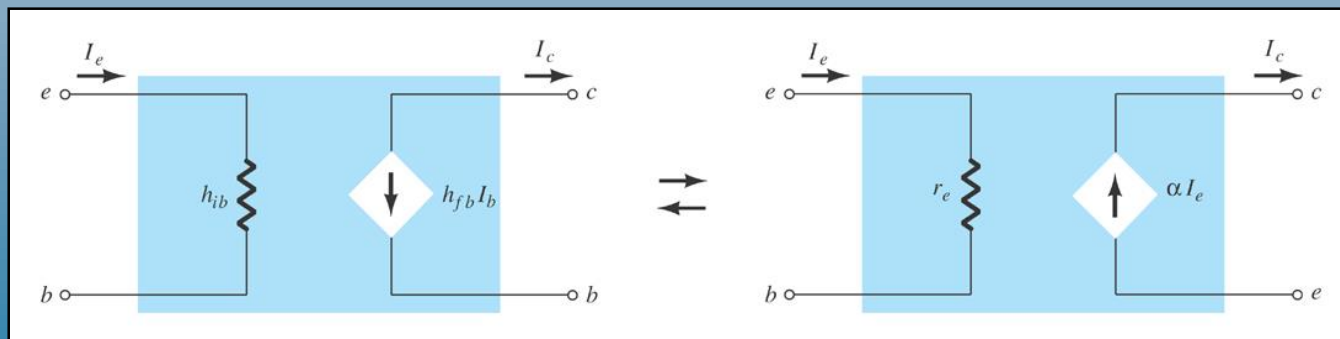

Ch.5 Summary


Common-Emitter Fixed-Bias Configuration

The input is applied to the base
The output is taken from the collector

High input impedance
Low output impedance



High voltage and current gain

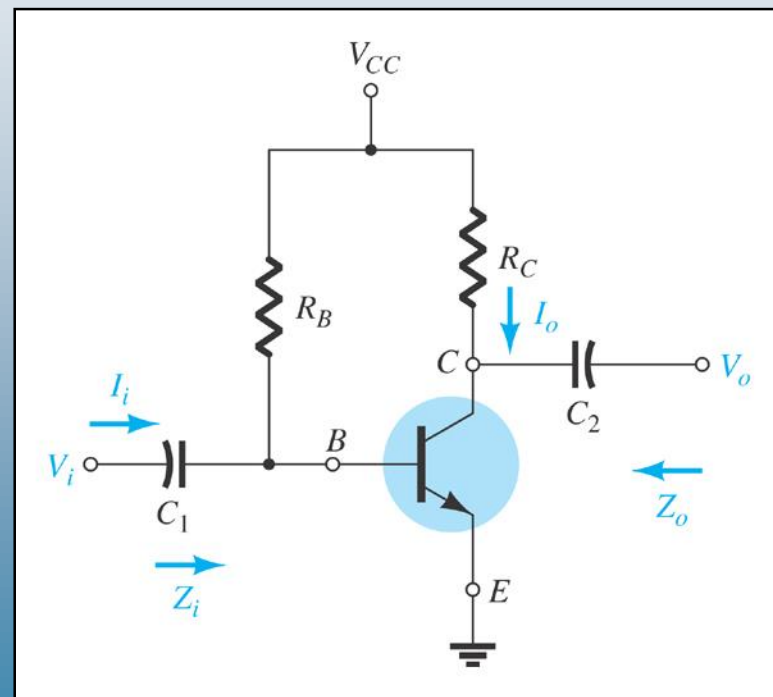Phase shift between input and output is 180°




Ch.5 Summary

Common-Emitter Fixed-Bias Configuration

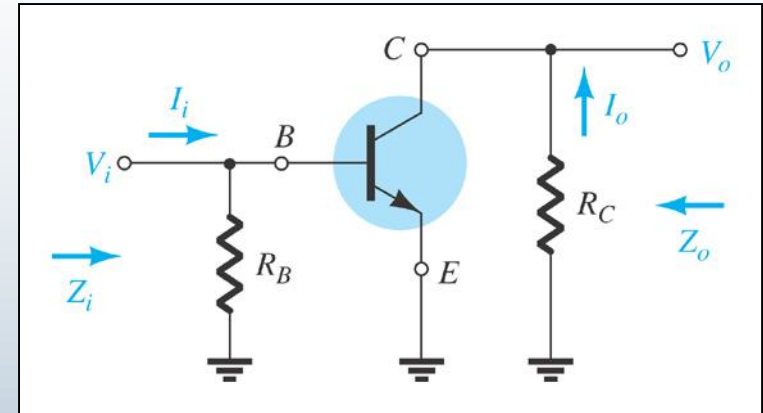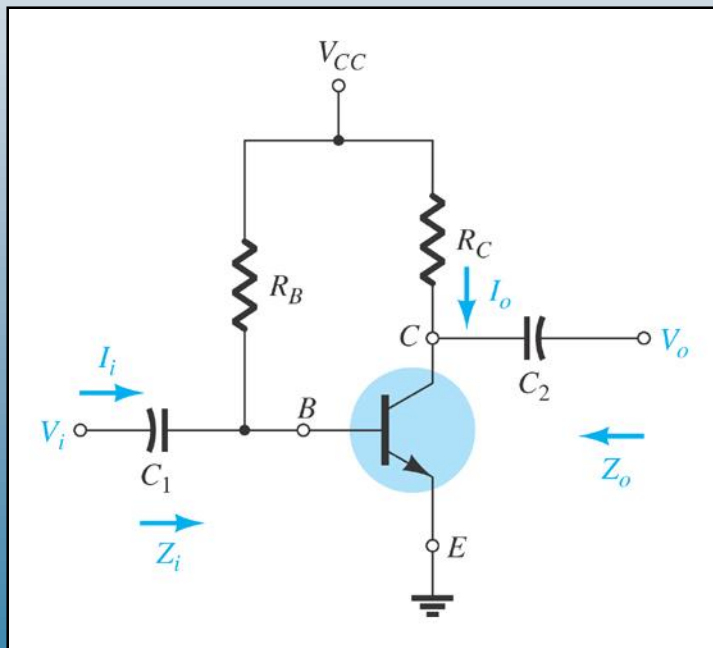

AC equivalent

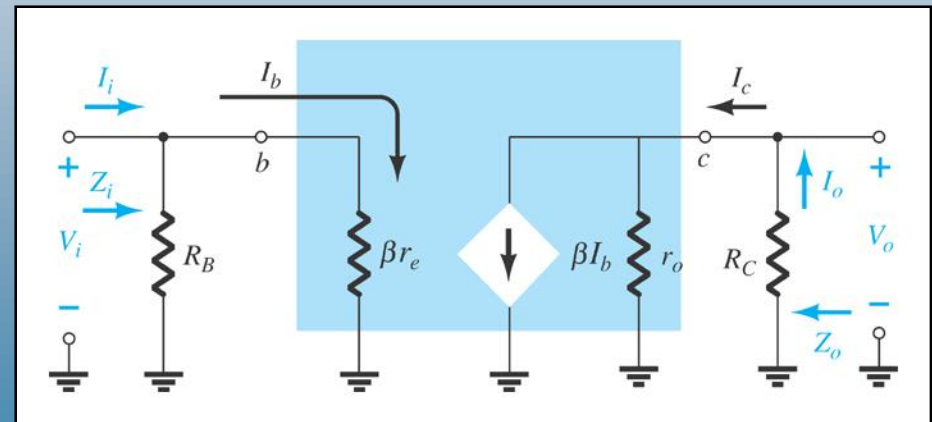

r_e model

Ch.5 Summary

Common-Emitter Fixed-Bias Calculations

Input
impedance:

$$Z_i = R_B \parallel \beta r_e$$

$$Z_i \cong \beta r_e \quad R_B \geq 10\beta r_e$$

Output
impedance:


$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \quad r_o \geq 10R_C$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$
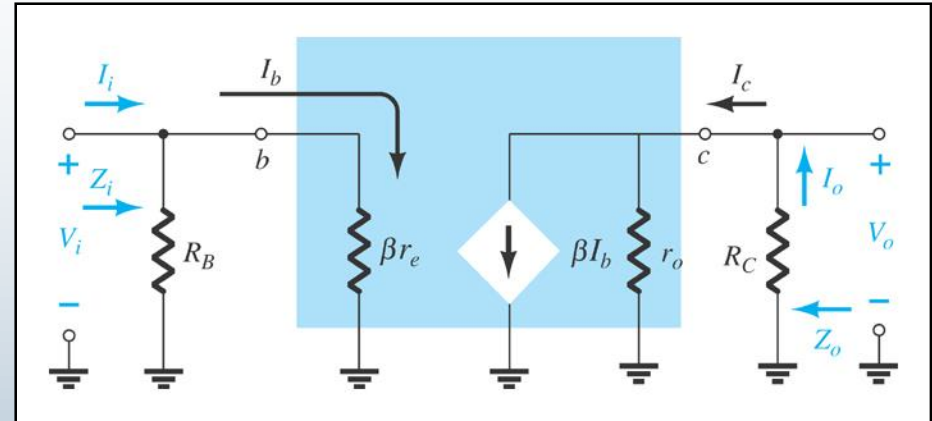
$$A_v = -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$



Current gain: $A_i \cong \beta \quad r_o \geq 10R_C, R_B \geq 10\beta r_e$


$$A_{i_L} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$

Current gain
from voltage gain:


$$A_i = -A_v \frac{Z_i}{R_C}$$

Ch.5 Summary

Common-Emitter Voltage-Divider Bias

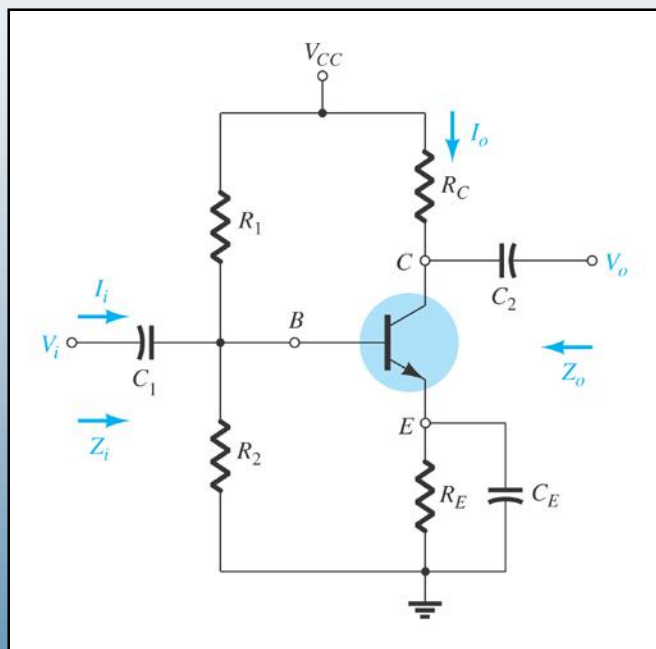

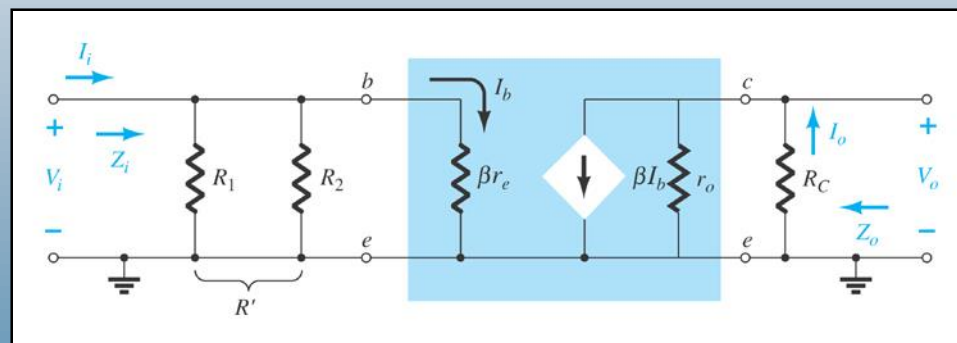r_e model requires you to determine β , r_e , and r_o .



Ch.5 Summary

Common-Emitter Voltage-Divider Bias Calculations

Input impedance

$$R' = R_1 \parallel R_2$$

$$Z_i = R' \parallel \beta r_e$$

Output impedance

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \Big|_{r_o \geq 10R_C}$$

$$A_{i_L} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$


Current gain from A_v

$$A_i = -A_v \frac{Z_i}{R_C}$$

Voltage gain



$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \Big|_{r_o \geq 10R_C}$$

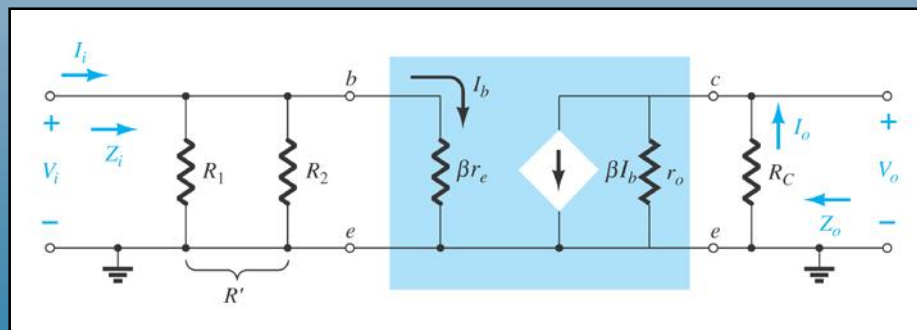

Ch.5 Summary

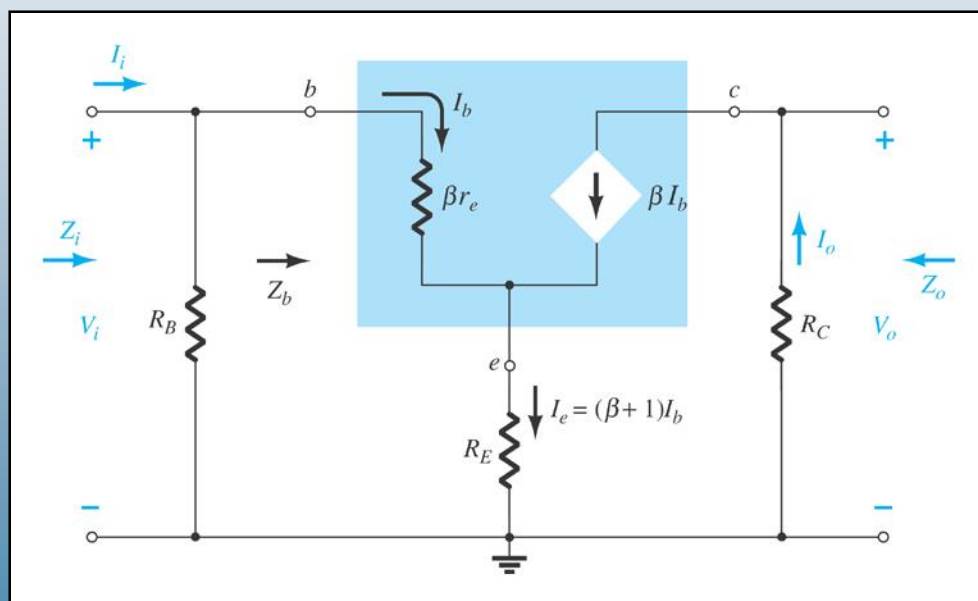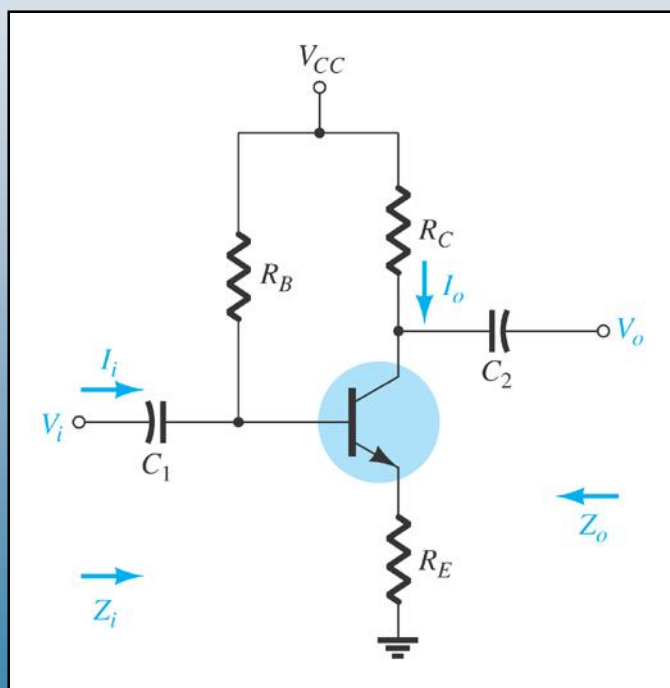Common-Emitter Emitter-Bias Configuration



Ch.5 Summary

Impedance Calculations

Input impedance:

$$Z_i = R_B \parallel Z_b$$


$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta R_E$$

Output impedance:

$$Z_o = R_C$$

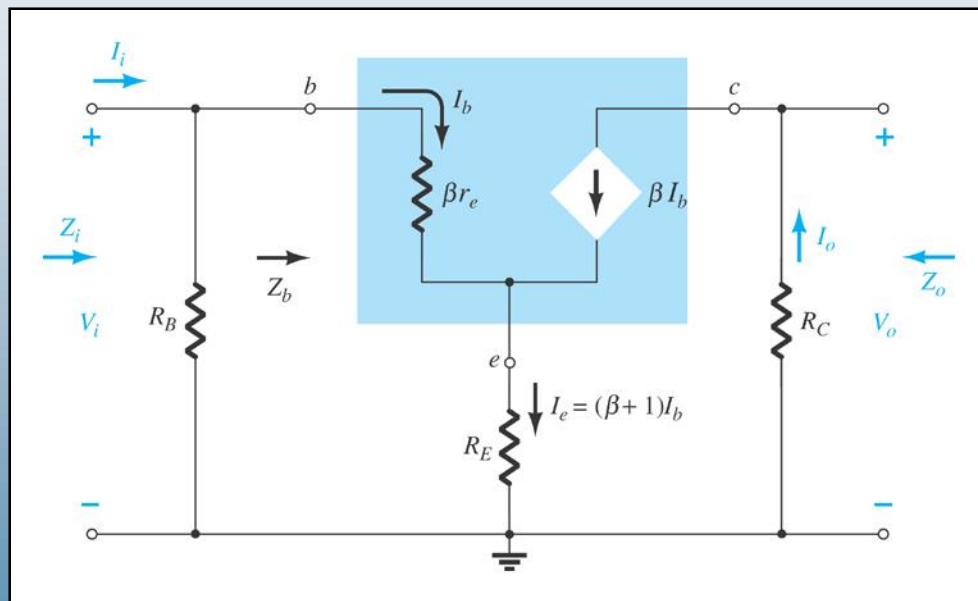

Ch.5 Summary


Gain Calculations

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e + R_E} \Big|_{Z_b = \beta(r_e + R_E)}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E} \Big|_{Z_b \cong \beta R_E}$$


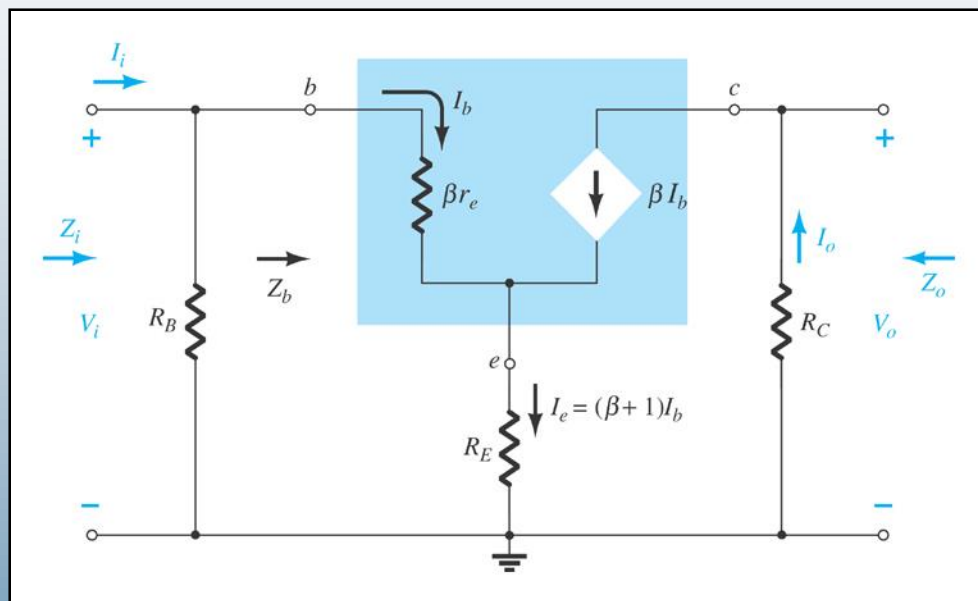


Current gain from A_v :

$$A_i = -A_v \frac{Z_i}{R_C}$$

Ch.5 Summary

Emitter-Follower Configuration

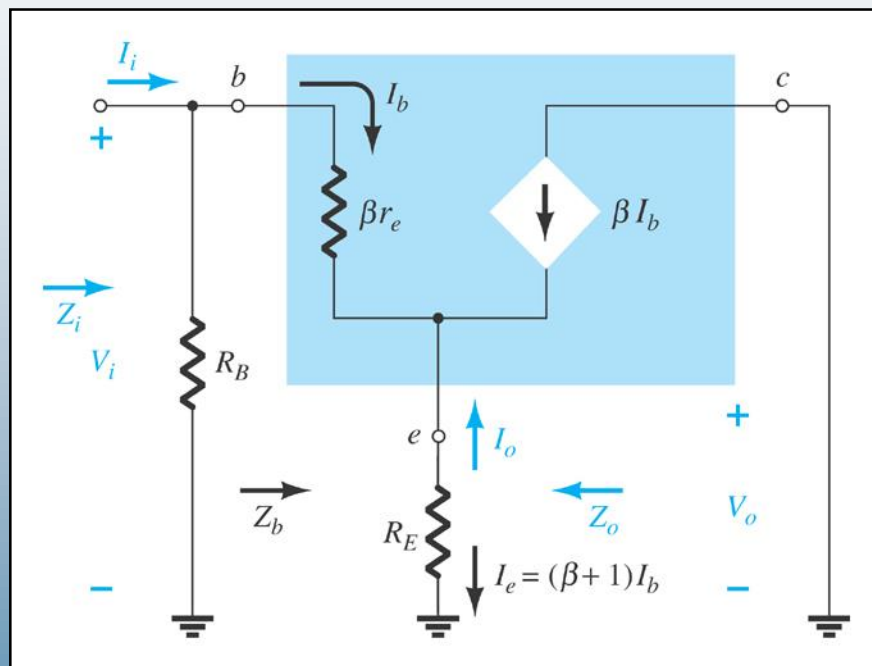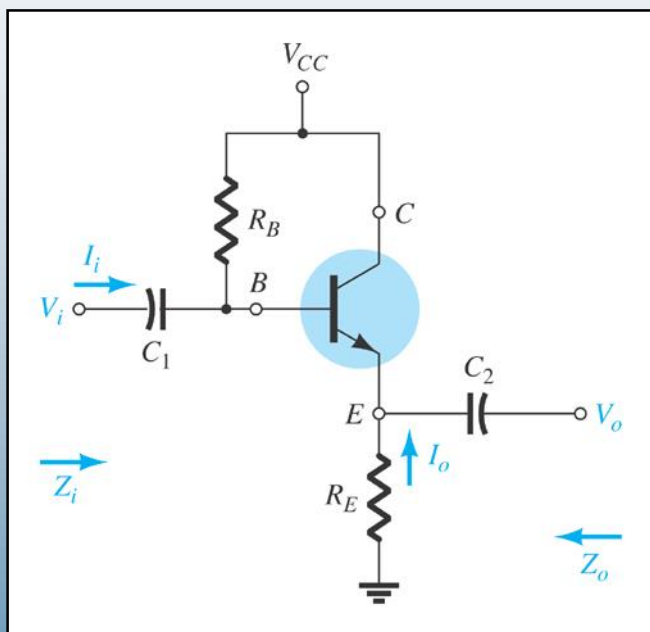

This is also known as the *common-collector* configuration. The input is applied to the base and the output is taken from the emitter. There is no phase shift between input and output.

Ch.5 Summary

Impedance Calculations

Input impedance:

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$



$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta R_E$$

Output impedance:

$$Z_o = R_E \parallel r_e$$

$$Z_o \cong r_e \mid R_E \gg r_e$$

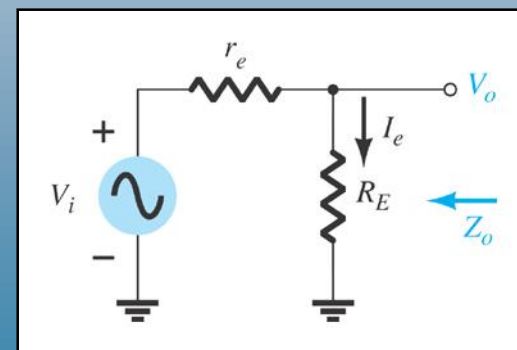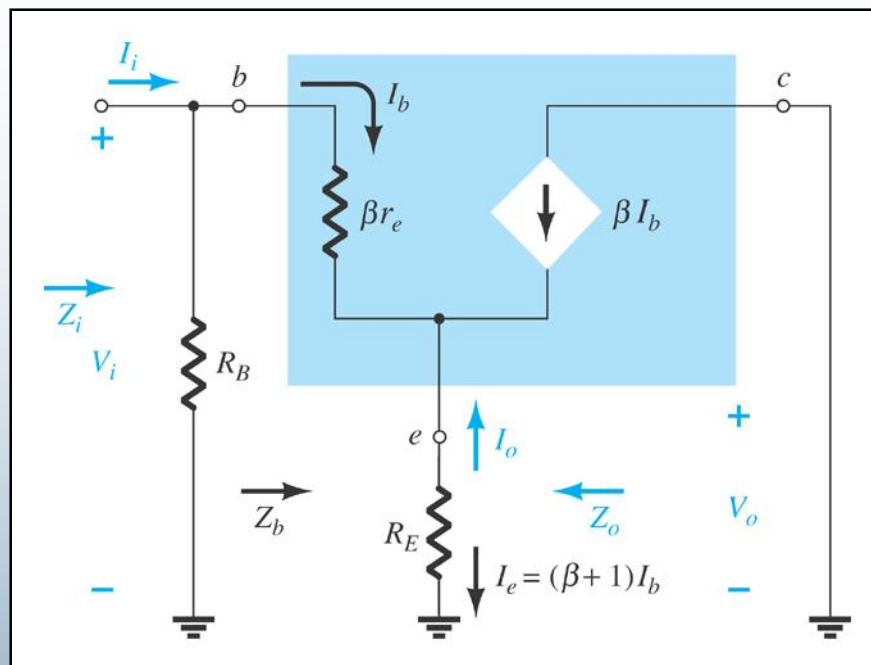


Ch.5 Summary

Gain Calculations

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$

$$A_v = \frac{V_o}{V_i} \cong 1 \Big|_{R_E \gg r_e, R_E + r_e \cong R_E}$$

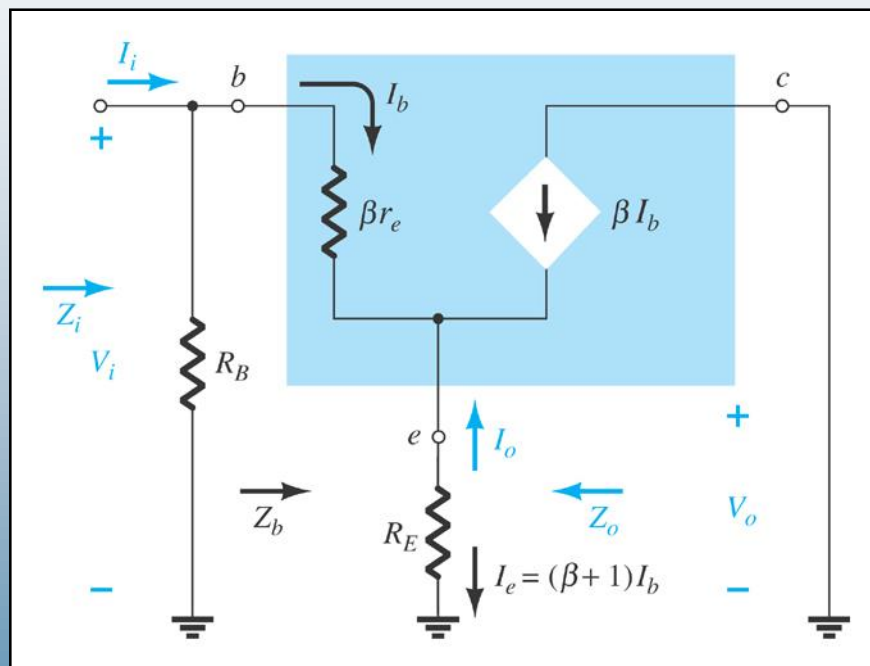

Current gain from voltage gain:

$$A_i = -A_v \frac{Z_i}{R_E}$$

Ch.5 Summary

Common-Base Configuration

The input is applied to the emitter

The output is taken from the collector



Low input impedance.

High output impedance

Current gain less than unity

Very high voltage gain

No phase shift between input and output

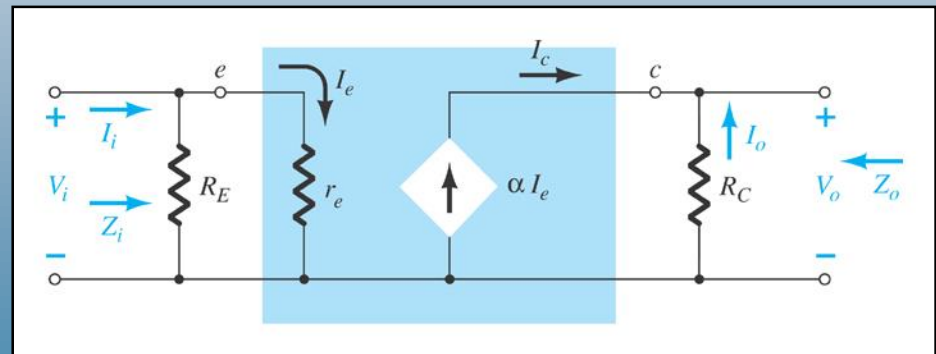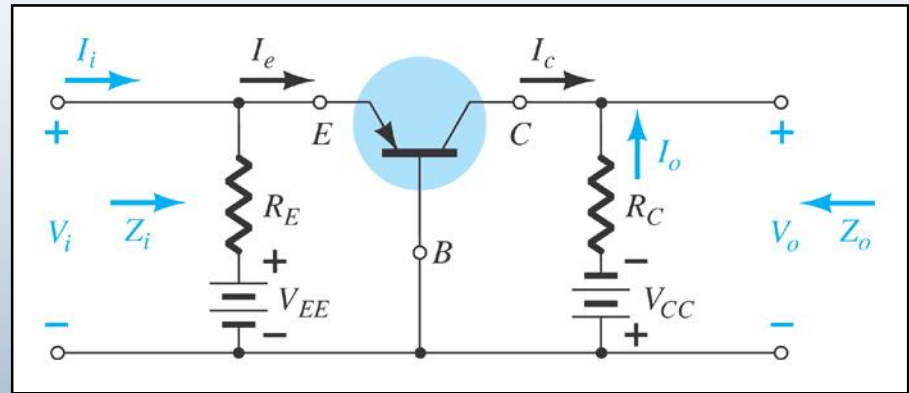

Ch.5 Summary

Calculations

Input impedance:

$$Z_i = R_E \parallel r_e$$

Output impedance:



$$Z_o = R_C$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$$



Current gain:
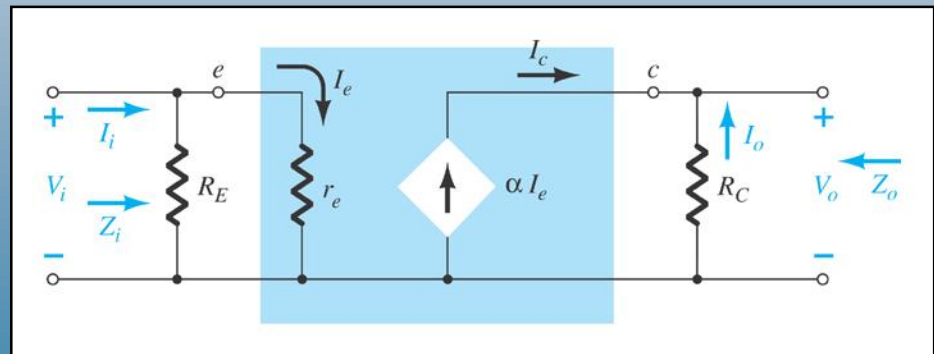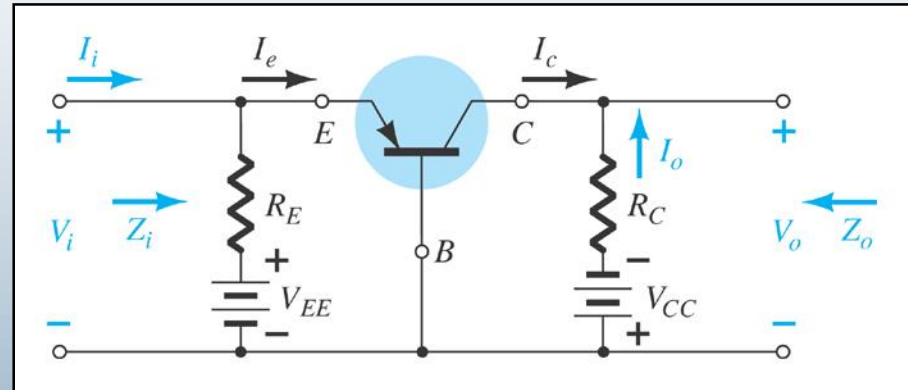
$$A_i = \frac{I_o}{I_i} = -\alpha \cong -1$$



Ch.5 Summary

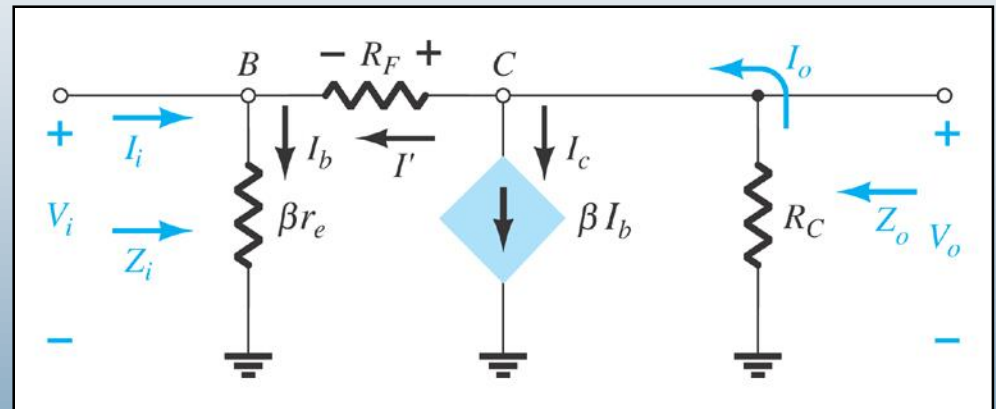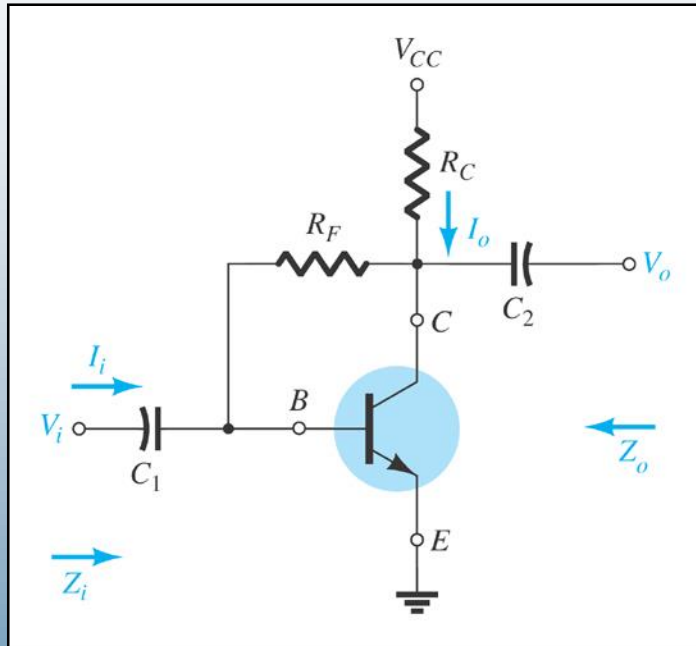Common-Emitter Collector Feedback Configuration



- A variation of the common-emitter fixed-bias configuration
- Input is applied to the base
- Output is taken from the collector
- There is a 180° phase shift between the input and output

Ch.5 Summary

Calculations

Input impedance:

$$Z_i = \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$$

Output impedance:



$$Z_o \cong R_C \parallel R_F$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e}$$

Current gain:
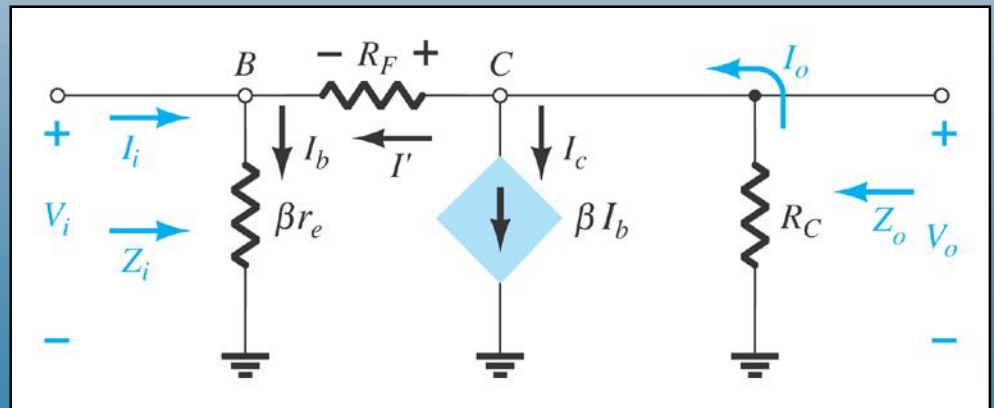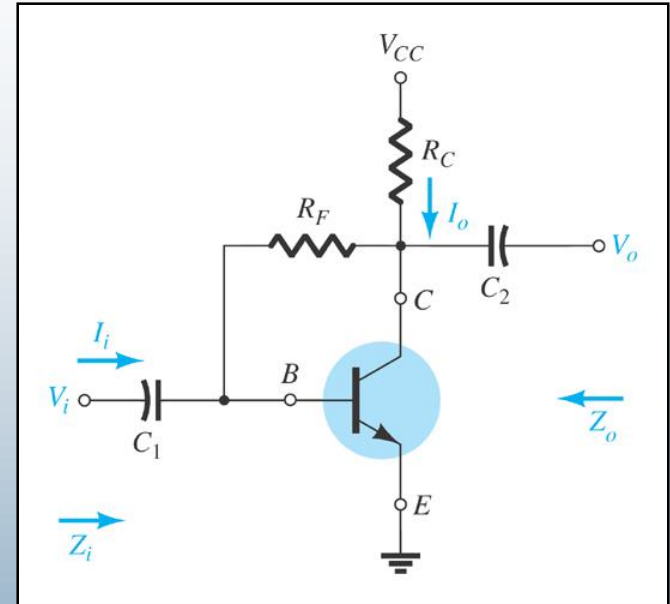
$$A_i = \frac{I_o}{I_i} = \frac{\beta R_F}{R_F + \beta R_C}$$
$$A_i = \frac{I_o}{I_i} \cong \frac{R_F}{R_C}$$



Ch.5 Summary

Two-Port Systems Approach


With V_i set to 0 V:

$$Z_{Th} = Z_o = R_o$$

The voltage across the open terminals is:

$$E_{Th} = A_{vNL} V_i$$

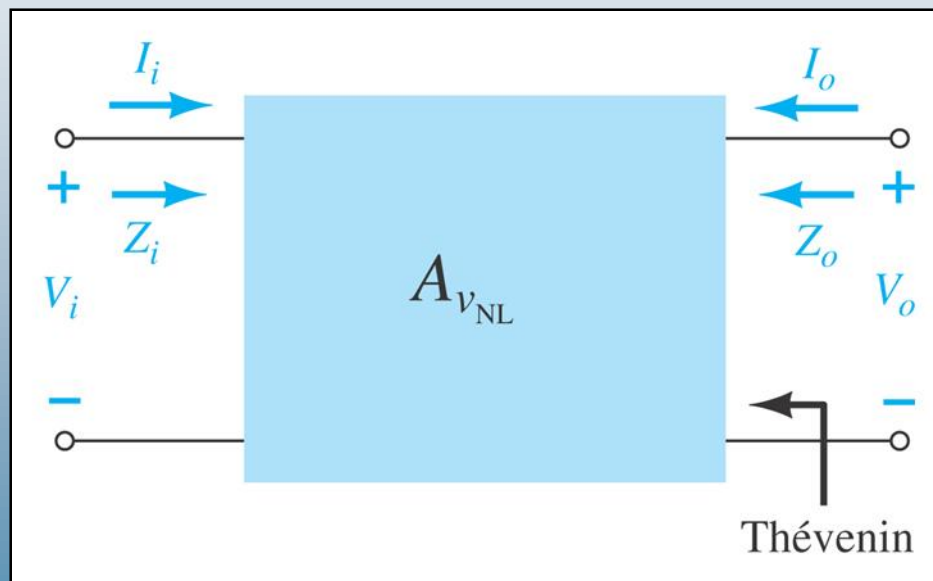where A_{vNL} is the no-load voltage gain




Ch.5 Summary

Effect of Load Impedance on Gain

This model can be applied to any current- or voltage-controlled amplifier.

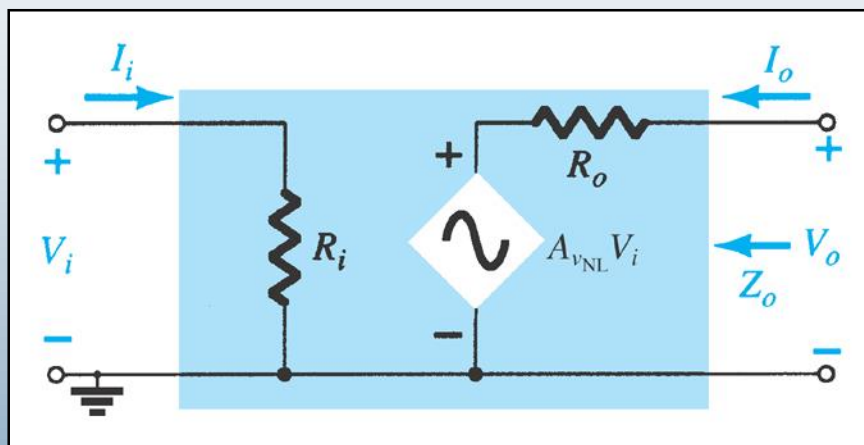Adding a load reduces the gain of the amplifier:



$$A_v = \frac{V_o}{V_i} = \frac{R_L}{R_L + R_o} A_{vNL}$$


$$A_i = -A_v \frac{Z_i}{R_L}$$

Ch.5 Summary

Effect of Source Impedance on Gain

The amplitude of the applied signal that reaches the input of the amplifier is:

$$V_i = \frac{R_i V_s}{R_i + R_s}$$

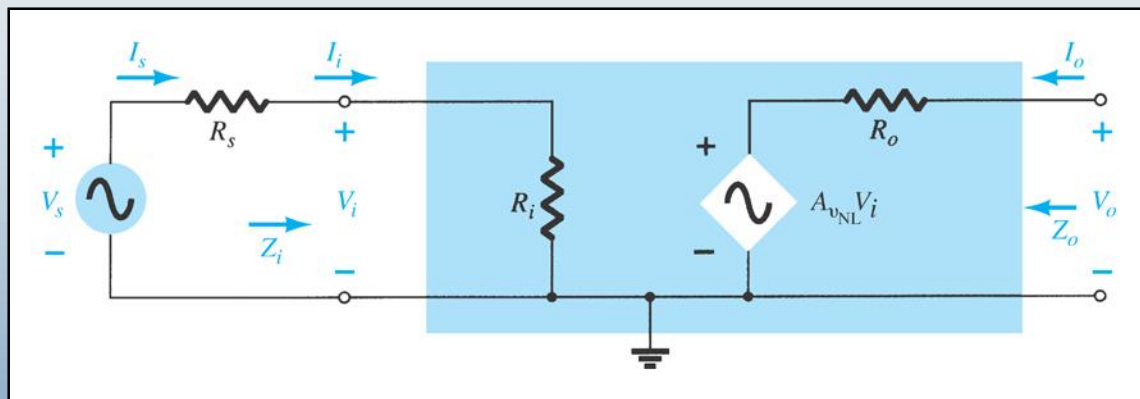

The internal resistance of the signal source reduces the overall gain:

$$A_{vs} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} A_{vNL}$$


Ch.5 Summary

Combined Effects of R_s and R_L on Voltage Gain

Effects of R_L :

$$A_v = \frac{V_o}{V_i} = \frac{R_L A_{vNL}}{R_L + R_o}$$

$$A_i = -A_v \frac{R_i}{R_L}$$

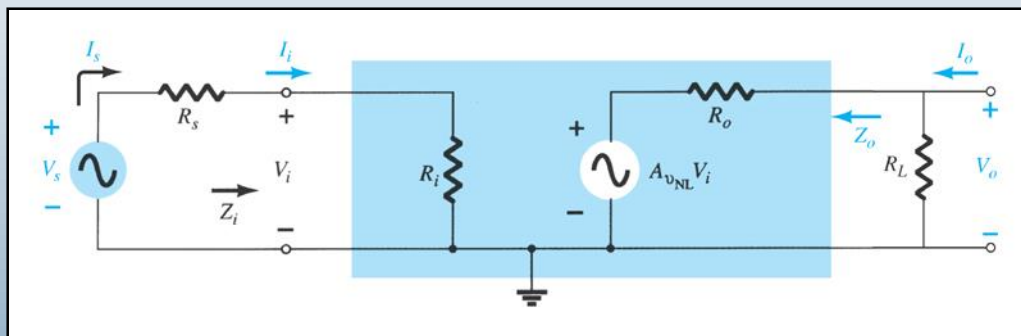

Effects of R_L and R_s :

$$A_{vs} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o} A_{vNL}$$

$$A_{is} = -A_{vs} \frac{R_s + R_i}{R_L}$$

Ch.5 Summary

Cascaded Systems

- The output of one amplifier is the input to the next amplifier
- The overall voltage gain is determined by the product of gains of the individual stages
- The DC bias circuits are isolated from each other by the coupling capacitors
- The DC calculations are independent of the cascading
- The AC calculations for gain and impedance are interdependent

Ch.5 Summary

R-C Coupled BJT Amplifiers

Voltage gain:


$$A_{v1} = \frac{R_C \parallel R_1 \parallel R_2 \parallel \beta R_e}{r_e}$$

$$A_{v2} = \frac{R_C}{r_e}$$

$$A_v = A_{v1} A_{v2}$$

**Input impedance,
first stage:**
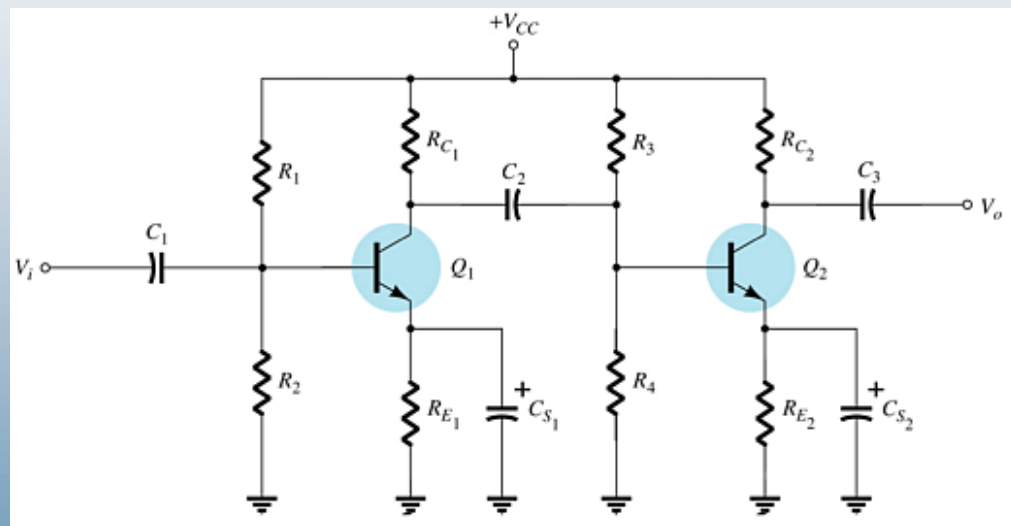
$$Z_i = R_1 \parallel R_2 \parallel \beta R_e$$



**Output impedance,
second stage:**


$$Z_o = R_C$$

Ch.5 Summary

Cascade Connection

This example is a CE–CB combination. This arrangement provides high input impedance but a low voltage gain.

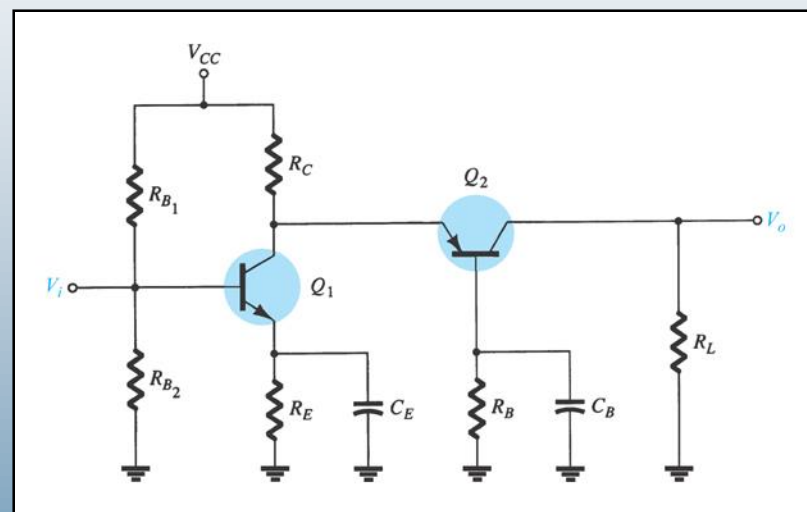The low voltage gain of the input stage reduces the Miller input capacitance, making this combination suitable for high-frequency applications.




Ch.5 Summary

Darlington Connection

The Darlington circuit provides very high current gain, equal to the product of the individual current gains:

$$\beta_D = \beta_1 \beta_2$$

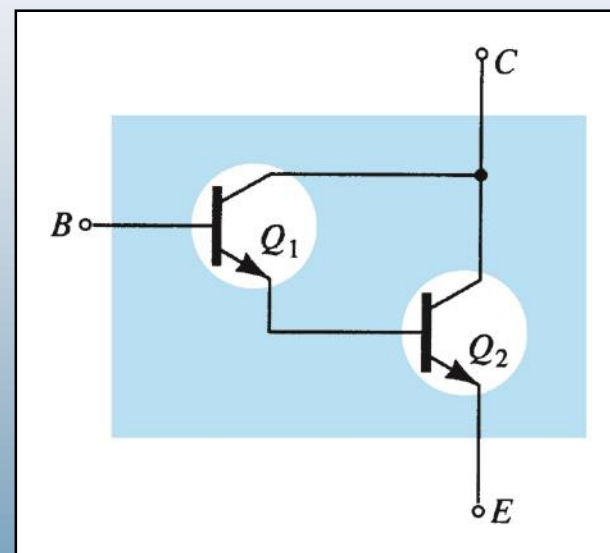The practical significance is that the circuit provides a very high input impedance.



Ch.5 Summary

DC Bias of Darlington Circuits

Base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E}$$

Emitter current:


$$I_E = (\beta_D + 1)I_B \cong \beta_D I_B$$

Emitter voltage:

$$V_E = I_E R_E$$

Base voltage:

$$V_B = V_E + V_{BE}$$

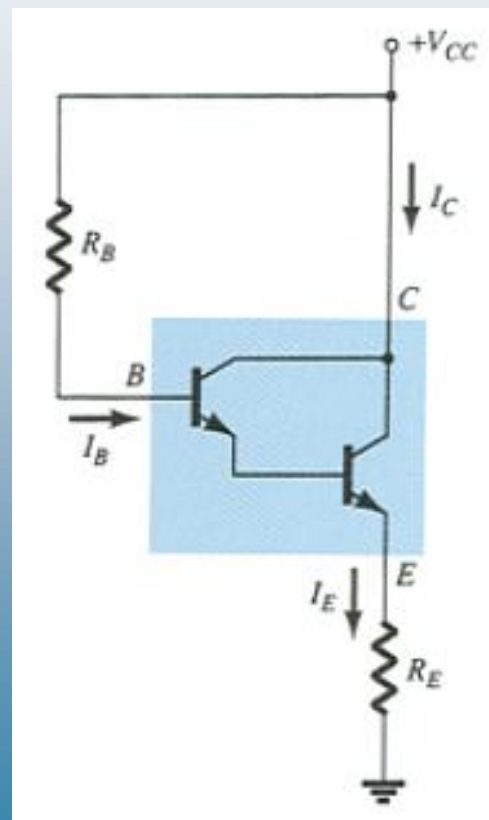


Ch.5 Summary

Feedback Pair

This is a two-transistor circuit that operates like a Darlington pair, *but it is not a Darlington pair*.

It has similar characteristics:

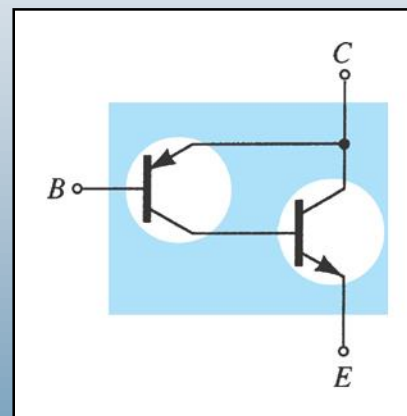
- High current gain
- Voltage gain near unity
- Low output impedance
- High input impedance



The difference is that a Darlington uses a pair of like transistors, whereas the feedback-pair configuration uses complementary transistors.

Current Mirror Circuits

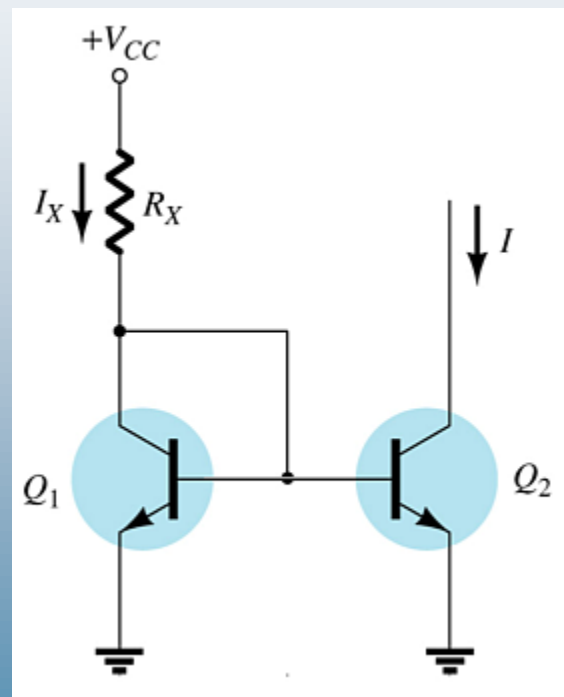
Current mirror circuits provide constant current in integrated circuits.




Ch.5 Summary

Current Source Circuits

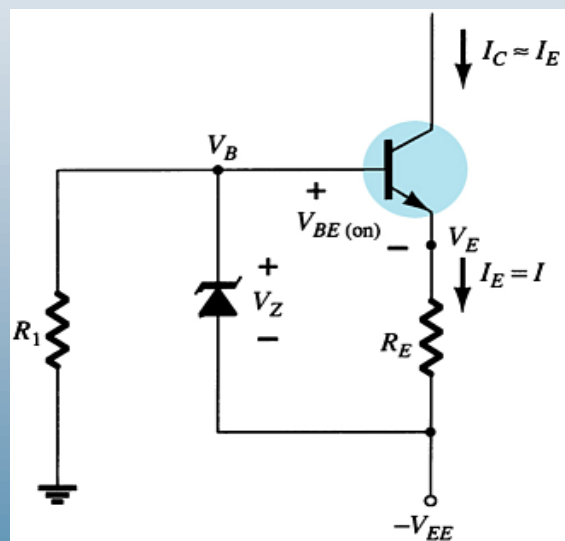Constant-current sources can be built using FETs, BJTs, and combinations of these devices.


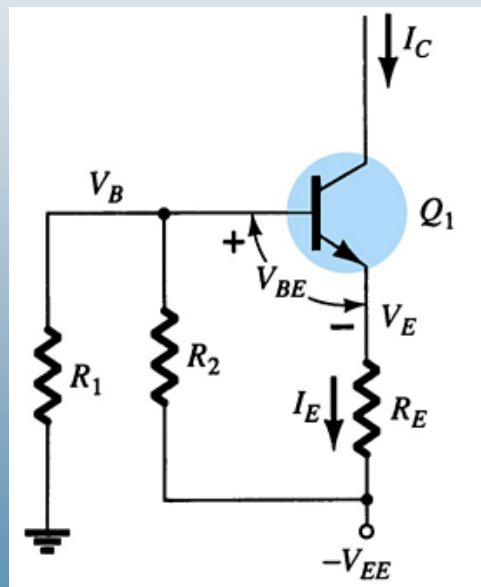
$$I \cong I_E = \frac{V_Z - V_{BE}}{R_E}$$




$$I_E \cong I_C$$

Ch.5 Summary

Current Source Circuits
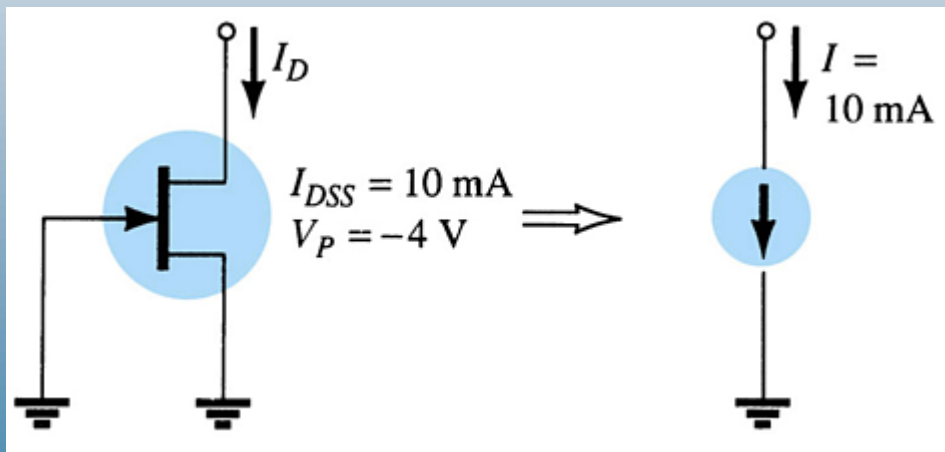
$$V_{GS} = 0V$$
$$I_D = I_{DSS} = 10 \text{ mA}$$



Ch.5 Summary

Fixed-Bias

Input impedance:



$$Z_i = R_B \parallel h_{ie}$$

Output impedance:

$$Z_o = R_C \parallel 1/h_{oe}$$

Voltage gain:
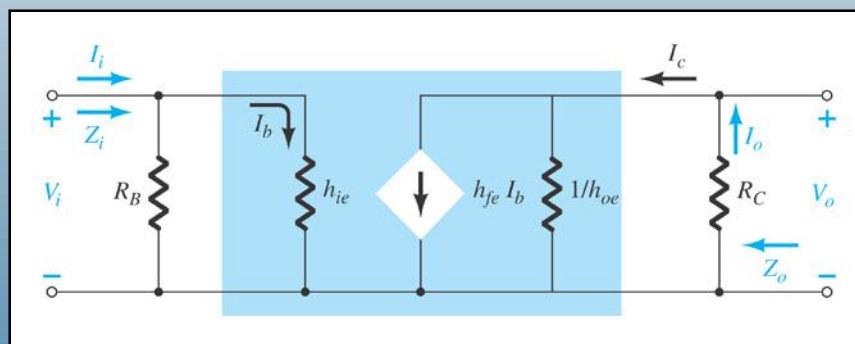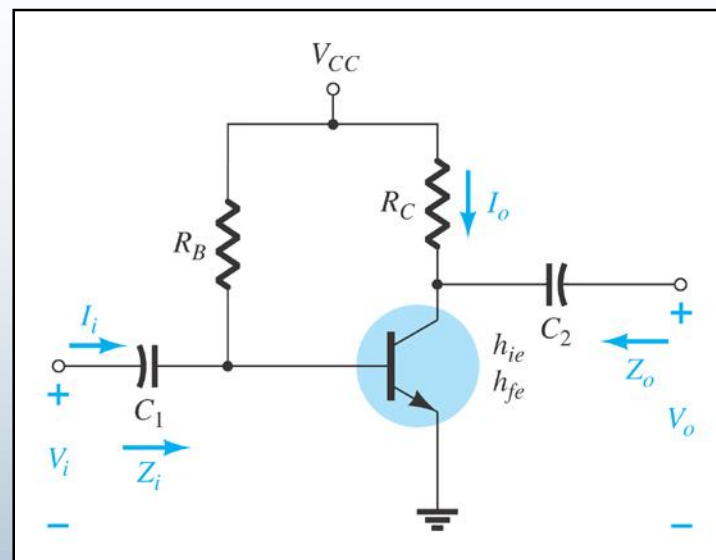
$$A_v = \frac{V_o}{V_i} = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}}$$



Current gain:

$$A_i = \frac{I_o}{I_i} \cong h_{fe}$$

Ch.5 Summary

Voltage-Divider Configuration

Input impedance:

$$Z_i = R' \parallel h_{ie}$$

Output impedance:


$$Z_o \cong R_C$$

Voltage gain:

$$A_v = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}}$$

Current gain:

$$A_i = -\frac{h_{fe}R'}{R' + h_{ie}}$$

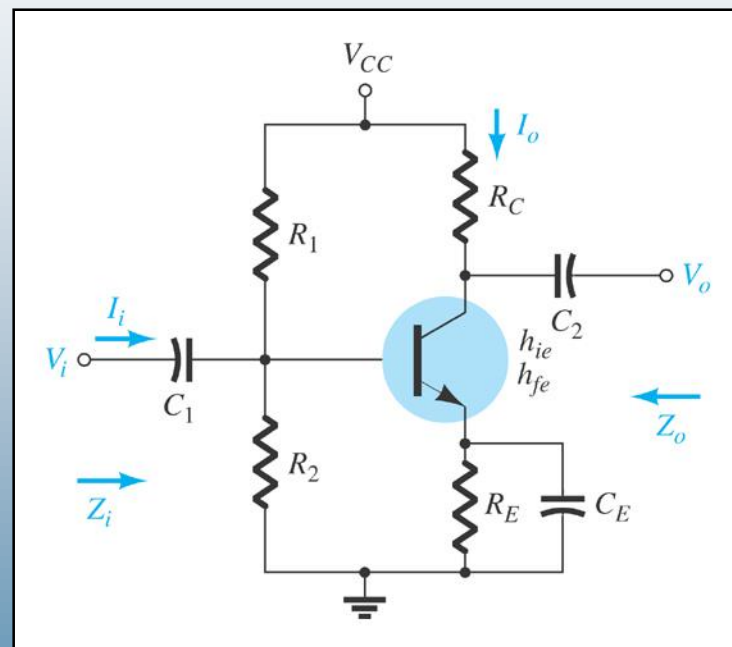

Ch.5 Summary

Emitter-Follower Configuration

Input impedance:

$$Z_b = h_{fe} R_E$$


$$Z_i = R_o \parallel Z_b$$

Output impedance:

$$Z_o \cong R_E \parallel \frac{h_{ie}}{h_{fe}}$$

Voltage gain:
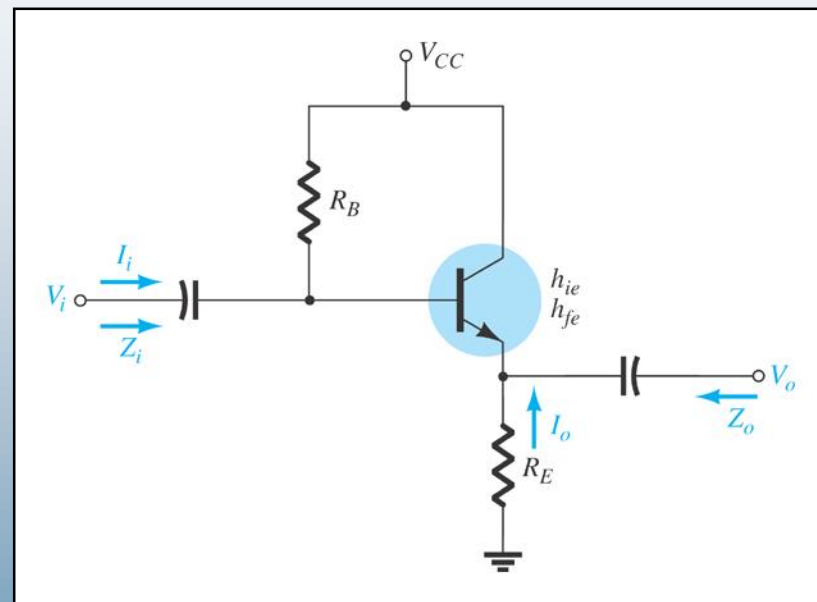
$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + h_{ie} / h_{fe}}$$



Current gain:

$$A_i = \frac{h_{fe} R_B}{R_B + Z_b}$$

$$A_i = -A_v \frac{Z_i}{R_E}$$

Ch.5 Summary

Common-Base Configuration

Input impedance:

$$Z_i = R_E \parallel h_{ib}$$

Output impedance:



$$Z_o = R_C$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -\frac{h_{fb} R_C}{h_{ib}}$$

Current gain:
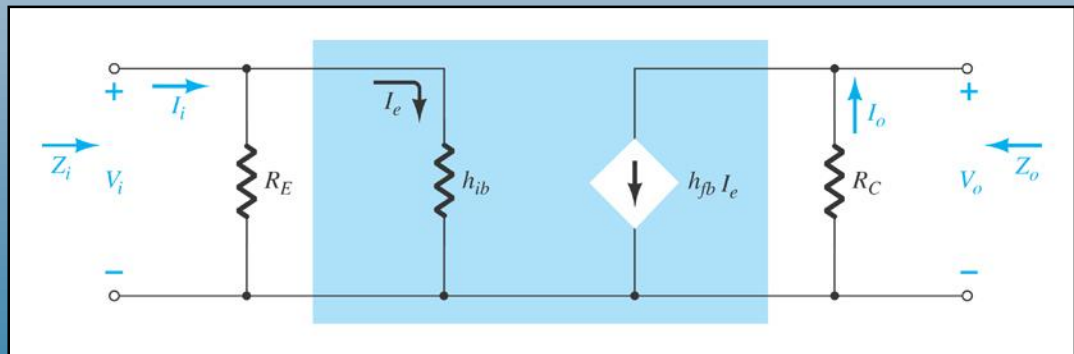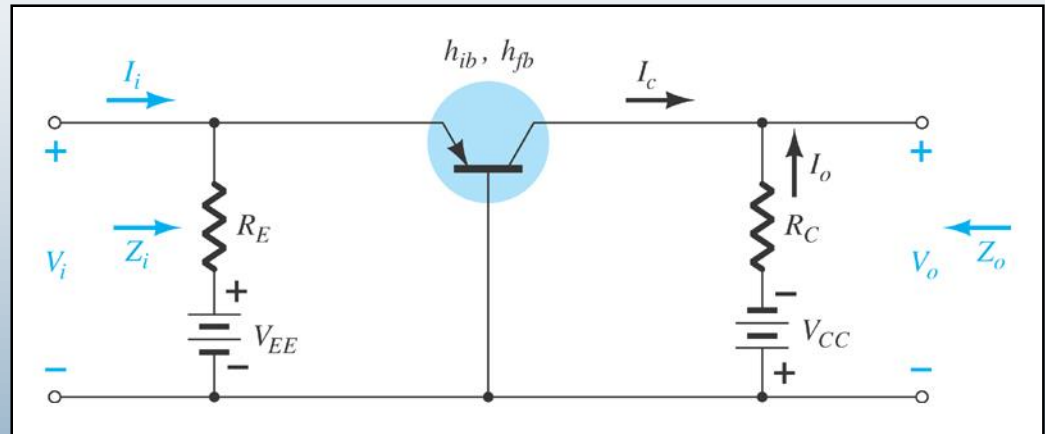
$$A_i = \frac{I_o}{I_i} = h_{fb} \cong -1$$



Ch.5 Summary

Troubleshooting

Check the DC bias voltages

- ✓ If not correct, check power supply, resistors, transistor. Also check the coupling capacitor between amplifier stages.

Check the AC voltages

- ✓ If not correct check transistor, capacitors and the loading effect of the next stage.