

Electronic Devices and Circuit Theory

Boylestad


Diode Applications

Chapter 2

Ch.2 Summary

Load-Line Analysis

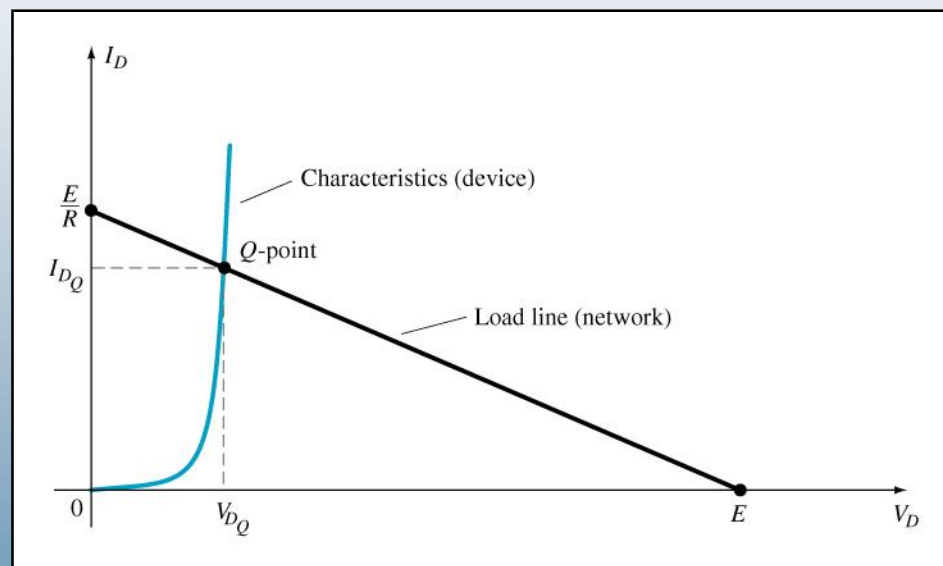The load line plots all possible combinations of diode current (I_D) and voltage (V_D) for a given circuit. The maximum I_D equals E/R , and the maximum V_D equals E .



The point where the load line and the characteristic curve intersect is the Q-point, which identifies I_D and V_D for a particular diode in a given circuit.

Ch.2 Summary


Series Diode Configurations

Forward Bias

Constants

Silicon Diode: $V_D = 0.7 \text{ V}$

Germanium Diode: $V_D = 0.3 \text{ V}$

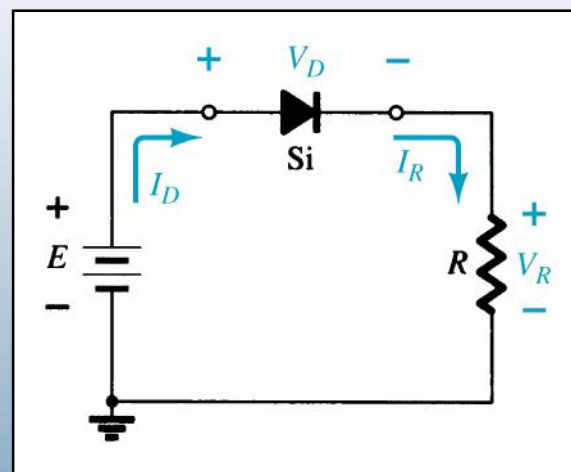

Analysis (for silicon)

$$V_D = 0.7 \text{ V} \quad (\text{or } V_D = E \text{ if } E < 0.7 \text{ V})$$

$$V_R = E - V_D$$

$$I_D = I_R = I_T = V_R / R$$

Ch.2 Summary

Series Diode Configurations

Reverse Bias



Diodes ideally behave as open circuits

Analysis

$$V_D = E$$

$$V_R = 0 \text{ V}$$

$$I_D = 0 \text{ A}$$

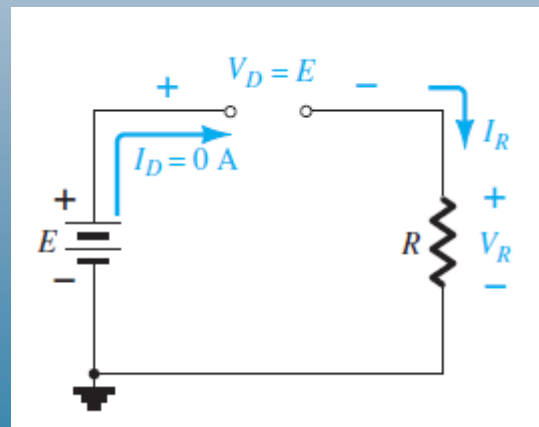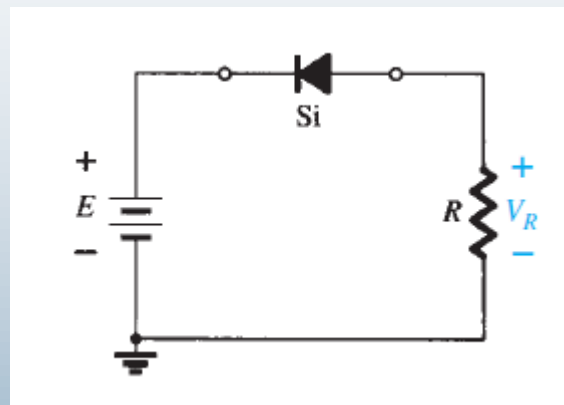

Ch.2 Summary

Parallel Diode Configurations


$$V_D = 0.7 V$$

$$V_{D1} = V_{D2} = V_o = 0.7 V$$

$$V_R = 9.3 V$$

$$I_R = \frac{E - V_D}{R} = \frac{10 V - .7 V}{.33 k\Omega} = 28 mA$$

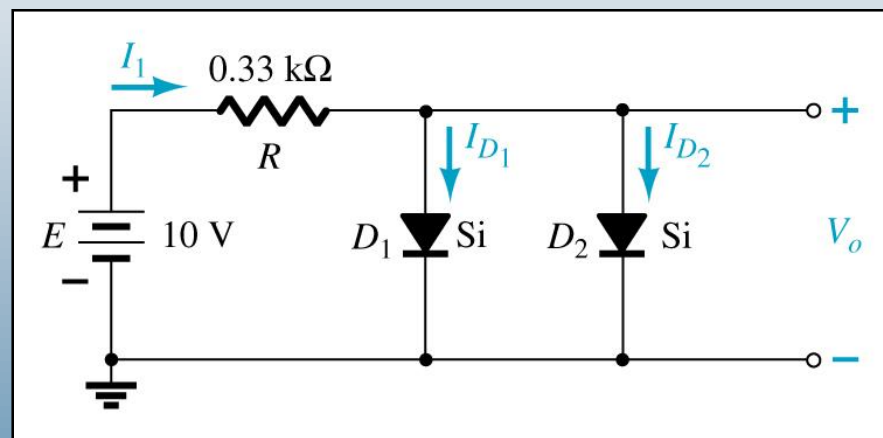
$$I_{D1} = I_{D2} = \frac{28 mA}{2} = 14 mA$$



Ch.2 Summary

Half-Wave Rectification

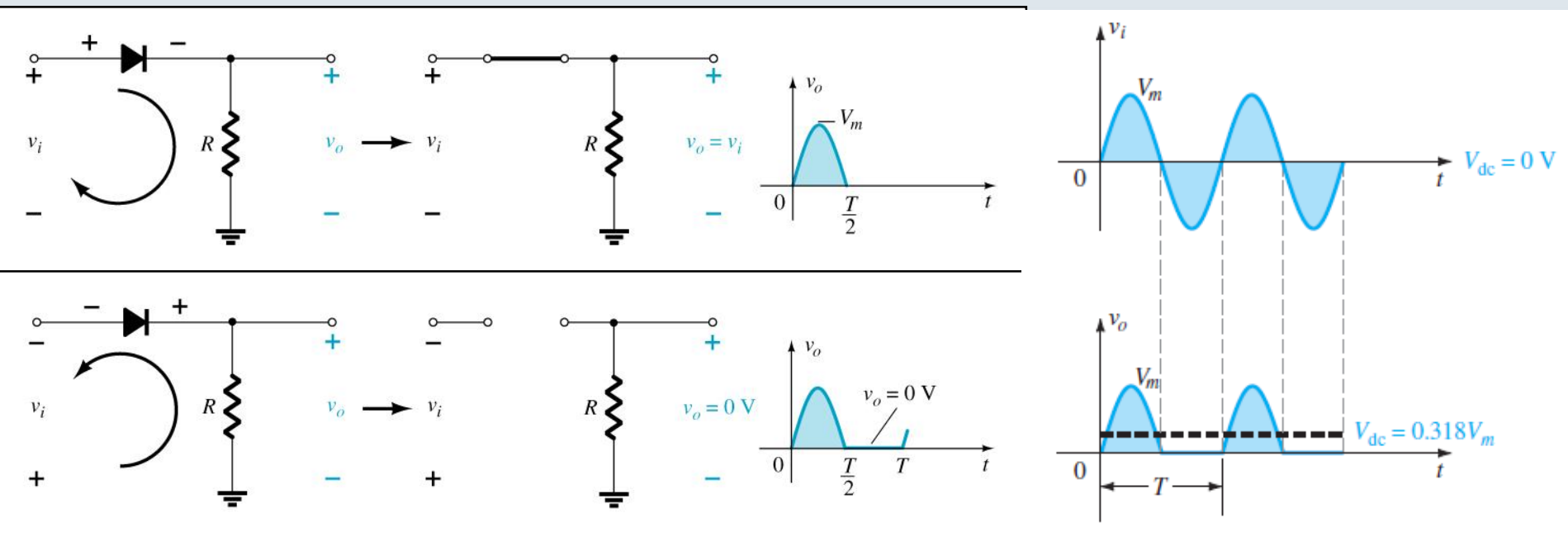The diode conducts only when it is forward biased, therefore only half of the AC cycle passes through the diode to the output.



The DC output voltage is $(1/\pi) \times V_m = 0.318V_m$, where V_m = the peak AC voltage.

Ch.2 Summary

PIV (PRV)

Because the diode is only forward biased for one-half of the AC cycle, it is also reverse biased for one-half cycle.

It is important that the reverse breakdown voltage rating of the diode be high enough to **withstand** the peak, reverse-biasing AC voltage.

$$\text{PIV (or PRV)} > V_m$$

Where **PIV** = Peak inverse voltage

PRV = Peak reverse voltage

V_m = Peak AC voltage

Ch.2 Summary


Full-Wave Rectification

The rectification process can be improved by using a full-wave rectifier circuit.

Full-wave rectification produces a greater DC output:


Half-wave: $V_{dc} = 0.318 V_m$

Full-wave: $V_{dc} = 0.636 V_m$

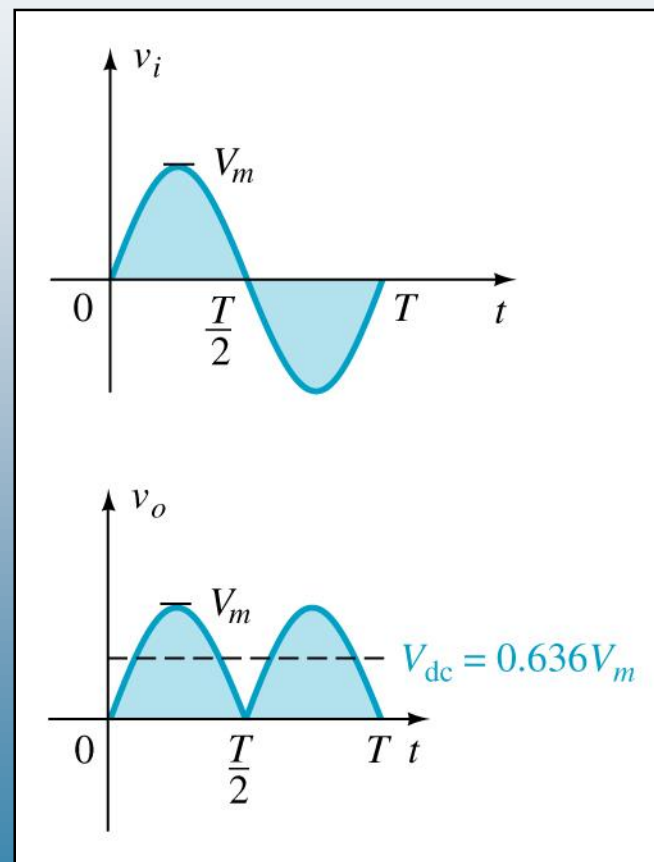

Ch.2 Summary


Full-Wave Rectification

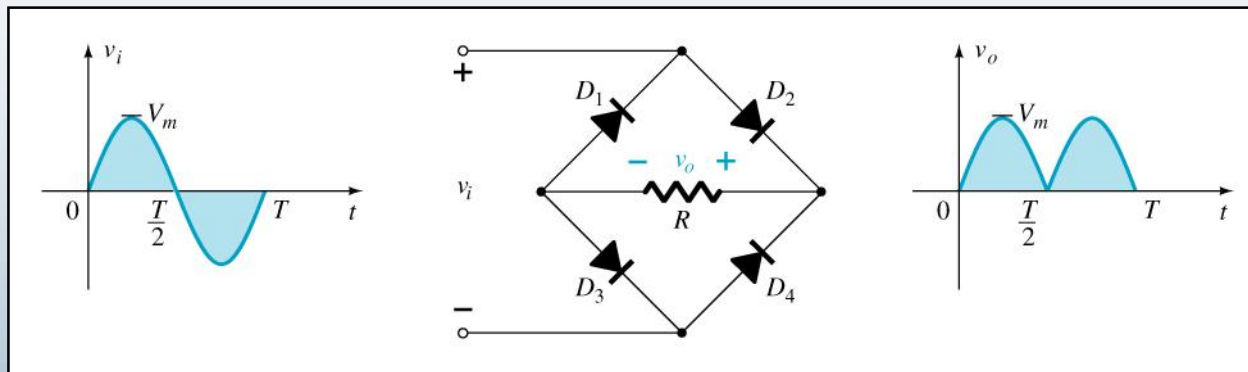

Bridge Rectifier


A full-wave rectifier with four diodes that are connected in a bridge configuration

$$V_{DC} = 0.636 V_m$$

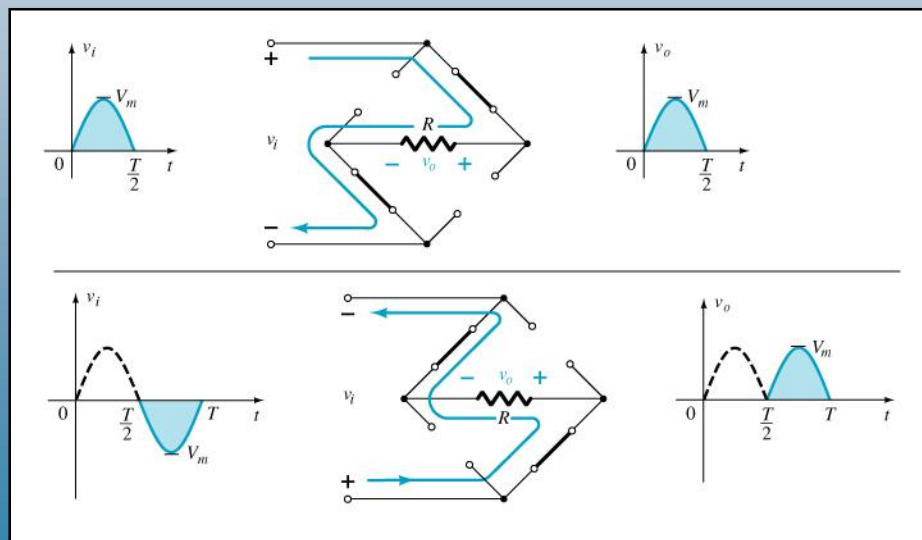

Ch.2 Summary


Full-Wave Rectification

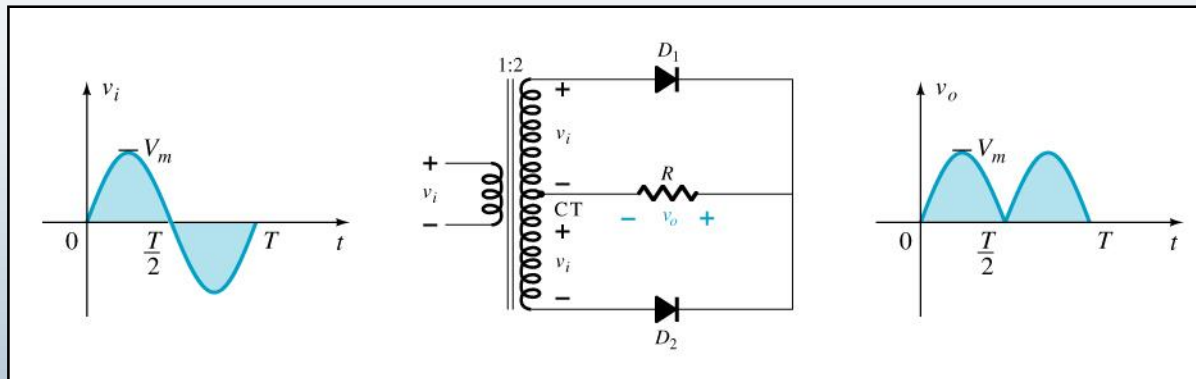

Center-Tapped Transformer Rectifier

Requires two diodes and a center-tapped transformer

$$V_{DC} = 0.636 V_m$$

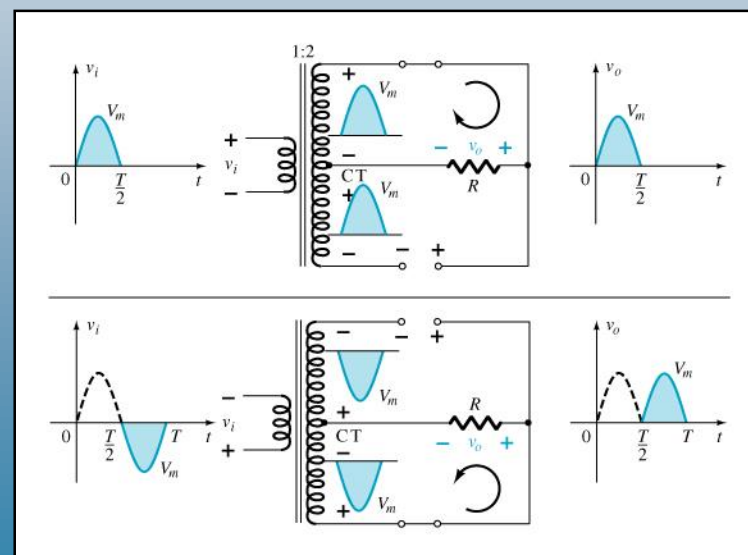

Ch.2 Summary

Summary of Rectifier Circuits

Rectifier	Ideal V_{DC}	Realistic V_{DC}
Half Wave Rectifier	$V_{DC} = 0.318 V_m$	$V_{DC} = 0.318 V_m - 0.7$
Bridge Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 2(0.7 \text{ V})$
Center-Tapped Transformer Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 0.7 \text{ V}$


V_m = the peak AC voltage

Ch.2 Summary

Diode Clippers

The diode in a series clipper “clips” any voltage that does not forward bias it:

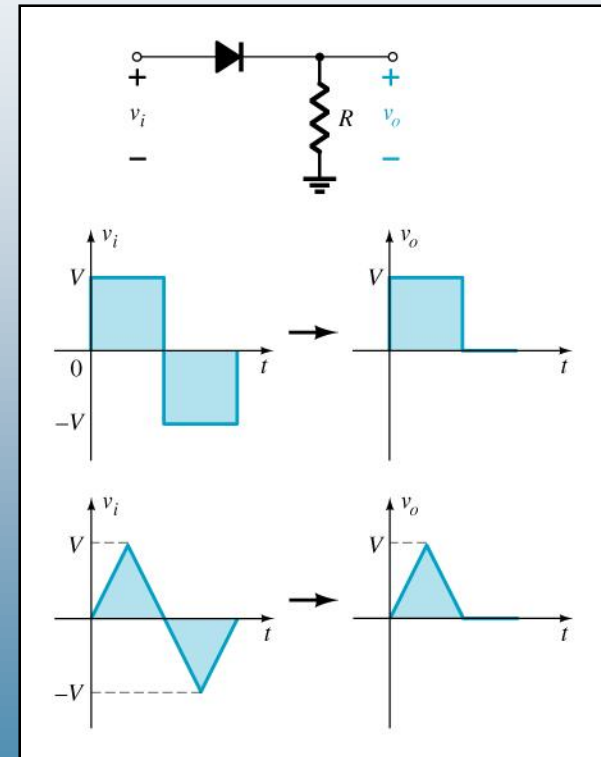- A reverse-biasing polarity
- A forward-biasing polarity less than 0.7 V (for a silicon diode)



Biased Clippers




Ch.2 Summary

Parallel Clippers

The diode in a parallel clipper circuit “clips” any voltage that forward biases it.

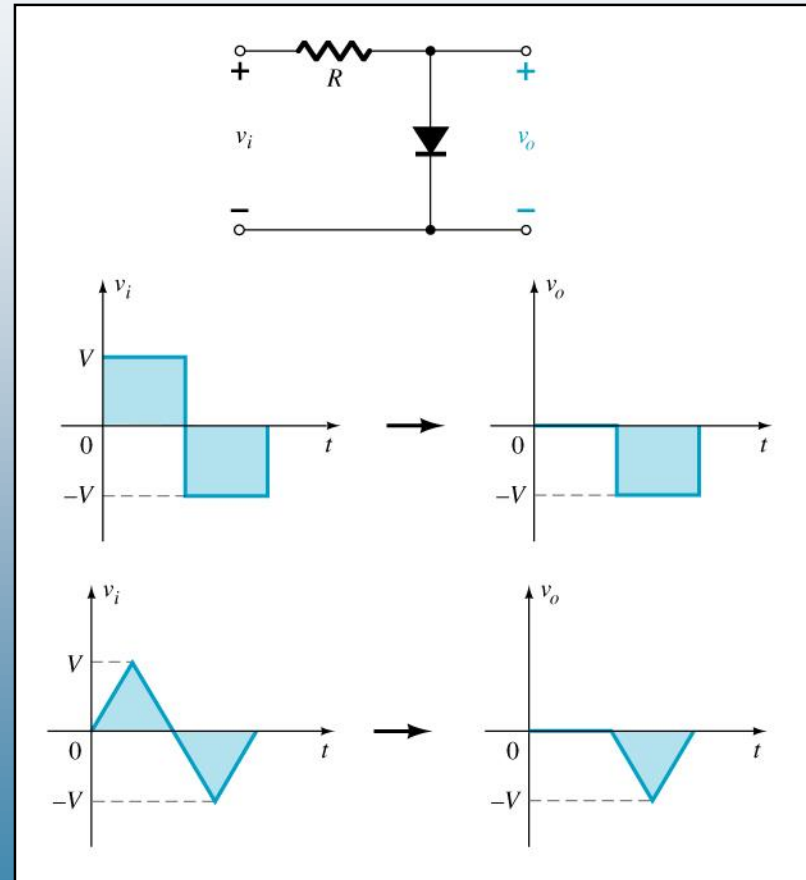DC biasing can be added in series with the diode to change the clipping level.




Ch.2 Summary


Summary of Clipper Circuits

Simple Series Clippers (Ideal Diodes)





POSITIVE

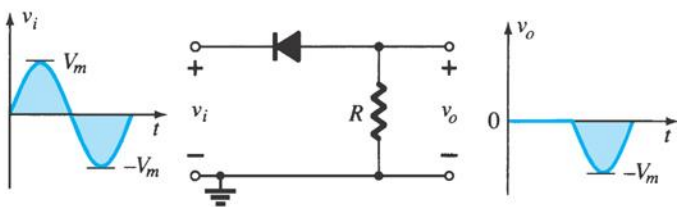

NEGATIVE

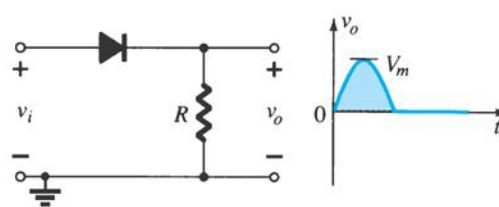



Biased Series Clippers (Ideal Diodes)

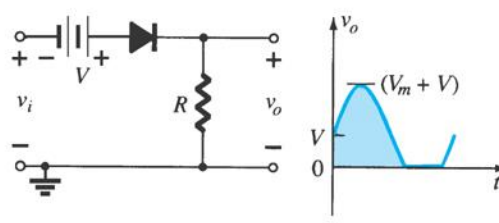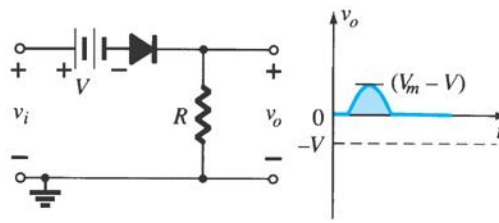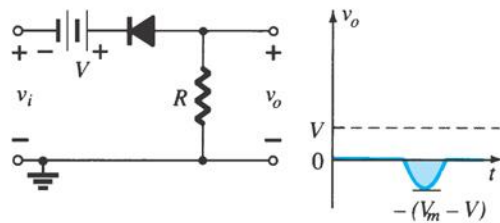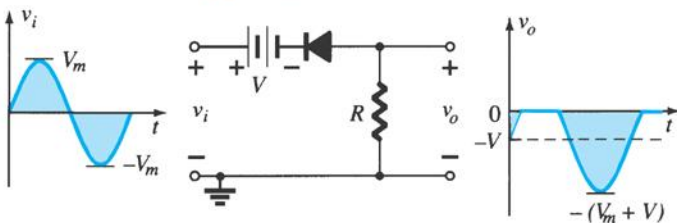






Ch.2 Summary

Summary of Clipper Circuits

Simple Parallel Clippers (Ideal Diodes)

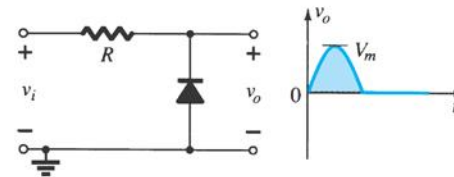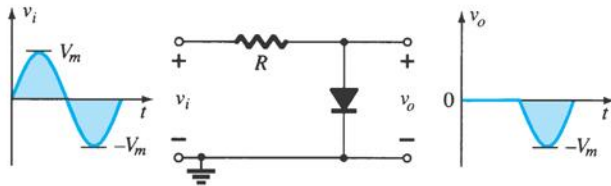



Biased Parallel Clippers (Ideal Diodes)

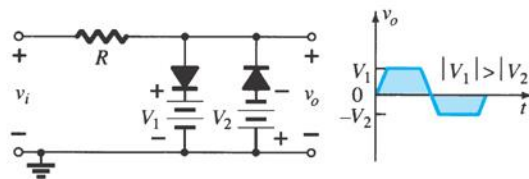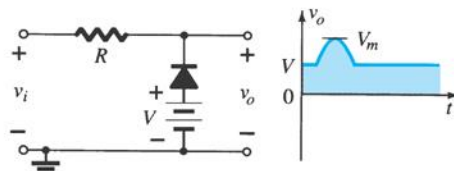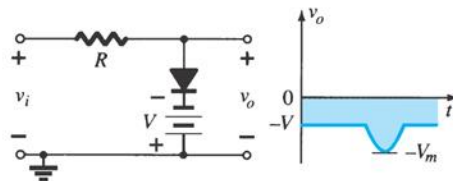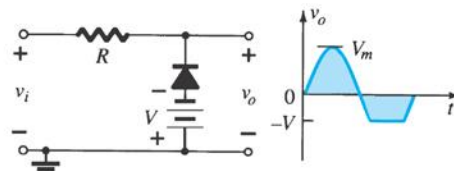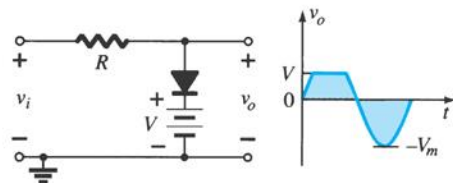

Ch.2 Summary

Clampers

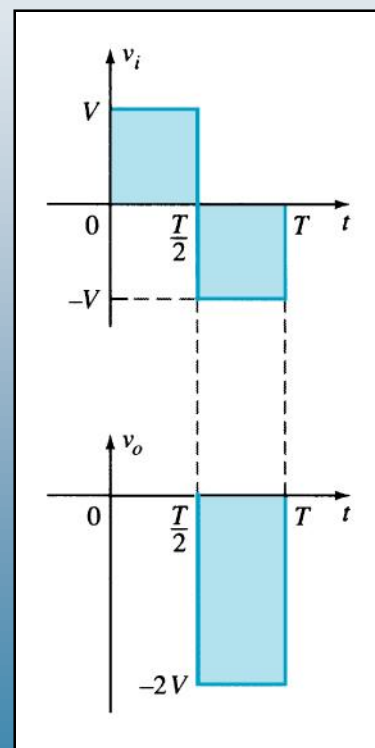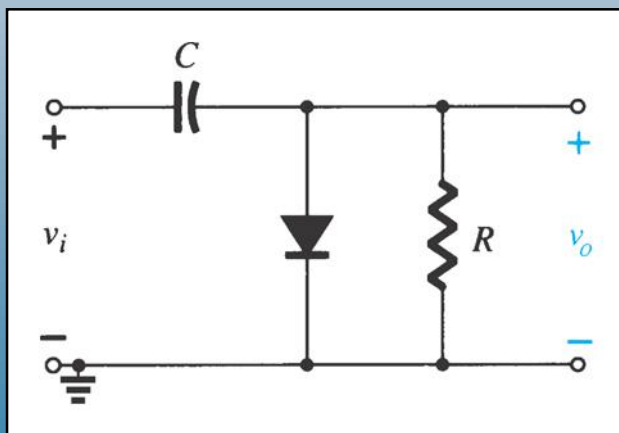
A diode and capacitor can be combined to “clamp” an AC signal to a specific DC level.




Ch.2 Summary

Biased Clamper Circuits

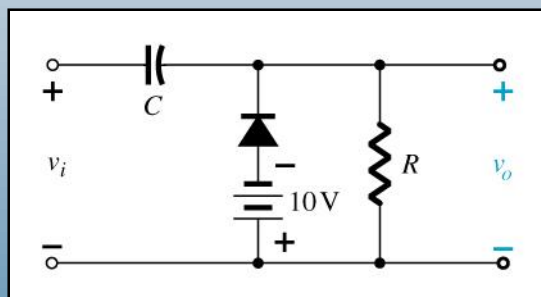The input signal can be any type of waveform such as a sine, square, or triangle wave.



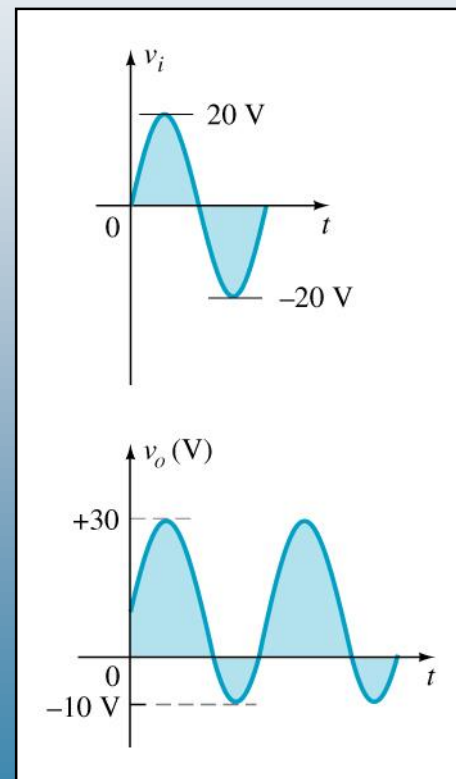
The DC source lets you adjust the DC clamping level.



Ch.2 Summary

Summary of Clamper Circuits

Clamping Networks

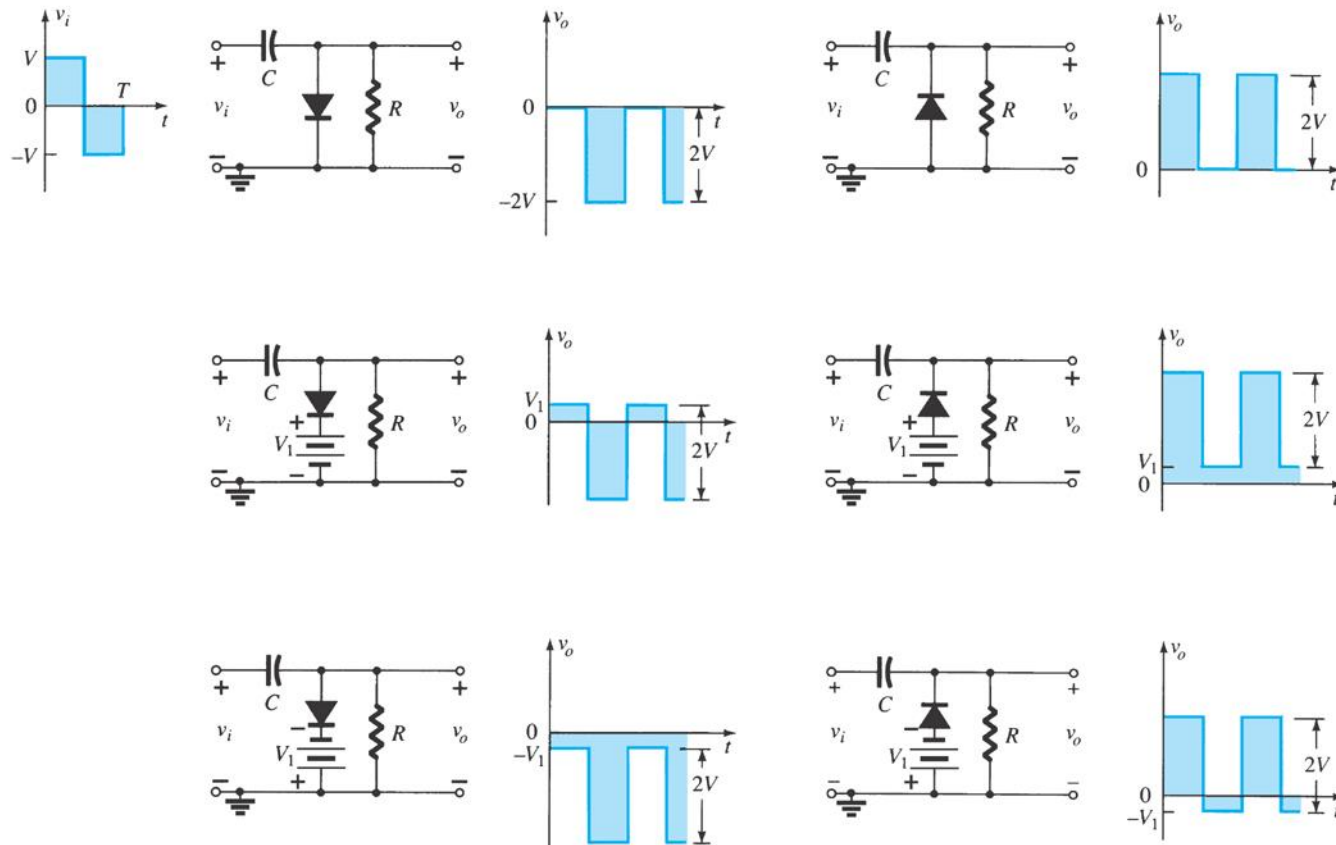

Ch.2 Summary

Zener Diodes



The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

When $V_i \geq V_Z$

- The Zener is on
- Voltage across the Zener is V_Z
- Zener current: $I_Z = I_R - I_{RL}$
- The Zener Power: $P_Z = V_Z I_Z$

When $V_i < V_Z$

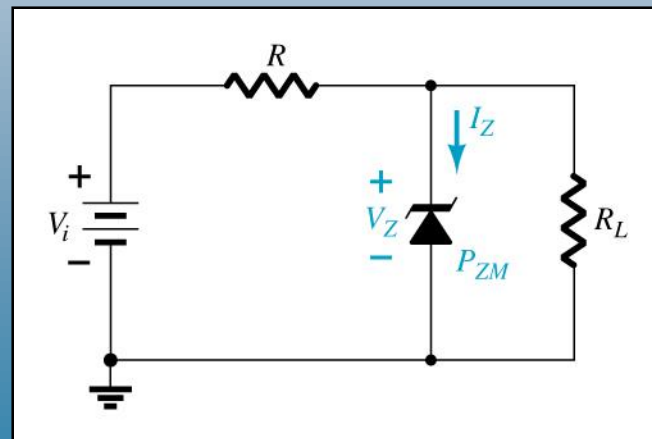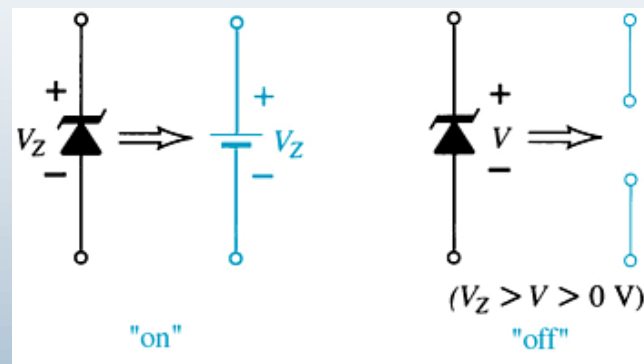- The Zener is off
- The Zener acts as an open circuit



Ch.2 Summary

Zener Resistor Values

If R is too large, the Zener diode cannot conduct because $I_Z < I_{ZK}$. The minimum current is given by:

$$I_{Lmin} = I_R - I_{ZK}$$

The *maximum* value of resistance is:


$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

If R is too small, $I_Z > I_{ZM}$. The maximum allowable current for the circuit is given by:

$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$

The *minimum* value of resistance is:

$$R_{Lmin} = \frac{RV_Z}{V_i - V_Z}$$

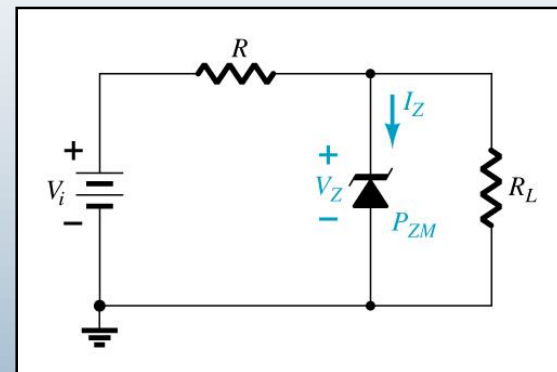

Voltage-Multiplier Circuits

Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:


Voltage Doubler

Voltage Tripler

Voltage Quadrupler

Ch.2 Summary

Voltage Doubler

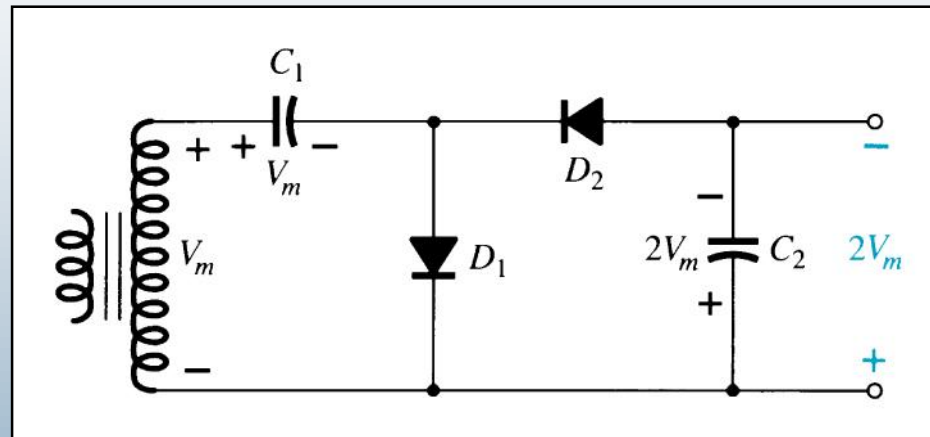

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

Ch.2 Summary

Voltage Doubler

Positive Half-Cycle

D_1 conducts

D_2 is switched off

Capacitor C_1 charges to V_m


Negative Half-Cycle

D_1 is switched off

D_2 conducts


Capacitor C_2 charges to V_m

$$V_{\text{out}} = V_{C2} = 2V_m$$

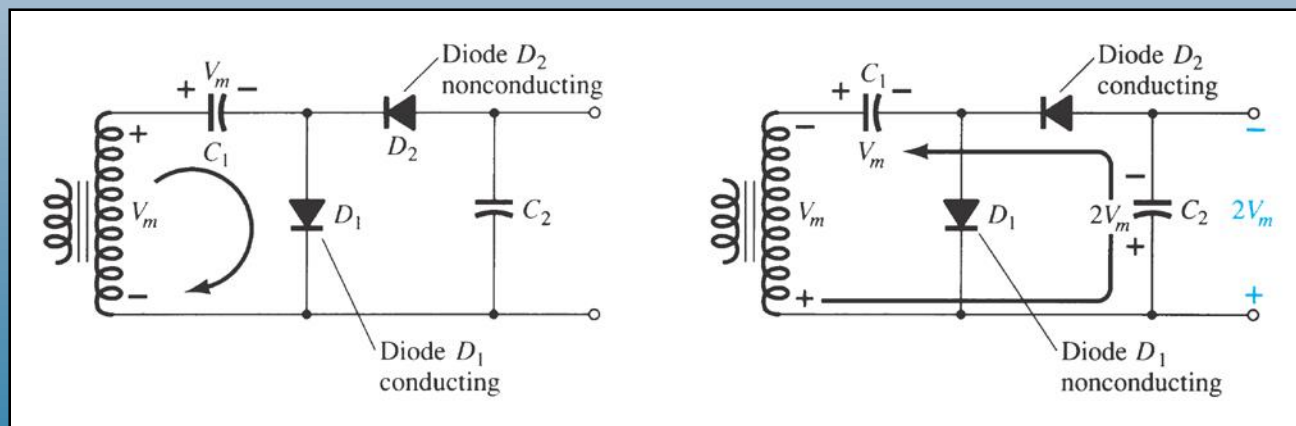

Ch.2 Summary

Voltage Tripler and Quadrupler

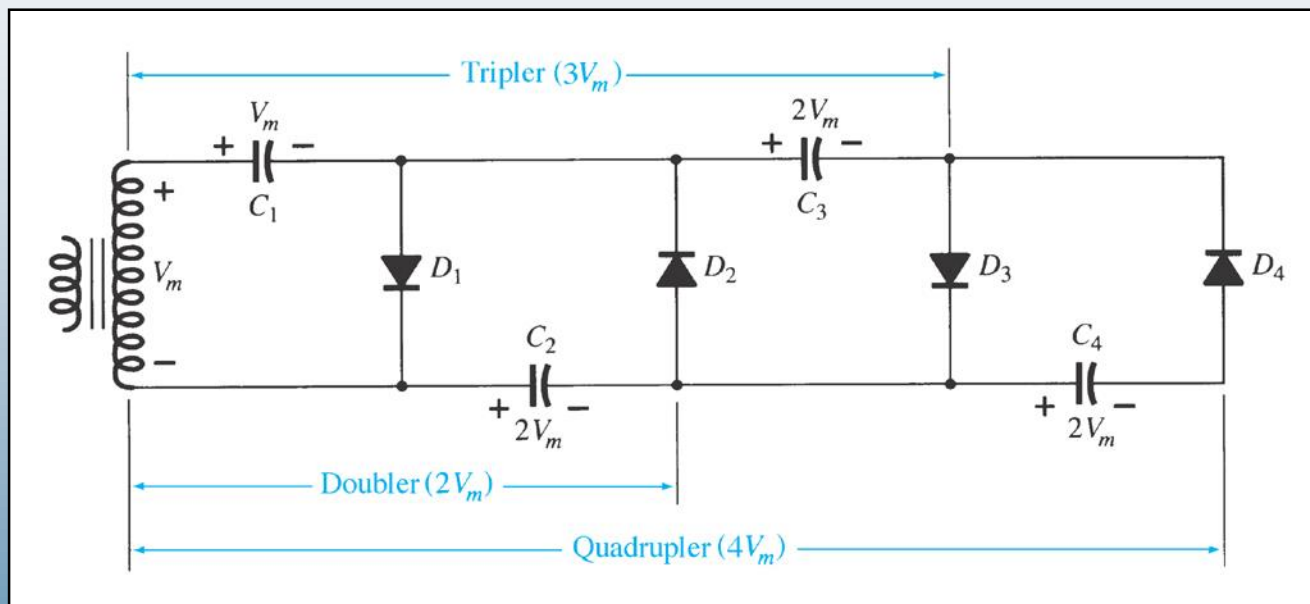

Ch.2 Summary

Practical Applications

Rectifier Circuits

Conversions of AC to DC for DC operated circuits
Battery Charging Circuits

Simple Diode Circuits

Protective Circuits against
Overcurrent
Polarity Reversal
Currents caused by an inductive kick in a relay circuit

Zener Circuits

Overvoltage Protection
Setting Reference Voltages