

# **Electronic Devices and Circuit Theory**

Boylestad

## **Bipolar Junction Transistors**

### **Chapter 3**

## Ch.3 Summary

# Transistor Construction

There are two types of transistors:


*pnp* and *npn*

The terminals are labeled:

**E - Emitter**

**B - Base**

**C - Collector**

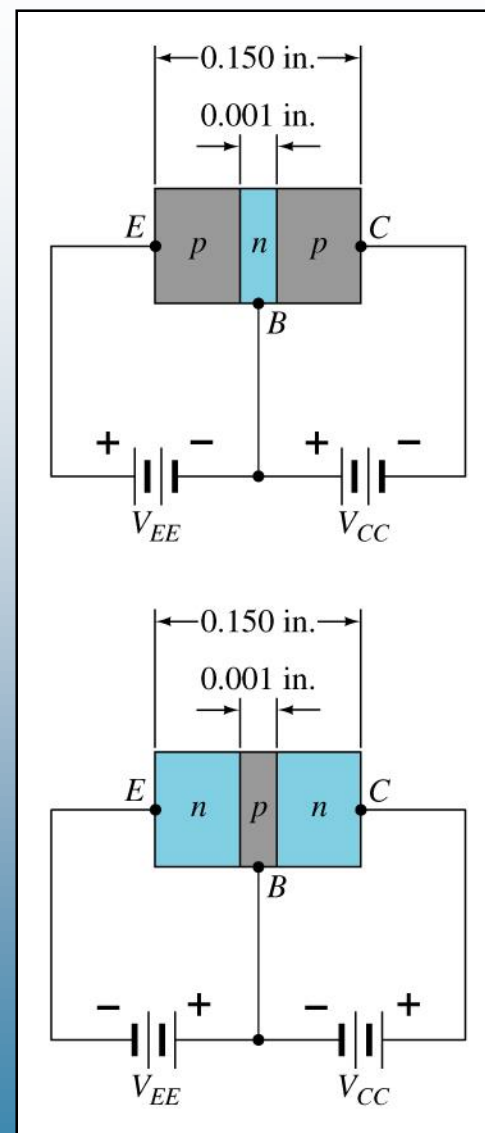

*pnp*

*npn*


## Ch.3 Summary

# Transistor Operation

With the external sources,  $V_{EE}$  and  $V_{CC}$ , connected as shown:

The emitter-base junction is forward biased

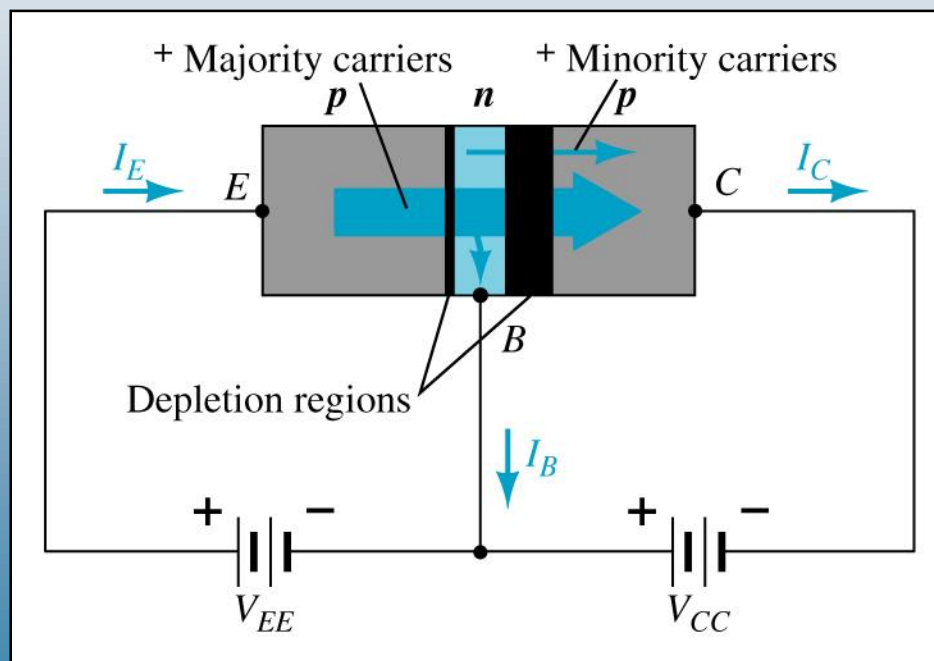The base-collector junction is reverse biased



## Ch.3 Summary


# Currents in a Transistor

Emitter current is the sum of the collector and base currents:

$$I_E = I_C + I_B$$


The collector current is comprised of two currents:
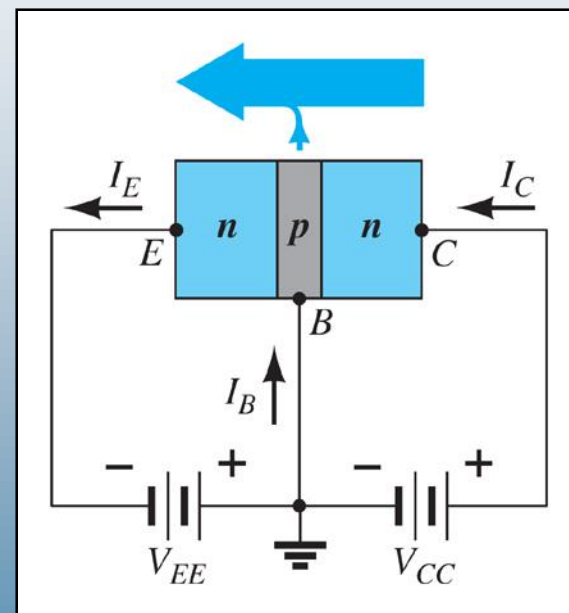
$$I_C = I_{C(\text{majority})} + I_{CO(\text{minority})}$$



## Ch.3 Summary

# Common-Base Configuration

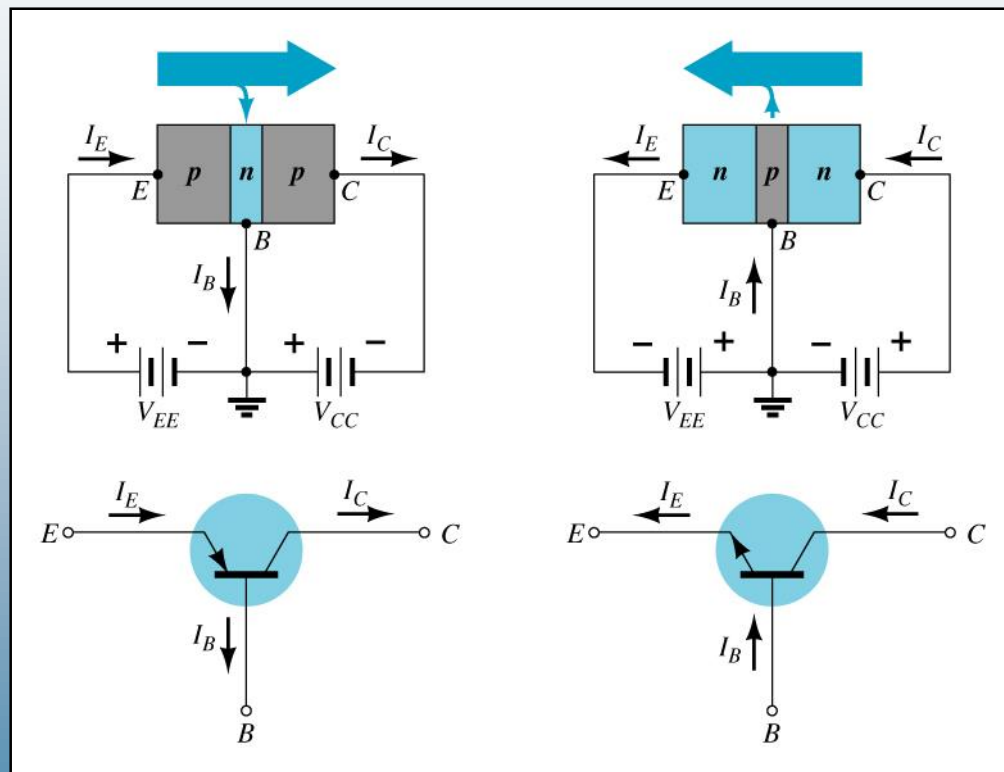


The base is common to both input (emitter–base) junction and output (collector–base) junction of the transistor.

## Ch.3 Summary

# Common-Base Amplifier
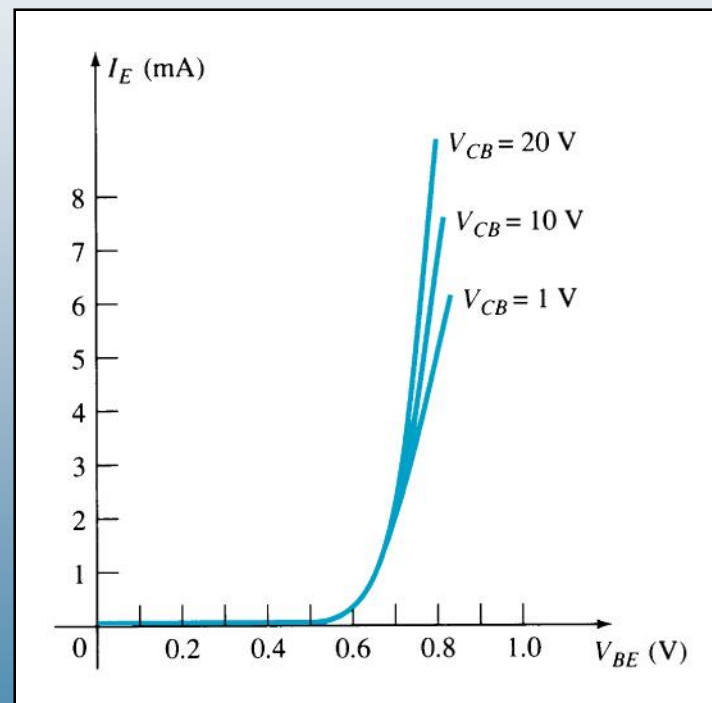
### Input Characteristics

This curve shows the relationship between of input current ( $I_E$ ) to input voltage ( $V_{BE}$ ) for three output voltage ( $V_{CB}$ ) levels.




## Ch.3 Summary

# Common-Base Amplifier
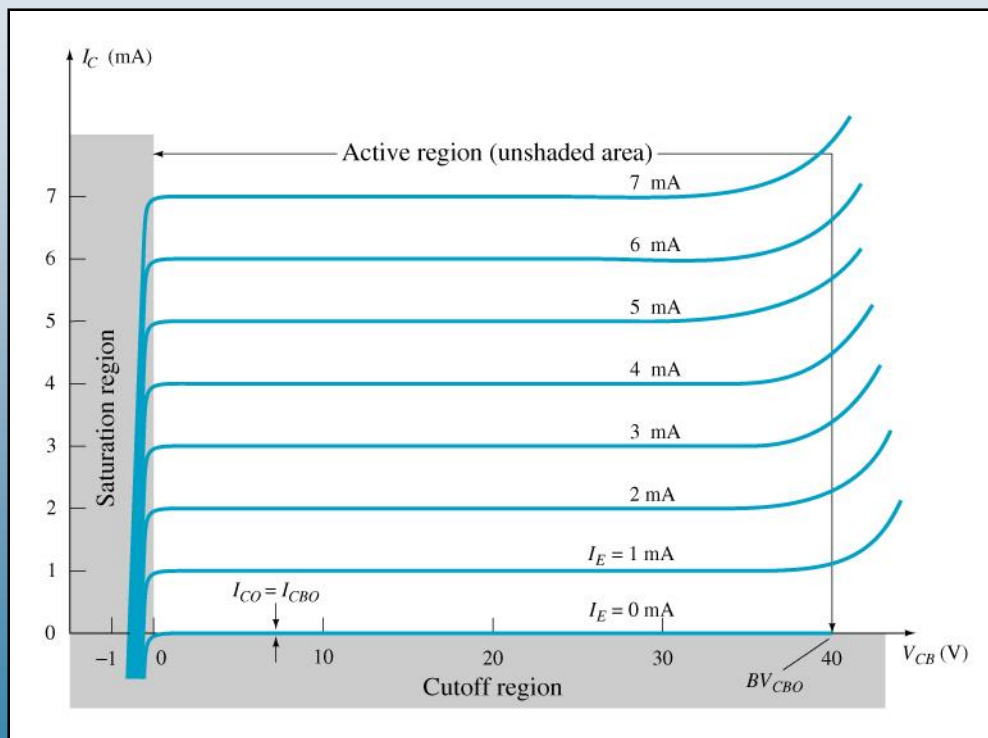
## Output Characteristics

This graph demonstrates the output current ( $I_C$ ) to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).



## Ch.3 Summary

# Operating Regions

### Active

Operating range of the amplifier.

### Cutoff

The amplifier is basically off. There is voltage, but little current.

### Saturation

The amplifier is fully on. There is current, but little voltage.



# Approximations

**Emitter and collector currents:**

$$I_C \cong I_E$$

**Base-emitter voltage:**

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$

## Ch.3 Summary

# Alpha ( $\alpha$ )

Alpha ( $\alpha$ ) is the ratio of  $I_C$  to  $I_E$ :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$I_C = I_{C(\text{majority})} + I_{CO(\text{minority})}$$

Ideally:  $\alpha = 1$

In reality:  $\alpha$  falls somewhere between 0.9 and 0.998


$$I_C = \alpha I_E + I_{CBO}$$

Alpha ( $\alpha$ ) in the AC mode:

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$

## Ch.3 Summary

# Transistor Amplifier

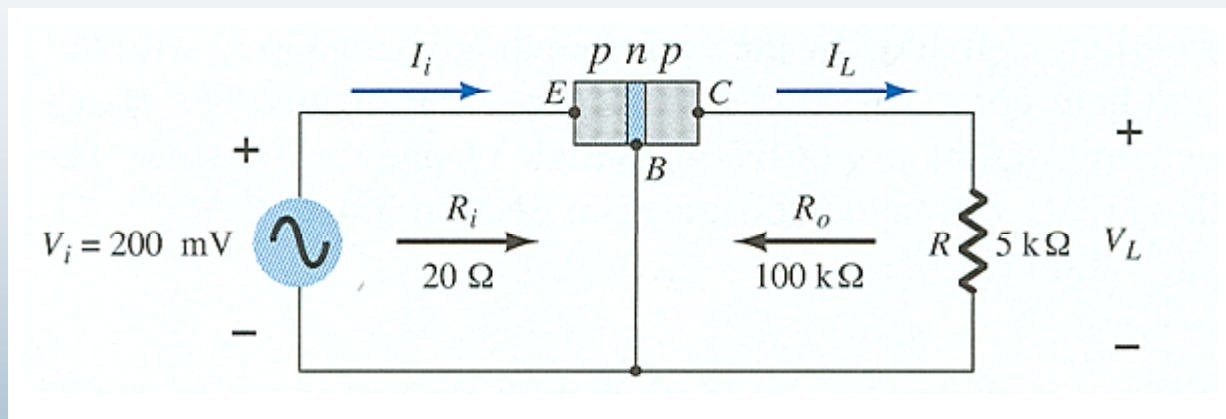

### Currents and Voltages:

$$I_E = I_i = \frac{V_i}{R_i} = \frac{200\text{mV}}{20\Omega} = 10\text{mA}$$

$$I_C \cong I_E$$

$$I_L \cong I_i = 10\text{mA}$$

$$V_L = I_L R = (10\text{mA})(5\text{k}\Omega) = 50\text{V}$$

### Voltage Gain:


$$A_V = \frac{V_L}{V_i} = \frac{50\text{V}}{200\text{mV}} = 250$$

## Ch.3 Summary
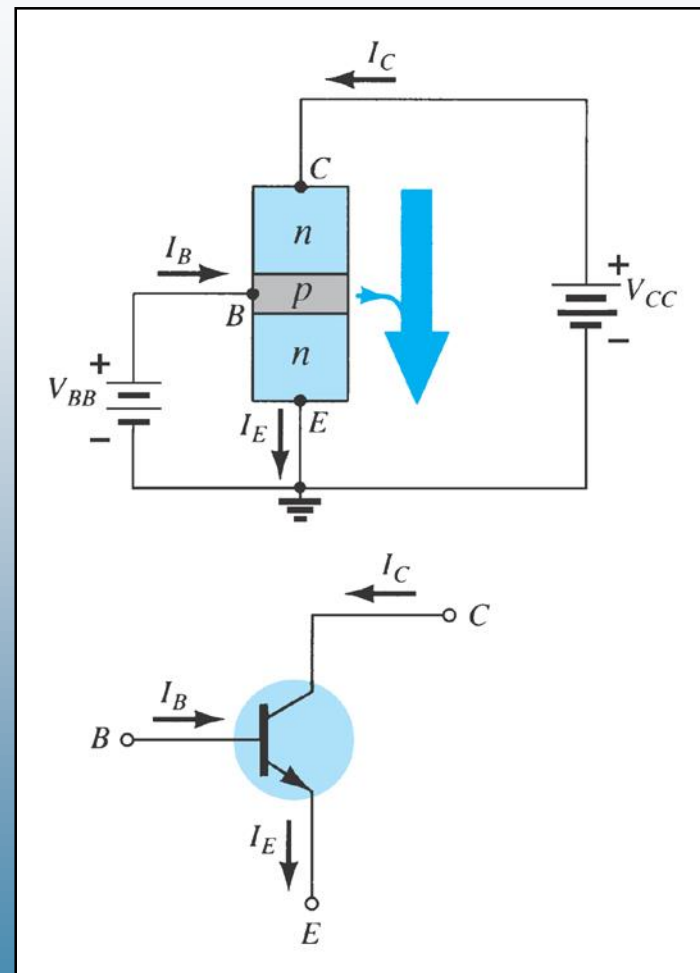
# Common-Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter) circuits.

The input is applied to the base and the output is taken from the collector.




## Ch.3 Summary

# Common-Emitter Characteristics

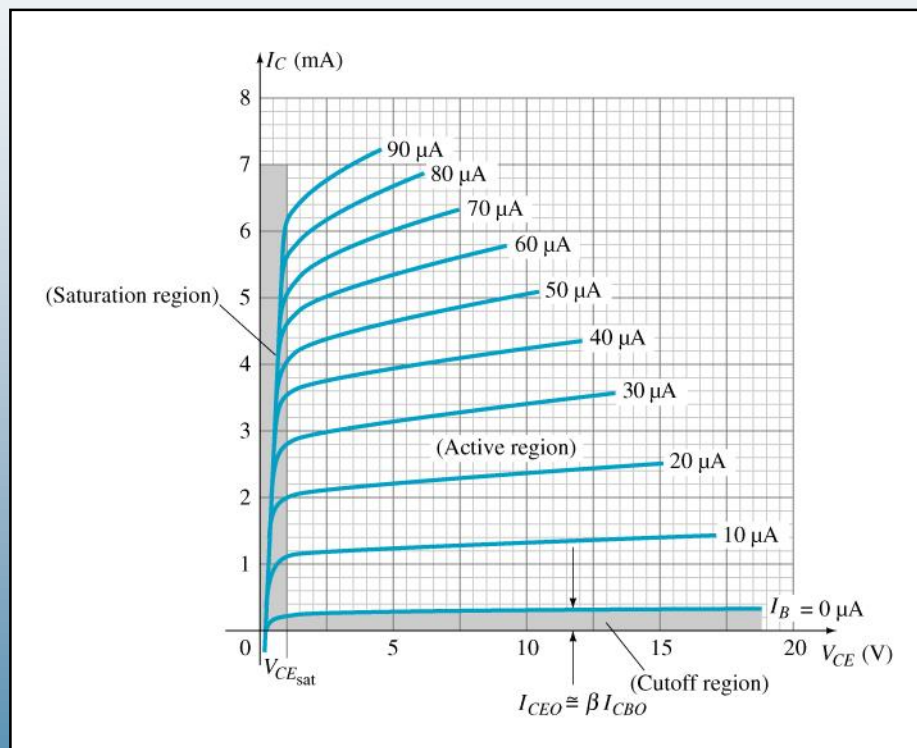

### Collector Characteristics

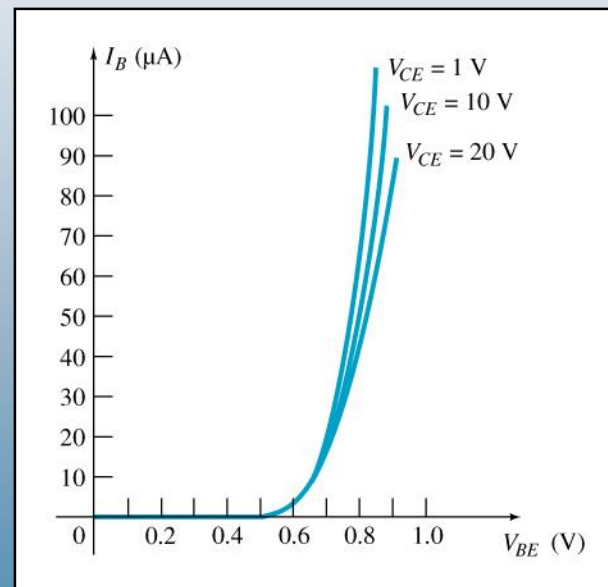

### Base (input) Characteristics

## Ch.3 Summary

# Common-Emitter Amplifier Currents

### Ideal Currents

$$I_E = I_C + I_B \qquad I_C = \alpha I_E$$

### Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

$I_{CBO}$  is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When  $I_B = 0 \mu\text{A}$  the transistor is in cutoff, but there is some minority current flowing called  $I_{CEO}$ .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

## Ch.3 Summary

# Beta ( $\beta$ )

$\beta$  represents the amplification factor of a transistor.

*In DC mode:*

$$\beta_{dc} = \frac{I_C}{I_B}$$

*In AC mode:*

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}}$$

$\beta_{ac}$  is sometimes referred to as  $h_{fe}$ , a term used in transistor modeling calculations


# Ch.3 Summary

## Beta ( $\beta$ )

### Determining $\beta$ from a Graph

$$\begin{aligned}\beta_{AC} &= \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu\text{A} - 20 \mu\text{A})} \\ &= \frac{1 \text{ mA}}{10 \mu\text{A}} \Big|_{V_{CE}=7.5 \text{ V}} \\ &= 100\end{aligned}$$

$$\begin{aligned}\beta_{DC} &= \frac{2.7 \text{ mA}}{25 \mu\text{A}} \Big|_{V_{CE}=7.5 \text{ V}} \\ &= 108\end{aligned}$$

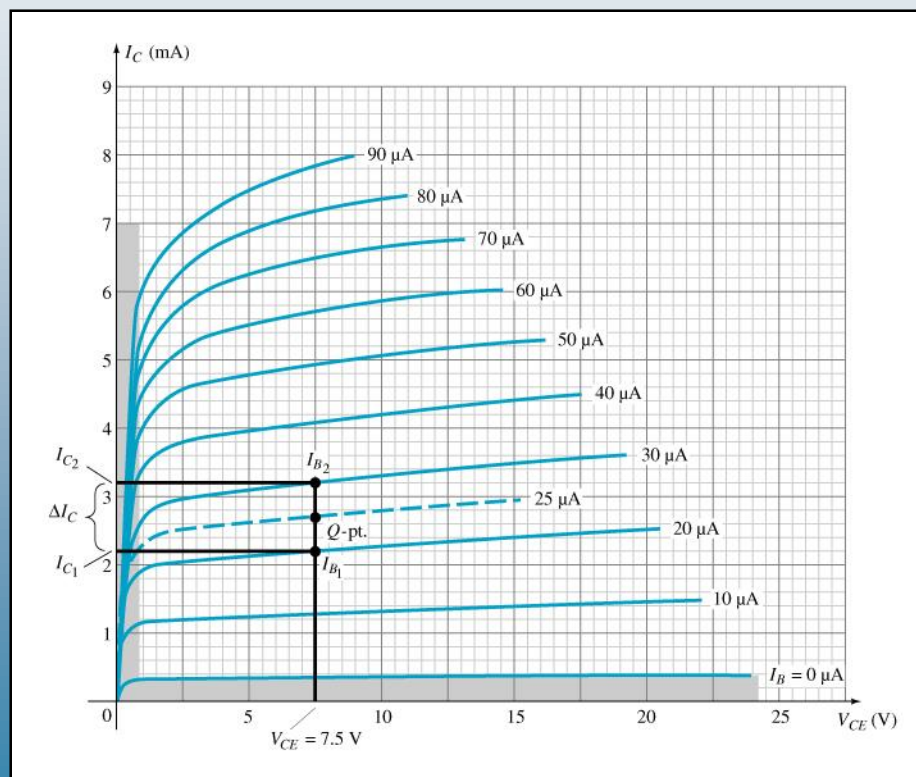



## Ch.3 Summary

### Beta ( $\beta$ )

Relationship between amplification factors  $\beta$  and  $\alpha$  :

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{\alpha - 1}$$

Relationship Between Currents:


$$I_C = \beta I_B$$

$$I_E = (\beta + 1)I_B$$

## Ch.3 Summary
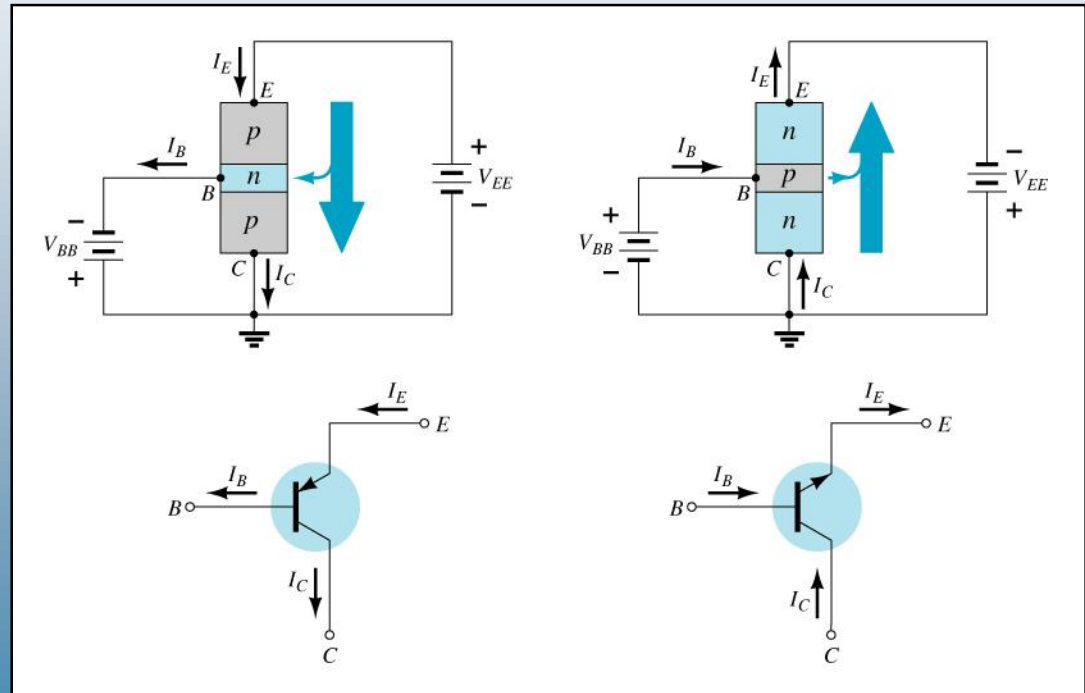
# Common-Collector Configuration


The input is on the base and the output is on the emitter.



## Ch.3 Summary
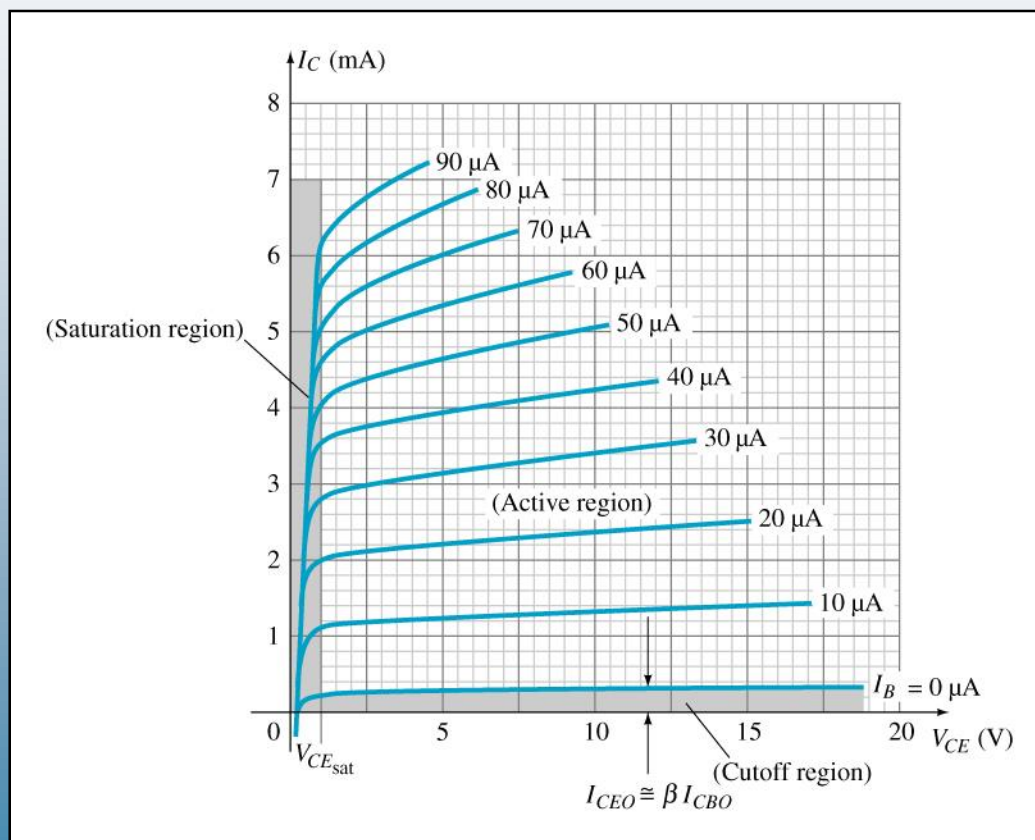
# Common-Collector Configuration

The characteristics are similar to those of the common-emitter amplifier, except the vertical axis is  $I_E$ .



## Ch.3 Summary


# Operating Limits

$V_{CE}$  is maximum and  $I_C$  is minimum in the cutoff region.

$$I_{C(\max)} = I_{CEO}$$

$I_C$  is maximum and  $V_{CE}$  is minimum in the saturation region.

$$V_{CE(\max)} = V_{CE(sat)} = V_{CEO}$$

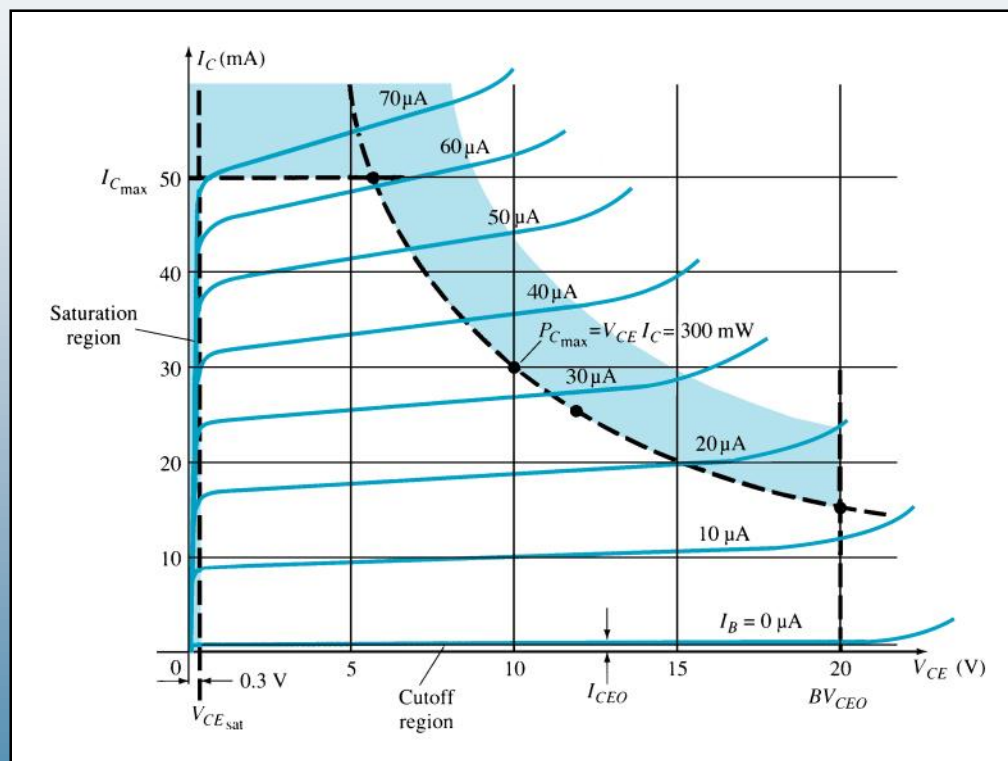

The transistor operates in the active region between saturation and cutoff.

## Ch.3 Summary

# Power Dissipation

**Common-base:**

$$P_{Cmax} = V_{CB} I_C$$

**Common-emitter:**

$$P_{Cmax} = V_{CE} I_C$$

**Common-collector:**

$$P_{Cmax} = V_{CE} I_E$$

## Ch.3 Summary

# Transistor Specification Sheet

### MAXIMUM RATINGS

| Rating   | Symbol         | 2N4123      | Unit        |
|--|----------------|-------------|-------------|
| Collector-Emitter Voltage  | $V_{CEO}$      | 30          | Vdc         |
| Collector-Base Voltage   | $V_{CBO}$      | 40          | Vdc         |
| Emitter-Base Voltage   | $V_{EBO}$      | 5.0         | Vdc         |
| Collector Current – Continuous   | $I_C$          | 200         | mAdc        |
| Total Device Dissipation @ $T_A = 25^\circ\text{C}$<br>Derate above $25^\circ\text{C}$ | $P_D$          | 625<br>5.0  | mW<br>mW/°C |
| Operating and Storage Junction<br>Temperature Range                                    | $T_j, T_{stg}$ | -55 to +150 | °C          |

### THERMAL CHARACTERISTICS

| Characteristic                          | Symbol          | Max  | Unit |
|---|-----------------|------|------|
| Thermal Resistance, Junction to Case    | $R_{\theta JC}$ | 83.3 | °C W |
| Thermal Resistance, Junction to Ambient | $R_{\theta JA}$ | 200  | °C W |



## Ch.3 Summary

# Transistor Specification Sheet

### ELECTRICAL CHARACTERISTICS ( $T_A = 25^\circ\text{C}$ unless otherwise noted)

| Characteristic | Symbol | Min | Max | Unit |
|----------------|--------|-----|-----|------|
|----------------|--------|-----|-----|------|

#### OFF CHARACTERISTICS

|  |               |     |    |      |
|--|---------------|-----|----|------|
| Collector-Emitter Breakdown Voltage (1)<br>( $I_C = 1.0 \text{ mAdc}$ , $I_E = 0$ )  | $V_{(BR)CEO}$ | 30  |    | Vdc  |
| Collector-Base Breakdown Voltage<br>( $I_C = 10 \text{ }\mu\text{Adc}$ , $I_E = 0$ ) | $V_{(BR)CBO}$ | 40  |    | Vdc  |
| Emitter-Base Breakdown Voltage<br>( $I_E = 10 \text{ }\mu\text{Adc}$ , $I_C = 0$ )   | $V_{(BR)EBO}$ | 5.0 | –  | Vdc  |
| Collector Cutoff Current<br>( $V_{CB} = 20 \text{ Vdc}$ , $I_E = 0$ )                | $I_{CBO}$     | –   | 50 | nAdc |
| Emitter Cutoff Current<br>( $V_{BE} = 3.0 \text{ Vdc}$ , $I_C = 0$ )                 | $I_{EBO}$     | –   | 50 | nAdc |

#### ON CHARACTERISTICS

|   |               |          |          |     |
|---|---------------|----------|----------|-----|
| DC Current Gain(1)<br>( $I_C = 2.0 \text{ mAdc}$ , $V_{CE} = 1.0 \text{ Vdc}$ )<br>( $I_C = 50 \text{ mAdc}$ , $V_{CE} = 1.0 \text{ Vdc}$ ) | $h_{FE}$      | 50<br>25 | 150<br>– | –   |
| Collector-Emitter Saturation Voltage(1)<br>( $I_C = 50 \text{ mAdc}$ , $I_B = 5.0 \text{ mAdc}$ )   | $V_{CE(sat)}$ | –        | 0.3      | Vdc |
| Base-Emitter Saturation Voltage(1)<br>( $I_C = 50 \text{ mAdc}$ , $I_B = 5.0 \text{ mAdc}$ )  | $V_{BE(sat)}$ | –        | 0.95     | Vdc |

## Ch.3 Summary

# Transistor Specification Sheet

### SMALL-SIGNAL CHARACTERISTICS

|  |           |           |          |     |
|--|-----------|-----------|----------|-----|
| Current-Gain – Bandwidth Product<br>( $I_C = 10 \text{ mAdc}$ , $V_{CE} = 20 \text{ Vdc}$ , $f = 100 \text{ MHz}$ )  | $f_T$     | 250       |          | MHz |
| Output Capacitance<br>( $V_{CB} = 5.0 \text{ Vdc}$ , $I_E = 0$ , $f = 100 \text{ MHz}$ )   | $C_{obo}$ | –         | 4.0      | pF  |
| Input Capacitance<br>( $V_{BE} = 0.5 \text{ Vdc}$ , $I_C = 0$ , $f = 100 \text{ kHz}$ )  | $C_{ibo}$ | –         | 8.0      | pF  |
| Collector-Base Capacitance<br>( $I_E = 0$ , $V_{CB} = 5.0 \text{ V}$ , $f = 100 \text{ kHz}$ )   | $C_{cb}$  | –         | 4.0      | pF  |
| Small-Signal Current Gain<br>( $I_C = 2.0 \text{ mAdc}$ , $V_{CE} = 10 \text{ Vdc}$ , $f = 1.0 \text{ kHz}$ )  | $h_{fe}$  | 50        | 200      | –   |
| Current Gain – High Frequency<br>( $I_C = 10 \text{ mAdc}$ , $V_{CE} = 20 \text{ Vdc}$ , $f = 100 \text{ MHz}$ )<br>( $I_C = 2.0 \text{ mAdc}$ , $V_{CE} = 10 \text{ V}$ , $f = 1.0 \text{ kHz}$ ) | $h_{fe}$  | 2.5<br>50 | –<br>200 | –   |
| Noise Figure<br>( $I_C = 100 \text{ } \mu\text{Adc}$ , $V_{CE} = 5.0 \text{ Vdc}$ , $R_S = 1.0 \text{ k ohm}$ , $f = 1.0 \text{ kHz}$ )  | NF        | –         | 6.0      | dB  |

(1) Pulse Test: Pulse Width = 300  $\mu\text{s}$ . Duty Cycle = 2.0%





## Ch.3 Summary

# Transistor Testing

**Curve Tracer** Provides a graph of the characteristic curves.

**DMM** Some DMMs measure  $\beta_{DC}$  or  $h_{FE}$ .

**Ohmmeter:**

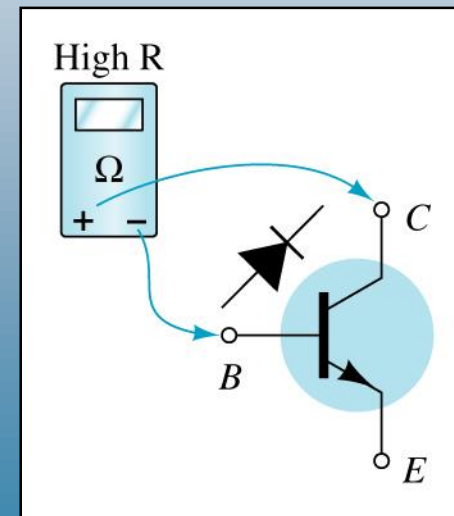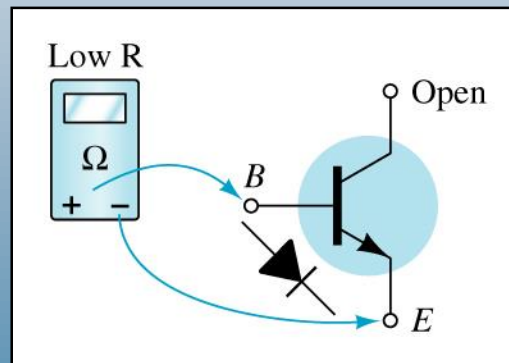

## Ch.3 Summary

# Transistor Terminal Identification

