

# **Electronic Devices and Circuit Theory**


Boylestad

## **Power Supplies (Voltage Regulators)**

### **Chapter 15**

## Ch.15 Summary

# Power Supply Diagram

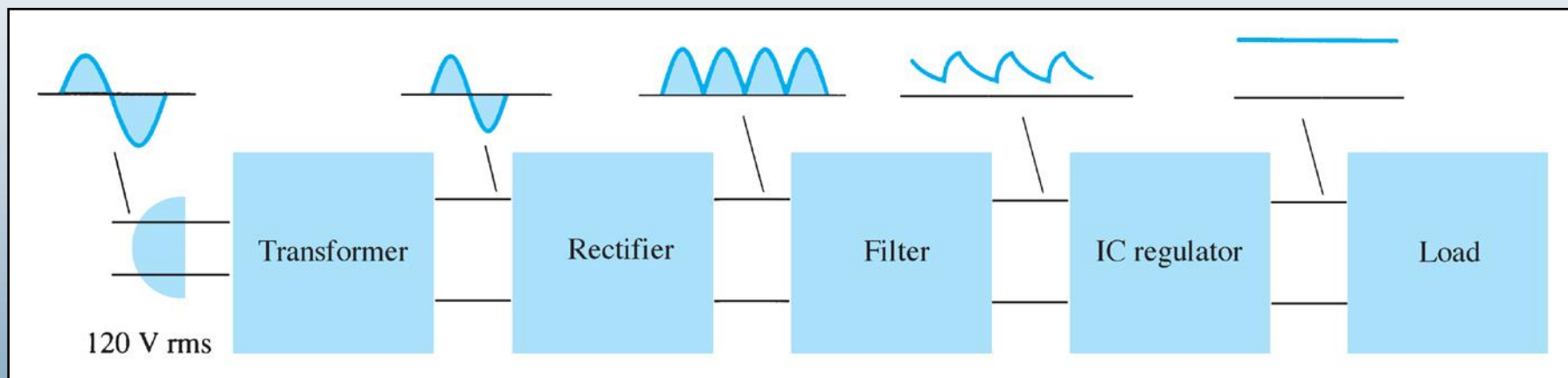

## Ch.15 Summary

# Filters


The output from the power supply **rectifier** is a pulsating DC.

The **filter** reduces the peak-to-peak pulses to a small ripple voltage.

## Ch.15 Summary
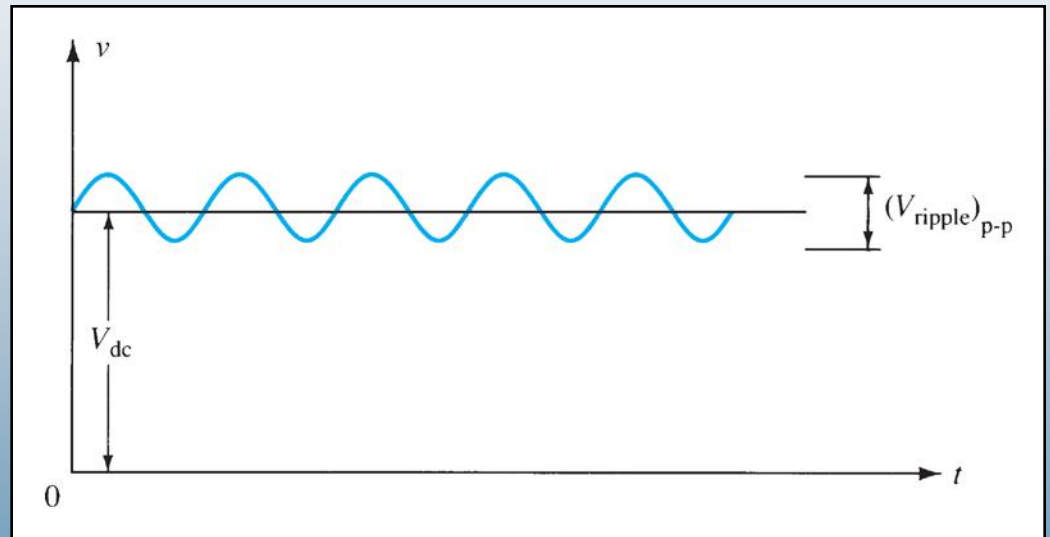
# Ripple Factor

After the filter circuit a small amount of AC is still remaining. The amount of ripple voltage can be rated in terms of **ripple factor** (%r).



$$\%r = \frac{\text{ripple voltage (rms)}}{\text{dc voltage}} = \frac{V_{r(\text{rms})}}{V_{dc}} \times 100$$

# Ch.15 Summary

## Rectifier Ripple Factor

### Half-Wave

DC output:

$$V_{dc} = 0.318V_m$$

AC ripple output:

$$V_{r(rms)} = 0.385V_m$$

Ripple factor:

$$\begin{aligned}\%r &= \frac{V_{r(rms)}}{V_{dc}} \times 100 \\ &= \frac{0.385V_m}{0.318V_m} \times 100 = 121\%\end{aligned}$$

### Full-Wave

DC output:

$$V_{dc} = 0.636V_m$$

AC ripple output:

$$V_{r(rms)} = 0.308V_m$$

Ripple factor:

$$\begin{aligned}\%r &= \frac{V_{r(rms)}}{V_{dc}} \times 100 \\ &= \frac{0.308V_m}{0.636V_m} \times 100 = 48\%\end{aligned}$$

# Types of Filter Circuits

**Capacitor Filter**

***RC Filter***

## Ch.15 Summary

# Capacitor Filter

### Ripple voltage


$$V_{r(rms)} = \frac{I_{dc}}{4\sqrt{3}fC} = \frac{2.4I_{dc}}{C} = \frac{2.4V_{dc}}{R_L C}$$

### DC output

$$V_{dc} = V_m - \frac{I_{dc}}{4fC} = V_m - \frac{4.17I_{dc}}{C}$$
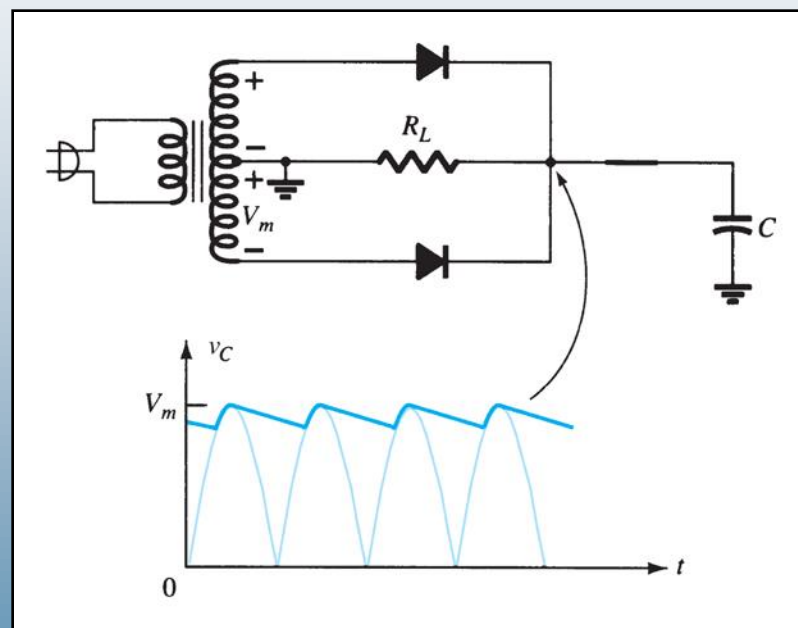
### Ripple factor

$$\%r = \frac{V_{r(rms)}}{V_{dc}} \times 100 = \frac{2.4I_{dc}}{CV_{dc}} \times 100 = \frac{2.4}{R_L C} \times 100$$



## Ch.15 Summary

# Diode Ratings With Capacitor Filter

The greater the value of the capacitor, the higher the current drawn through the rectifier diode(s).

Peak Current vs. capacitance:

$$I = \frac{CV}{t}$$

where

C = capacitance

V = change in capacitor voltage during charge/discharge

t = the charge/discharge time




# Ch.15 Summary
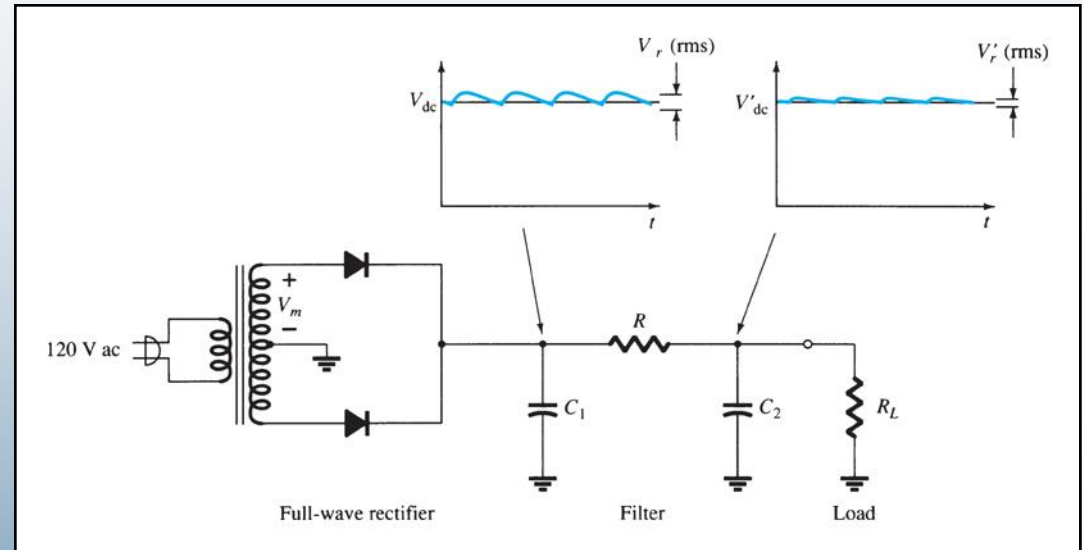
## RC Filter Circuit

Adding an RC section further reduces the ripple voltage and decrease the surge current through the diodes.

$$V'_{r(rms)} \approx \frac{X_C}{R} V_{r(rms)}$$



$V'_{r(rms)}$  = ripple voltage after the RC filter  
 $V_{r(rms)}$  = ripple voltage before the RC filter  
 $R$  = resistor in the added RC filter  
 $X_C$  = reactance of the capacitor in the added RC filter

$$\%V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$V_{NL}$  = no-load voltage  
 $V_{FL}$  = full-load voltage

# Voltage Regulation Circuits

There are two common types of circuitry for voltage regulation:

**Discrete Transistors**

**IC's**

# Discrete-Transistor Regulators

**Series voltage regulator**

**Current-limiting circuit**


**Shunt voltage regulator**

## Ch.15 Summary
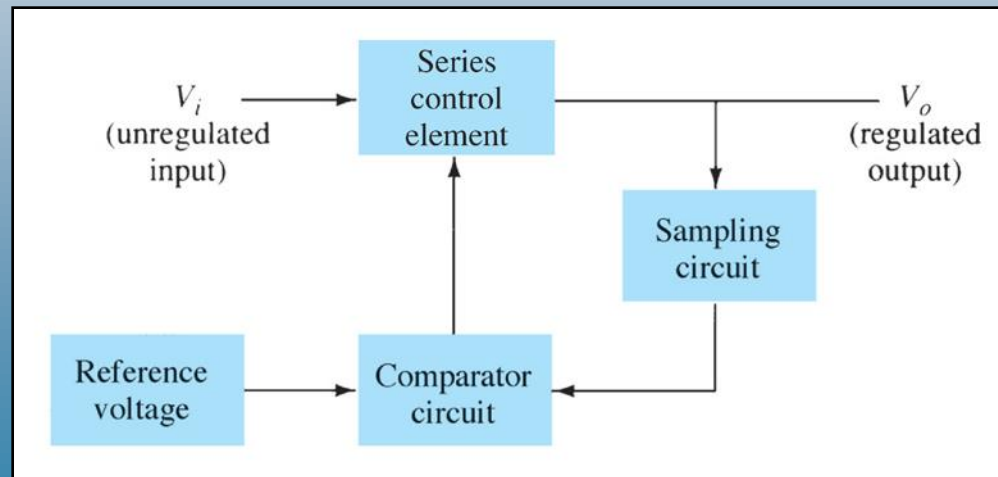
# Series Voltage Regulator

The series element determines how much of the input voltage that passes through to the output.


If the output voltage increases (or decreases), the comparator circuit provides a control signal to cause the series control element to decrease (or increase) the amount of the output voltage.



## Ch.15 Summary
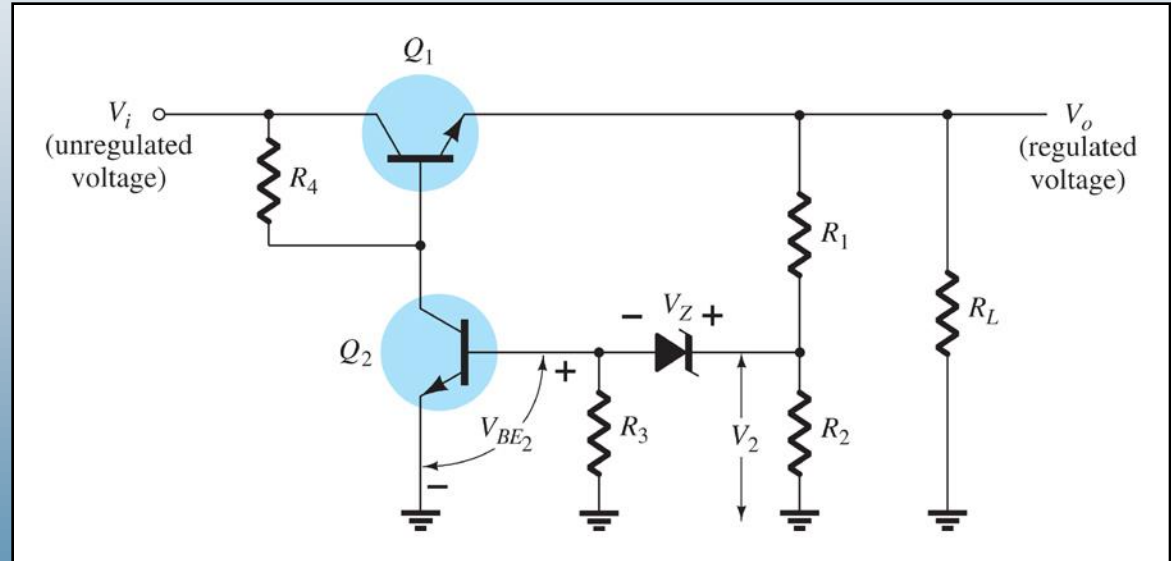
# Series Voltage Regulator

- $R_1$  and  $R_2$  act as the sampling circuit
- The zener provides the reference voltage
- $Q_2$  controls the base current to  $Q_1$
- $Q_1$  maintains the constant output voltage




## Ch.15 Summary

# Series Voltage Regulator

### When the output increases:

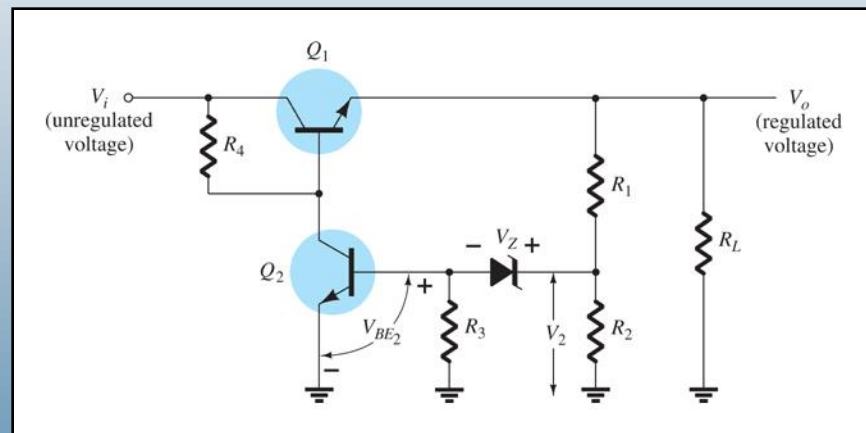1. The voltage at  $V_2$  and  $V_{BE}$  of  $Q_2$  increases
2. The conduction of  $Q_2$  increases
3. The conduction of  $Q_1$  decreases
4. The output voltage decreases




## Ch.15 Summary

# Series Voltage Regulator

### When the output decreases:

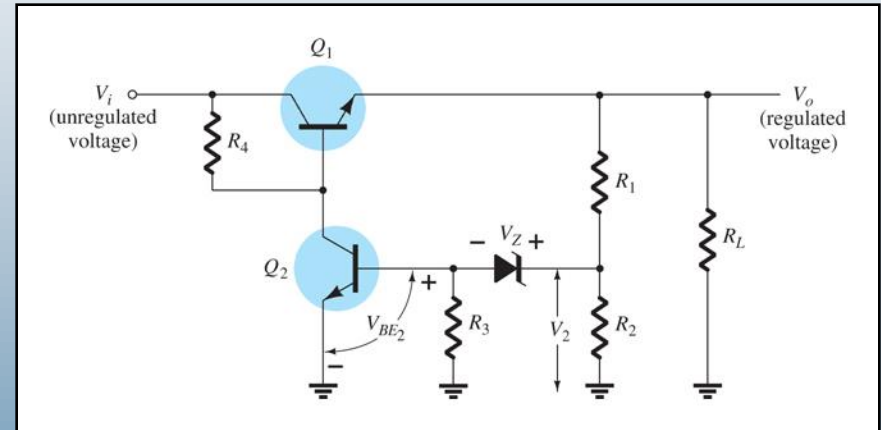
1. The voltage at  $V_2$  and  $V_{BE}$  of  $Q_2$  decreases
2. The conduction of  $Q_2$  decreases
3. The conduction of  $Q_1$  increases
4. The output voltage increases



## Ch.15 Summary
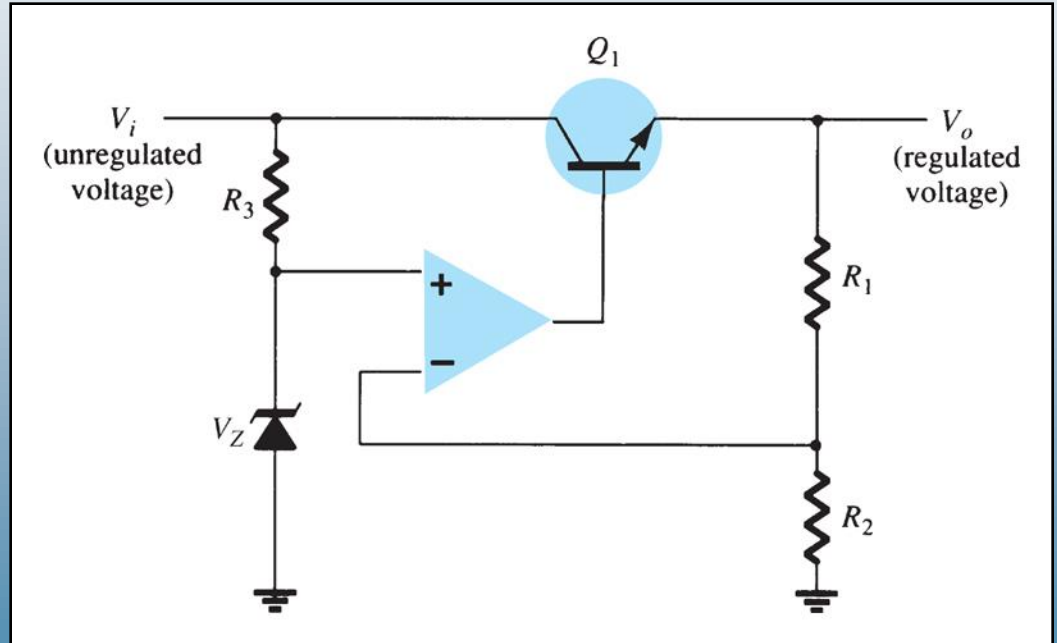
# Series Voltage Regulator

The op-amp compares the Zener diode voltage with the output voltage (at  $R_1$  and  $R_2$ ) and controls the conduction through  $Q_1$ .






## Ch.15 Summary

# Current-Limiting Circuit

When  $I_L$  increases:

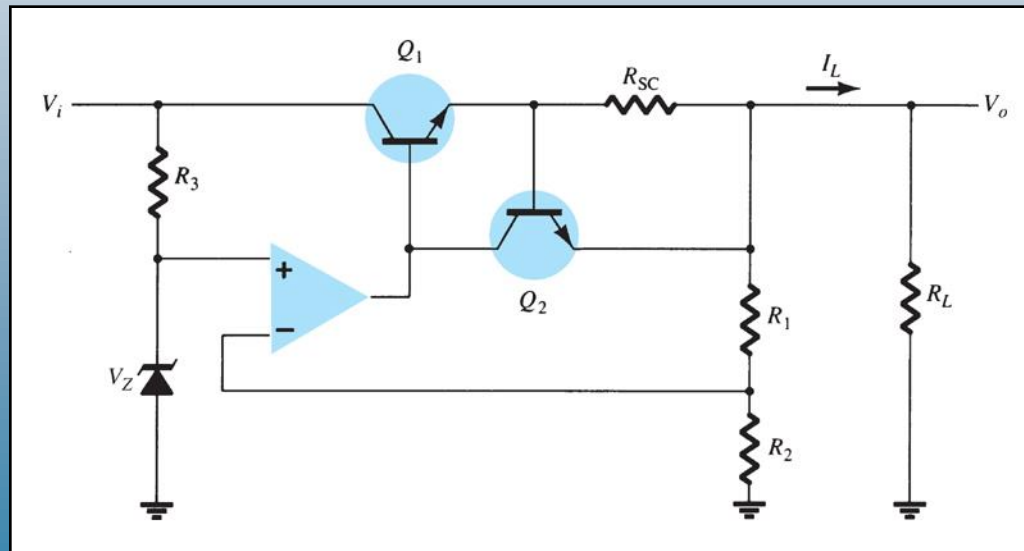1. The voltage across  $R_{SC}$  increases
2. The increasing voltage across  $R_{SC}$  drives  $Q_2$  on
3. Conduction of  $Q_2$  reduces current for  $Q_1$  and the load




## Ch.15 Summary
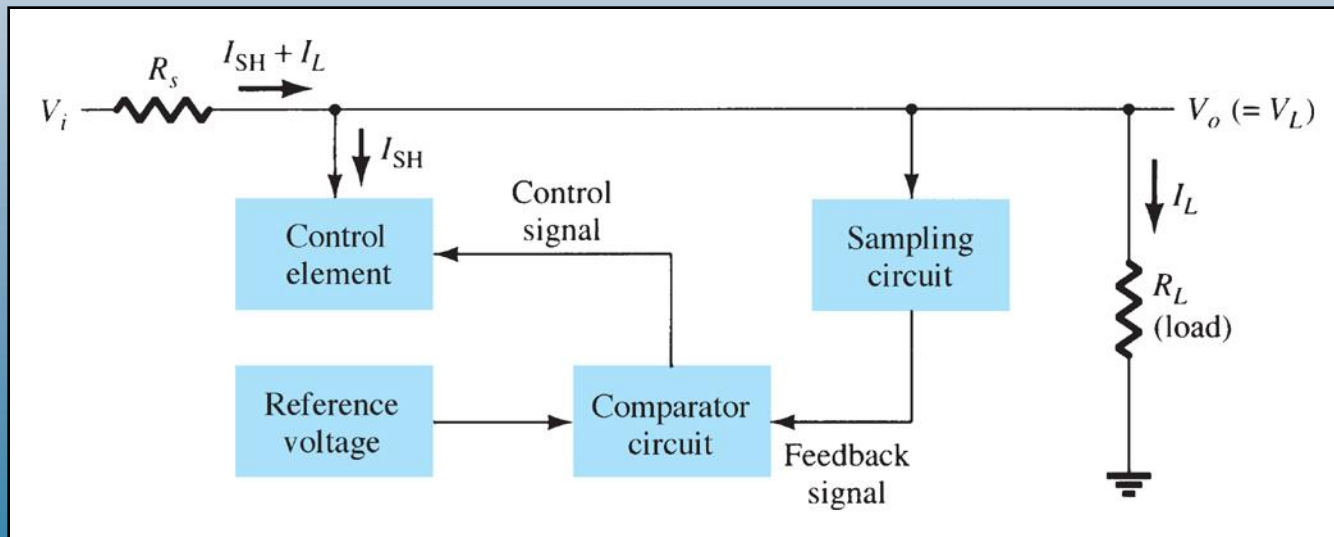
# Shunt Voltage Regulator

The shunt voltage regulator shunts current away from the load.

The load voltage is sampled and fed back to a comparator circuit. If the load voltage is too high, control circuitry shunts more current away from the load.




## Ch.15 Summary

# Shunt Voltage Regulator
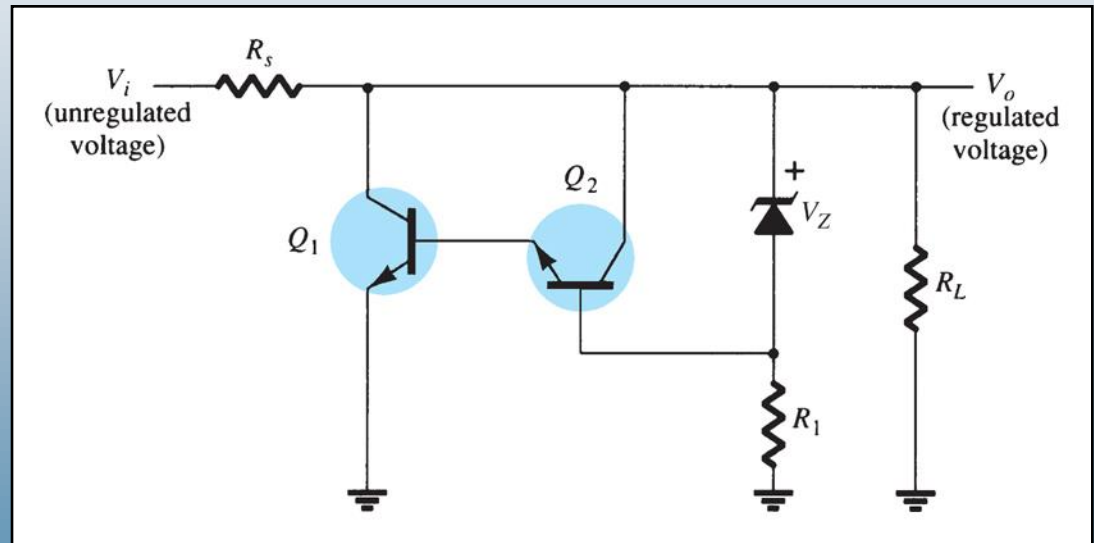
### When the output voltage increases:

- The zener current increases
- The conduction of  $Q_2$  increases
- The voltage drop at  $R_S$  increases
- The output voltage decreases




## Ch.15 Summary

# Shunt Voltage Regulator

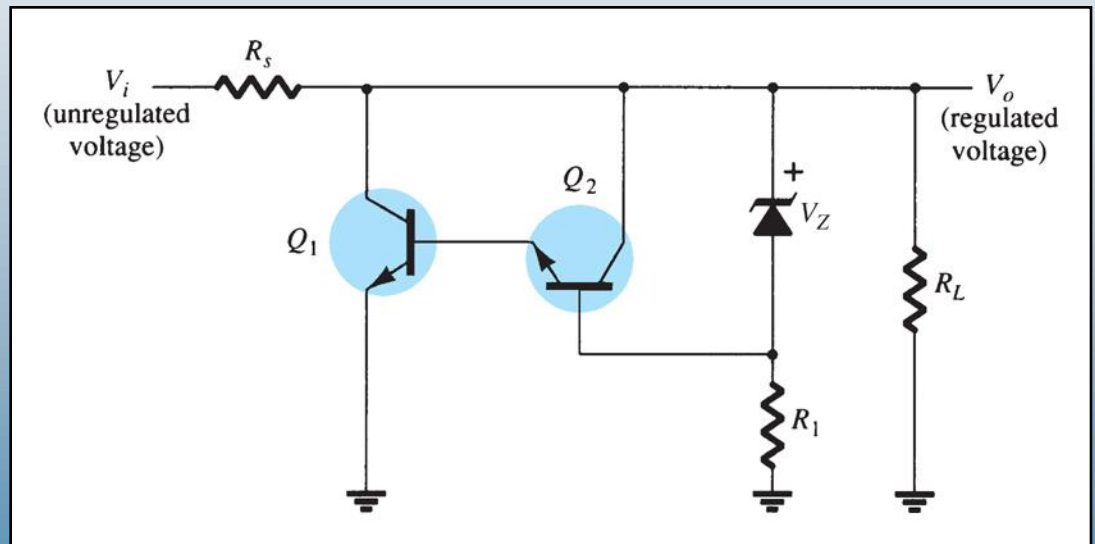
### When the output voltage decreases:

- The zener current decreases
- The conduction of  $Q_2$  decreases
- The voltage drop at  $R_S$  decreases
- The output voltage increases



## Ch.15 Summary

# Shunt Voltage Regulator

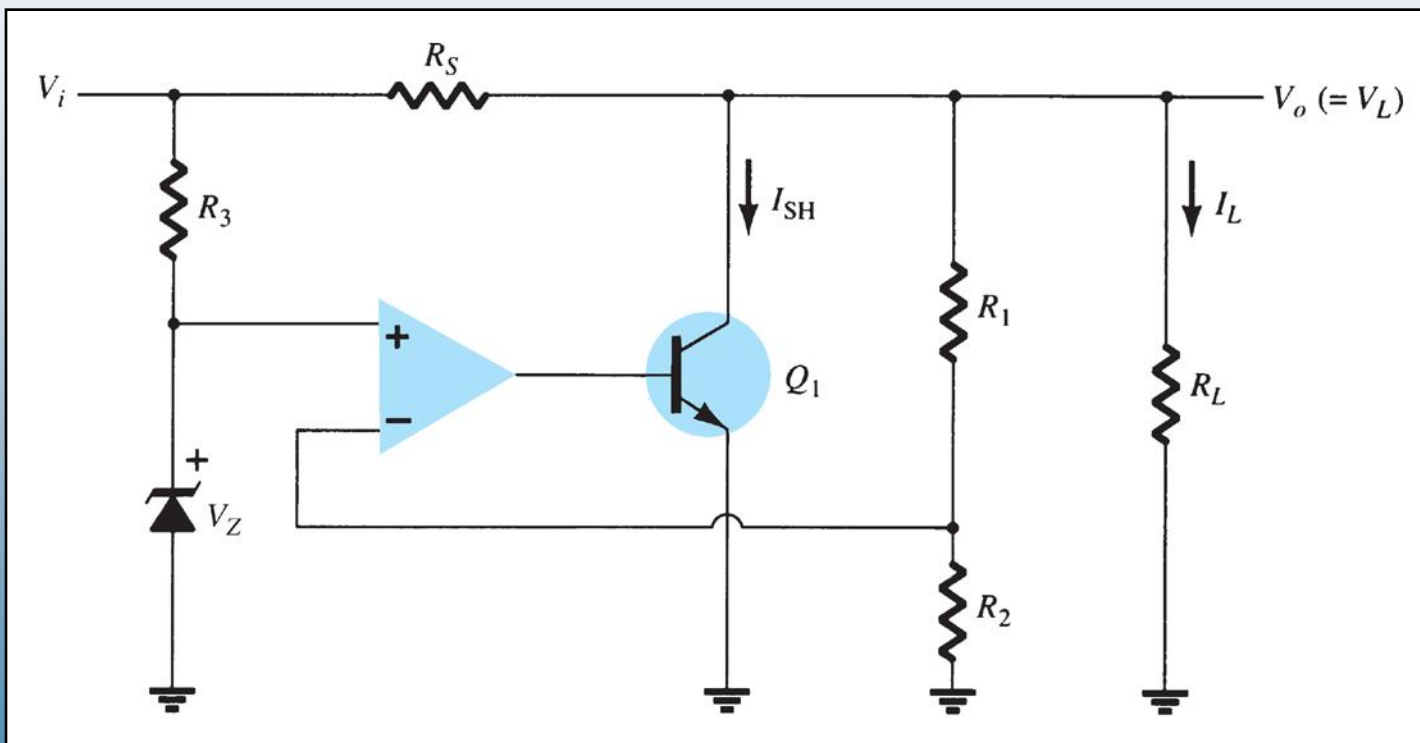

# IC Voltage Regulators

**Regulator ICs contain:**

**Comparator circuit  
Reference voltage  
Control circuitry  
Overload protection**

**Types of three-terminal IC voltage regulators:**


**Fixed positive voltage regulator  
Fixed negative voltage regulator  
Adjustable voltage regulator**

## Ch.15 Summary
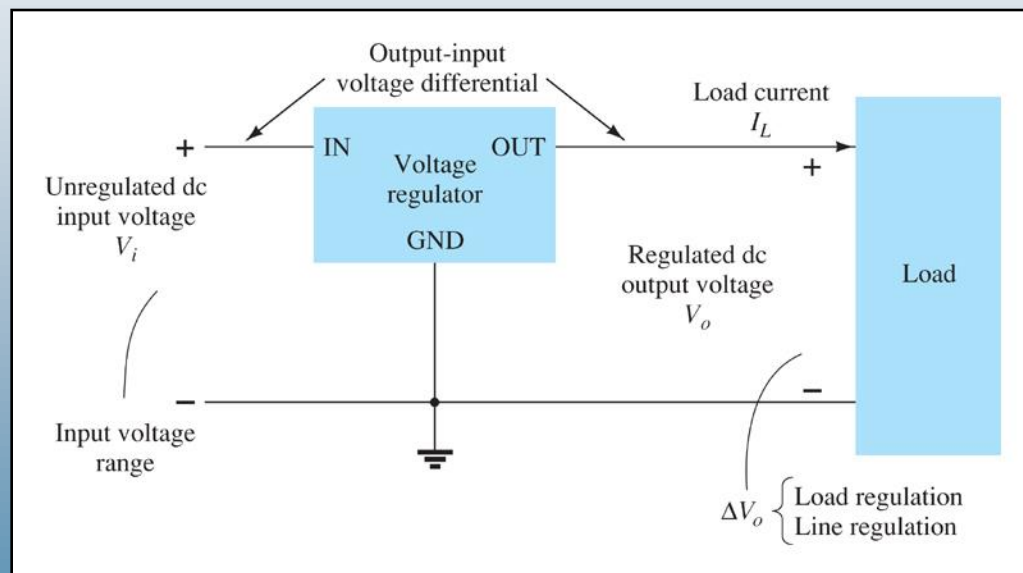
# Three-Terminal Voltage Regulators

The specifications for this IC indicate:


- The range of input voltages that can be regulated for a specific range of output voltage and load current
- Load regulation—variations in output voltage with variations in load current
- Line regulation—variations in output voltage with variations in input voltage



## Ch.15 Summary
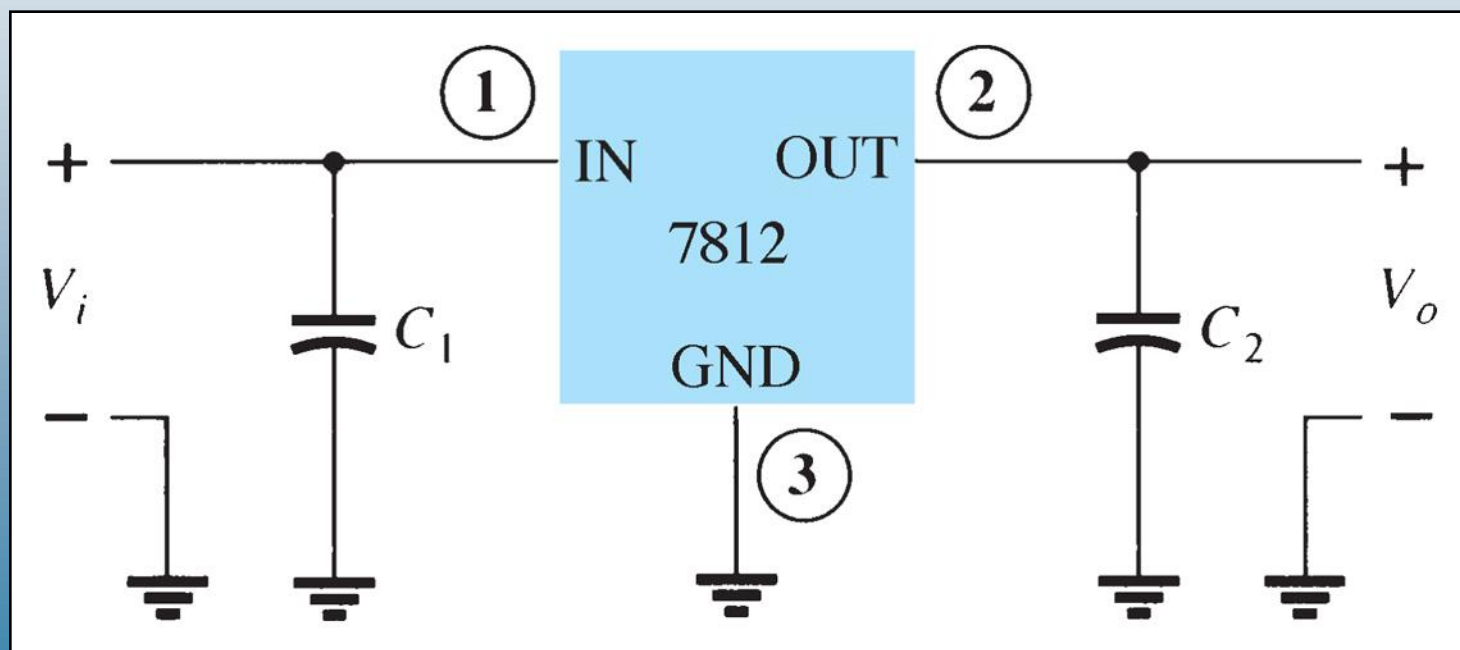
# Fixed Positive Voltage Regulator

These ICs provide a fixed positive output voltage.






## Ch.15 Summary
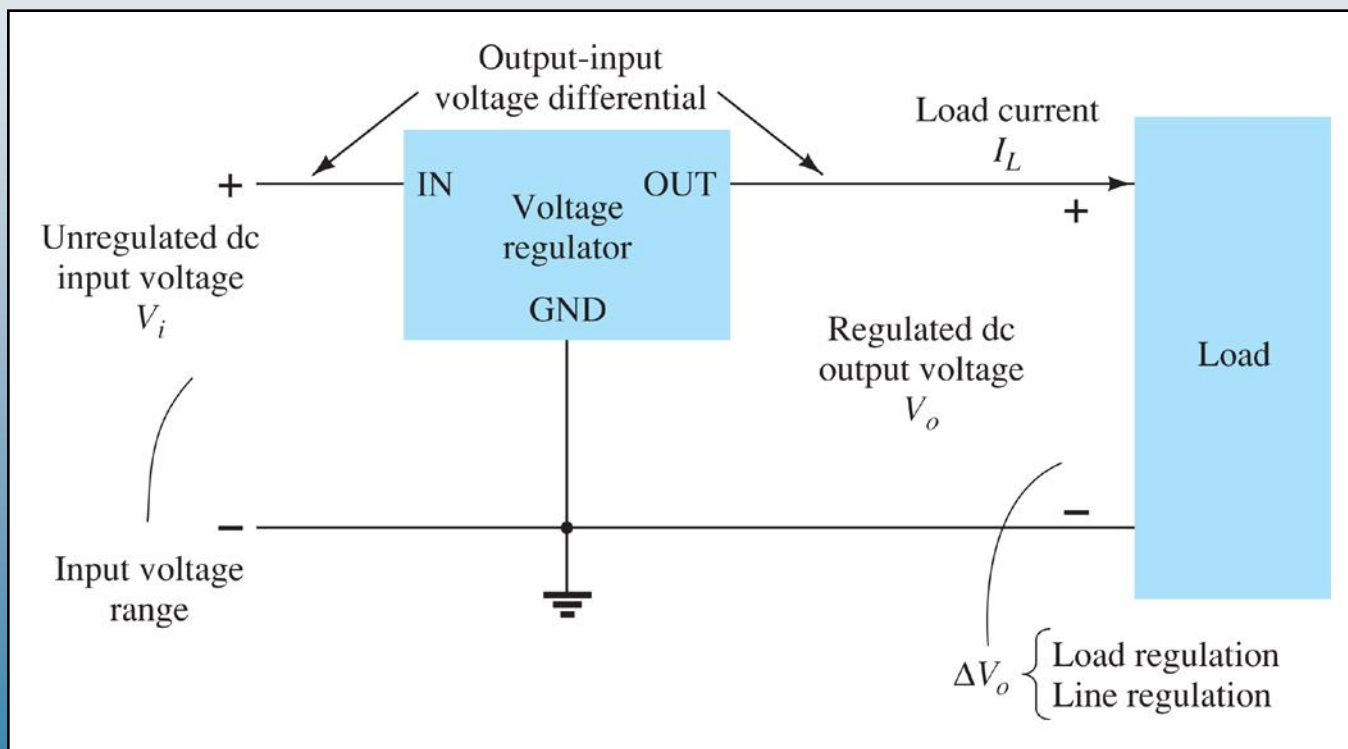
# Fixed Negative Voltage Regulator

These ICs output a fixed negative output voltage.




## Ch.15 Summary
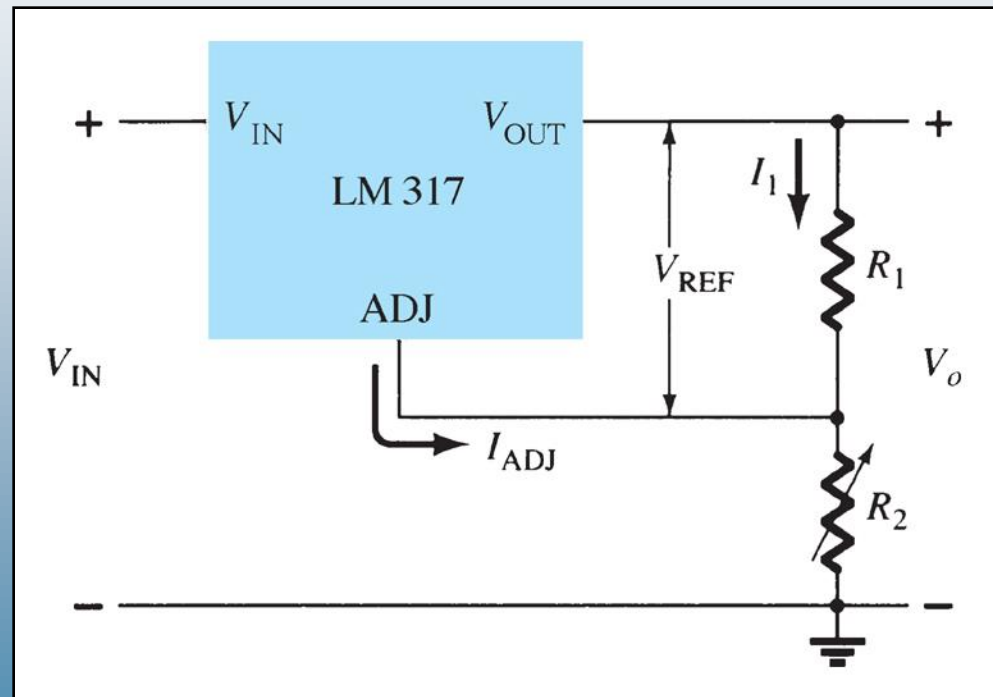
# Adjustable Voltage Regulator

These regulators have adjustable output voltages.

The output voltage is commonly selected using a potentiometer.



# Practical Power Supplies

**DC supply (linear power supplies)**

**Chopper supply (switching power supplies)**

**TV horizontal high voltage supply**

**Battery chargers**