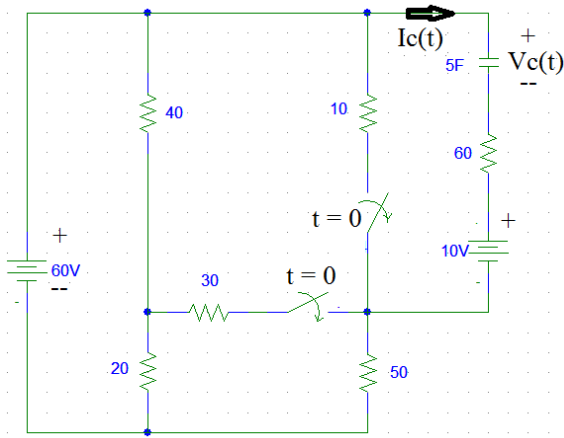


İsim :


No:

İmza:




S-1) Şekilde verilen devrede anahtar $t = 0$ anında kapatılıyor.

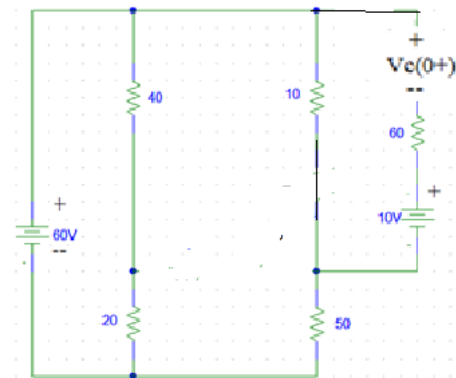$t > 0$ için $V_c(t)$ ve $I_c(t)$ 'yi bulunuz.



$$+V_c(0-) + 10 - \frac{60}{10+50} \times 10 = 0$$


$$V_c(0-) = 0 = V_c(0+)$$

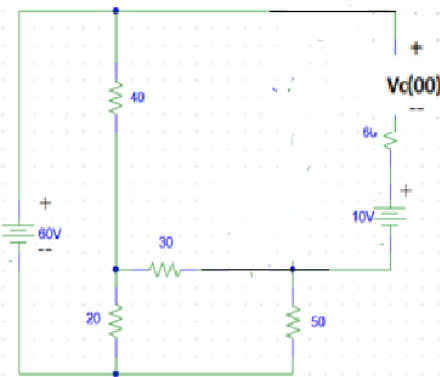

$$\frac{60}{\frac{80 \times 20}{80 + 28}} \times 40 + \frac{60}{\frac{80 \times 20}{80 + 28}} \times \frac{20}{20 + 30 + 50} \times 30 - V_c(\infty) = 0$$

$$42,85714 + 6,42817 - 10 = V_c(\infty) \quad V_c(\infty) = 39,2857V$$

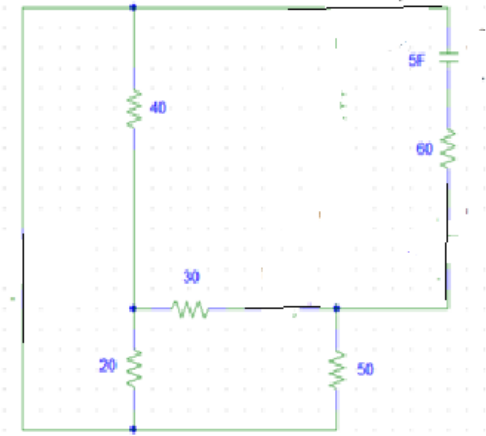Zaman sabiti $\tau = R_{eş} \times C R_{eş} \Rightarrow R_{eş} =$ (2. durumda selften görülen eşdeğer direnç, gerilim kaynağı kısa devre, akım kaynağı açık devre yapılarak bulunur.)



$$R_{eş} = \frac{\left(\frac{40 \times 20}{40 + 20} + 30\right) \times 50}{\left(\frac{40 \times 20}{40 + 20} + 30\right) + 50} + 60 = 83,214$$

$$\tau = R_{eş} \times C = 83,214 \times 5 = 416$$

$$V_c(t) = A e^{-t/\tau} + V_c(\infty)$$

$$V_c(t) = A e^{-t/416} + 39,2857$$


$$t = 0 \text{ için } V_c(0+) = 0V$$

$$0 = A \cdot 1 + 39,2857 \quad A = -39,2857$$


$$V_c(t) = -39,2857 x e^{-t/416} + 39,2857$$

$$I_c(t) = C \frac{dv_c}{dt} = 5 x \left(-\frac{1}{416}\right) x (-39,2857) x e^{-t/416}$$

$$I_c(t) = 0,472 x e^{-t/416}$$

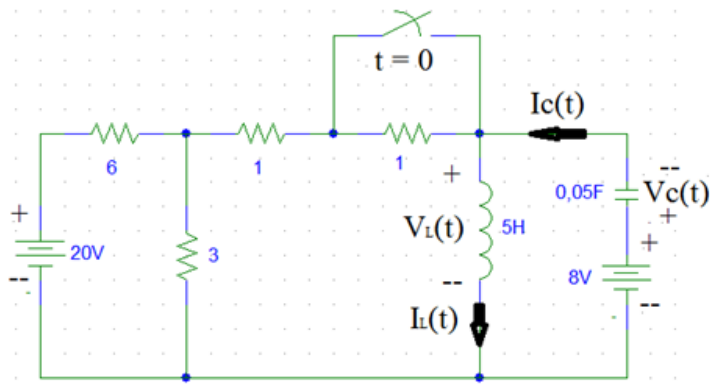

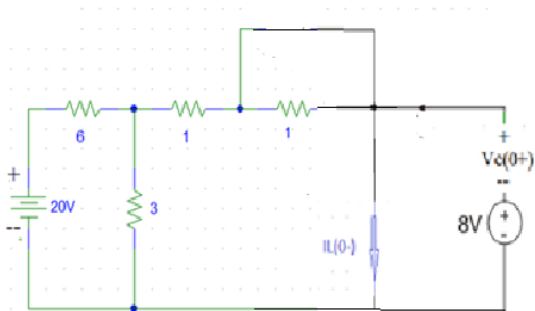
S-2)Yukarıda verilen devrede $t = 0$ anında açılıyor. $t > 0$ için $I_L(t)$ ve $V_L(t)$ 'yi yada $V_C(t)$ ve $I_C(t)$ 'yi bulunuz.



$$I_L(0^-) = \frac{6,66666}{2+1} = 2,222A = I_L(0^+)$$

$$-V_C(0^-) + 8 = 0$$

$$V_C(0^-) = 8 = V_C(0^+)$$

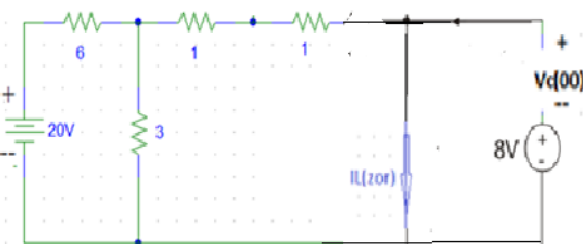

$$I_L(\infty) = \frac{6,66666}{2+1} = 2,222A$$


$$-V_C(\infty) + 8 = 0$$

$$V_C(\infty) = 8V$$

$$V_{L1}(0^+) = 0 \quad V_{L2}(0^+) = 0 \quad V_{L3}(0^+) = 0 \quad V_L(0^+) = 0+0+0=0$$

$$I_{C1}(0^+) = 1,666A \quad I_{C2}(0^+) = -2,222A \quad I_{C3}(0^+) = 0A$$
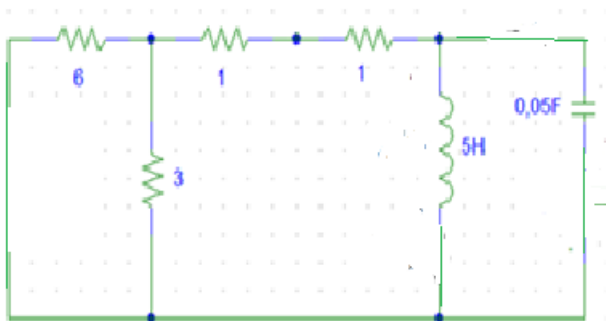
$$I_C(0^+) = 1,666 - 2,222 + 0 = -0,555A$$



$$\frac{1}{4} + \frac{1}{r.5} + \frac{1}{\frac{r.1}{20}} = 0$$

$$\frac{1}{4} + \frac{1}{r.5} + \frac{r}{20} = 0 \quad \frac{1}{4} + \frac{1}{r.5} + \frac{r}{20} = 0 \quad r^2 + .5.r + 4 = 0$$

$$r_1, r_2 = \frac{-b \mp \sqrt{b^2 - 4.a.c}}{2.a} = \frac{-5 \mp \sqrt{5^2 - 4.1.4}}{2x1} = \frac{-5 \mp \sqrt{25 - 16}}{2} = \frac{-5 \mp 3}{2}$$

$$r_1 = -1 \quad r_2 = -4 \quad (r_1 + 1). (r_2 + 4) = 0$$

$$I_L(t) = A.e^{r_1.t} + B.e^{r_2.t} + I_L(\infty)$$

$$I_L(t) = A.e^{-4.t} + B.e^{-1.t} + 1,6666$$

$$t = 0 \text{ için } I_L(0^+) = 2,222 = A.1 + B.1 + 1,6666$$

$$A + B = 0,555$$

$$4.A + 4.B = 2,222$$

$$V_L(t) = L.\frac{d_{iL}}{dt} = 5.(-4.A.e^{-4.t} - 1.B.e^{-1.t})$$

$$t = 0 \text{ için } V_L(0^+) = 0 = 5.((-4).A.1 + (-1).B.1)$$

$$-4.A - 1.B = 0$$

$$4.A + 4.B = 2,222$$

$$3.B = 2,222 \quad B = 0,74074$$

$$A + B = 0,555 \quad A + 0,74074 = 0,555 \quad A = -0,1852$$

$$I_L(t) = A.e^{r_1.t} + B.e^{r_2.t} + I_L(\infty)$$

$$I_L(t) = -0,1852.e^{-4.t} + 0,7474.e^{-1.t} + 1,666$$

$$V_L(t) = L.\frac{d_{iL}}{dt} = 5.(-4.(-0,1852.e^{-4.t} - 1.0,74074.e^{-1.t}))$$

$$V_L(t) = 3,7.e^{-4.t} - 3,7e^{-1.t}$$

s DOMENİ ÇÖZÜMÜ

$$\begin{vmatrix} 5s+4 & -4 \\ -4 & \frac{20}{s}+4 \end{vmatrix} \begin{vmatrix} I_{L(s)} \\ I_{C(s)} \end{vmatrix} = \begin{vmatrix} 11,111 + \frac{6,66}{s} \\ -\frac{6,666}{s} \end{vmatrix}$$

$$I_L(s) = \frac{\begin{bmatrix} 11,111 + \frac{6,666}{s} & -4 \\ -\frac{6,666}{s} & \frac{20}{s} + 4 \end{bmatrix}}{\begin{bmatrix} 5s+4 & -4 \\ -4 & \frac{20}{s} + 4 \end{bmatrix}} = \frac{\frac{222,22}{s} + 44,444 + \frac{133,333}{s^2} + \frac{26,666}{s} - \frac{26,666}{s}}{100 + 20s + \frac{80}{s} + 16 - 16}$$

$$= \frac{\frac{222,22}{s} + 44,444 + \frac{133,333}{s^2}}{100 + 20s + \frac{80}{s}} = \frac{222,22s + 44,444s^2 + 133,33}{s \cdot (100s + 20s^2 + 80)}$$

$$= \frac{44,444s^2 + 222,22s + 133,33}{s \cdot (20s^2 + 100s + 80)} = \frac{222,22s + 44,444s^2 + 133,33}{s \cdot (100s + 20s^2 + 80)}$$

$$= \frac{2,222s^2 + 11,111s + 6,666}{s \cdot (s+4) \cdot (s+1)} = \frac{A}{s} + \frac{B}{(s+4)} + \frac{C}{(s+1)}$$

$$s^2(A + B + C) + s(5A + B + 4C) + 4A$$

$$A = \frac{6,666}{4} = 1,666 \quad A + B + C = 2,222$$

$$B + C = 2,222 - 1,666 = 0,5555$$

$$(5A + B + 4C) = 11,111 \quad (5 \times 1,666 + B + 4C) = 11,111$$

$$(B + 4C) = 11,111 - 8,333 = 2,777$$

$$+B + 4C = 2,777$$

$$-B - C = -0,5555 \quad 3C = 2,222 \quad C = 0,7407$$


$$+B + 4 \times 0,7407 = 2,777 \quad B = -0,1871$$

$$I_L(s) = \frac{A}{s} + \frac{B}{(s+4)} + \frac{C}{(s+1)}$$


$$I_L(s) = \frac{1,6666}{s} - \frac{0,1851}{(s+4)} + \frac{0,7047}{(s+1)}$$

$$I_L(t) = 1,666 - 0,1871 \cdot e^{-4 \cdot t} + 0,7047 \cdot e^{-1 \cdot t}$$
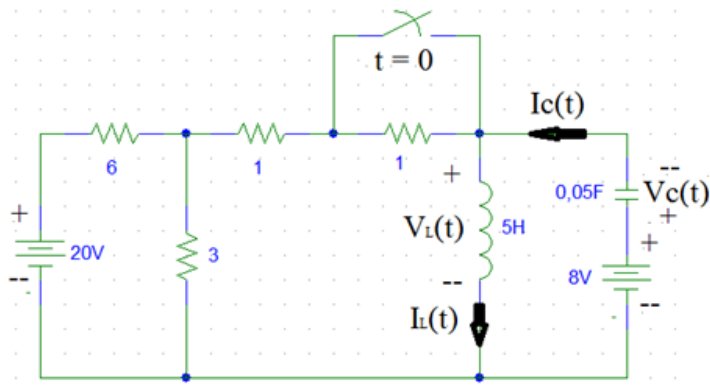
$$V_L(t) = L \cdot \frac{d_{iL}}{dt} = 5 \cdot (-4 \cdot (-0,1852 \cdot e^{-4 \cdot t} - 1,0,74074 \cdot e^{-1 \cdot t})) = 3,7 \cdot e^{-4 \cdot t} - 3,7 e^{-1 \cdot t}$$



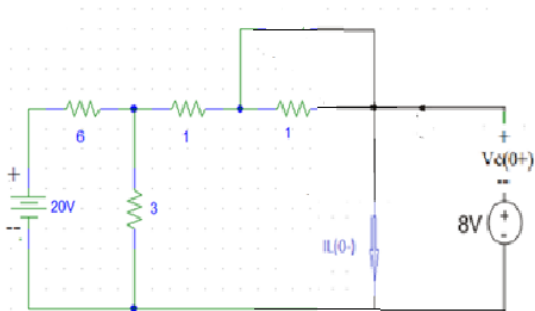
S-2)Yukarıda verilen devrede $t = 0$ anında açılıyor. $t > 0$ için $I_L(t)$ ve $V_L(t)$ 'yi yada $V_C(t)$ ve $I_C(t)$ 'yi bulunuz.



$$I_L(0^-) = \frac{6,66666}{2+1} = 2.222A = I_L(0^+)$$

$$-V_C(0^-) + 8 = 0$$

$$V_C(0^-) = 8 = V_C(0^+)$$

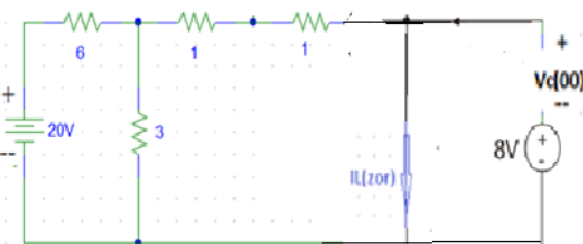

$$I_L(\infty) = \frac{6,66666}{2+1} = 2.222A$$


$$-V_C(\infty) + 8 = 0$$

$$V_C(\infty) = 8V$$

$$V_{L1}(0^+) = 0 \quad V_{L2}(0^+) = 0 \quad V_{L3}(0^+) = 0 \quad V_L(0^+) = 0+0+0=0$$

$$I_{C1}(0^+) = 1,666A \quad I_{C2}(0^+) = -2,222A \quad I_{C3}(0^+) = 0A$$
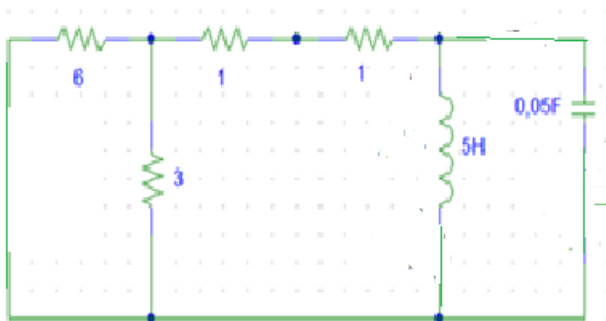
$$I_C(0^+) = 1,666 - 2,222 + 0 = -0,555A$$



$$\frac{1}{4} + \frac{1}{r.5} + \frac{1}{\frac{r.1}{20}} = 0$$

$$\frac{1}{4} + \frac{1}{r.5} + \frac{r}{20} = 0 \quad \frac{1}{4} + \frac{1}{r.5} + \frac{r}{20} = 0 \quad r^2 + .5.r + 4 = 0$$

$$r_1, r_2 = \frac{-b \mp \sqrt{b^2 - 4.a.c}}{2.a} = \frac{-5 \mp \sqrt{5^2 - 4.1.4}}{2x1} = \frac{-5 \mp \sqrt{25 - 16}}{2} = \frac{-5 \mp 3}{2}$$

$$r_1 = -1 \quad r_2 = -4 \quad (r_1 + 1). (r_2 + 4) = 0$$

$$V_c(t) = A.e^{-r_1.t} + B.e^{-r_2.t} + V_c(\infty)$$

$$V_c(t) = A.e^{-4.t} + B.e^{-1.t} + 8$$

$$t = 0 \text{ için } V_c(0^+) = 8 = A.1 + B.1 + 8 \quad A + B = 0$$

$$I_c(t) = C.\frac{d_{VC}}{dt} = 0,05.(-4.A.e^{-4.t} - 1.B.e^{-1.t})$$

$$t = 0 \text{ için } I_c(0^+) = -0,5555 = 0.05.((-4).A.1 + (-1).B.1)$$

$$-4.A - B = -11,111$$

$$A + B = 0$$

$$-3.A = -11,111$$

$$A = 3,705666 \quad B = -3,705666$$

$$V_c(t) = A.e^{-4.t} + B.e^{-1.t} + 8$$

$$V_c(t) = 3,705666.e^{-4.t} - 3,705666.e^{-1.t} + 8$$

$$I_c(t) = C.\frac{d_{VC}}{dt} = 0,05.(-4x3,705666.e^{-4.t} - 1.(-1x3,705666).e^{-1.t})$$

s DOMENİ ÇÖZÜMÜ

$$\begin{vmatrix} 5s + 4 & -4 \\ -4 & \frac{20}{s} + 4 \end{vmatrix} \begin{vmatrix} I_{L(s)} \\ I_{C(s)} \end{vmatrix} = \begin{vmatrix} 11,111 + \frac{6,66}{s} \\ -\frac{6,666}{s} \end{vmatrix}$$

$$I_C(s) = \frac{\begin{bmatrix} 5s + 4 & 11,111 + \frac{6,66}{s} \\ -4 & -\frac{6,666}{s} \end{bmatrix}}{\begin{bmatrix} 5s + 4 & -4 \\ -4 & \frac{20}{s} + 4 \end{bmatrix}} = \frac{-33,333 - \frac{26,666}{s} + 44,444 + \frac{26,666}{s}}{100 + 20s + \frac{80}{s} + 16 - 16}$$

$$= \frac{11,111}{100 + 20s + \frac{80}{s}} = \frac{11,111}{100 + 20s + \frac{80}{s}} = \frac{11,111 \cdot s}{(100s + 20s^2 + 80)}$$

$$= \frac{11,111}{(20s^2 + 100s + 80)} = \frac{0,5555 \cdot s}{(s^2 + 5s + 4)} = \frac{0,5555 \cdot s}{(s + 4) \cdot (s + 1)}$$

$$= \frac{A}{(s + 4)} + \frac{B}{(s + 1)}$$

$$(A + B) \cdot s + (4A + B)$$

$$A + B = 0,5555$$

$$4A + B = 0$$

$$-A - B = -0,5555$$

$$3A = -0,5555$$

$$A = -0,185$$

$$A + B = 0,5555$$

$$-0,185 + B = 0,5555$$


$$B = 0,7407$$

$$I_C(s) = \frac{A}{(s + 4)} + \frac{B}{(s + 1)}$$


$$I_C(s) = \frac{-0,1851}{(s + 4)} + \frac{0,7047}{(s + 1)}$$

$$I_C(t) = -0,1871 \cdot e^{-4 \cdot t} + 0,794 \cdot e^{-1 \cdot t}$$

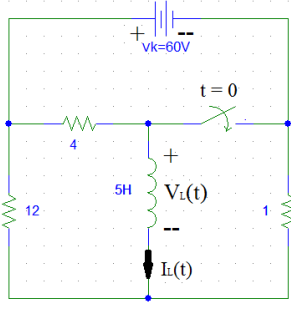
$$V_C(t) = 3,705666 \cdot e^{-4 \cdot t} - 3,705666 \cdot e^{-1 \cdot t} + 8$$



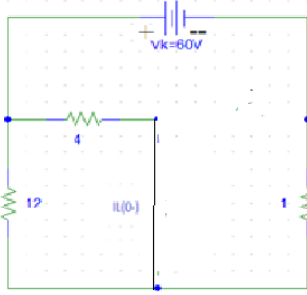
S-3) Şekilde verilen devrede $t = 0$ anında kapatılıyor. $t > 0$ için $I_L(t)$ ve $V_L(t)$ 'yi bulunuz.


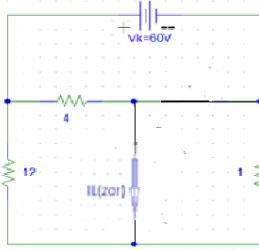
$$I_L(0^-) = \frac{60}{\frac{12 \times 4}{12 + 4} + 1} \cdot \frac{12}{12 + 4} = 11,25A$$


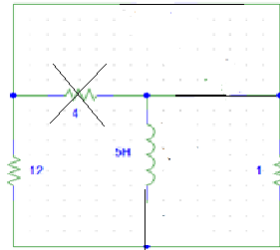
$$I_L(\infty) = -\frac{60}{\frac{12 \times 4}{12 + 4}} \cdot \frac{4}{16} = -5A$$



$$R_{eş} = \frac{12 \times 1}{12 + 1}$$

$$\tau = L/R_{eş} = 5/(12 \times 1/(12 + 1)) = 65/12$$


$$I_L(t) = A \cdot e^{-\frac{t}{\tau}} + I_L(\infty) \quad I_L(t) = A \cdot e^{-\frac{t}{(65/12)}} - 5$$

$$t = 0 \text{ için } I_L(0^+) = 11,25A \quad 11,25 = A \cdot 1 - 5 \quad A = 16,25$$

$$I_L(t) = 16,25 \cdot e^{-(12/65)t} + 11,25A$$

$$V_L(t) = L \cdot \frac{dI_L}{dt} = 5 \times ((16,25 \times (-12/65)) \cdot e^{-(12/65)t})$$

$$V_L(t) = -15 \cdot e^{-(12/65)t}$$

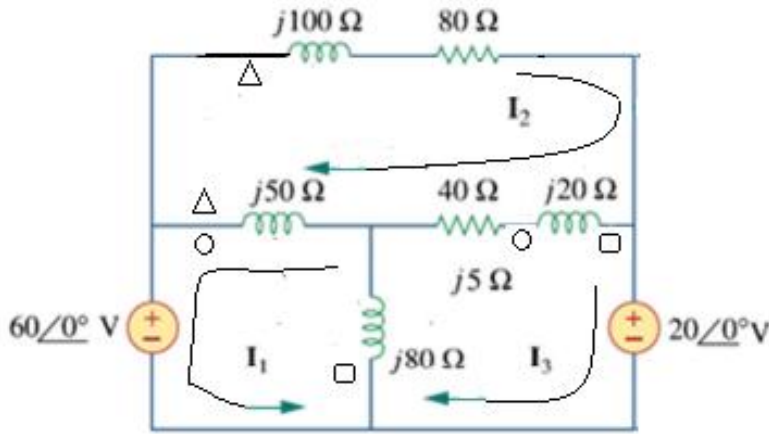

S-4) Şekildeki magnetik kuplajlı devrenin i_1 , i_2 , i_3 akımlarını matrisel biçimde yazınız. $\triangle = j15 \text{ Ohm}$, $\square = j5 \text{ Ohm}$, $\bigcirc = j25 \text{ Ohm}$

Cevap4

$$j.50.(I_1 + I_2) + j.80.(I_1 + I_3) - j.15.I_2 + j.5.I_2 - j.5.I_3 + j.25.I_2 - j.25.I_3 = -60\angle 0^\circ \quad 10\text{puan}$$

$$j.50.(I_2 - I_1) + (40+j.20).(I_2 - I_3) + (80+j.100).(I_2) - j.15.I_1 - 2x j.15.I_2 + j.5.I_1 + j.5.I_3 + j.25.I_1 + 2xj.5.I_2 - j.25.I_3 = 0 \quad 10\text{puan}$$


$$(40+j.20).(I_3 - I_2) + j.80.(I_1 + I_3) - j5.I_1 + j5.I_2 + 2xj5.I_3 - j25.I_1 - j25.I_2 = -20 \quad 10\text{puan}$$

$$(j.50 + j.80).I_1 (j.50 - j.15 + j.5 + j.5 + j.25).I_2 + (j.80 - j.5.I_2 - j.25).I_3 = -60\angle 0^\circ$$

$$(j.50 - j.15 + j.5 + j.25).I_1 + (j.50 + 40 + j.20 + 80 + j.100 - j.30 + j.50).I_2 (-40 - j.20 + j.15 - j25).I_3 = 0$$

$$(j.80 - j.5.-25).I_1 + (-40 - j.20 + j.5.I_3 - j.25).I_2 + (40 + j.20 + j.80 - j.10).I_3 = -20\angle 0^\circ$$
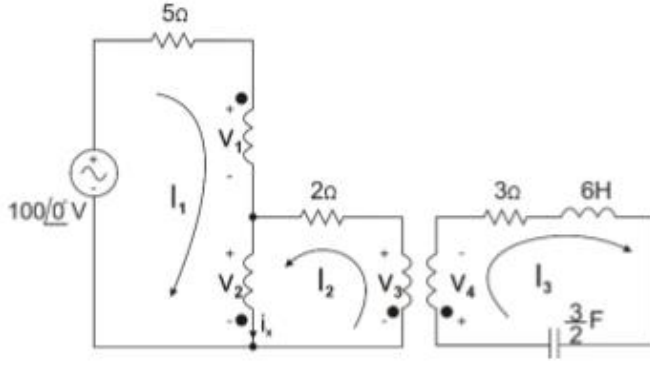
$$\begin{vmatrix} j.130 & +j.65 & j.50 \\ -j.65 & 120 + j.90 & -40 - j.39 \\ j.50 & -40 - j.30 & 40 + j.90 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} -60 \\ 0 \\ -20 \end{vmatrix}$$



S-5) Şekildeki verilen devrede, $V_1=1$ sarım, $V_2=2$ sarım, $V_3=3$ sarım , $V_4=4$ sarım ve $w = 1/3$ ' dir. V_1 , V_2 , V_3 , V_4 , I_1 , I_2 , I_3 bulunuz.

$$\frac{V_1}{V_2} = \frac{N_1}{-N_2}$$

$$V_1 = -\frac{N_1}{N_2} \cdot V_2 = -\frac{1}{2} \cdot V_2$$

$$V_2 = -\frac{N_2}{N_1} \cdot V_1 = -\frac{2}{1} \cdot V_1 = -2 \cdot V_1$$


$$\frac{V_3}{V_4} = \frac{-N_3}{N_4} = \frac{-3}{4} \quad V_3 = \frac{-3}{4} \cdot V_4$$

$$\frac{I_1}{I_2} = -\left(\frac{-N_2}{N_1 - N_2}\right) = -\left(\frac{-2}{1-2}\right) = -2$$

$$I_2 = -\left(\frac{N_1 - N_2}{-N_2}\right) \cdot I_1 = -\left(\frac{1-2}{-2}\right) \cdot I_1 = -\frac{1}{2} \cdot I_1$$

$$\frac{I_2}{I_3} = -\left(\frac{N_4}{N_3}\right) = -\left(\frac{4}{3}\right)$$
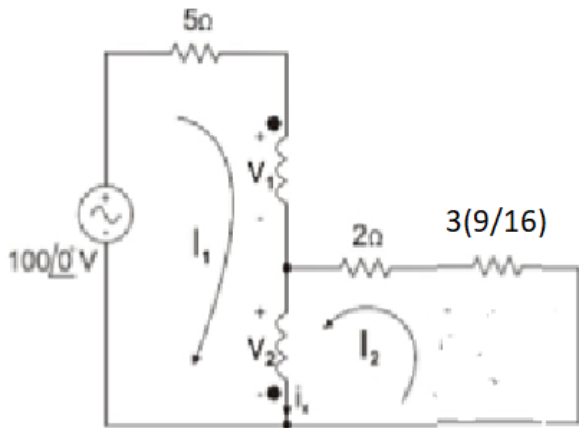
$$I_3 = -\left(\frac{N_3}{N_4}\right) \cdot I_2 = -\left(\frac{3}{4}\right) \cdot I_2$$



$$5.I_1 + V_1 + V_2 = 100$$

$$\left(\frac{27}{16} + 2\right).I_2 + V_2 = 0$$

$$5.I_1 + V_1 - 2.V_1 = 100$$

$$\frac{59}{16}.I_2 - 2V_1 = 0$$

$$5.I_1 - V_1 = 100$$

$$\frac{59}{16}.\left(\frac{-1}{2}\right).I_1 - 2V_1 = 0$$

$$5.I_1 - V_1 = 100$$

$$-1,84375.I_1 - 2V_1 = 0$$

$$-10.I_1 + 2.V_1 = -200$$

$$-1,84375.I_1 - 2V_1 = 0$$

$$I_1 = \frac{-200}{-11,84375} = 16,88654354A$$

$$-1,8475.I_1 - 2V_1 = 0$$

$$V_1 = -\frac{1,84375}{2}.I_1 = -\frac{1,84375}{2} \times 16,88654354 = -15,6728232V$$

$$V_2 = -2.V_1 = -15,6728232 = 31,136464V$$

$$I_2 = -\left(\frac{1}{2}\right).I_1 = -\frac{1}{2} \times 16,88654354 = -8,443271768A$$

$$I_3 = -\left(\frac{3}{4}\right).I_2 = -\left(\frac{3}{4}\right).(-8,443271768) = 6,332453826A$$

$$V_4 + 3.I_3 = 0$$

$$V_4 = -3.I_3 = -3 \times 6,332453826 = 19V$$

$$V_3 = \frac{-3}{4} \times V_4 = \frac{-3}{4} \times 19 = -14,25V$$