

1. Dual converters provide four quadrant operation

Dual converters provide four quadrant operation, which means voltage can be positive or negative and so can be the current. Hence, AC-DC, DC-AC any converter configuration can be used.

2. A dual converters has two full converters in anti-parallel

Dual converters have two full converters connected in anti-parallel which provides a four quadrant operation.

3. The major advantage of using dual converters is that no mechanical switch is required to change the mode of operation

No mechanical arrangement is required to change from inverter to converter and converter to inverter, which was required in earlier methods.


4. The four quadrant operation of dual converters can be obtained by changing the firing angle value

The four quadrant operation can be obtained simply by adjusting appropriate values of firing angles for both the connected converters.

5. A single full converter alone can give a two quadrant operation

A single full converter alone gives two quadrant operation, hence for all four quadrant operation two full converter circuits are connected in anti-parallel.

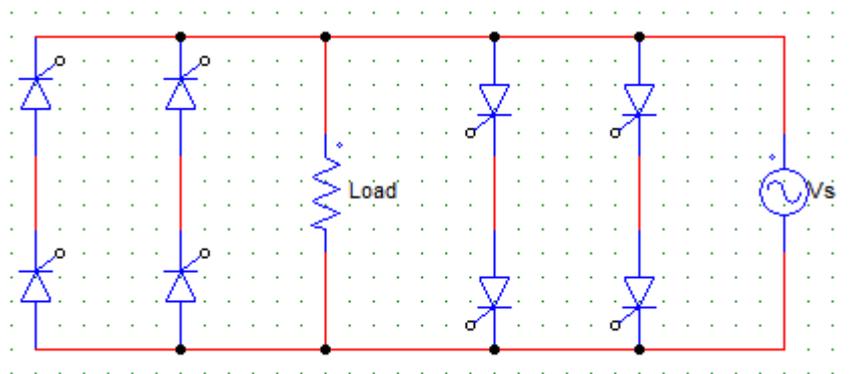
6. Find the error in the below given dual converter circuit.




Voltage source is not connected for one of the converter circuit

Voltage source is not connected in the proper place

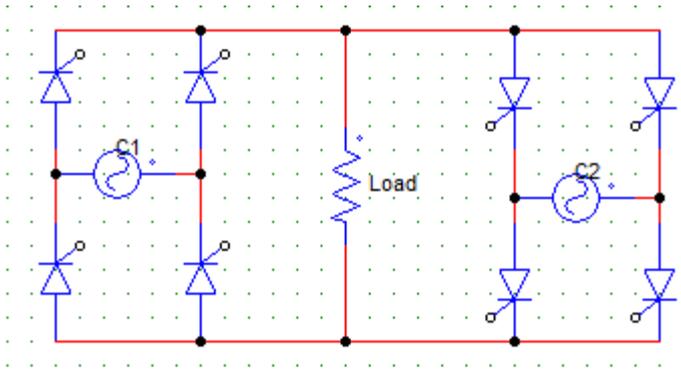Explanation: The right connection for single-phase dual converter is shown below.




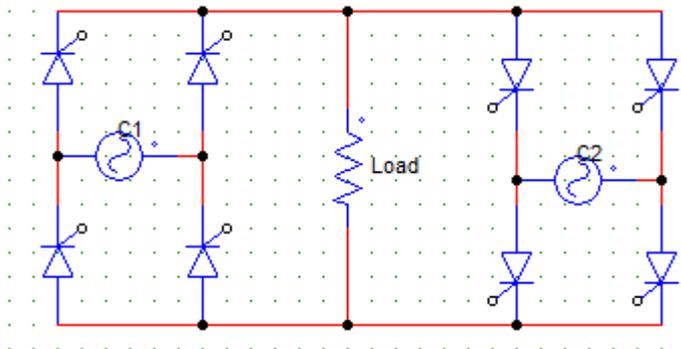7. In the below given circuit, the right side converter C2 operates in the second and third quadrant.



The C2 converter will supply the load current in direction opposite to that supplied by the converter C1. For converter C2, when $\alpha > 90$ it operates in 2nd quadrant and if $\alpha < 90$ both current and voltage are negative, C2 is in inverter mode and operates in 3rd quadrant.

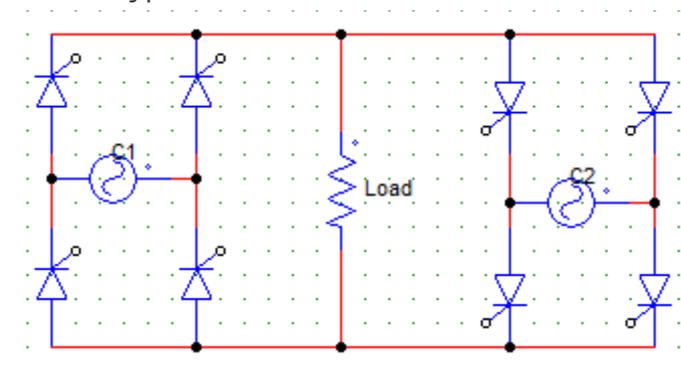8. Name the below given circuit. Single-phase dual converter non-circulating current type



The circuit is a single phase dual converter circuit. As there is no reactor (inductor) in series, it is a non-circulating type.

9. For a single-phase dual converter, with converters C1 and C2 connected in anti-parallel, which relation among the following is true to keep the average voltages from C1 and C2 equal? C1 and C2 have firing angles α_1 and α_2 respectively.

$$\alpha_1 + \alpha_2 = 180^\circ$$

10. In non-circulating current mode dual converters, the circulating current is avoided by operating only one converter

Reactor is added in circulating current mode not in non-circulating mode. The circulating current is avoided by using only one of the converters.

1. In circulating current mode dual converters, the circulating current is avoided by connecting a series reactor

Reactor is added in circulating current mode not in non-circulating mode. The reactor limits the current to a reasonable value.

2. Choose the correct statement


c) Circulating current exists in both the circulating and non-circulating current mode
The circulating current does exist in both the converter circuits, but it is avoided by using a reactor in non-circulating type and by operating only one circuit in case of circulating type.

3. What causes circulating current in dual converters?

c) Out of phase voltages from both the converters

In case of practical dual converters, the voltages from both the converter circuits though equal in magnitude is out of phase. This indifference in voltages causes circulating currents to flow.

4. Name the below given circuit.

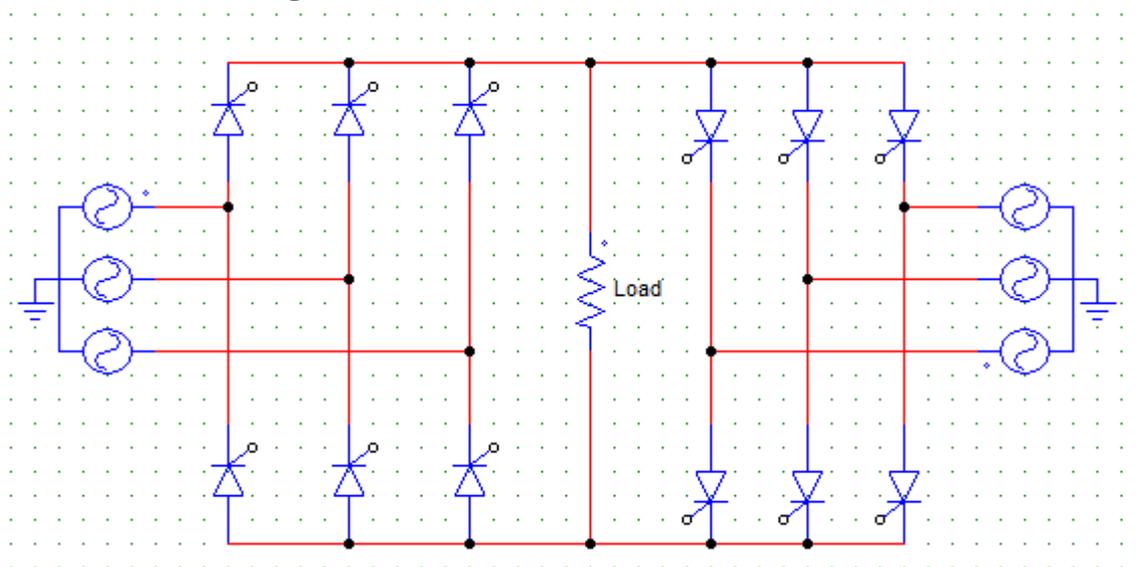

Three-phase dual converter with non-circulating current type

The circuit is a three phase dual converter circuit. As there is no reactor (inductor) in series, it is a non-circulating type.

5. In case of three-phase dual converter, one of the converter circuits is fired at an angle of 60° . For both the converter circuits to have equal average output voltage, what is the value of the firing angle for the other converter circuit?

120°

For equal average output voltage, $\alpha_1 + \alpha_2 = 180^\circ$.

6. In case of circulating current type dual converters, the reactor is inserted between the converters

Reactor (inductance) is added in circulating current mode between both the converters. The reactor limits the current to a reasonable value.

7. Choose the correct statement.

Circulating current type is faster in operation

In case of non-circulating type, to shift the operation from one mode to another mode a delay of 10 to 20msec is required to let the current decay to zero value and let the outgoing SCRs safely turn off. This delay is not required in case of circulating current mode.

8. Circulating current flows from one converter to another converter

The circulating current flows only between the converters and not through the load.

9. The reactor in circulating current type dual converters
increases losses,
reduces power factor
increase the weight of the circuit


All of the above mentioned are the major drawbacks of using reactors to reduce circulation current.

10. If V_1 and V_2 are the instantaneous voltages of the two converter circuits in the dual convert, then the output voltage is

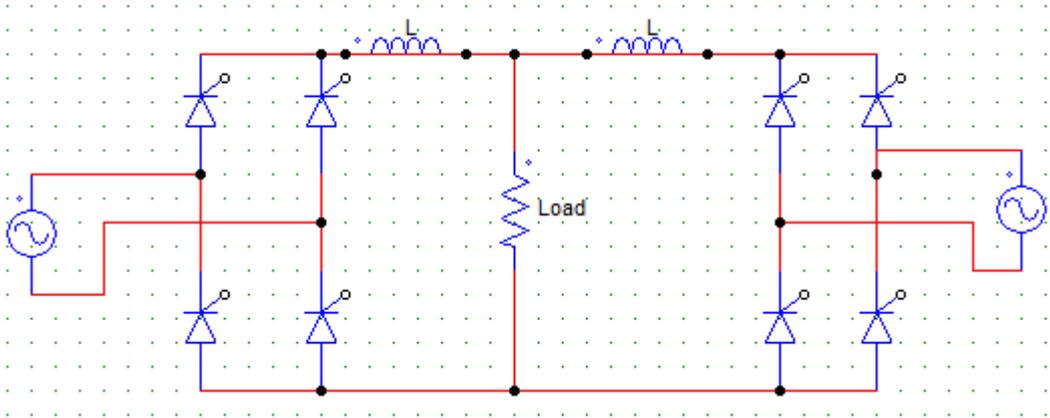b) $(V_1 + V_2)/2$

The load voltage is the average value of the instantaneous converter outputs.

Name the circuit shown in the figure below.



The converters are connected in parallel not in anti-parallel.

2. Dual converters handle only circulating current during no load.


a) very high temperature

During no load period, both the converters handle only the circulating current as the load current is zero.

3. In a three phase dual converter, converter 1 is operating with $\alpha = 95^\circ$ and converter 2 is operating with $\alpha_2 = 85^\circ$. Choose the correct statement.

c) Converter 1 is operating as a inverter and converter 2 as an rectifier
 As $\alpha_1 > 90$, converter 1 is operating as a inverter and with $\alpha_2 < 90$, converter 2 is working as an inverter.

4. The circuit shown below is that of a

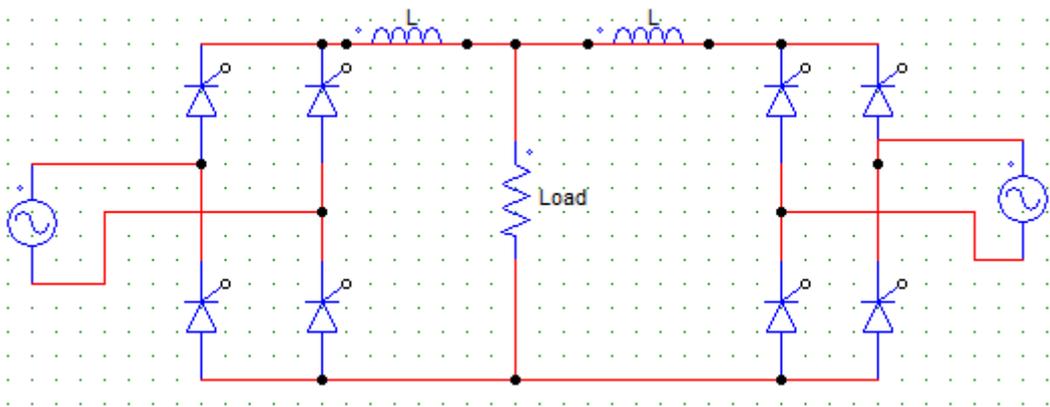

c) three-phase circulating current type dual converter

It is a 3-phase as it uses 6 SCRs on either sides, it is circulating current type as there is a reactor (L) placed on either sides of the load to compensate for the circulating current.

5. In circulating current type of dual converters, the nature of voltage across the reactor is alternating

The current is alternating in nature.


6. When a line commutated converter operates in the inverter mode then it delivers real power to the supply

A converter is given an AC supply, when it is in the inverter mode, it is sending power (only real power) to the AC supply and absorbing power (only reactive) power from the supply.

7. The reactor is required in a circulating current type dual converter to limit the circulating current

Reactor (inductance) is introduced in the circulating current mode between both the converters. The reactor limits the current to a reasonable value.

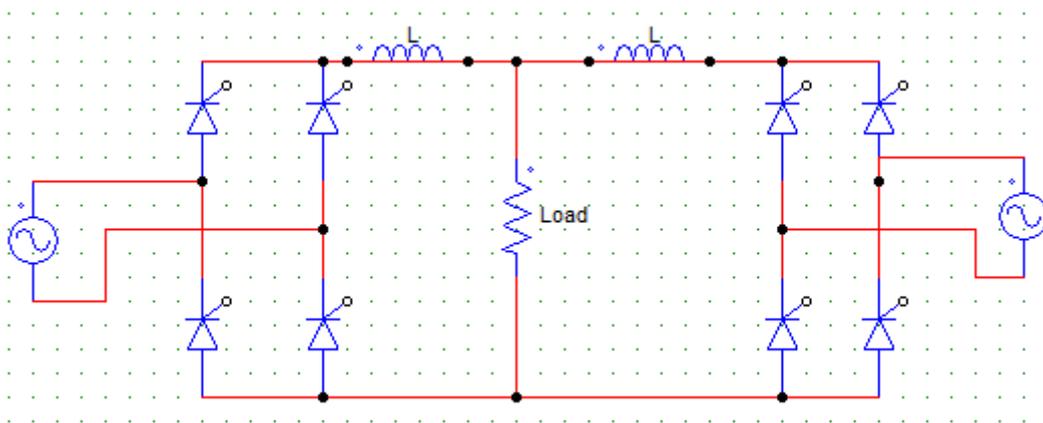8. In the below given figure the converter 1 (to the right side) has firing angle = α_1 , converter 2 has firing angle = α_2 . For the dual converter to operate in the second quadrant.




$$\alpha_2 > 90^\circ$$

Converter 1 would control the first and the fourth quadrant and converter 2 would operate in the second and the third quadrant. In the second quadrant, voltage should be positive and current should be negative, hence inverter operation hence $\alpha_2 > 90^\circ$.

9. If V_1 and V_2 are the converter output voltages then the reactor voltage is $V_1 - V_2$

The reactor voltage V_r is the difference of the converter output voltages.

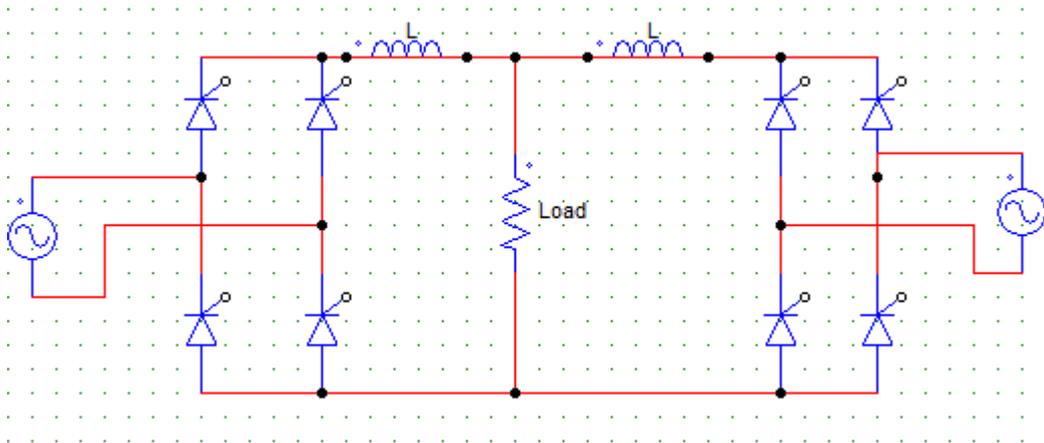10. In the below given figure, the converter 1 (to the right side) has firing angle = α_1 , converter 2 has firing angle = α_2 . For the dual converter to operate in the fourth quadrant.



$\alpha_1 > 90^\circ$

Converter 1 would control the first and the fourth quadrant and converter 2 would operate in the second and the third quadrant. In the fourth quadrant, voltage should be negative and current should be positive, hence C1 as an inverter is operated with $\alpha_1 > 90^\circ$.

Question

A single-phase dual converter is fed from 230 V, 50 Hz source. The load is $R = 30 \Omega$ and current limiting reactor has $L = 0.05 \text{ H}$. For $\alpha_1 = 30^\circ$, calculate the peak value of circulating current.

Solution

$$i_{cp} = 2V_m \omega L [1 - \cos \alpha_1]$$

$$= 2\sqrt{2} \times 230 \times \pi \times 50 \times 0.05 [1 - \cos 30^\circ] = 5.548 \text{ Amp}$$

A three phase dual converter, operating in the circulating current mode, has the following data:

Per phase supply voltage = 230V

Supply frequency, $f=50\text{Hz}$

Firing angle $\alpha_1=60^\circ$

Current limiting reactor, $L=15\text{mH}$

The peak value of circulating current is _____ A.

Solution

The peak value of circulating current

$$i_{cp} = \sqrt{3} V_{mL\omega} L [1 - \sin \alpha_1]$$

$$= \sqrt{3} \cdot \sqrt{6} \cdot 230 \cdot 2\pi \times 50 \times 15 \times 10^{-3} [1 - \sin 60^\circ]$$

$$= 27.74\text{A}$$

Two 3- ϕ full converters are connected in antiparallel to form a 3- ϕ dual converter of the circulating current type. The input to the dual converter is 3- ϕ , 400 V, 50 Hz. Peak value of the circulating current is to be limited to 15 A. If the firing angle $\alpha_1=30^\circ$, value of inductance needed is

Solution

Peak circulating current,

$$i_{CP} = \sqrt{3} V_{m1\omega} L (1 - \sin \alpha_1)$$

$$15 = \sqrt{3} \times 400 \sqrt{2} \cdot 100\pi L (1 - \sin 30^\circ)$$

$$L = 104.0 \text{ mH}$$

Question

A 3- ϕ 3 pulse converter, fed from 3- ϕ , 400 V, 50 Hz supply, has a load $R=2\Omega$, $E = 200$ V and large inductance so that load current is constant at 20 A. If source has an inductance of 2 mH, then the value of overlap angle for inverter operation is

$$V_0 = -E_0 + I_0 R$$

$$3V_m / 2\pi \cos \alpha - 3\omega L_s 2\pi I_0 = -E_0 + I_0 R$$

$$270.094 \cos \alpha = -154$$

$$\alpha = \cos^{-1}(-154/270.094)$$

$$\alpha = 124.76^\circ$$

For a 3- ϕ converter,

$$I_0 = V_m L_s 2\omega [\cos \alpha - \cos(\alpha + \mu)]$$

$$20 = \sqrt{2} \times 400 \times 2\pi \times 50 \times 2 \times 10^{-3} [-0.5701 - \cos(\alpha + \mu)]$$

$$= 450.1581(-0.5701 - \cos(\alpha + \mu))$$

$$\cos(\alpha + \mu) = -0.6145$$

$$\mu = 127.91^\circ - 124.76^\circ$$

$$\mu = 3.15^\circ$$

Question

A single phase full converter is supplied from 230V, 50Hz source. The load consists of $R=10\Omega$ and a large inductance so as to render the load current constant. For a firing angle of 30° , the average and rms values of thyristor currents respectively are


Solution

Average output voltage of single phase full converter is

$$V_0 = 2V_m \pi \cos \alpha$$

$$V_0 = 2\sqrt{2} \times 230 \pi \cos 30^\circ = 179.33 \text{ V}$$
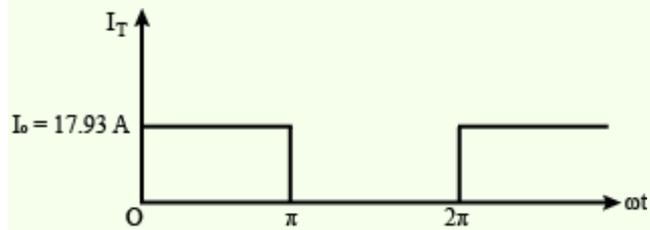
$$I_0 = V_0 R = 179.33 / 10 = 17.93 \text{ A}$$



The average value of thyristor current,

$$I_{T, \text{avg}} = 17.93 \times \pi / 2\pi = 8.96 \text{ A}$$

The rms value of thyristor current,

$$I_{T, \text{rms}} = 17.93 \times \sqrt{\pi / 2\pi} = 12.67 \text{ A}$$