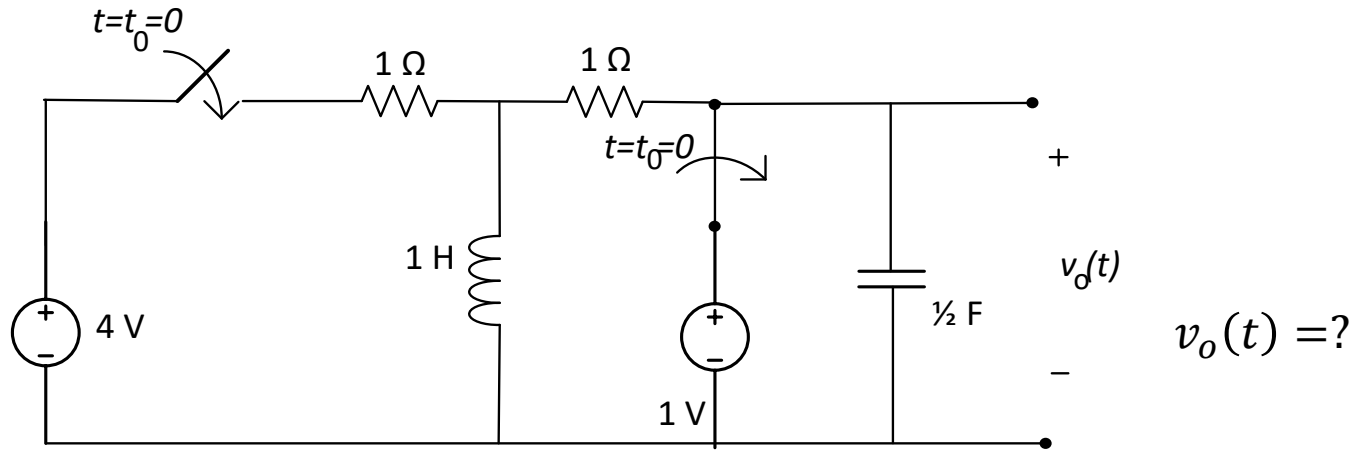


Homework – 3

Submission deadline: 31.12.2022 / 23.59



Obtain the $v_o(t)$ voltage by using s-domain analysis.

Obtain the same voltage value by simulating the circuit when $t>0$ at t-domain.

Compare the result by drawing the simulation and analysis results on the same graph.