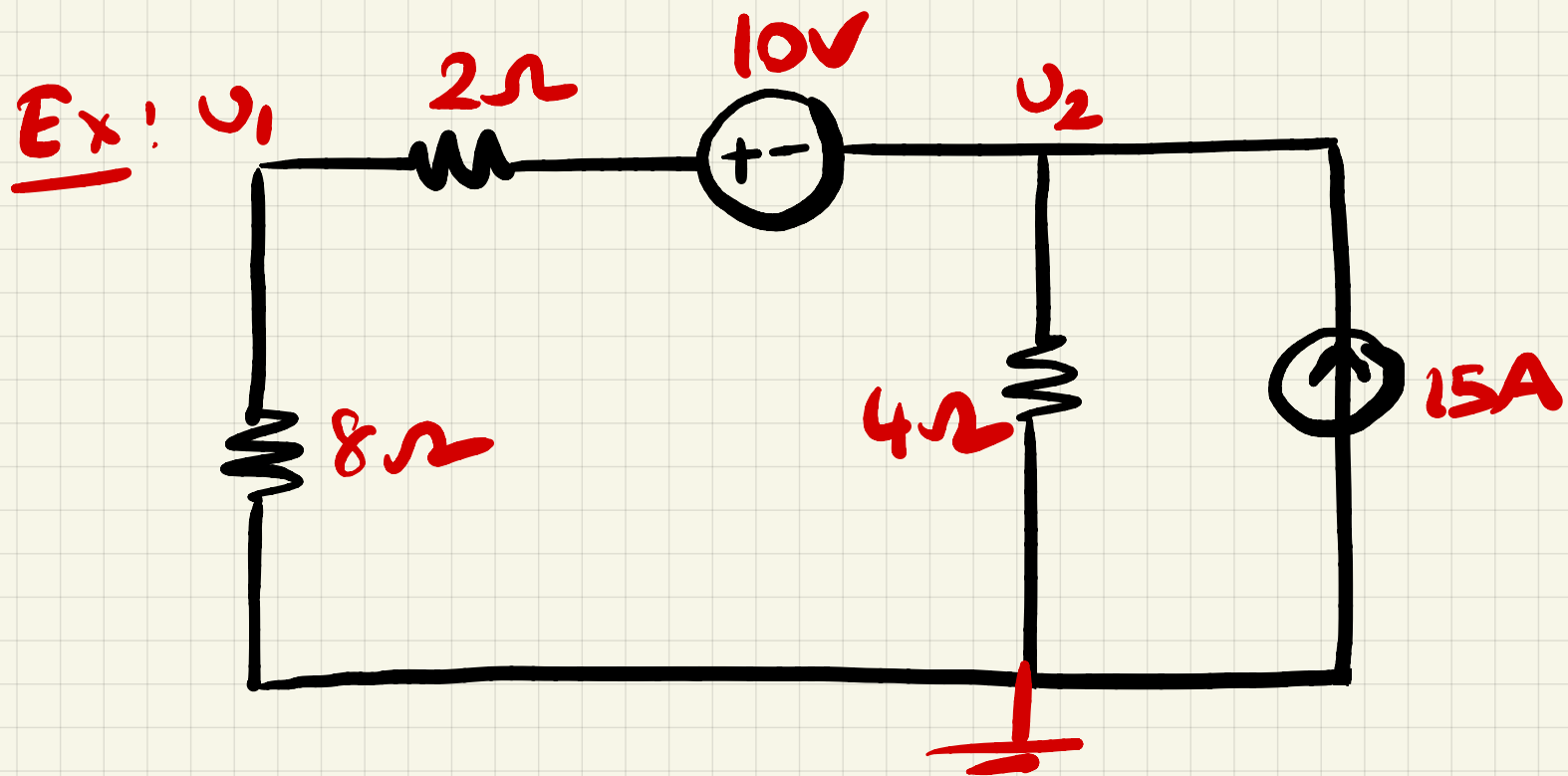



# EXERCISES





Calculate  $v_1$  and  $v_2$ :

Sol:

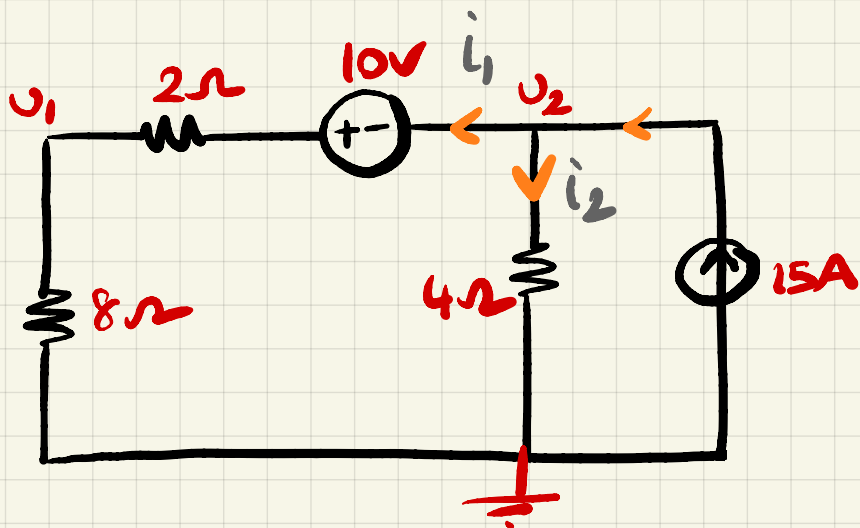

$$\frac{v_2 + 10}{10} + \frac{v_2}{4} - 15A = 0$$

$$2v_2 + 20 + 5v_2 = 300$$


$$7v_2 = 280 \quad v_2 = 40V$$

$$\frac{v_2 + 10}{10} = i_1$$

$$i_1 = 5A$$


$$v_1 = 8 \times 5 = 40V \checkmark$$

Ex:

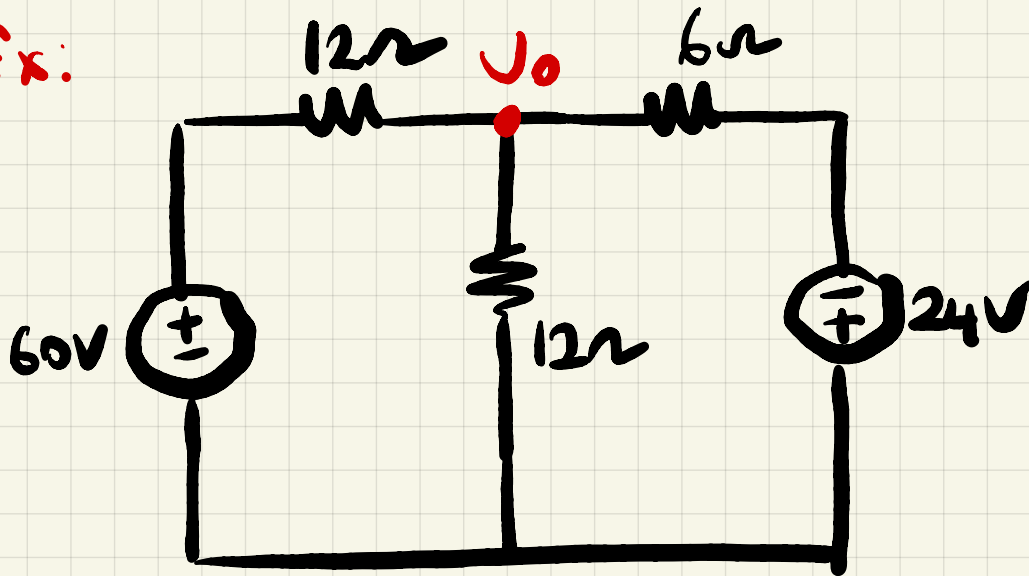

Find  $V_o$   
and  
power  
absorbed  
by all  
resistors.

Sol

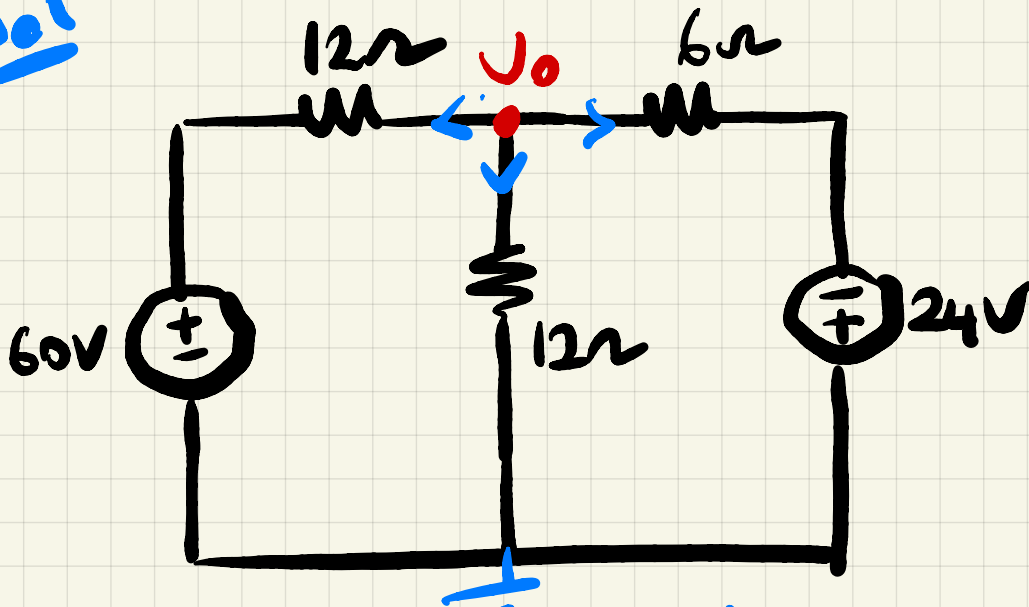

$$\frac{V_o - 60}{12} + \frac{V_o}{12} + \frac{V_o - (-24)}{6} = 0$$

$$V_o - 60 + V_o + 2V_o + 48 = 0$$

$$4V_o = 12V \quad \underline{V_o = 3V}$$

$$P_{12} = \frac{(60 - 3)^2}{R} =$$


$$P_{12} = \frac{57^2}{12}$$

$$P_{12} = 270.75W$$

$$P_{12} = \frac{V_o^2}{R} = \frac{9}{12} = 0.75W$$


$$P_{6\Omega} = \frac{3 - (-24)^2}{6} = 121.5W$$

Ex:

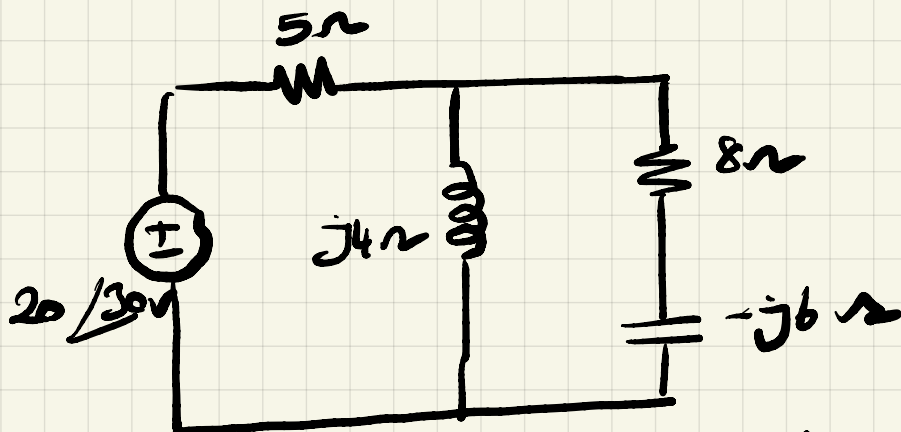

Find the average power delivered by the 5Ω

Sol:

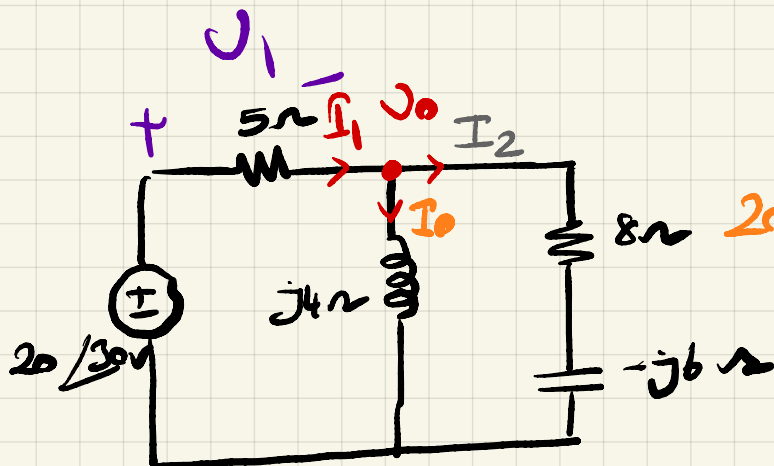

$$20\angle 30^\circ = 20 \cos 30^\circ + j20 \sin 30^\circ = 17,32 + j10 \text{ V}$$

$$\frac{20\angle 30^\circ - V_0}{5} = \frac{V_0}{4j} + \frac{V_0}{8 - j6}$$

(20)      (-25j)      (8 + j6)

$$I_1 = \frac{20\angle 30^\circ - 11,82\angle 64^\circ}{5}$$

$$400\angle 30^\circ - 20V_0 = -25jV_0 + 8V_0 + 6jV_0$$

$$400\angle 30^\circ = 28V_0 - 19jV_0$$

$$V_0 = \frac{400\angle 30^\circ}{\sqrt{28^2 + 19^2} \angle \arctan \frac{19}{28}}$$

$$V_0 = \frac{400}{33,83} = 11,82 \angle +64,16^\circ \text{ V}$$

$$I_1 = \frac{17,32 + j10 - (5,15 - j11,82)}{5}$$

$$I_1 = \frac{12,17 - j1,82}{5}$$

$$I_1 = 2,43 \angle -3^\circ \text{ A}$$

$$V_0 = 11,82 \cos 64,16^\circ + j11,82 \sin 64,16^\circ$$

$$V_0 = 5,15 + j10,63 \text{ V}$$

$$V_1 = 12,17 - j1,82$$

$$V_1 = 12,30 \angle -8,5^\circ \text{ V}$$

$$P_1 = 29,89 \text{ W}$$

$$I_0 = \frac{V_0}{j4} = \frac{11,82 \angle 64,16}{4 \angle 90} = 2,95 \angle -25,84$$

$$I_2 = \frac{V_0}{8 - j6} = \frac{11,82 \angle 64,16}{10 \angle -36,86} = 1,18 \angle 101,02$$

$$S_{\text{supply}} = 20 \angle 30 \cdot (2,43 \angle +3) = 48,6 \angle 33 \text{ VA}$$


$$S_{\text{supply}} = 40,75 + j 26,46$$

$$P_{8\Omega} = (1,18)^2 \cdot 8 = 11,13 \text{ W}$$

$$P_{\text{rep}} = 29,89 + 11,13 = 41,02 \text{ W}$$

~  
40,75 W


Ex:

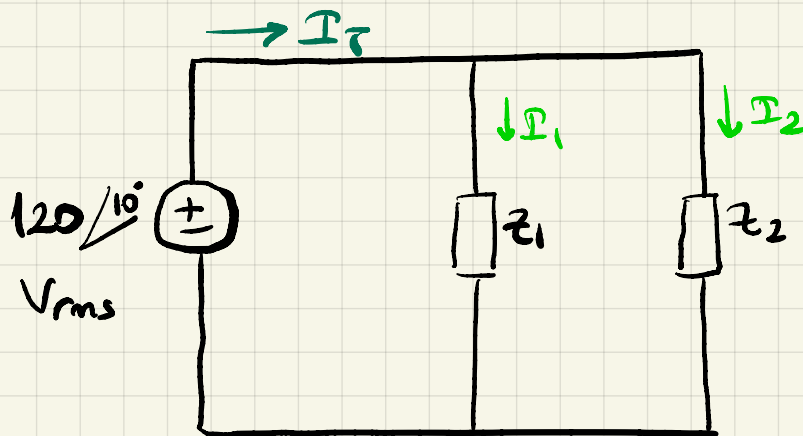

$$Z_1 = 60 \angle -30^\circ \Omega \text{ and } Z_2 = 40 \angle 45^\circ \Omega$$

Calculate total apparent power,  
b) real power, c) reactive power, d) pf

Sol:

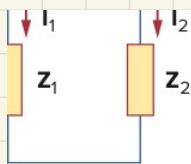

**Solution:**

The current through  $Z_1$  is

$$I_1 = \frac{V}{Z_1} = \frac{120 \angle 10^\circ}{60 \angle -30^\circ} = 2 \angle 40^\circ \text{ A rms}$$

while the current through  $Z_2$  is

$$I_2 = \frac{V}{Z_2} = \frac{120 \angle 10^\circ}{40 \angle 45^\circ} = 3 \angle -35^\circ \text{ A rms}$$

The complex powers absorbed by the impedances are

$$S_1 = \frac{V_{\text{rms}}^2}{Z_1^*} = \frac{(120)^2}{60 \angle 30^\circ} = 240 \angle -30^\circ = 207.85 - j120 \text{ VA}$$

$$S_2 = \frac{V_{\text{rms}}^2}{Z_2^*} = \frac{(120)^2}{40 \angle -45^\circ} = 360 \angle 45^\circ = 254.6 + j254.6 \text{ VA}$$

The total complex power is

$$S_t = S_1 + S_2 = 462.4 + j134.6 \text{ VA}$$

(a) The total apparent power is

$$|S_t| = \sqrt{462.4^2 + 134.6^2} = 481.6 \text{ VA.}$$

(b) The total real power is

$$P_t = \text{Re}(S_t) = 462.4 \text{ W or } P_t = P_1 + P_2.$$

(c) The total reactive power is

$$Q_t = \text{Im}(S_t) = 134.6 \text{ VAR or } Q_t = Q_1 + Q_2.$$

(d) The pf =  $P_t / |S_t| = 462.4 / 481.6 = 0.96$  (lagging).

We may cross check the result by finding the complex power  $S_s$  supplied by the source.

$$I_t = I_1 + I_2 = (1.532 + j1.286) + (2.457 - j1.721)$$

$$= 4 - j0.435 = 4.024 \angle -6.21^\circ \text{ A rms}$$

$$S_s = VI_t^* = (120 \angle 10^\circ)(4.024 \angle 6.21^\circ)$$

$$= 482.88 \angle 16.21^\circ = 463 + j135 \text{ VA}$$

which is the same as before.

