
WEEK - 4

■ Root Mean Square (RMS Value)




◦ AC Cont <

IMPORTANT (EQUATIONS, LAWS, ETC.)


Root-Mean-Square (RMS)-Effective

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2}$$

NOTES


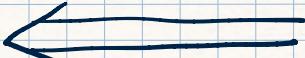
 Root-Mean-Square
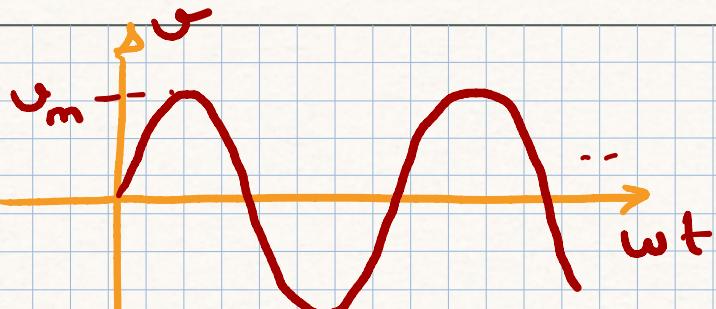
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2}$$



RMS of Sinusoidal Signal is $\frac{V_m}{\sqrt{2}} = V_{rms}$

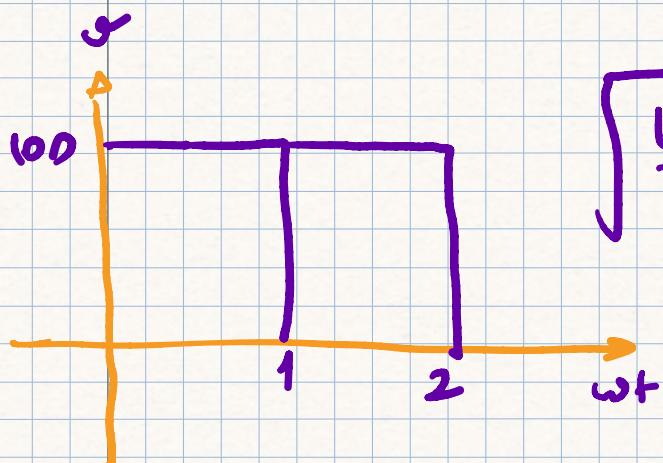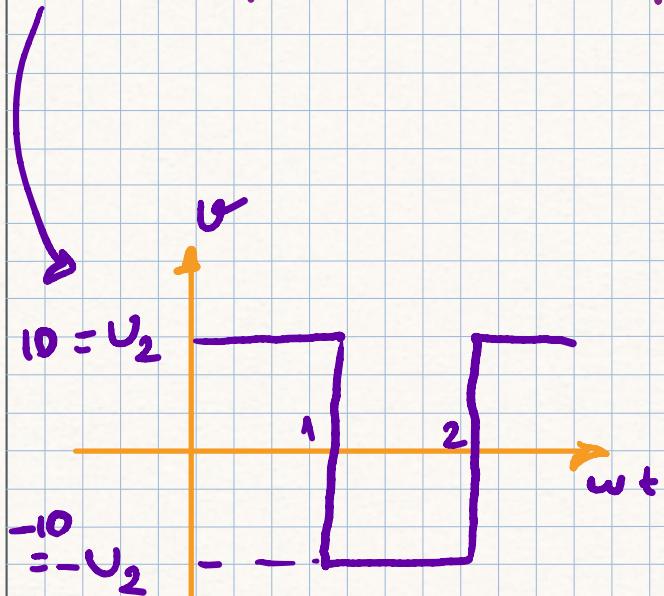
RMS of Square Signal is $\frac{V_m}{1} = V_{rms}$




$$\sqrt{\frac{10^2 \cdot 2}{2}} = 10$$

RMS of Triangular Signal is $V_{rms} =$

V_m of 220 V(rms) =

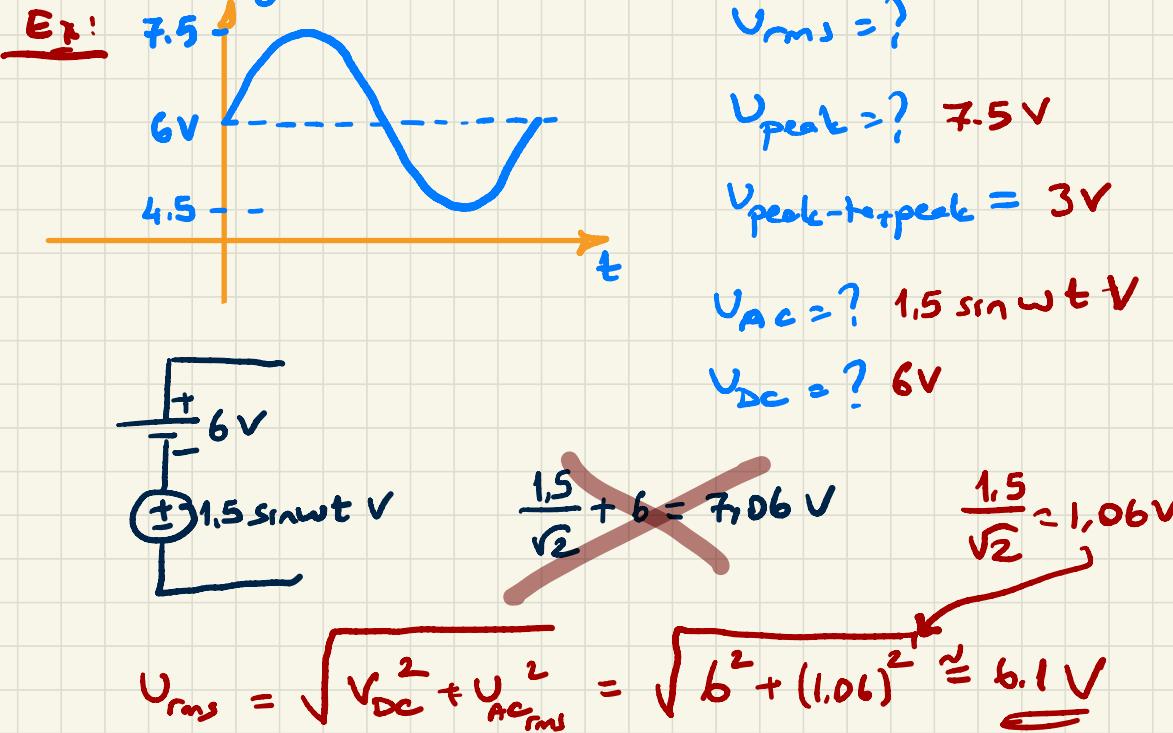

COMPLEX NUMBERS

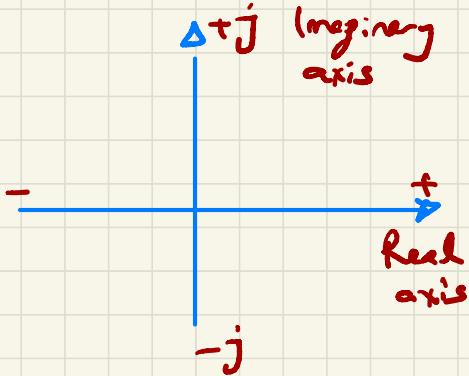




$$i = j = \sqrt{-1}$$

$$j^2 = -1$$

Rectangular form $C = x + jy$

Polar form $C = z \angle \theta$

Exponential form $C = Ae^{j\theta}$

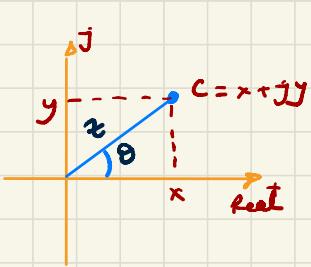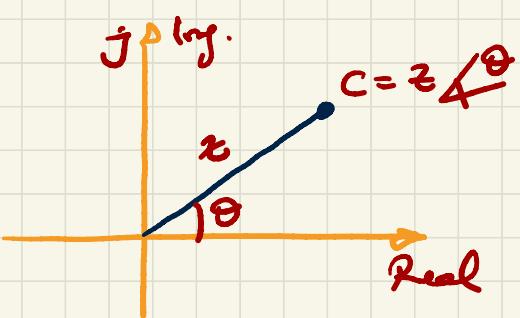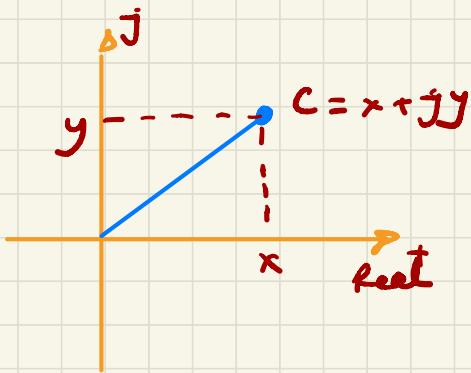

Rectangular to Polar

$$c = x + jy$$

$$z = \sqrt{x^2 + y^2}$$

$$\theta = \arctan \frac{y}{x}$$

$$c = z \angle \theta$$

Polar to Rectangular

$$c = z \angle \theta$$


$$x = z \cdot \cos \theta$$

$$y = z \cdot \sin \theta$$

$$c = x + jy$$

Ex: Convert $c = 10 \angle 45^\circ$ to rectangular

Ex: Convert $c = -6 + j3$ to polar form.

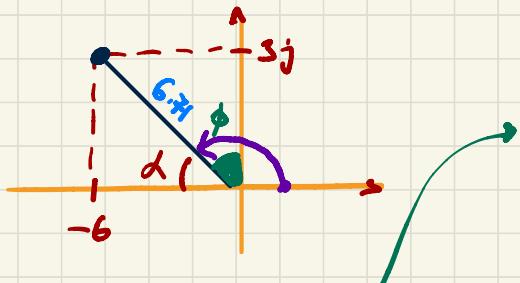

$$\left. \begin{array}{l} C_1 = x_1 + jy_1 \\ C_2 = x_2 + jy_2 \end{array} \right\} \quad \begin{array}{l} + \\ \text{Summing} \end{array} \quad \begin{array}{l} - \\ \text{Subtraction} \end{array}$$

$$C_1 \pm C_2 = (x_1 \pm x_2) \pm j(y_1 \pm y_2)$$


$$\left. \begin{array}{l} C_1 = z_1 \angle \theta_1 \\ C_2 = z_2 \angle \theta_2 \end{array} \right\}$$

Multiplication and Division

$$C_1 \cdot C_2 = z_1 \cdot z_2 \angle \theta_1 + \theta_2$$

$$\frac{C_1}{C_2} = \frac{z_1}{z_2} \angle \theta_1 - \theta_2$$

PHASORS

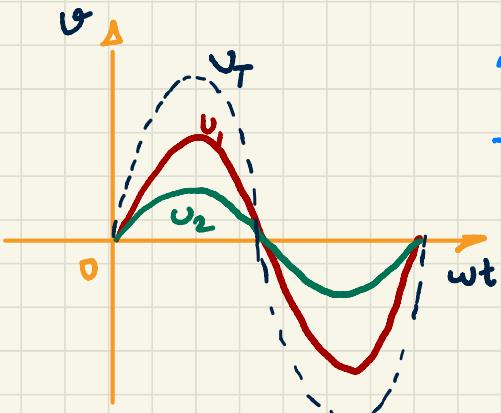


The addition (or subtraction) of two sinusoidal voltages of the same frequency and phase angle is simply the sum (or difference) of the peak values of each with the sum (or difference) having the same phase angle.

$$V_1 = 3 \sin \omega t \rightarrow \text{Polar form} = \frac{3}{\sqrt{2}} \angle 0^\circ = 2.12 \angle 0^\circ$$

$$V_2 = 2 \sin \omega t \rightarrow \text{Polar form} = \frac{2}{\sqrt{2}} \angle 0^\circ = 1.41 \angle 0^\circ$$
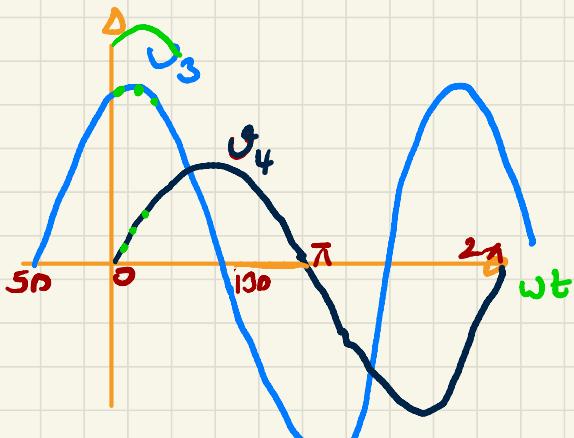
$$V_r = 5 \sin \omega t \rightarrow \text{Polar form} = \frac{5}{\sqrt{2}} \angle 0^\circ = 3.53 \angle 0^\circ$$



$$V_3 = 4 \sin(\omega t + 50^\circ)$$

$$V_4 = 2 \sin \omega t$$

$$V_3 = \frac{4}{\sqrt{2}} \angle 50^\circ$$

$$V_4 = \frac{2}{\sqrt{2}} \angle 0^\circ$$

Time

$$5 \sin \omega t$$

\downarrow

$$V_m \sin \omega t$$

!

(PHASOR) Polar-Form

$$\frac{5}{\sqrt{2}} \angle 0^\circ$$

$$\sqrt{\frac{V_m}{2}} = V_{rms}$$

!

$$4 \sin(\omega t + 90^\circ)$$

$$\frac{4}{\sqrt{2}} \angle 90^\circ$$

$$\frac{5}{\sqrt{2}} \cos 0 + j \frac{5}{\sqrt{2}} \sin 0$$

$$\frac{4}{\sqrt{2}} \cos 90 + j \frac{4}{\sqrt{2}} \sin 90$$

$j 2.82$

IMPEDANCE

Resistor


$$V_m = V_{max}, I_m = I_{max}$$

!

$$V_R = V_m \sin \omega t \Rightarrow V_R = V_{rms} \angle 0^\circ = \frac{V_m}{\sqrt{2}} \angle 0^\circ$$

$$i_R = I_m \sin \omega t \Rightarrow I_R = I_{rms} \angle 0^\circ = \frac{I_m}{\sqrt{2}} \angle 0^\circ$$
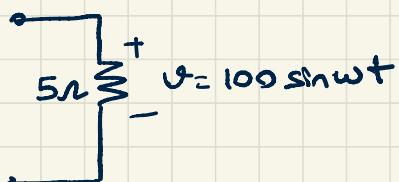
$$\boxed{\text{Impedance } Z_R = \frac{V_{rms} \angle 0^\circ}{I_{rms} \angle 0^\circ} = R \angle 0^\circ}$$



$$V = \frac{100}{\sqrt{2}} \angle 0^\circ = 100 \sin \omega t$$

$$Z_R = 5 \angle 0^\circ$$

$$I = \frac{V}{Z_R} = \frac{100/\sqrt{2} \angle 0^\circ}{5 \angle 0^\circ} = 14.14 \angle 0^\circ$$

$$i = (14.14)\sqrt{2} \cos 0 + j (14.14) (\sqrt{2}) \sin 0 = 20 \sin \omega t$$

should be
max !

(POLAR FORM)
PHASOR

$$\frac{U_m}{\sqrt{2}} \angle 0^\circ = U_{rms} \angle 0^\circ \text{ USE RMS}$$

TIME ($U_m \sin \omega t$) USE MAX. VALUE?

INDUCTANCE

$$Z_L = \frac{V \angle 0^\circ}{I \angle -90^\circ} = X_L \angle +90^\circ = \omega L \angle +90^\circ$$

Reactance

$$= j \omega L = j X_L$$

CAPACITANCE

Unit $\rightarrow \Omega$ (ohm)

$$Z_C = \frac{V \angle 0^\circ}{I \angle -90^\circ} = X_C \angle -90^\circ = \frac{1}{\omega C} \angle -90^\circ$$
$$= -j \frac{1}{\omega C} = -j X_C$$

RESISTANCE


Unit $\rightarrow \Omega$ (ohm)

$$Z_R = \frac{V \angle 0^\circ}{I \angle 0^\circ} = R \angle 0^\circ$$


Unit $\rightarrow \Omega$ (ohm)

$$Z = R + jX$$

↓ Impedance ↓ Resistance → Reactance

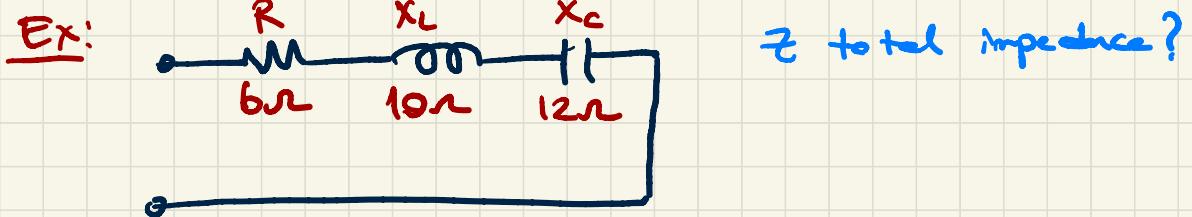

Z total impedance?

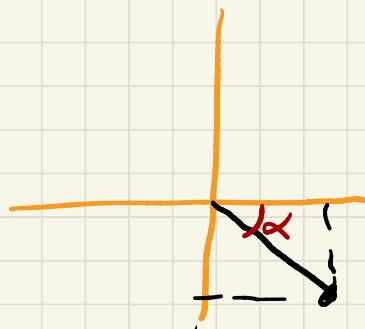


$$\alpha = \arctan \frac{2}{6} = 18^\circ$$

A Impedances

A Admittances

D Int. to AC Power

IMPEDANCES

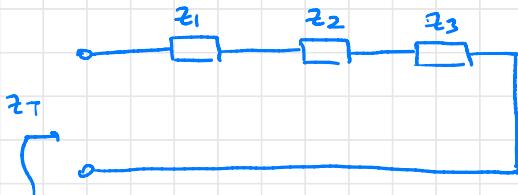

$$Z_1 = R_1 \pm jX_1$$

$$Z_2 = R_2 \pm jX_2$$


$$Z_3 = R_3 \pm jX_3$$

$$Z_T = Z_1 + Z_2 + Z_3$$

$$Z_T = R_T \pm jX_T$$


↓ ↓ ↓
impedance Resistance Reactance
Unit is OHM (Ω)

Ex:

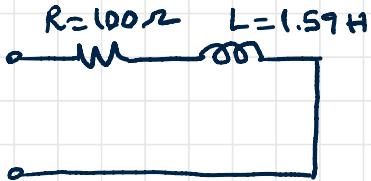

If $f = 50\ Hz$ find $Z_T = ?$
find rectangular and phasor form

Ex:

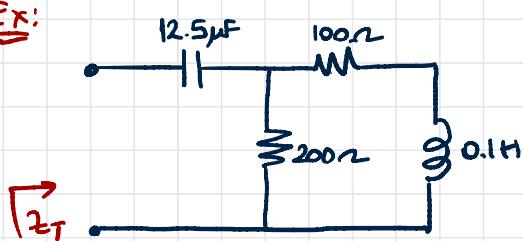



Determine the complex impedance between terminals shown in figure $\omega = 1000 \frac{\text{rad}}{\text{s}}$

ADMITTANCE (γ)

$$\gamma = \frac{1}{z}$$

$$Y = G \pm jB$$

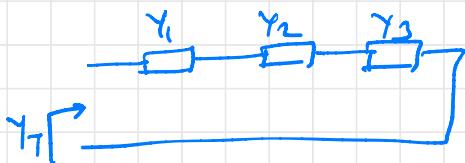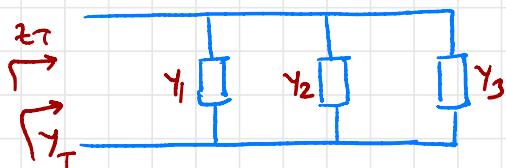Admittance Conductance Susceptance
 (Siemens) (S) (MHz 2π)



$$\gamma_T = \gamma_1 + \gamma_2 + \gamma_3$$

$$\frac{1}{z_T} = \frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3}$$

$$\frac{1}{\gamma_T} = \frac{1}{\gamma_1} + \frac{1}{\gamma_2} + \frac{1}{\gamma_3}$$


$$z_T = z_1 + z_2 + z_3$$

$$\gamma_R = \frac{1}{z_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ \quad (\text{Siemens, S})$$

$$B = \frac{1}{X}$$

$$\gamma_L = \frac{1}{z_L} = \frac{1}{X_L \angle -90^\circ} = \frac{1}{X_L} \angle -90^\circ = B_L \angle -90^\circ \quad (\text{S})$$

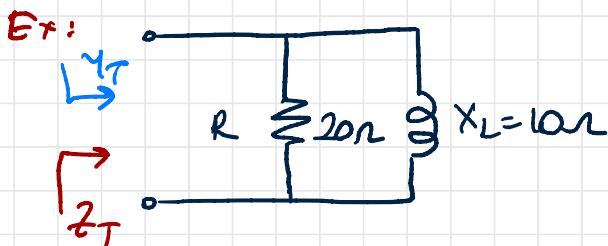
$$\gamma_C = \frac{1}{z_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ = B_C \angle 90^\circ \quad (\text{S})$$







for the network:

- Calculate input impedance
- Find the admittance of each parallel branch.
- Determine input admittance

9

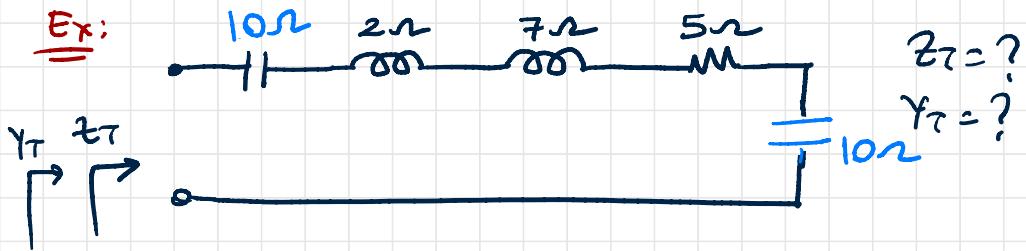

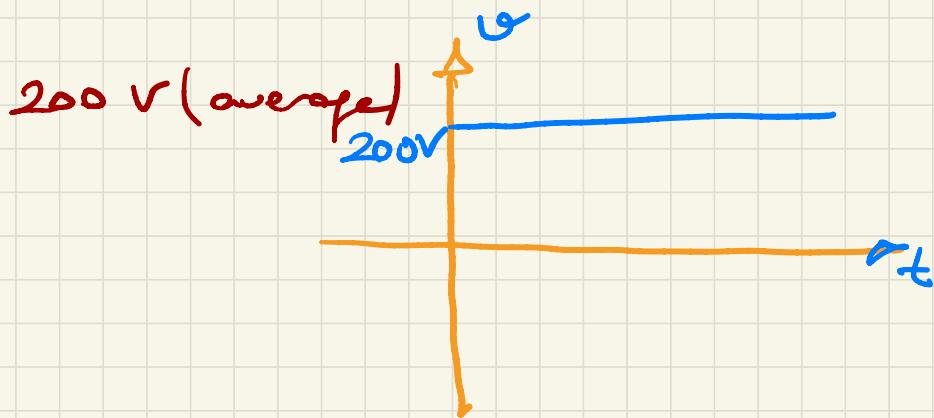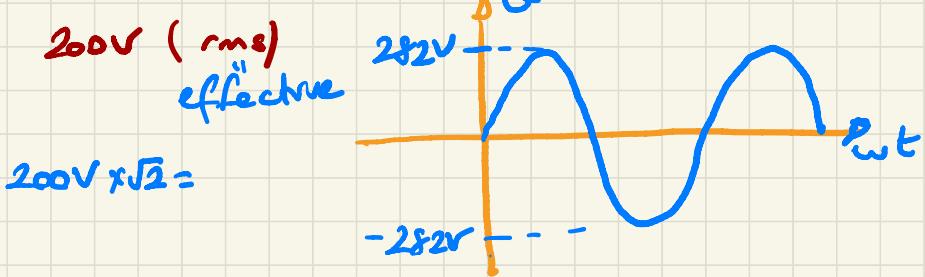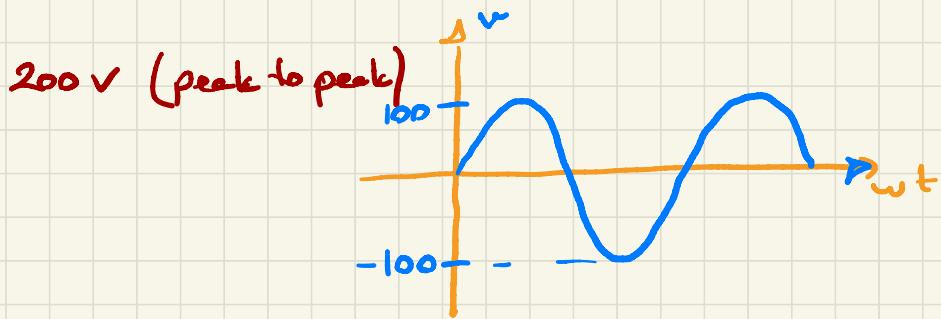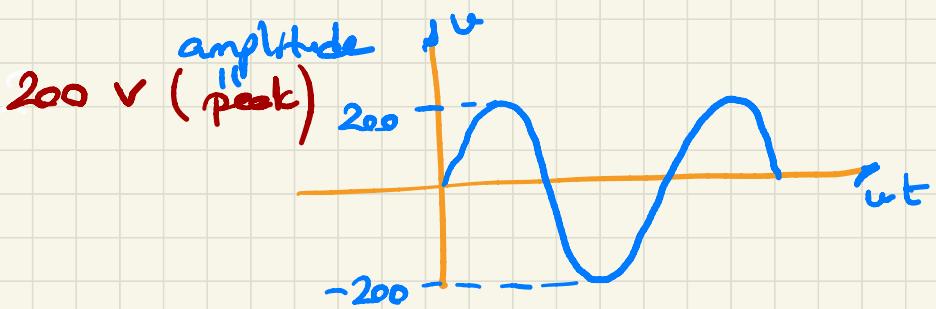




POWER



POWER IN AC CIRCUITS

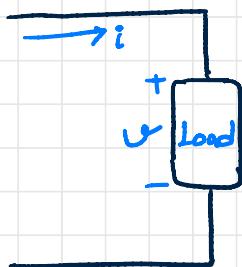

$$P = V \cdot i$$

$$V = V_m \sin(\omega t + \phi)$$

$$i = I_m \sin \omega t$$

$$P = V_m \sin(\omega t + \phi) I_m \sin \omega t$$

$$P = \frac{1}{2} V_m I_m \cos \phi (1 - \cos 2\omega t) + \frac{1}{2} V_m I_m \sin \phi (\sin 2\omega t)$$

$$P = \frac{1}{2} V_m I_m \cos \phi \quad [\text{Watt, W}] \quad \left. \begin{array}{l} \text{REAL POWER} \\ \text{AVERAGE POWER} \\ \text{ACTIVE POWER} \end{array} \right\}$$

$$\text{||} \quad P = V_{rms} I_{rms} \cos \phi \quad [\text{Watt, W}]$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

POWER FACTOR $\rightarrow \cos \phi = F_p, f_p, pf$

$\phi \rightarrow$ power angle $\phi = \phi_v - \phi_i$

$$\cos(\phi_v - \phi_i) = \cos(\phi_i - \phi_v)$$

$$\cos(-\alpha) = \cos(\alpha)$$

REACTIVE POWER

$$Q = \frac{1}{2} V_m I_m \sin \phi$$

$$Q = V_{rms} I_{rms} \sin \phi$$

Unit
[Var]

[Var]

$$\text{? } \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} \cdot I_{rms}$$

Volt-Amper Reactive
Volt-Amper reactive
Reactive Power factor

LAGGING POWER FACTOR \Rightarrow current lags voltage \Rightarrow

INDUCTIVE LOAD

LEADING POWER FACTOR \Rightarrow current leads voltage \Rightarrow

CAPACITIVE LOAD

ELI the ICE man
Inductive Capacitive

COMPLEX POWER


$$S = P + jQ$$

supplier
consumer
Watts
VA


inductive
capacitive

$$S = |S| \angle \theta$$

Complex Apparent Power

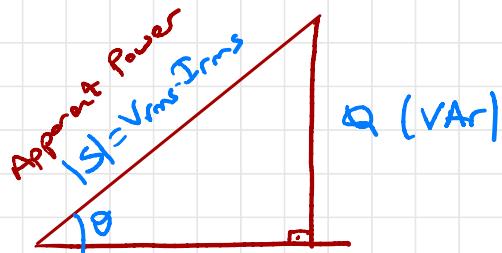

P (W)
Inductive (θ positive)

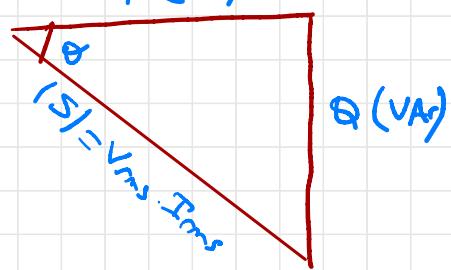

Capacitive (θ negative)


Complex Power

$$S = P \pm jQ$$

active P. reactive power

$$S = |S| \angle \theta$$

complex power Apparent power

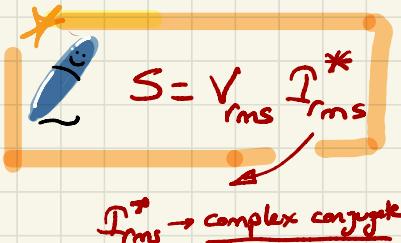

$$I_{rms} = 2 \angle 30^\circ A \quad I_{rms}^* = 2 \angle -30^\circ A$$

$$S = V_{rms} \cdot I_{rms} e^{j(\theta_v - \theta_i)}$$

$$S = V_{rms} e^{j\theta_v} \cdot I_{rms} e^{-j\theta_i}$$

$$\boxed{S = V_{rms} \cdot I_{rms}^*}$$

Ex: find average power, reactive power, apparent power and complex power

if $V = 100 \angle 15^\circ V, I = 4 \angle -105^\circ A$

b) find average power, reactive power, apparent power and complex power

if $v = 141.42 \sin(\omega t + 15^\circ)$ and $i = 5.66 \sin(\omega t - 105^\circ) A$

c) find average power, reactive power, apparent power and complex power

if $v = 100 (\cos 15 + j \sin 15)$ $i = 4 (\cos 105 - j \sin 105)$
 $v = 96.59 + j 25.88 V$ $i = -1.03 - j 3.86 A$


Solution

$$P =$$

Additional Power Relationships

Impedance is z

$$z = |z| \angle \theta = R + jX$$

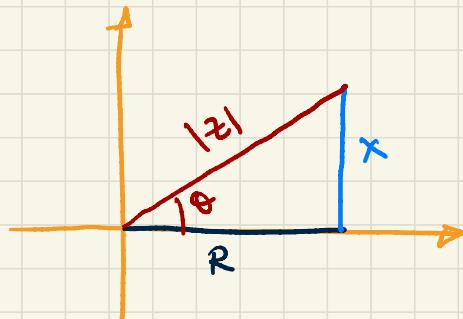

$$\cos \theta = \frac{R}{|z|}$$

$$\sin \theta = \frac{X}{|z|}$$

$$P = \frac{V_m \cdot I_m \cos \theta}{2} = \frac{V_m I_m}{2} \cdot \frac{R}{|z|}$$


$$I_m = \frac{V_m}{|z|} \quad P = \frac{I_m^2}{2} \cdot R = I_{rms}^2 \cdot R$$

$$Q = \frac{I_m^2}{2} \cdot X = I_{rms}^2 \cdot X = \frac{V_{rms}^2}{X}$$


$$S = V_{rms} I_{rms} \cdot \cos \phi + j V_{rms} I_{rms} \cdot \sin \phi$$

$$P = |S| \cdot \cos \phi \quad \cos \phi = \frac{P}{|S|}$$

$$\text{PF} = \frac{P}{|S|} = \cos \phi$$

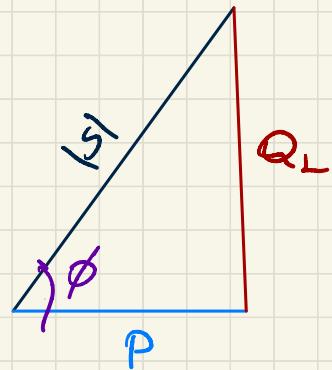

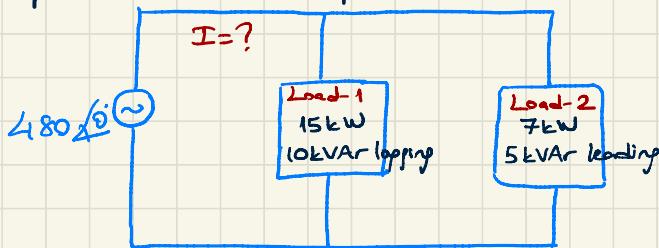
Ex: Two parallel loads draw from a 480 V (rms) source as shown below, where Load-1 draws 15 kW and 10 kVAr lagging, and Load-2 draws 7 kW and 5 kVAr leading. Determine the combined power factor and total apparent power drawn from the source.



b) $I = ?$ $S_1 \rightarrow \text{Inductive } (L) + \text{VAC}$ $S_2 \rightarrow \text{capacitive } (C) -$

Solution:


Ex:

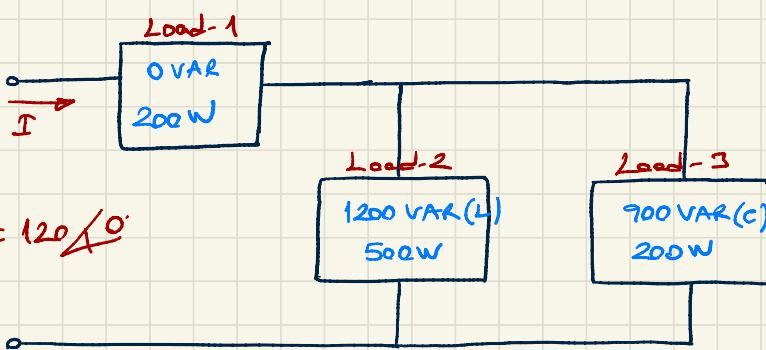

$$E = 120 \text{ V}$$

Find the total number of Active Power, Apparent Power
Reactive Power, and Power factor of the system.
Find $I = ?$

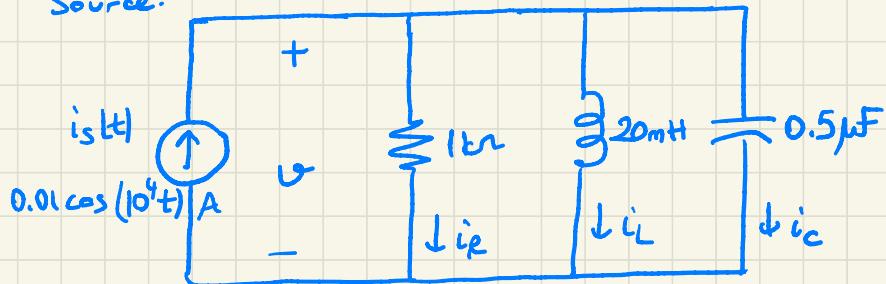Ex: Consider the circuit shown in figure. find the phasors I_S , V , I_R , I_L and I_C . Find the Apparent power for the source.



Solution:

$$i_s(t) = 10 \sin(10^4 t + 90^\circ) \text{ mA} \quad \omega = 10^4$$

$$I_S = \frac{10}{\sqrt{2}} \angle 90^\circ = 7.07 \angle 90^\circ \text{ mA}$$

$$Z_1 = 1000 \Omega$$

$$X_L = \omega L = 10^4 \cdot 20 \cdot 10^{-3} = 200 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{10^4 \cdot 0.5 \times 10^{-6}} = 200 \Omega$$

$$V = I \cdot R \Rightarrow V = 7.07 \angle 90^\circ \cdot 1000 = 7.07 \angle 90^\circ \text{ V}$$

$$I_L = \frac{7.07 \angle 90^\circ}{200 \angle 90^\circ} = 0.035 \angle 0^\circ \text{ A}$$

$$I_C = \frac{7.07 \angle 90^\circ}{200 \angle 90^\circ} = 0.035 \angle 180^\circ \text{ A} \quad S = 49.98 \angle 0^\circ \text{ mVA}$$

$$S = V_{rms} \cdot I_{rms}^*$$

$$= 7.07 \angle 90^\circ \cdot 7.07 \angle 90^\circ \text{ mA}$$