




WEEK -5

AC POWER



POWER IN AC CIRCUITS

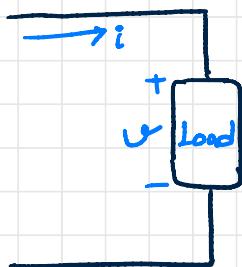

$$P = V \cdot i$$

$$V = V_m \sin(\omega t + \phi)$$

$$i = I_m \sin \omega t$$

$$P = V_m \sin(\omega t + \phi) I_m \sin \omega t$$

$$P = \frac{1}{2} V_m I_m \cos \phi (1 - \cos 2\omega t) + \frac{1}{2} V_m I_m \sin \phi (\sin 2\omega t)$$

$$P = \frac{1}{2} V_m I_m \cos \phi \quad [\text{Watt, W}] \quad \begin{cases} \text{REAL POWER} \\ \text{AVERAGE POWER} \\ \text{ACTIVE POWER} \end{cases}$$

$$\text{||} \quad P = V_{rms} I_{rms} \cos \phi \quad [\text{Watt, W}]$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

POWER FACTOR $\rightarrow \cos \phi = F_p, f_p, pf$

$\phi \rightarrow$ power angle $\phi = \phi_v - \phi_i$

$$\cos(\phi_v - \phi_i) = \cos(\phi_i - \phi_v)$$

$$\cos(-\alpha) = \cos(\alpha)$$

REACTIVE POWER

$$Q = \frac{1}{2} V_m I_m \sin \phi$$

$$Q = V_{rms} I_{rms} \sin \phi$$

Unit
[Var]

[VAR]

$$\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms}$$

Volt-Amper Reactive
Volt-Amper reactive

Reactive Power
factor

LAGGING POWER FACTOR \Rightarrow current lags voltage \Rightarrow

INDUCTIVE
LOAD

LEADING POWER FACTOR \Rightarrow current leads voltage \Rightarrow

CAPACITIVE
LOAD

ELI the ICE man
Inductive Capacitive

COMPLEX POWER


$$S = P + jQ$$

supplier
consumer
Watts
VA


inductive
capacitive

$$S = |S| \angle \theta$$

Complex Apparent Power

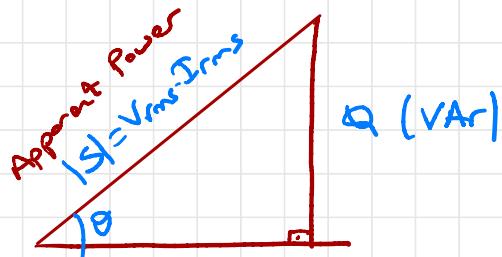

P (W)
Inductive (θ positive)

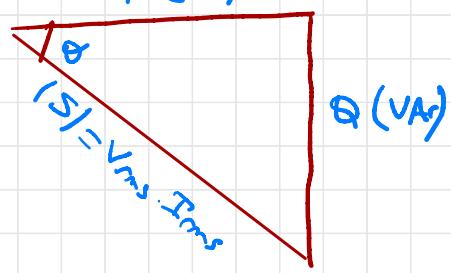

Capacitive (θ negative)


Complex Power

$$S = P \pm jQ$$

active P. reactive power

$$S = |S| \angle \theta$$

complex power Apparent power

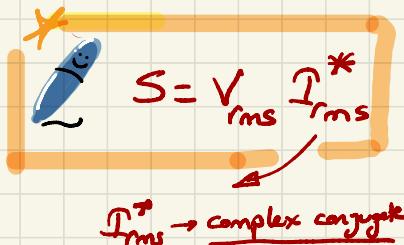

$$I_{\text{rms}} = 2 \angle 30^\circ \text{ A} \quad I_{\text{rms}}^* = 2 \angle -30^\circ \text{ A}$$

$$S = V_{\text{rms}} \cdot I_{\text{rms}} \angle (\theta_v - \theta_i) \quad I_{\text{rms}} = -4 \angle -40^\circ \text{ A} \quad I_{\text{rms}}^* = -4 \angle 40^\circ \text{ A}$$

$$S = V_{\text{rms}} I_{\text{rms}} e^{j(\theta_v - \theta_i)}$$

$$S = V_{\text{rms}} e^{j\theta_v} \cdot I_{\text{rms}} e^{-j\theta_i}$$

$$\boxed{S = V_{\text{rms}} \cdot I_{\text{rms}}^*}$$

Ex: find average power, reactive power, apparent power and complex power

if $V = 100 \angle 15^\circ \text{ V}$, $I = 4 \angle -105^\circ \text{ A}$

b) find average power, reactive power, apparent power and complex power

if $v = 141.42 \sin(\omega t + 15)$ and $i = 5.66 \sin(\omega t - 105)$

c) find average power, reactive power, apparent power and complex power

if $v = 100 (\cos 15 + j \sin 15)$ $i = 4 (\cos 105 - j \sin 105)$

$$v = 96.59 + j 25.88 \text{ V} \quad i = -1.03 - j 3.86 \text{ A}$$

Solution

$$P = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \phi$$

$$V = 100 \angle 15^\circ V, I = 4 \angle +105^\circ A$$

$$S = V_{rms} \cdot I_{rms}^*$$

$$S = 100 \angle 15^\circ \cdot 4 \angle +105^\circ$$

$$S = 100 \cdot 4 \angle 120^\circ = 400 \angle 120^\circ \text{ VA} = |S| \angle 120^\circ \text{ VA}$$

$$S = P \pm jQ \quad S = 400 (\cos 120 + j \sin 120)$$

$$S = -200 + j 346,4 \text{ VA}$$

complex power

$\begin{matrix} P \\ Q \end{matrix}$
Average Power
Active Power
(Watt)

$\begin{matrix} Q \\ \text{Reactive Power} \end{matrix}$
(VAR)

$$S = -200 + j 346,4 \text{ VA} \quad \text{Complex Power}$$

$$P = -200 \text{ Watts} \quad \text{Average Power (Active Power)}$$

$$Q = 346,4 \text{ VAR} \quad (\text{Reactive Power} - (\text{Inductive}))$$

$$|S| = 400 \text{ VA} \quad (\text{Apparent Power})$$


$$\text{power factor} \rightarrow \theta_u - \theta_i = \theta_i - \theta_u = 120^\circ$$

$$\cos 120^\circ = 0.5 \text{ lagging}$$

Additional Power Relationships

Impedance is z

$$z = |z| \angle \theta = R + jX$$

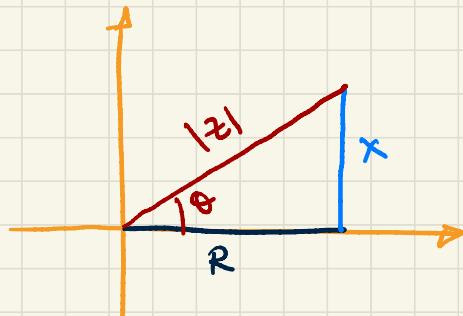

$$\cos \theta = \frac{R}{|z|}$$

$$\sin \theta = \frac{X}{|z|}$$

$$P = \frac{V_m \cdot I_m \cos \theta}{2} = \frac{V_m I_m}{2} \cdot \frac{R}{|z|}$$


$$I_m = \frac{V_m}{|z|} \quad P = \frac{I_m^2}{2} \cdot R = I_{rms}^2 \cdot R$$

$$Q = \frac{I_m^2}{2} \cdot X = I_{rms}^2 \cdot X = \frac{V_{rms}^2}{X}$$


$$S = V_{rms} I_{rms} \cdot \cos \phi + j V_{rms} I_{rms} \cdot \sin \phi$$

$$P = |S| \cdot \cos \phi \quad \cos \phi = \frac{P}{|S|}$$

$$\text{PF} = \frac{P}{|S|} = \cos \phi$$

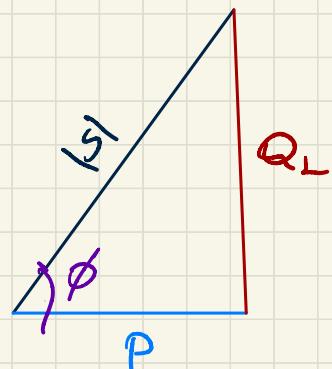

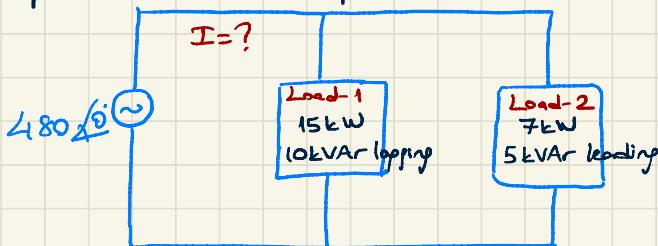Ex: Two parallel loads draw from a 480 V (rms) source as shown below, where Load-1 draws 15 kW and 10 kVar lagging, and Load-2 draws 7 kW and 5 kVar leading. Determine the combined power factor and total apparent power drawn from the source.



b) $I = ?$

$$S_1 \rightarrow \text{inductive } + j L + V \text{ A}$$

$S_2 \rightarrow \text{capacitive } (c) -$

Solution:

$$S_1 = 15 + j 10 \text{ kVA}$$

$$S_2 = 7 - j 5 \text{ kVA}$$


$$+$$

$$S_T = 22 + j 5 \text{ kVA (lagging)}$$

$$(S_T = \sqrt{22^2 + 5^2}) = 22.56 \text{ kVA}$$

↳ Apparent Power

$$\arctg \frac{5}{22} = 12.8^\circ$$

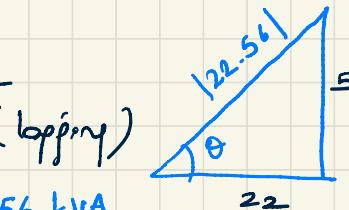

$$S = |22.56| \angle 12.8^\circ \text{ kVA}$$

$$PF = \cos(12.8) = 0.975 \text{ (lagging)} (L)$$


b) $S = V_{\text{rms}} \cdot I_{\text{rms}}^*$

$$22.56 \angle 12.8^\circ = 480 \angle 0^\circ \cdot I_{\text{rms}}^* \quad I_{\text{rms}}^* = \frac{22.56 \angle 12.8^\circ}{480 \angle 0^\circ}$$

$$I_{\text{rms}}^* = 0.047 \angle 12.8^\circ$$

$$I_{\text{rms}} = 0.047 \angle -12.8^\circ \text{ kA}$$

Ex:

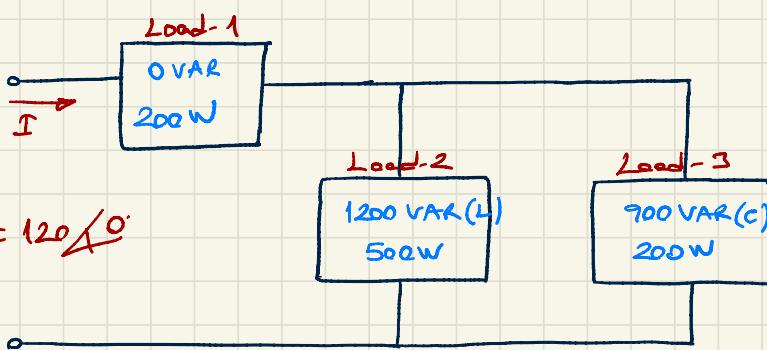

Find the total number of Average Power, Apparent Power, Reactive Power, and Power factor of the system.

Find $I = ?$

<u>Loads</u>	<u>W</u>	<u>VAR</u>	<u>VA</u>
1	200 W	0 VAR	$\sqrt{200^2 + 0^2} = 200 \text{ VA}$
2	500 W	1200 VAR(L)	$\sqrt{500^2 + 1200^2} = 1300 \text{ VA}$
3	200 W	900 VAR(C)	$\sqrt{200^2 + 900^2} \approx 922 \text{ VA}$
<u>+ Total</u>	<u>900 W</u>	<u>300 VAR(L)</u>	<u>$\sqrt{900^2 + 300^2} = 948.68 \text{ VA}$</u>

$$\text{Total Average Power} = 900 \text{ W}$$

$$\text{Total Reactive Power} = 300 \text{ VAR(L)}$$

$$\text{Total Apparent Power} = 948.68 \text{ VA}$$

$$S_T = 948.68 \text{ VA}$$

$$\cos \theta = \frac{P}{S} = \frac{900}{948.68}$$

$$\cos \theta = 0.94 \text{ (L)}$$

$$E = 120 \angle 0^\circ$$

$$S_T = 948.68$$

$$I = \frac{948.68}{120} = 7.9 \text{ A}$$

$$\theta = ? \quad \arccos(0.94) = 19.94^\circ \text{ (Inductive)} \rightarrow$$

$$120 \angle 0^\circ \\ 7.9 \angle 19.94^\circ$$


$$I = 7.9 \text{ A} \quad 7.9 \angle 19.94^\circ \text{ A}$$

$$S = V_{rms} \cdot I_{rms}$$

$$948.68 \angle 19.94^\circ = 120 \angle 0^\circ \cdot I_{rms}$$

$$I_{rms} = 7.9 \angle 19.94^\circ$$

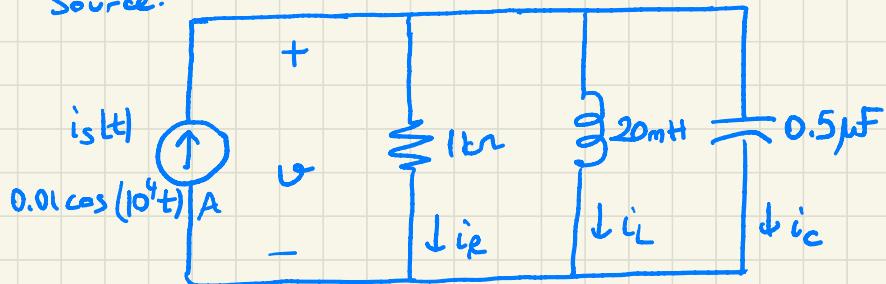Ex: Consider the circuit shown in figure. find the phasors I_S , V , I_R , I_L and I_C . Find the Apparent power for the source.



Solution:

$$i_s(t) = 10 \sin(10^4 t + 90^\circ) \text{ mA} \quad \omega = 10^4$$

$$I_S = \frac{10}{\sqrt{2}} \angle 90^\circ = 7.07 \angle 90^\circ \text{ mA}$$

$$Z_1 = 1000 \Omega$$

$$X_L = \omega L = 10^4 \cdot 20 \cdot 10^{-3} = 200 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{10^4 \cdot 0.5 \times 10^{-6}} = 200 \Omega$$

$$V = I \cdot R \Rightarrow V = 7.07 \angle 90^\circ \cdot 1000 = 7.07 \angle 90^\circ \text{ V}$$

$$I_L = \frac{7.07 \angle 90^\circ}{200 \angle 90^\circ} = 0.035 \angle 0^\circ \text{ A}$$

$$I_C = \frac{7.07 \angle 90^\circ}{200 \angle 90^\circ} = 0.035 \angle 180^\circ \text{ A}$$

$$S = V_{rms} \cdot I_{rms}^*$$

$$= 7.07 \angle 90^\circ \cdot 7.07 \angle 90^\circ \text{ mA}$$

$$S = 49.98 \angle 0^\circ \text{ mVA}$$

