

# BME2322 – Logic Design

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN


[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/nakkan>

# **LECTURE 4**
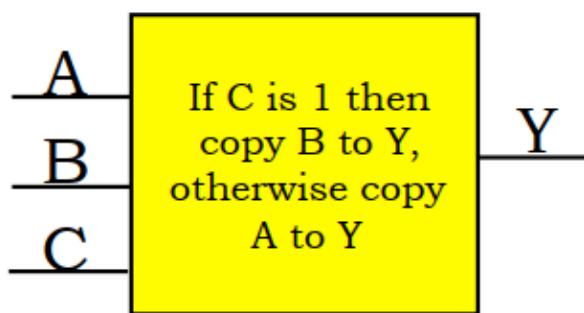
# Functional Specifications



There are many ways of specifying the function of a combinational device, for example:



unless the words are very carefully crafted, there may be ambiguities introduced by words with multiple interpretations or by lack of completeness
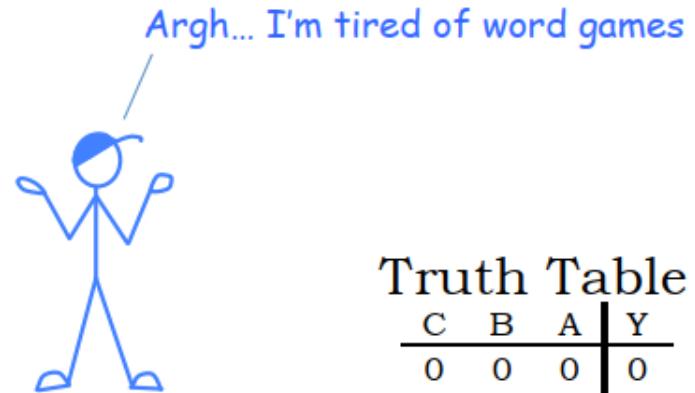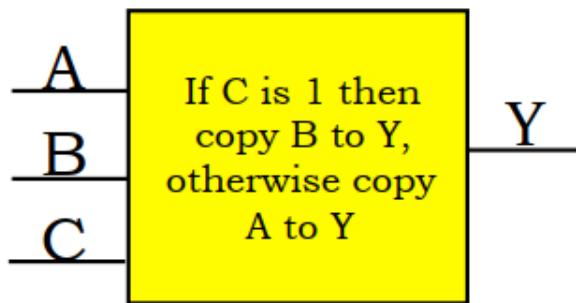
# Functional Specifications

There are many ways of specifying the function of a combinational device, for example:



Concise alternatives:

- *truth tables* are a concise description of the combinational system's function.
- *Boolean expressions* form an algebra whose operations are AND (multiplication), OR (addition), and inversion (overbar).

Truth Table			
C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Y = \bar{C} \cdot \bar{B} \cdot A + \bar{C}BA + CBA + CBA$$

Any combinational (Boolean) function can be specified as a truth table or an equivalent sum-of-products Boolean expression!

# Boolean Algebra

A **Boolean algebra**  $B$  is a finite set over which two binary operations  $+$  (sum) and  $\cdot$  (product) and satisfy five postulates.

# Boolean Algebra Postulates

P 1 - Operations + and · are internal:  $\forall a, b \in B, a + b \in B \text{ y } a \cdot b \in B$

P 2 – To each operation corresponds a **neutral element**:  $\forall a \in B, a + 0 = a, a \cdot 1 = a$

P 3 – To each element corresponds an **inverse element**:  $\forall a \in B, \exists \bar{a} \in B \mid a + \bar{a} = 1, a \cdot \bar{a} = 0$


P 4 – Operations + and · are **commutative**:  $a + b = b + a, a \cdot b = b \cdot a$

P 5 –Operations + and · are **distributive**:  $a \cdot (b + c) = a \cdot b + a \cdot c, a + b \cdot c = (a + b) \cdot (a + c)$

# Boolean Algebra

The set  $\{0, 1\}$  is a Boolean algebra if the operations are defined as follows:

$a \ b$	$a \cdot b$	$a + b$	$\bar{a}$
0 0	0	0	1
0 1	0	1	1
1 0	0	1	0
1 1	1	1	0

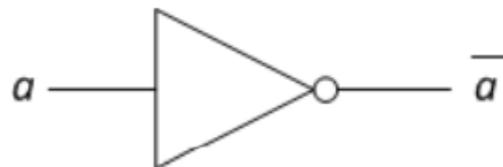

# Boolean Algebra (distributive rule)

Example: check that  $a \cdot (b+c) = a \cdot b + a \cdot c$


$a\ b$	$a \cdot b$	$a + b$	$\bar{a}$
00	0	0	1
01	0	1	1
10	0	1	0
11	1	1	0

$a\ b\ c$	$b+c$	$a \cdot (b+c)$	$a \cdot b$	$a \cdot c$	$a \cdot b + a \cdot c$
000	0	0	0	0	0
001	1	0	0	0	0
010	1	0	0	0	0
011	1	0	0	0	0
100	0	0	0	0	0
101	1	1	0	1	1
110	1	1	1	0	1
111	1	1	1	1	1

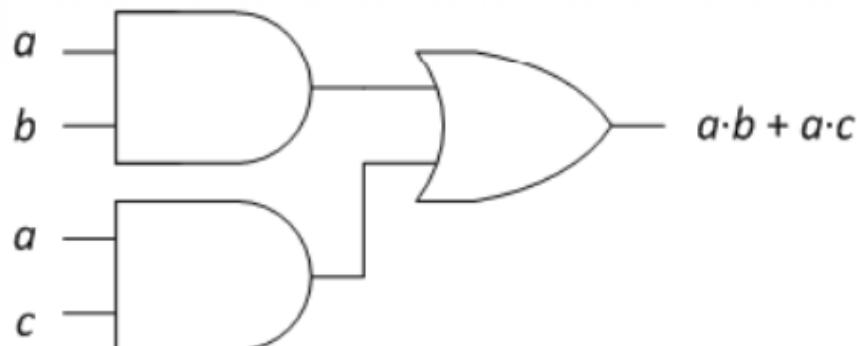
# Boolean Algebra (distributive rule)

Comment:

$$a \cdot (b+c) = a \cdot b + a \cdot c \Rightarrow$$



|||

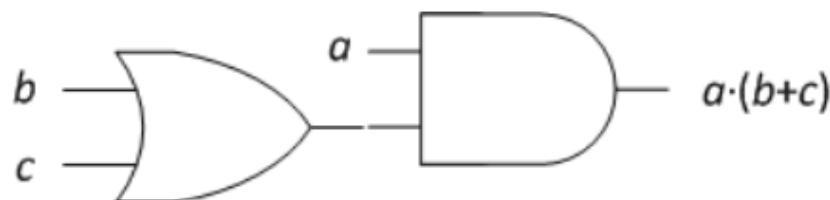

# Some useful properties

1 – Neutral element properties:  $\bar{0} = 1$ ,  $\bar{1} = 0$

2 – Idempotence:  $a + a = a$ ,  $a \cdot a = a$

$$\begin{aligned} a &= a + 0 = a + (a \cdot \bar{a}) = (a + a) \cdot (a + \bar{a}) = \\ &(a + a) \cdot 1 = a + a \end{aligned}$$

P1 -  $\forall a, b \in B, a + b \in B \text{ y } a \cdot b \in B$

P2 -  $\forall a \in B, a + 0 = a, a \cdot 1 = a$

P3 -  $\forall a \in B, \exists \bar{a} \in B \mid a + \bar{a} = 1, a \cdot \bar{a} = 0$

P4 -  $a + b = b + a, a \cdot b = b \cdot a$

P5 -  $a \cdot (b + c) = a \cdot b + a \cdot c, a + b \cdot c = (a + b) \cdot (a + c)$

# Some useful properties - Exercise

Demonstrate that  $a \cdot a = a$

*Hint: Use the second part of P2, P3 and P5.*

$$P1 - \forall a, b \in B, a + b \in B \text{ y } a \cdot b \in B$$

$$P2 - \forall a \in B, a + 0 = a, a \cdot 1 = a$$

$$P3 - \forall a \in B, \exists \bar{a} \in B \mid a + \bar{a} = 1, a \cdot \bar{a} = 0$$

$$P4 - a + b = b + a, a \cdot b = b \cdot a$$

$$P5 - a \cdot (b + c) = a \cdot b + a \cdot c, a + b \cdot c = (a + b) \cdot (a + c)$$

# Some useful properties - Exercise

Demonstrate that  $a \cdot a = a$

*Hint: Use the second part of P2, P3 and P5.*

$$\begin{aligned} a &= a \cdot 1 = a \cdot (a + \bar{a}) = (a \cdot a) + (a \cdot \bar{a}) = \\ &(a \cdot a) + 0 = a \cdot a \end{aligned}$$

$$\begin{aligned} a &= a + 0 = a + (a \cdot \bar{a}) = (a + a) \cdot (a + \bar{a}) = \\ &(a + a) \cdot 1 = a + a \end{aligned}$$

P1 -  $\forall a, b \in B, a + b \in B \text{ y } a \cdot b \in B$

P2 -  $\forall a \in B, a + 0 = a, a \cdot 1 = a$

P3 -  $\forall a \in B, \exists \bar{a} \in B \mid a + \bar{a} = 1, a \cdot \bar{a} = 0$

P4 -  $a + b = b + a, a \cdot b = b \cdot a$

P5 -  $a \cdot (b + c) = a \cdot b + a \cdot c, a + b \cdot c = (a + b) \cdot (a + c)$

# Some useful properties

1 – Neutral element properties:  $\bar{0} = 1$ ,  $\bar{1} = 0$

2 – Idempotence:  $a + a = a$ ,  $a \cdot a = a$

3 – Involution:  $\bar{\bar{a}} = a$

4 – Asociativity:  $a + (b + c) = (a + b) + c$ ,  $a \cdot (b \cdot c) = (a \cdot b) \cdot c$

5 – Absortion law:  $a + a \cdot b = a$ ,  $a \cdot (a + b) = a$

6 - (nameless):  $a + \bar{a} \cdot b = a + b$ ,  $a \cdot (\bar{a} + b) = a \cdot b$

7 - de Morgan law:  $(\overline{a + b}) = \bar{a} \cdot \bar{b}$ ,  $\overline{a \cdot b} = \bar{a} + \bar{b}$

8 – generalized de Morgan law:  $(\overline{a_1 + a_2 + \dots + a_n}) = \bar{a}_1 \cdot \bar{a}_2 \cdot \dots \cdot \bar{a}_n$ ,  $\overline{a_1 \cdot a_2 \cdot \dots \cdot a_n} = \bar{a}_1 + \bar{a}_2 + \dots + \bar{a}_n$

# Boolean functions and truth tables

Any Boolean function can be explicitly defined by a truth table

$$f(a,b,c) = b \cdot \bar{c} + \bar{a} \cdot b$$

$a$	$b$	$c$	$\bar{c}$	$b \cdot \bar{c}$	$\bar{a}$	$\bar{a} \cdot b$	$f$
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	0
0	1	0	1	1	1	1	1
0	1	1	0	0	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	1	0	0	0
1	1	0	1	0	0	0	1
1	1	1	0	0	0	0	0

# Boolean functions and truth tables

Given a truth table can we find an equivalent Boolean function?...

Answer is YES

## LITERAL

A variable or an inverted variable :  $a, \bar{a}, b, \bar{b}, c, \bar{c}, \dots$

## $n$ -variable MINTERM

A product of  $n$  literals such that each variable appears only once. Example: if  $n=3$ , there are eight *minterms*.

$$a.b.c, a.b.\bar{c}, a.\bar{b}.c, a.\bar{b}.\bar{c}, \bar{a}.b.c, \bar{a}.b.\bar{c}, \bar{a}.\bar{b}.c, \bar{a}.\bar{b}.\bar{c}$$

# Boolean functions and truth tables

Given a **MINTERM**  $m$ , there is one, an only one, set of variable values such that  $m = 1$ .

With  $n = 3$ :

	$a$	$b$	$c$	
$\bar{a}.\bar{b}.\bar{c} = 1$	$\Leftrightarrow$	0	0	0
$\bar{a}.\bar{b}.c = 1$	$\Leftrightarrow$	0	0	1
$\bar{a}.b.\bar{c} = 1$	$\Leftrightarrow$	0	1	0
$a.b.c = 1$	$\Leftrightarrow$	0	1	1
$a.\bar{b}.\bar{c} = 1$	$\Leftrightarrow$	1	0	0
$a.\bar{b}.c = 1$	$\Leftrightarrow$	1	0	1
$a.b.\bar{c} = 1$	$\Leftrightarrow$	1	1	0
$a.b.c = 1$	$\Leftrightarrow$	1	1	1

# From Truth Table to Boolean Function

**MINTERMS** of an  $n$ -variable Boolean function  $f$  ?

= *minterms* that correspond to the 1s of  $f$ .

$a$	$b$	$c$	$f(a,b,c)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

# From Truth Table to Boolean Function

Canonical sum of products representation of an  $n$ -variable Boolean function.

Any Boolean function can be represented by the sum of its *minterm*.

$$f(a,b,c) = \Sigma(m_2, m_3, m_6)$$

$$f(a,b,c) = \bar{a} \cdot b \cdot \bar{c} + \bar{a} \cdot b \cdot c + a \cdot b \cdot \bar{c}$$


$a$	$b$	$c$	$f(a,b,c)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$\rightarrow m_2 = \bar{a} \cdot b \cdot \bar{c}$   
 $\rightarrow m_3 = \bar{a} \cdot b \cdot c$   
 $\rightarrow m_6 = a \cdot b \cdot \bar{c}$

# From Truth Table to Boolean Function

```
if ((a=1 and b=1 and c=0) or (a=0 and b=1)) then f=1;  
else f=0;  
end if;
```

$a$	$b$	$c$	$f(a,b,c)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0



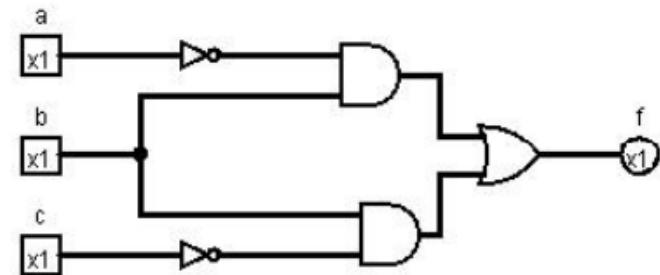


$$\begin{aligned}f(a,b,c) &= \bar{a} \cdot \bar{b} \cdot \bar{c} + \bar{a} \cdot b \cdot c + a \cdot b \cdot \bar{c} = \\&= \bar{a} \cdot b (\bar{c} + c) + b \cdot \bar{c} (\bar{a} + a) = \bar{a} \cdot b + b \cdot \bar{c}\end{aligned}$$


$$f(a,b,c) = \Sigma(m_2, m_3, m_6)$$

$$f(a,b,c) = \bar{a} \cdot \bar{b} \cdot \bar{c} + \bar{a} \cdot b \cdot c + a \cdot b \cdot \bar{c}$$

# Example: 4 bit-adder

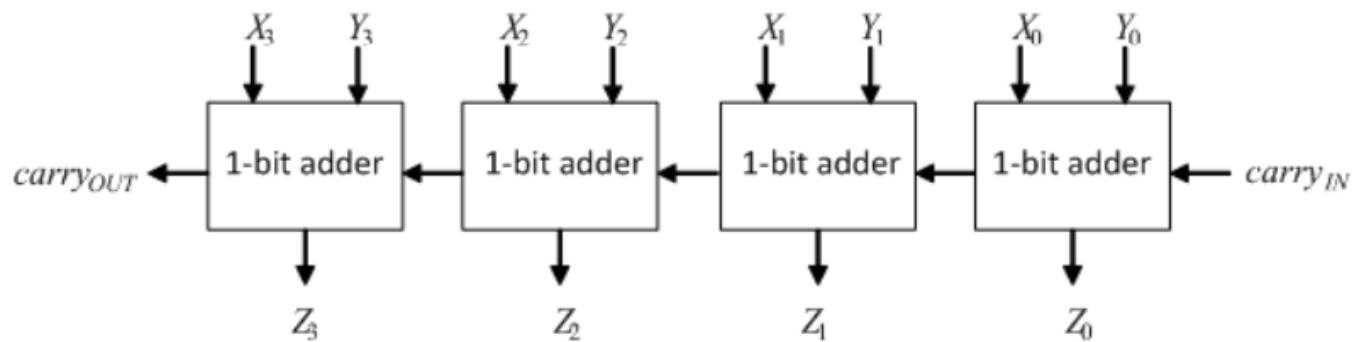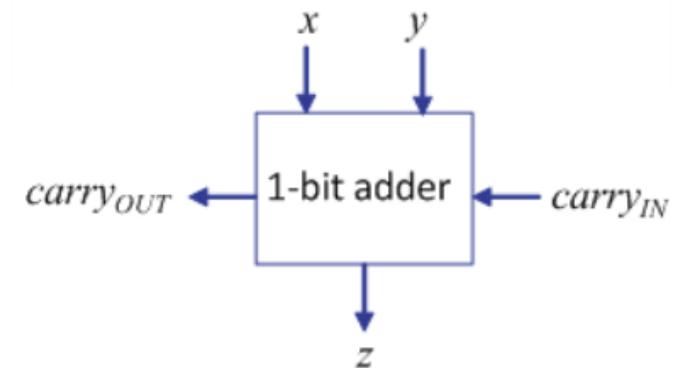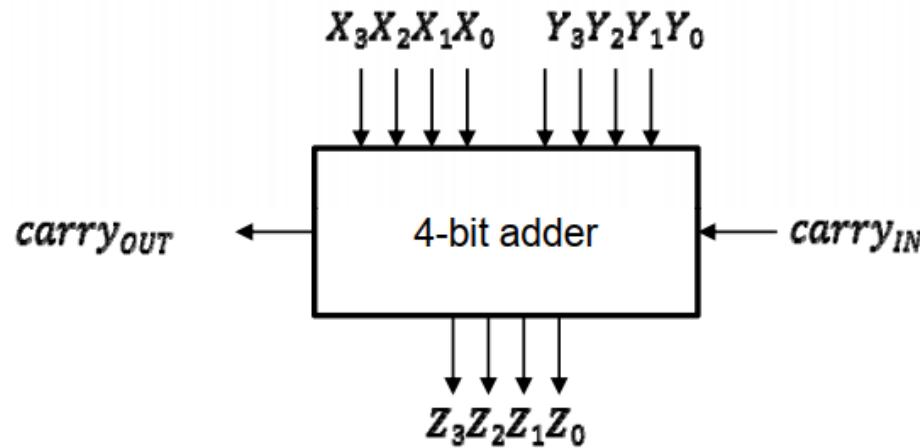

# Example: 4 bit-adder

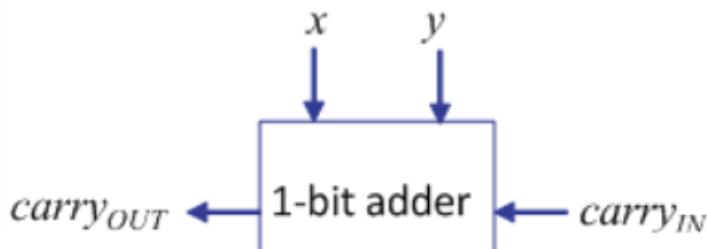

$x$	$y$	$c_i$	$c_o$	$z$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$c_0 = \overline{x}y c_i + x\overline{y} c_i + xy\overline{c}_i + xy c_i$$



$\downarrow$        $\downarrow$

$$\underbrace{(\overline{x}+x)y c_i}_{y c_i + x c_i + xy} + xy$$
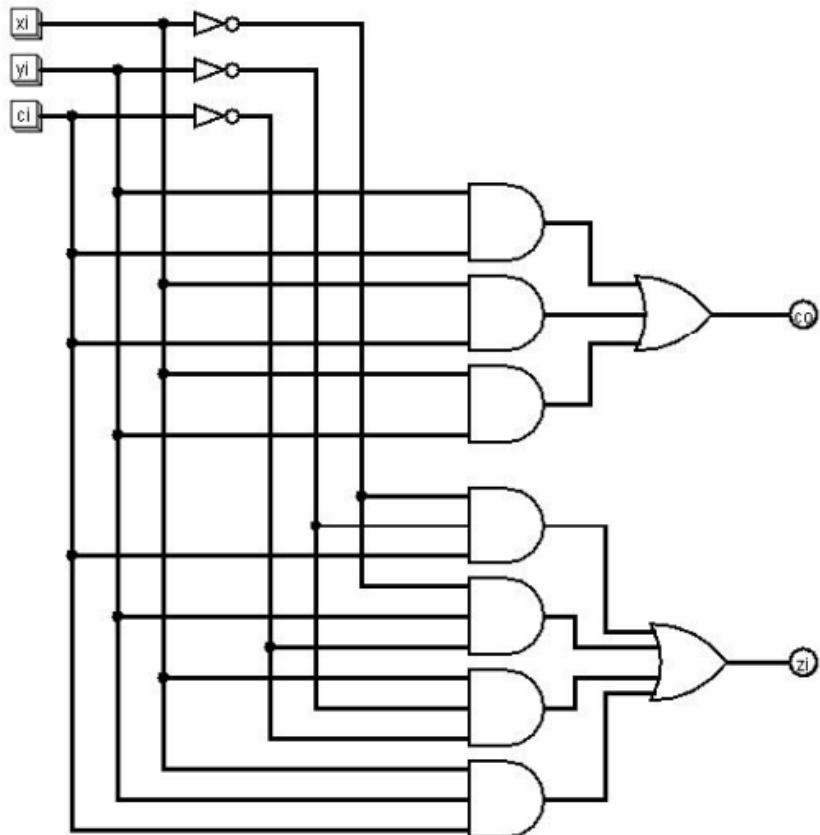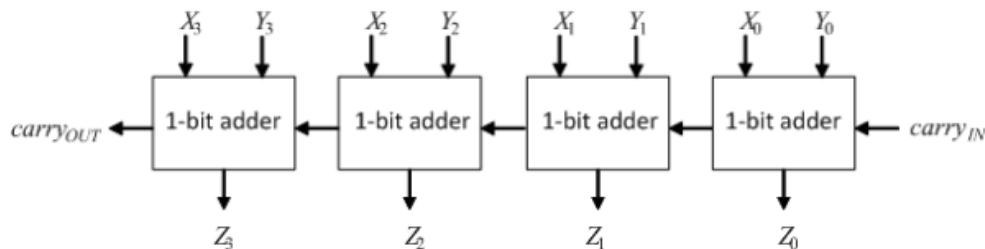
# Example: 4 bit-adder

$$c_o = y \cdot c_i + x \cdot c_i + x \cdot y$$



$$z = \bar{x} \cdot \bar{y} \cdot c_i + \bar{x} \cdot y \cdot \bar{c}_i + x \cdot \bar{y} \cdot \bar{c}_i + x \cdot y \cdot c_i$$



Circuit generation from a functional description:

(functional description  $\rightarrow$  truth table  $\rightarrow$  Boolean function(s)  $\rightarrow$  circuit)

# NAND – NOR Gates

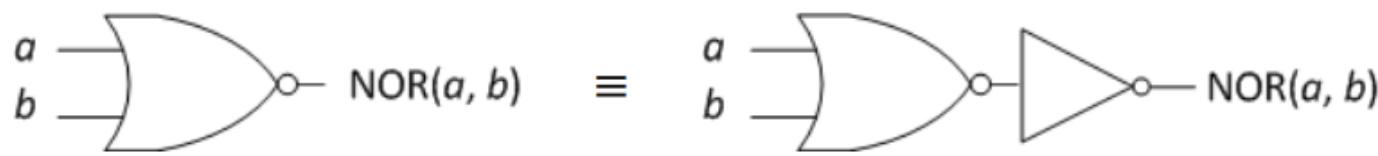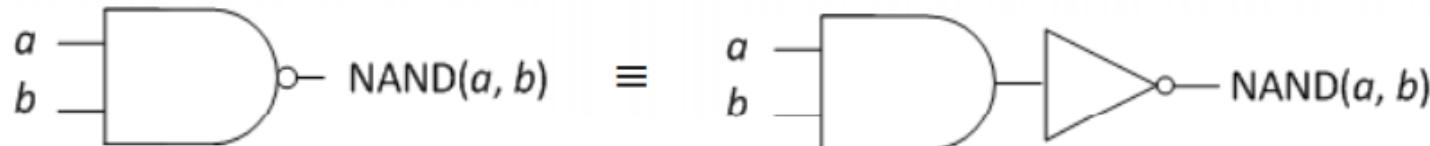

$a$ $b$	$\text{NAND}(a, b)$	$\text{NOR}(a, b)$
0 0	1	1
0 1	1	0
1 0	1	0
1 1	0	0


**Algebraic symbols:**

$$\text{NAND}(a, b) = a \uparrow b,$$


$$\text{NOR}(a, b) = a \downarrow b.$$
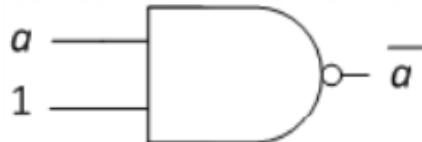
# NAND – NOR Gates


NAND and NOR gates are **universal modules**. For example, with NAND gates:



$\equiv$

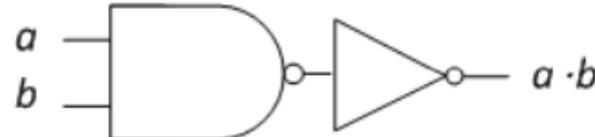

$\equiv$

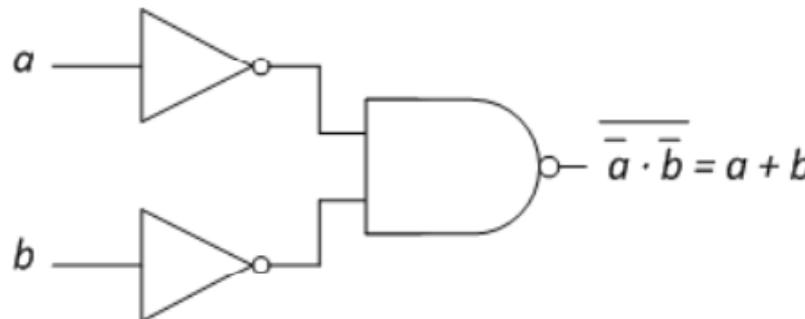


$\equiv$



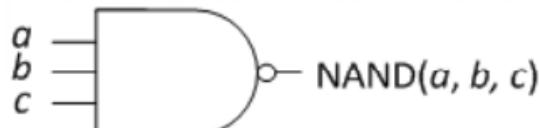
# NAND – NOR Gates

3-input, 4-input, ... NAND and NOR gates can be defined:



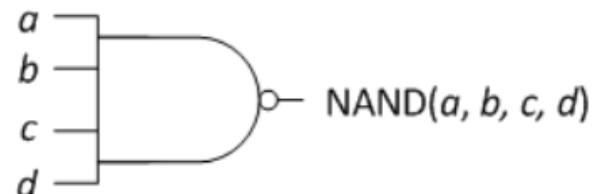
$$\text{NAND}(a, b, c) = 0 \text{ iff } a = b = c = 1$$




$$\text{NAND}(a, b, c, d) = 0 \text{ iff } a = b = c = d = 1$$

.....

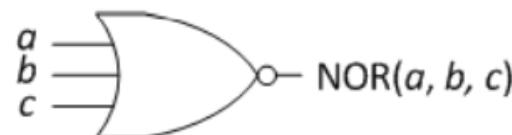

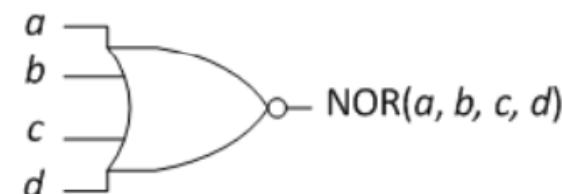
$$\text{NOR}(a, b, c) = 0 \text{ iff } (a = 1) \text{ OR } (b = 1) \text{ OR } (c = 1)$$




$$\text{NOR}(a, b, c, d) = 0 \text{ iff } (a = 1) \text{ OR } (b = 1) \text{ OR } (c = 1) \text{ OR } (d = 1)$$
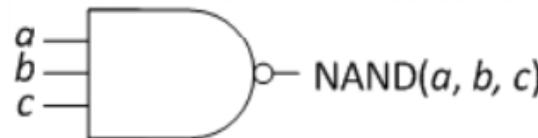
# NAND – NOR Gates

BUT NAND and NOR are not associative operations. In particular:




$\neq$

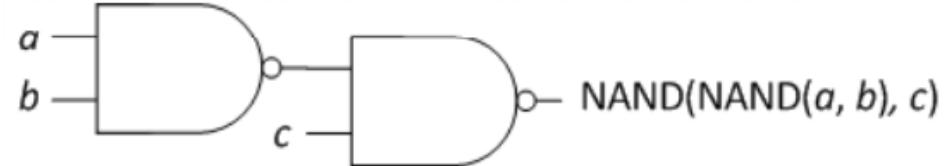


$$\text{NAND}(1, 1, 1) = 0$$
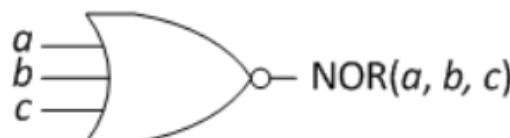
$$\text{NAND}(\text{NAND}(1, 1), 1) = \text{NAND}(0, 1) = 1$$



$\neq$

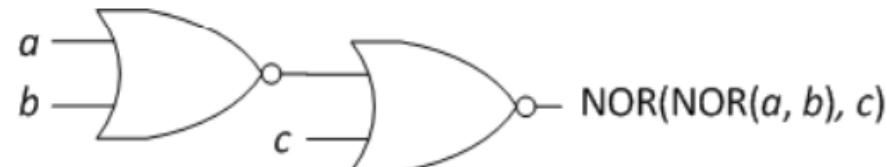

$$\text{NOR}(0, 0, 0) = 1$$


$$\text{NOR}(\text{NOR}(0, 0), 0) = \text{NOR}(1, 0) = 0$$

# Why NAND (or NOR) Gates?


**Why** do we use NAND gates ( or NOR gates) instead of AND and OR gates?

- If we use “of the shelf” components (laboratory) we only need one type of gate.
- In CMOS technology

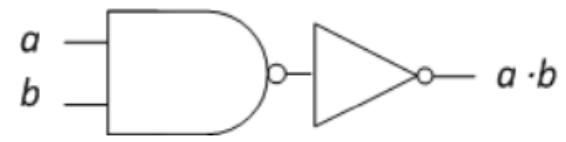- an AND gate is implemented with a NAND and an INV,





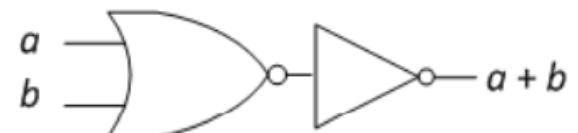- an OR gate is implemented with a NOR and an INV.



=> Within an IC (Integrated Circuit) NAND and NOR are “cheaper” than AND and OR.

# XOR – XNOR Gates

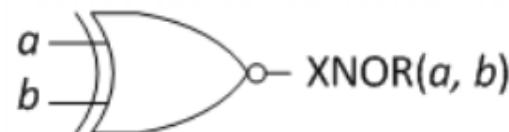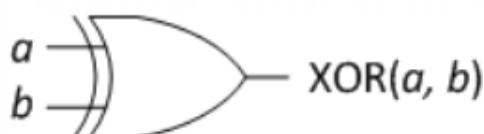

$a$	$b$	$\text{XOR}(a,b)$	$\text{XNOR}(a,b)$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

**XOR** (= eXclusive OR):  $\text{XOR}(a, b) = 1$  if  $a \neq b$ ;

**XNOR** (= eXclusive NOR):  $\text{XNOR}(a, b) = 1$  if  $a = b$ .

**Algebraic symbols:**

$$\text{XOR}(a, b) = a \oplus b,$$

$$(\text{XNOR}(a, b) = a \equiv b)$$

# XOR – XNOR Gates

Equivalent definition:

$$\text{XOR}(a, b) = (a + b) \bmod 2 = a \oplus b,$$

$$\text{XNOR}(a, b) = \text{INV}(a \oplus b).$$

=> 3-input, 4-input, ... XOR and XNOR gates can be defined:

$$\text{XOR}(a, b, c) = (a + b + c) \bmod 2 = a \oplus b \oplus c, \quad \text{XNOR}(a, b, c) = \text{INV}(a \oplus b \oplus c),$$

$$\text{XOR}(a, b, c, d) = (a + b + c + d) \bmod 2 = a \oplus b \oplus c \oplus d, \quad \text{XNOR}(a, b, c, d) = \text{INV}(a \oplus b \oplus c \oplus d),$$

...

XOR is an associative operation =>




# XOR – XNOR Gates

- XOR y NXOR are **not universal modules**,
- **useful functions.**

First example: magnitud comparator. Given two 4-input vectors  $a = a_3 a_2 a_1 a_0$  and  $b = b_3 b_2 b_1 b_0$ , generate  $comp = 1$  iff  $a = b$ .
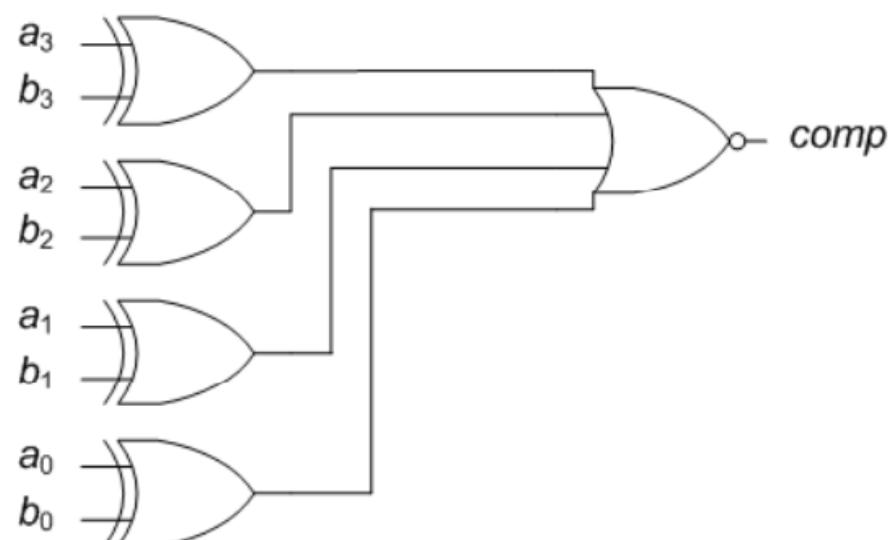
## Algorithm

```
if ( $a_3 \neq b_3$ ) or ( $a_2 \neq b_2$ ) or ( $a_1 \neq b_1$ ) or ( $a_0 \neq b_0$ )
then  $comp \leq 0$ ;
else  $comp \leq 1$ ;
end if;
```



# Summary

