

BUCK AND BOOST EXAMPLES

1.


A Buck converter operates at frequency of 2000 Hz from 200 V d.c supply. It supplies to a 5 Ω resistor. For output voltage of 100V, Find out ;

- The duty cycle (D , λ , conductance ratio)
- T_{on}
- The average value of output current
- I_T
- I_D
- For continuous current control L_{critic}

$$a) V_o = D \cdot V_g$$

$$D = \frac{V_o}{V_g} = \frac{100}{200}$$

$$D = \frac{1}{2}$$

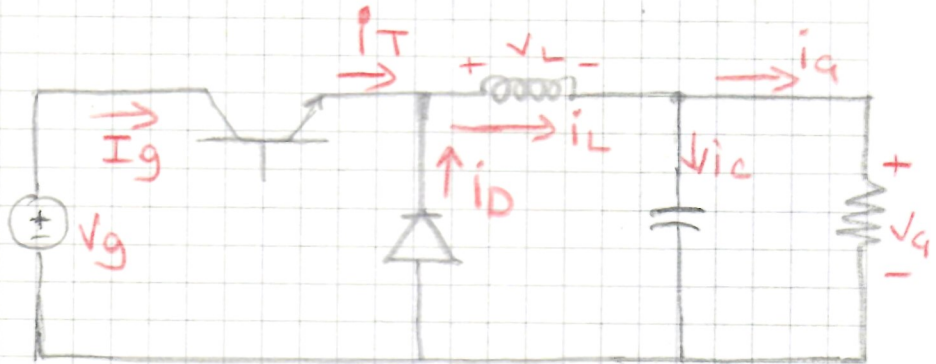

$$b) T = \frac{1}{f} = \frac{1}{2000} = 0.5 \text{ ms}$$

$$T_{on} = D \cdot T = \frac{1}{2} \cdot 0.5 \text{ ms} = 0.25 \text{ ms}$$

$$c) I_o = \frac{100}{5} = 20 \text{ A}$$

$$d) D = \frac{T_{on}}{T} = \frac{I_T}{I_L} \quad \text{and} \quad -i_T - i_D + i_L \Rightarrow$$

$$i_L = i_T + i_D$$

$$I_L = I_o = 20 \text{ A}$$

$$\frac{1}{2} = \frac{I_T}{I_L} \Rightarrow I_T = 10 \text{ A}$$

$$e) I_D = 20 - 10 = 10 \text{ A}$$

$$f) L_{critic} = \frac{(1 - \frac{1}{2}) \cdot 5 \cdot 0.5 \cdot 10^{-3}}{2} = \frac{(1 - D) \cdot R \cdot T}{2} = 625 \mu\text{H}$$

2.

A Buck converter has $V_g = 15$, $V_a = 5V$, $I_a = 5A$
 $f = 100 \text{ kHz}$, Find out;

- a) L value for Boundary Current Mode
- b) I_L
- c) I_D
- d) Peak value of Transistor voltage.

$$a) \quad L_{critic} = \frac{(1-D) R \cdot T}{2}$$

$$R = \frac{V_a}{I_a} = 1 \Omega$$

$$D = \frac{V_a}{V_g} = \frac{5}{15} = 0.33$$

$$T = \frac{1}{100 \cdot 10^3} = 10 \mu s$$

$$T_{on} = 3.3 \mu s$$

$$L_{critic} = \frac{(1 - 0.33) \cdot 1 \cdot 10 \cdot 10^{-6}}{2} = 3.3 \mu H$$

$$b) \quad I_L = \frac{V_g}{R} = \frac{5}{1} = 5A = I_a$$

$$c) \quad D = \frac{I_T}{I_L} = 0.33 = \frac{I_T}{5} \Rightarrow I_T = 1.65 A$$

$$d) \quad V_T = V_g = 15 V$$

3.

For a boost converter $V_g = 100V$, $V_q = 200V$
 $f = 100kHz$ and $P_q = 1kW$ What is the L value for
 BCM operation? If the output power is reduced to
 100W while the same output maintains as 200V,
 what about the operation mode of the boost
 converter?

$$\frac{V_q}{V_g} = \frac{1}{1-D} \text{ for boost converter}$$

$$\frac{200}{100} = \frac{1}{1-D}$$

$$D = 0.5$$

$$P_q = 1 \cdot 10^3 = \frac{V_q^2}{R} = \frac{200^2}{R}$$

$$R = 40 \Omega$$

$$T = \frac{1}{100 \cdot 10^3} = 10 \mu s \quad I_q = \frac{200}{40} = 5A$$

$$L_{critic} = \frac{(1-D)^2 \cdot D \cdot R \cdot T}{2} = \frac{(1-0.5)^2 \cdot 0.5 \cdot 40 \cdot 10 \cdot 10^{-6}}{2}$$

$$L_{critic} = 50 \mu H$$


$$I_L = I_g = \frac{I_q}{1-D} = 10A$$

For new power value

$$P_q = 100 = \frac{V_q^2}{R} = \frac{200^2}{R} \Rightarrow R = 400 \Omega$$

$$I_q = \frac{200}{400} = 0.5A \quad I_L = I_g = \frac{1}{1-D} \cdot I_q = \frac{0.5}{1-0.5} = 1A$$

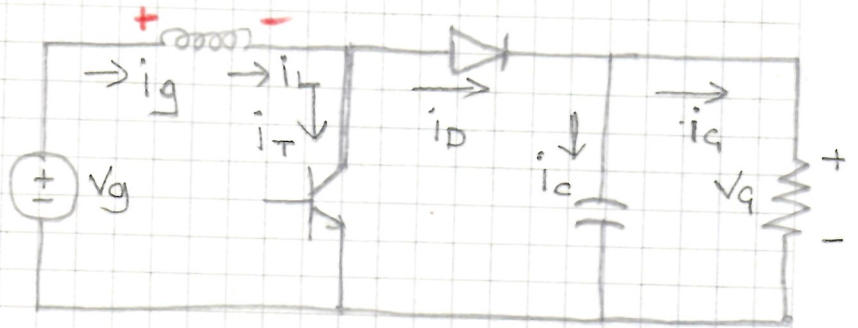Since the inductor current is lower than
 the one with BCM, the converter operates at
 discontinuous operation mode



4.

In a boost converter, the inductance current has $\Delta i_L = 2A$. It is operated in dc steady state under the following conditions: $V_g = 5V$, $V_q = 12V$, $P_q = 11W$ and $f = 200 \text{ kHz}$. (Load is pure resistive)

- Calculate L value
- Find out I_g and I_q values

$$\frac{V_q}{V_g} = \frac{12}{5} = \frac{1}{1-D} \Rightarrow D = 0.583$$

$$P_q = \frac{V_q^2}{R} \Rightarrow R = \frac{144}{11} = 13.1 \Omega$$

$$L \cdot \frac{di}{dt} = V_L = V_g \text{ for } \underline{\text{on state.}}$$

$$\frac{\Delta i_L}{T_{on}} = \frac{V_g}{L} \Rightarrow \Delta i_L = \frac{V_g \cdot D \cdot T}{L} \Rightarrow$$

$$T = \frac{1}{f} = \frac{1}{200 \cdot 10^3} = 5 \mu s \quad L = \frac{5 \cdot 0.583 \cdot 5 \cdot 10^{-6}}{2}$$

$$L = 7.29 \mu H$$

$$I_q = \frac{V_q}{R} = \frac{12}{13.1} = 0.91 A$$

$$I_g = \frac{1}{1-D} \cdot I_q = 0.91 \cdot \frac{1}{1-0.583} = 2.19 A$$