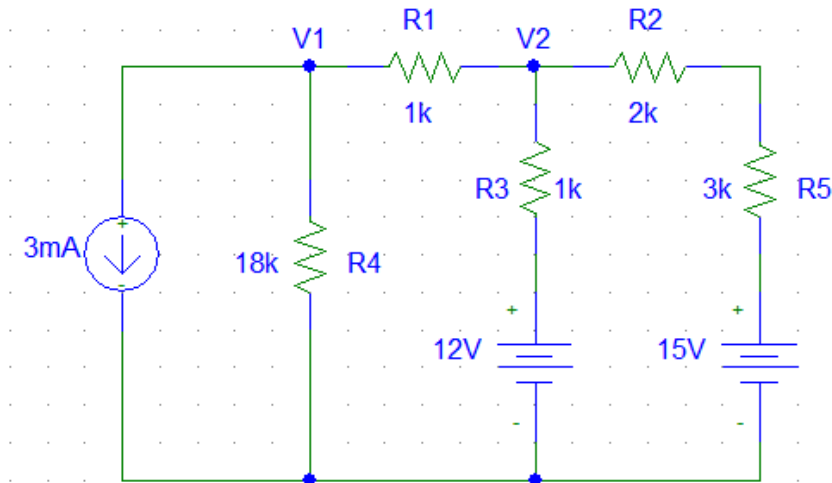


Düğüm Metodu ile çözüm



$$0,003 + \frac{V_1}{18000} + \frac{V_1 - V_2}{1000} = 0$$

$$\frac{V_2 - V_1}{1000} + \frac{V_2 - 12}{1000} + \frac{V_2 - 15}{2000 + 3000} = 0$$

$$V_1 \left[\frac{1}{18000} + \frac{1}{1000} \right] - \frac{V_2}{1000} = -\frac{3}{1000}$$

$$-V_1 \left[\frac{1}{1000} \right] + V_2 \left[\frac{1}{1000} + \frac{1}{1000} + \frac{1}{5000} \right] = \frac{12}{1000} + \frac{15}{5000}$$

$$V_1 \left[\frac{1}{18000} + \frac{1}{1000} \right] - \frac{V_2}{1000} = -\frac{3}{1000}$$

$$\left[\frac{1}{18} + \frac{1}{10} \right] V_1 - \frac{V_2}{10} = -\frac{3}{10}$$

$$-V_1 \left[\frac{1}{1000} \right] + V_2 \left[\frac{1}{1000} + \frac{1}{1000} + \frac{1}{5000} \right] = \frac{12}{1000} + \frac{15}{5000}$$

$$-\frac{V_1}{10} + V_2 \left[\frac{1}{10} + \frac{1}{10} + \frac{1}{50} \right] = \frac{12}{1000} + \frac{15}{5000}$$

$$(1 + 18).V_1 - 18.V_2 = -54$$

$$-18.V_1 + (18 + 18 + 3,6).V_2 = 216 + 54$$

$$19.V_1 - 18.V_2 = -54$$

$$-18.V_1 + 39,6.V_2 = 270$$

$$V_1 = \frac{\begin{vmatrix} -54 & -18 \\ 270 & 39,6 \\ 19 & -18 \\ -18 & 39,6 \end{vmatrix}}{\begin{vmatrix} 19 & -18 \\ -18 & 39,6 \end{vmatrix}} = \frac{(-54 \times 39,6) - (270 \times (-18))}{19 \times 39,6 - (-18) \cdot (-18)} = \frac{2138,4 + 4860}{752,4 - 324} = \frac{6998,4}{428,4} = 16,33613445V$$

$$V_2 = \frac{\begin{vmatrix} 19 & -54 \\ -18 & 270 \\ 19 & -18 \\ -18 & 39,6 \end{vmatrix}}{\begin{vmatrix} 19 & -18 \\ -18 & 39,6 \end{vmatrix}} = \frac{19 \times 270 - (-18) \times (-54)}{19 \times 39,6 - (-18) \cdot (-18)} = \frac{5130 + 972}{752,4 - 324} = \frac{6102}{428,4} = 14,24369748V$$

$$I_{R1} = \frac{V_1 - V_2}{1000} = \frac{16,33613445 - 14,24369748 - 54}{1000} = 2,09243745mA$$

$$I_{R4} = -\left(\frac{V_1}{18}\right) = -\left(\frac{16,33613445}{18}\right) = -0,907563025mA \text{ yada}$$

$$I_{R1} = 3 + I_{R4}$$

$$I_{R4} = -3 + I_{R1} = -3 + 2,09243745 = -0,90756255mA$$

$$I_{R2} = I_{R5} = -\left(\frac{V_1 - 15}{5}\right) = \frac{-14,24369748 + 15}{5} = 0,151260504mA$$

$$I_{R3} = -\left(\frac{V_1 - 12}{1}\right) = \frac{-14,24369748 + 12}{1} = -2,24369748mA$$

$$V_{R1} = R_1 \times I_{R1} = 1000 \times 0,00209243745 = 2,09243745$$

$$V_{R5} = R_5 \times I_{R5} = R_5 \times I_{R5} = 3000 \times 0,000151260504 = 0,453781512V$$

$$P_{R1} = R_1 \times I_{R1}^2 = 1000 \times (2,09243745 \times 10^{-3})^2 = 0,004378294482W$$


$$P_{R2} = R_2 \times I_{R2}^2 = 2000 \times (0,151260504 \times 10^{-3})^2 = 0,000004572653936W$$

$$P_{R3} = R_3 \times I_{R3}^2 = 1000 \times (-2,24369748 \times 10^{-3})^2 = 0,005034178382W$$

$$P_{R4} = R_4 \times I_{R4}^2 = 18000 \times (-0,90756255 \times 10^{-3})^2 = 0,014826056W$$

$$P_{R5} = R_5 \times I_{R5}^2 = 2000 \times (0,151260504 \times 10^{-3})^2 = 0,000004572653936W$$

Toplamsallık (Superpozisyon) Teoremi

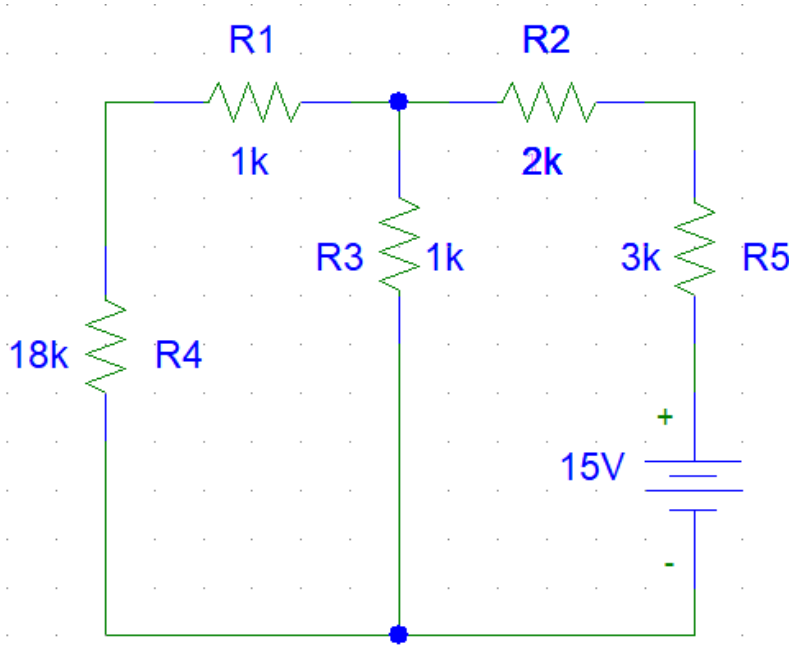


15 V'luk gerilim kaynak devrede Diğer gerilim kaynakları kısa devre

$$I_{R2} = I_{R5} = \frac{15}{\frac{(1+18) \cdot 1}{(1+18)+1} + (2+3)} = \frac{15}{\frac{19}{20} + 5} = \frac{15 \times 20}{19 + 100} = \frac{300}{119} = 2,521008403mA$$

$$I_{R3} = -0,002521008403 \times \frac{1+18}{1+18+1} = -2,394957983mA$$
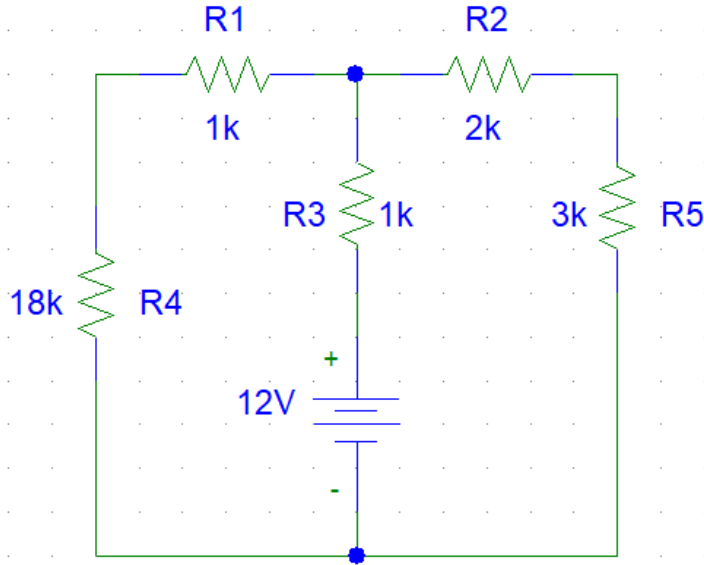
$$I_{R1} = -0,002521008403 \times \frac{1}{1+18+1} = -0,12605042mA$$




12 V'luk gerilim kaynak devrede Diğer gerilim kaynakları kısa devre

$$I_{R3} = \frac{12}{\frac{(1+18) \cdot (2+3)}{(1+18)+(2+3)} + 1} = \frac{12}{\frac{95}{24} + 1} = \frac{12 \times 24}{95 + 24} = \frac{288}{119} = 2,420168067mA$$

$$I_{R2} = I_{R5} = -0,002420168067 \times \frac{1+18}{1+18+2+3} = -1,915966387mA$$
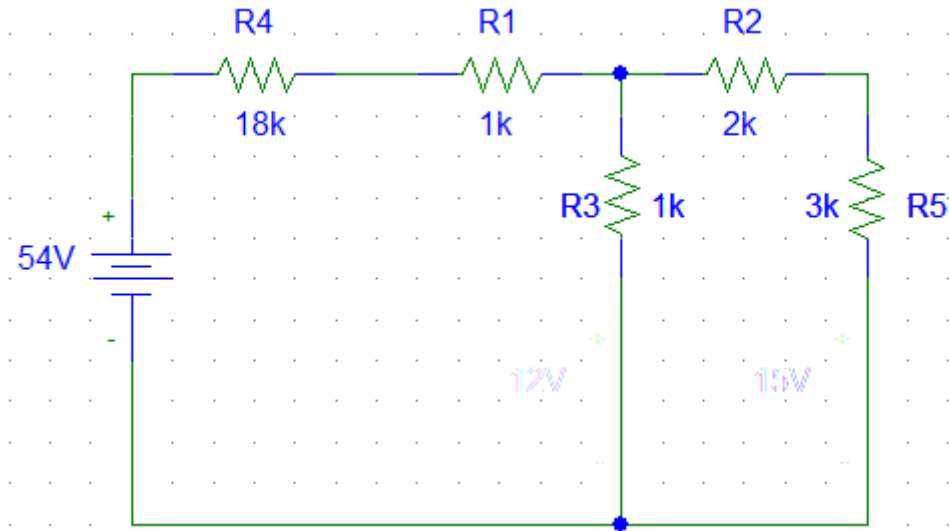
$$I_{R1} = -0,002420168067 \times \frac{2+3}{1+18+2+3} = -0,50420168mA$$



15 V'luk gerilim kaynak devrede Diğer gerilim kaynakları kısa devre (not: 3 mA'lik akım kaynağı gerilim kaynağına çevrildi $18\text{K}\Omega \times 3\text{mA} = 54\text{V}$ seri direnç $18\text{K}\Omega$)

$$I_{R1} = \frac{54}{18+1+\frac{(2+3) \times 1}{(2+3)+1}} = \frac{54}{18+1+0,8333} = 2,722689121\text{mA}$$

$$I_{R3} = -0,002722689121 \times \frac{2+3}{1+2+3} = -2,268907601\text{mA}$$

$$I_{R2} = I_{R5} = -0,002722689121 \times \frac{1}{1+2+3} = -0,45378152\text{mA}$$

Her kaynaktaki dirençlerin akımlarını toplarsak

$$I_{R2} = I_{R5} = \frac{15}{\frac{(1+18) \cdot 1}{(1+18)+1} + (2+3)} = \frac{15}{\frac{19}{20} + 5} = \frac{15 \times 20}{19+100} = \frac{300}{119} = 2,521008403mA$$

$$I_{R2} = I_{R5} = -0,002420168067x \frac{1+18}{1+18+2+3} = -1,915966387mA$$

$$I_{R2} = I_{R5} = -0,002722689121x \frac{1}{1+2+3} = -0,45378152mA$$

$$I_{R2} = I_{R5} = 2,521008403 - 1,915966387 - 0,45378152$$

$$I_{R2} = I_{R5} = 0,151260496$$

$$I_{R1} = -0,002521008403x \frac{1}{1+18+1} = -0,12605042mA$$

$$I_{R1} = -0,002420168067x \frac{2+3}{1+18+2+3} = -0,50420168mA$$

$$I_{R1} = \frac{54}{18+1+\frac{(2+3) \cdot 1}{(2+3)+1}} = \frac{54}{18+1+0,8333} = 2,722689121mA$$

$$I_{R1} = -0,12605042 - 0,50420168 + 2,722689121$$

$$I_{R1} = 2,092437021mA$$


$$I_{R3} = -0,002521008403x \frac{1+18}{1+18+1} = -2,394957983mA$$

$$I_{R3} = \frac{12}{\frac{(1+18) \cdot (2+3)}{(1+18)+(2+3)} + 1} = \frac{12}{\frac{95}{24} + 1} = \frac{12 \times 24}{95+24} = \frac{288}{119} = 2,420168067mA$$

$$I_{R3} = -0,002722689121x \frac{2+3}{1+2+3} = -2,268907601mA$$

$$I_{R3} = -2,394957983 + 2,420168067 - 2,268907601$$

$$I_{R3} = -2,243697517$$

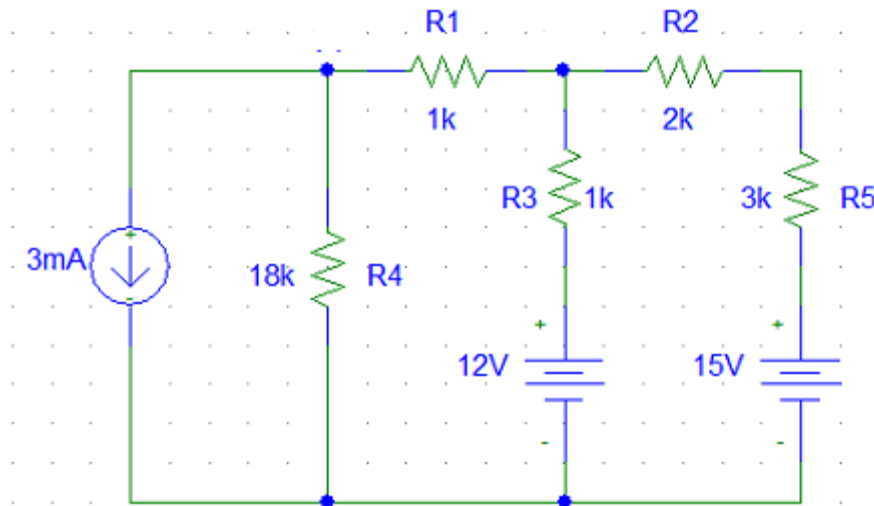

$$I_{R1} = 3 + I_{R4}$$

$$I_{R4} = -3 + I_{R1} = -3 = 2,09243745 = -0,90756255mA$$

$$V_{R1} = R_1 \times I_{R1} = 1000 \times 0,00209243745 = 2,09243745$$

$$V_{R5} = R_5 \times I_{R5} = R_5 \times I_{R5} = 3000 \times 0,000151260504 = 0,453781512V$$


$$P_{R1} = R_1 \times I_{R1}^2 = 1000 \times (2,09243745 \times 10^{-3})^2 = 0,004378294482W$$

$$P_{R2} = R_2 \times I_{R2}^2 = 2000 \times (0,1512060504 \times 10^{-3})^2 = 0,000004572653936W$$

$$P_{R3} = R_3 \times I_{R3}^2 = 1000 \times (-2,24369748 \times 10^{-3})^2 = 0,005034178382W$$

$$P_{R4} = R_4 \times I_{R4}^2 = 18000 \times (-0,90756255 \times 10^{-3})^2 = 0,014826056W$$
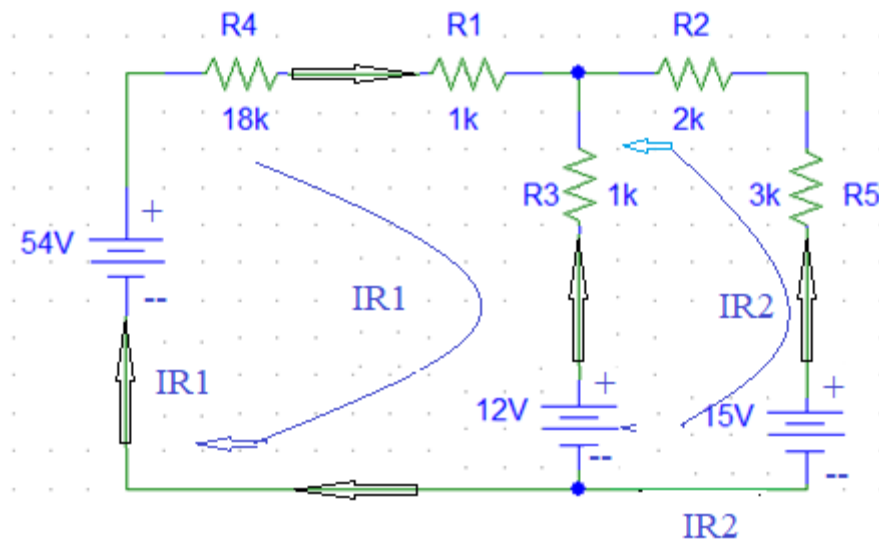
$$P_{R5} = R_5 \times I_{R5}^2 = 2000 \times (0,1512060504 \times 10^{-3})^2 = 0,000004572653936W$$



$$\begin{vmatrix} 18 + 1 + 1 & +1 \\ +1 & 1 + 2 + 3 \end{vmatrix} \begin{vmatrix} IR1 \\ IR5 \end{vmatrix} = \begin{vmatrix} 54 - 12 \\ 15 - 12 \end{vmatrix}$$

$$\begin{vmatrix} 18 + 1 + 1 & +1 \\ +1 & 1 + 2 + 3 \end{vmatrix} \begin{vmatrix} IR1 \\ IR5 \end{vmatrix} = \begin{vmatrix} +42 \\ 3 \end{vmatrix}$$


$$I_{R1} = \frac{\begin{vmatrix} 42 & 1 \\ 3 & 6 \end{vmatrix}}{\begin{vmatrix} 20 & 1 \\ 1 & 6 \end{vmatrix}} = \frac{42 \times 6 - 3 \times 1}{20 \times 6 - 1 \times 1} = \frac{252 - 3}{120 - 1} = \frac{249}{119} = 2,092436975mA$$

$$I_{R5} = I_{R2} = \frac{\begin{vmatrix} 20 & 42 \\ 1 & 3 \end{vmatrix}}{\begin{vmatrix} 20 & 1 \\ 1 & 6 \end{vmatrix}} = \frac{20 \times 3 - 1 \times 42}{20 \times 6 - 1 \times 1} = \frac{60 - 42}{120 - 1} = \frac{18}{119} =$$

$$I_{R5} = I_{R2} = 0,151260504mA$$

$$I_{R1} + I_{R3} + I_{R2} = 0$$
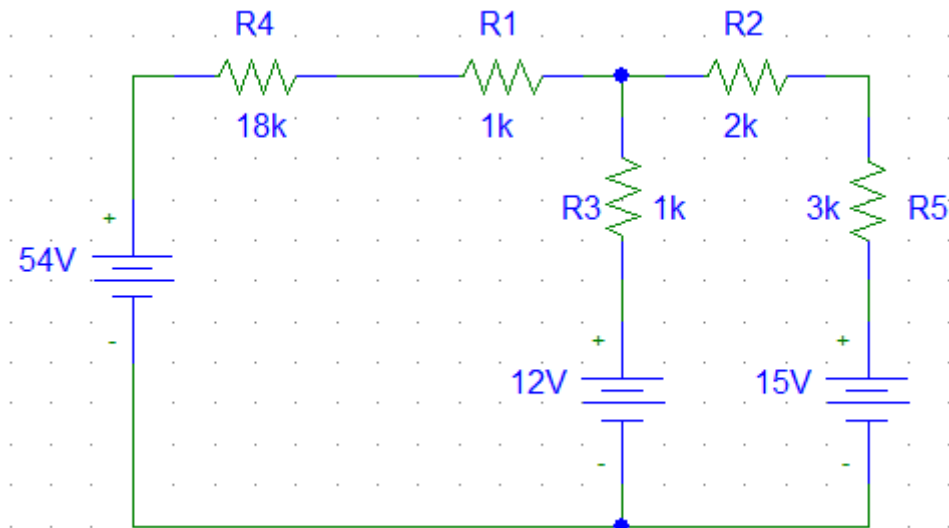
$$I_{R3} = -I_{R1} - I_{R2} = -2,092436975 - 0,151260504 = -2,243697479mA$$



$$\frac{V_1 - 54}{19} + \frac{V_1 - 12}{1} + \frac{V_1 - 15}{5} = 0$$

$$V_1 \left[\frac{1}{19} + \frac{1}{1} + \frac{1}{5} \right] = \frac{54}{19} + \frac{12}{1} + \frac{15}{5}$$

$$V_1(5 + 95 + 19) = (54 \times 5 + 12 \times 95 + 15 \times 19)$$

$$V_1(119) = (270 + 1140 + 285)$$

$$V_1 = \frac{1695}{119} = 14,24369748$$

$$I_{R3} = - \left(\frac{V_1 - 12}{1} \right) = \frac{-14,24369748 + 12}{1} = -2,24369748 \text{ mA}$$

$$I_{R2} = I_{R5} = - \left(\frac{V_1 - 15}{5} \right) = \frac{-14,24369748 + 15}{5} = 0,151260504 \text{ mA}$$

$$I_{R1} = - \left(\frac{V_1 - 54}{19} \right) = - \left(\frac{14,24369748 - 54}{19} \right) = 2,092436975 \text{ mA}$$

$$V_{R1} = R_1 \times I_{R1} = 1000 \times 0,00209243745 = 2,09243745$$

$$V_{R5} = R_5 \times I_{R5} = R_5 \times I_{R5} = 3000 \times 0,000151260504 = 0,453781512 \text{ V}$$

$$P_{R1} = R_1 \times I_{R1}^2 = 1000 \times (2,09243745 \times 10^{-3})^2 = 0,004378294482 \text{ W}$$

$$P_{R2} = R_2 \times I_{R2}^2 = 2000 \times (0,151260504 \times 10^{-3})^2 = 0,000004572653936 \text{ W}$$

$$P_{R3} = R_3 \times I_{R3}^2 = 1000 \times (-2,24369748 \times 10^{-3})^2 = 0,005034178382 \text{ W}$$

$$P_{R5} = R_5 \times I_{R5}^2 = 2000 \times (0,151260504 \times 10^{-3})^2 = 0,000004572653936 \text{ W}$$

