

∴ The voltage across $0.96 \Omega =$ voltage across resistors $a, b, c, d = V_1$
 $= 6.75 \times 0.96 = 6.5 \text{ V}$

The voltage across f and $g = 20 - 6.5 = 13.5 \text{ V}$

$$P = \frac{V^2}{R}$$

$$\therefore P_a = \frac{6.5^2}{2} = 21.1 \text{ W}, P_b = \frac{6.5^2}{4} = 10.6 \text{ W}$$

$$P_c = \frac{6.5^2}{6} = 7.05 \text{ W}, P_d = \frac{6.5^2}{8} = 5.34 \text{ W}$$

$$P_f = \frac{13.5^2}{3} = 60.7 \text{ W}, P_g = \frac{13.5^2}{8} = 30.3 \text{ W}$$

$$P_d = \frac{20^2}{5} = 80 \text{ W}$$


To halve the current, the total resistance should be doubled. Hence the resistance to be added in series

$$R_{AB} = 1.86 \Omega$$


Problem 5.45 A laboratory variable resistor has five 10Ω elements, which can be joined in series, parallel or series-parallel in any way desired. Find what combinations are possible when all five elements are used, and state the resistance in each case.

[2, 2.86, 3.75, 4.29, 5, 5.7, 6.25, 7.14, 8, 8.33, 8.57, 12, 12.5, 14, 16, 17.5, 20, 23.3, 26.7, 35, 50 Ω]







Solution






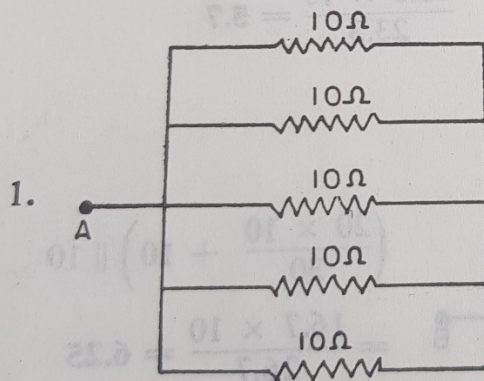









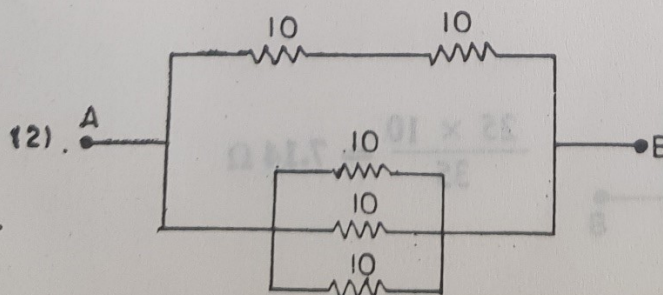
$$\text{All five in parallel} = R = \frac{10}{5} = 2 \Omega$$


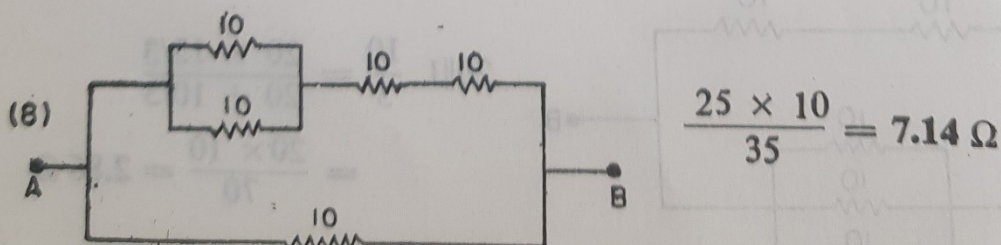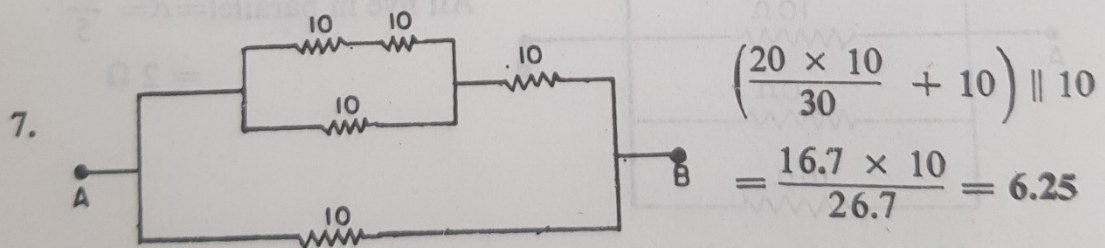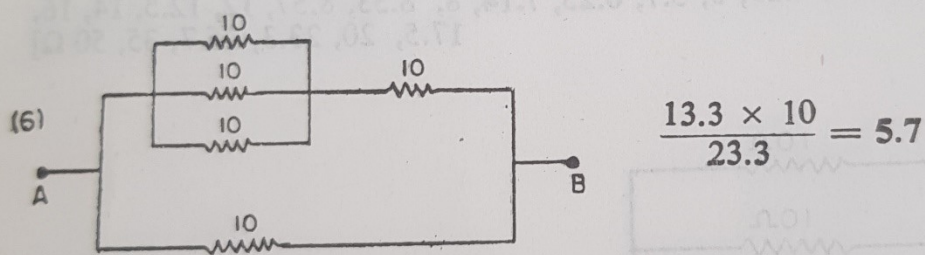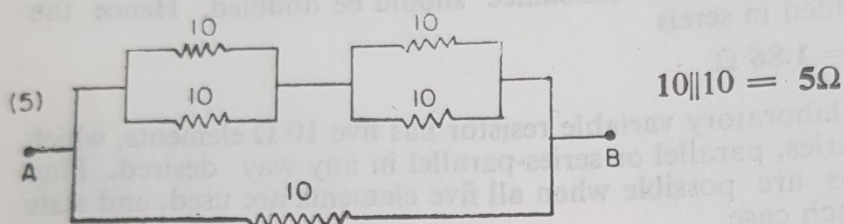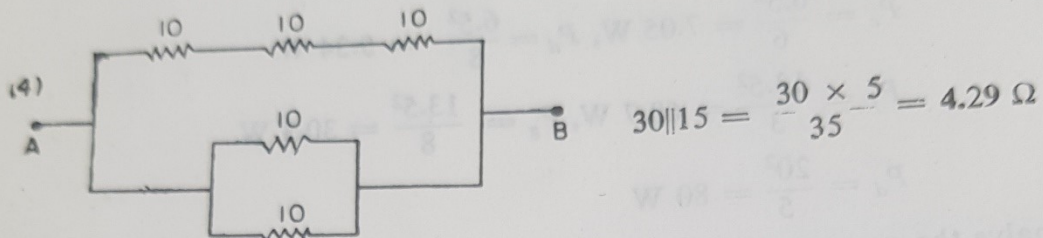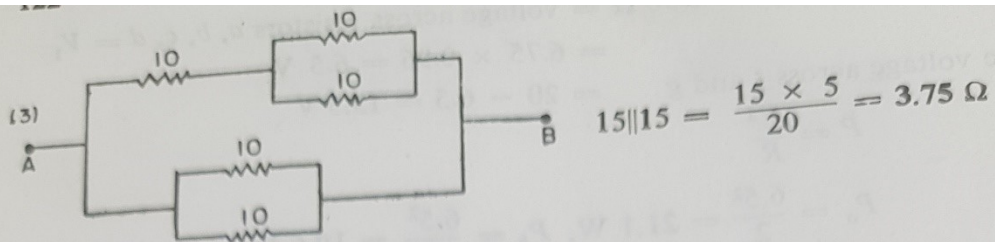
$$20 \parallel 1 \frac{10}{3} = \frac{20 \times 10/3}{20 + 10/3} = \frac{20 \times 10}{70} = 2.86 \Omega$$




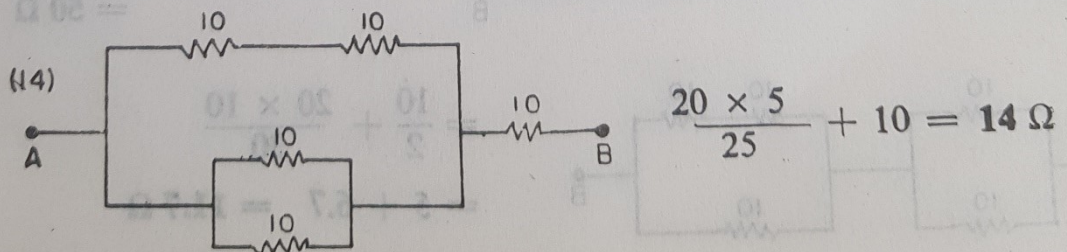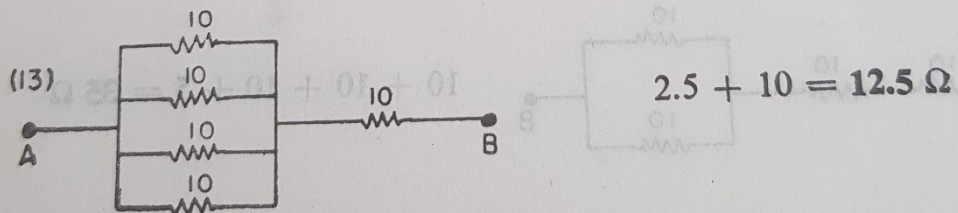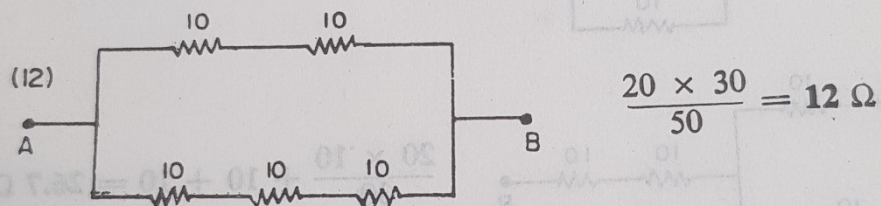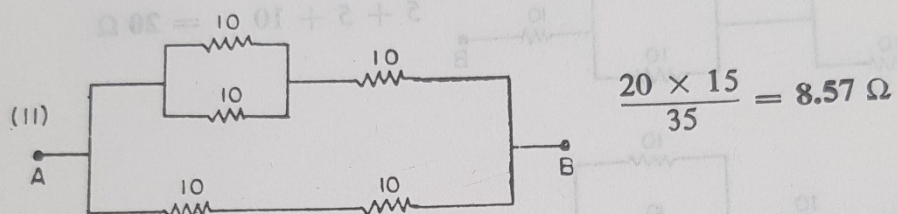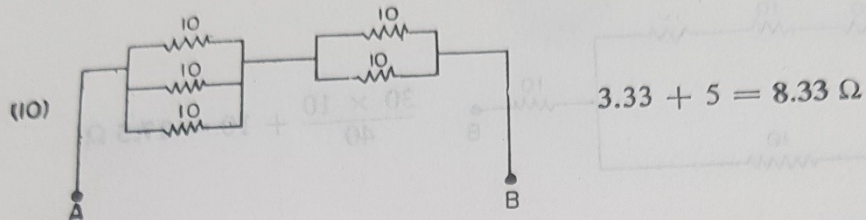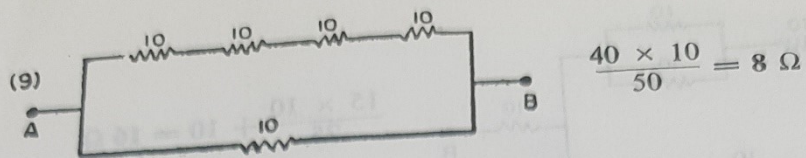

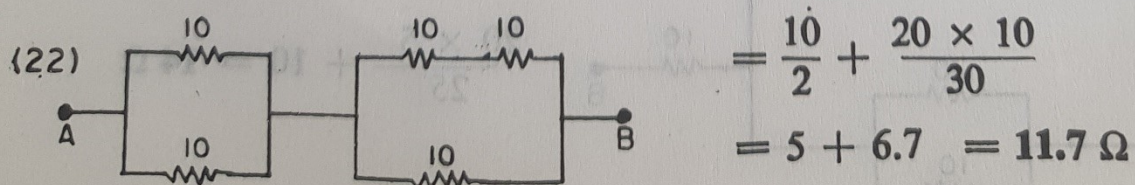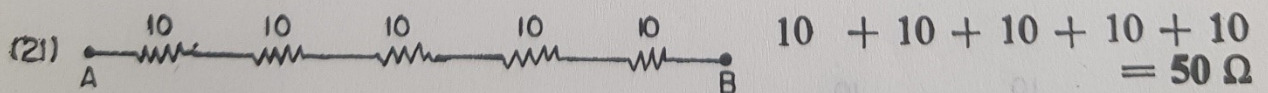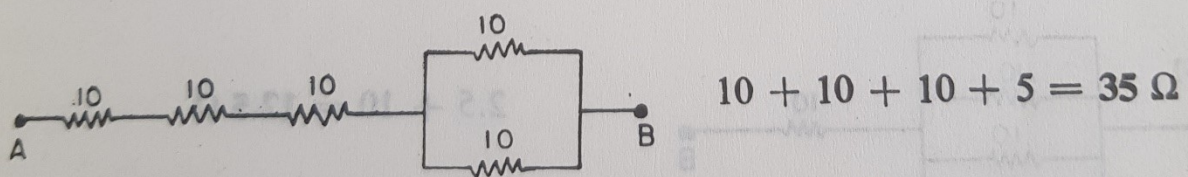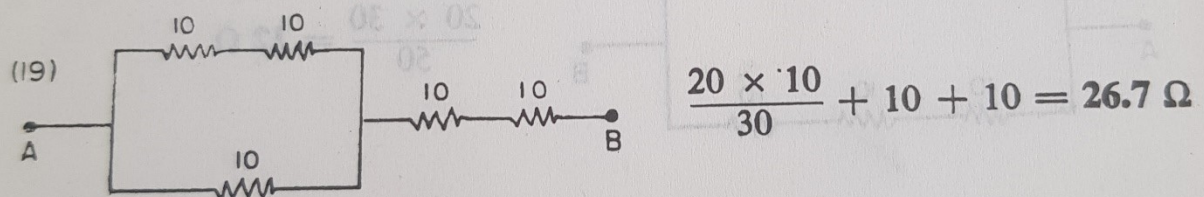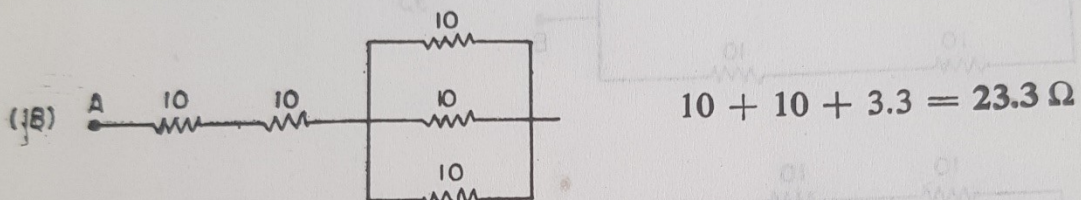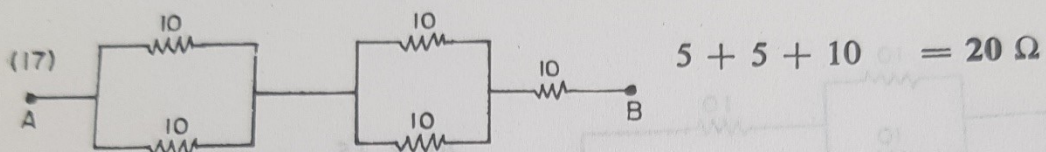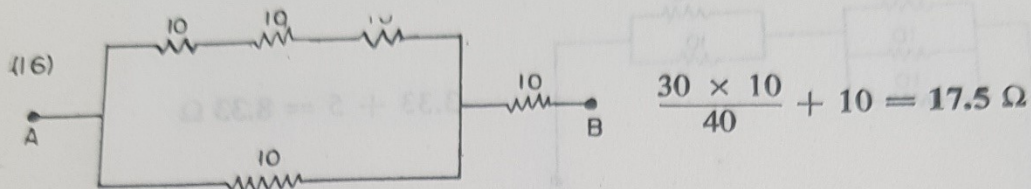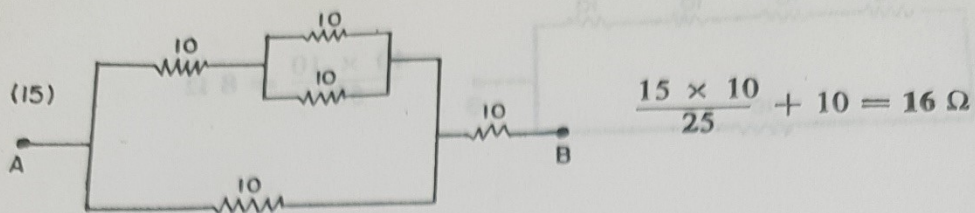


I - t'de DEVRE ÇÖZÜMÜ

1)

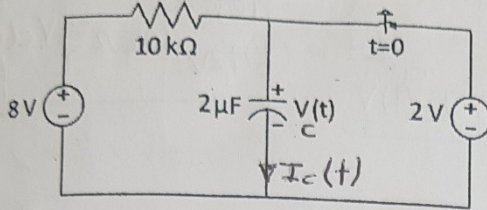

Anahtar $t = 0$ anında açılıyor.

$$v(0) = ? , v(t) = ? \quad I_C(t) = ?$$

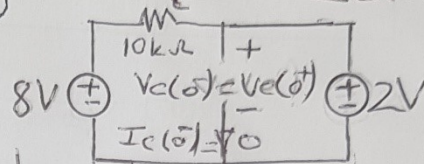

Çözüm:

$$v(0) = 2 \text{ V} = V_C(0+)$$

$$v_{öz} = A \cdot e^{-\frac{t}{RC}}$$

$$v_{öz} = A \cdot e^{-50t}$$

$$v(t) = A \cdot e^{-50t} + 8$$


$$v(0) = A + 8 = 2$$

$$v(t) = [-6 \cdot e^{-50t} + 8] u(t) \text{ V}$$

$$I_C(t) = C \cdot \frac{dv_C(t)}{dt} = 2 \times 10^{-6} [-6 \cdot (-50) \cdot e^{-50t}]$$

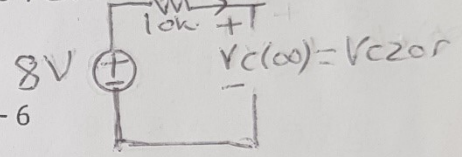
2. durumda Zaman sabiti $(\tau) = R_{es} \cdot C$
gerilim kaynağı kısa devre
 $\tau = RC = 10^4 \cdot 2 \cdot 10^{-6} = 0,02 \text{ s}$

$$v_{zor} = 8 \text{ V} = V_C(\infty) \quad I_C(\infty) = 0$$



$$A = -6$$


2)

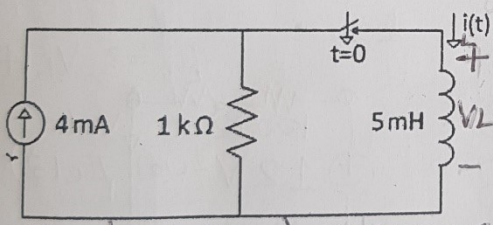

Anahtar $t = 0$ anında kapanıyor.

$$v_L(0) = ? \quad v_L(t) = ?$$

$$i_L(0) = 0 = I_L(0) \quad i_L(t) = ?$$

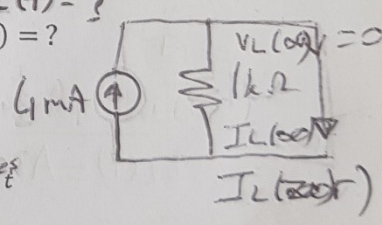

Çözüm:

2. durumda Zaman sabiti
Akım kaynağı açık devre
 $\tau = \frac{L}{R_{es}} \quad \tau = \frac{1}{\frac{1}{L}}$

$$\tau = \frac{R_{es}}{L} = \frac{1000}{5 \cdot 10^{-3}} = 2 \cdot 10^5 \frac{1}{s}$$

$$i_{zor} = 4 \text{ mA}$$

$$i_L(0) = 4 + A = 0$$

$$i_L(t) = [4 - 4 \cdot e^{-2 \cdot 10^5 t}] u(t) \text{ mA}$$

$$v_L(t) = L \cdot \frac{di_L(t)}{dt} = 5 \times 10^{-3} [-4 \cdot (-2 \times 10^5 e^{-2 \times 10^5 t})]$$

$$i_{öz} = A \cdot e^{-\frac{t}{\tau}}$$



$$i_{öz} = A \cdot e^{-2 \cdot 10^5 t}$$

$$I_L(t) = A \cdot e^{-\frac{t}{\tau}} + I_L(\infty)$$

$$i_L(t) = 4 + A \cdot e^{-2 \cdot 10^5 t}$$

$$A = -4$$

3)

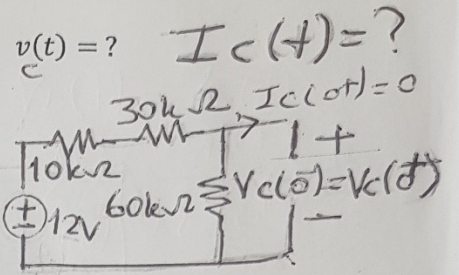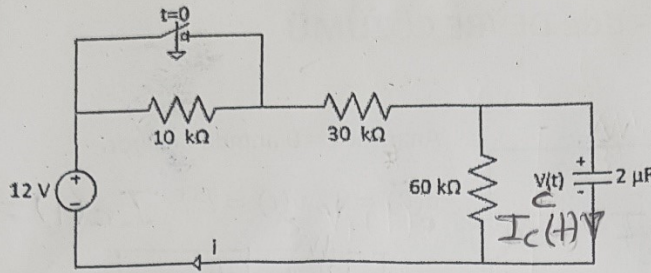

Çözüm:

$$i(0^-) = \frac{12}{(10 + 30 + 60) \cdot 10^3} = 0,12 \text{ mA}$$

$$v(0^-) = 0,12 \cdot 60 = 7,2 \text{ V} = V_C(0^+)$$

$$i(\infty) = \frac{12}{(60 + 30) \cdot 10^3} = 0,133 \text{ mA}$$

$$v(\infty) = \frac{12}{90} \cdot 60 = 8 \text{ V} = V_{\text{zor}}$$

Zaman sabiti 2 du umda

$$\tau = \frac{RC}{\epsilon_f} = \left(\frac{60 \cdot 30}{90}\right) \cdot 10^3 \cdot 2 \cdot 10^{-6} = 40 \cdot 10^{-3} \frac{1}{s}$$

$$v_{\text{öz}} = A \cdot e^{-\frac{t}{RC}}$$

$$v_{\text{öz}} = A \cdot e^{-25t}$$


$$v(0^+) = 7,2 = A + 8$$

$$v(t) = [8 - 0,8 \cdot e^{-25t}] u(t) \text{ V}$$



$$I_C(t) = C \cdot \frac{dv_C(t)}{dt} = 2 \cdot 10^{-6} \cdot 0,8(-25) e^{-25t}$$

$$v(t) = A \cdot e^{-25t} + 8$$

$$A = -0,8$$

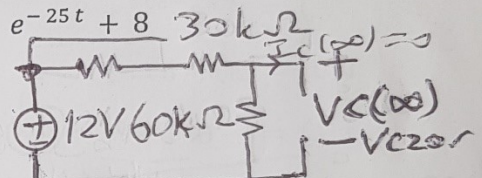

4)

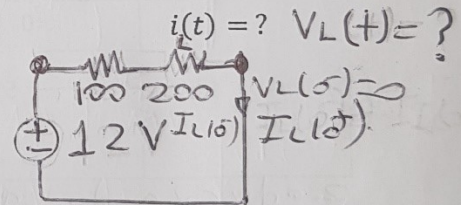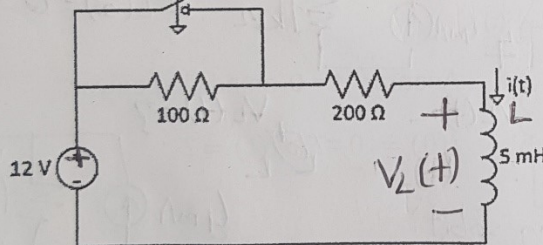

Çözüm:

$$i(0^-) = \frac{12}{300} = 0,04 \text{ A} = 40 \text{ mA} = I_L(0^+)$$

$$\tau = \frac{L}{R_{\text{es}}}$$

ik meidimunda

$$r = \frac{R_{\text{es}}}{L} = \frac{200}{5 \cdot 10^{-3}} = 40000 \frac{1}{s} \quad \tau = -\frac{1}{r}$$

$$i_{\text{öz}} = A \cdot e^{-\frac{R}{L}t}$$

$$i_{\text{öz}} = A \cdot e^{-40000t}$$

$$i(t) = A \cdot e^{-40000t} + 60$$


$$i_{\text{zor}} = \frac{12}{200} = 0,06 \text{ A} = 60 \text{ mA}$$

$$i(0^+) = A + 60 = 40$$

$$A = -20$$

$$i(t) = [60 - 20 \cdot e^{-40000t}] u(t) \text{ A}$$
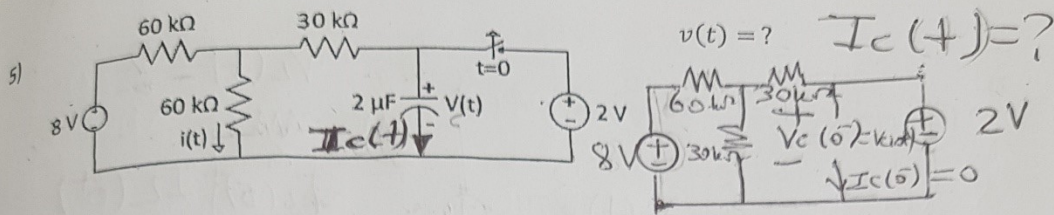
$$V_L(t) = L \cdot \frac{di_L(t)}{dt} = 5 \cdot 10^{-3} [-20 \cdot (-40000) e^{-40000t}]$$



Çözüm:

$$v(0^-) = 2V = V_c(0^+)$$

$$v_{\infty} = A \cdot e^{-\frac{t}{RC}}$$

$$V_c(t) = A e^{-\frac{t}{RC}} + V_c(\infty)$$

$$v(t) = v_{\infty} + A \cdot e^{-\frac{t}{RC}}$$

$$v(t) = 4 + A \cdot e^{-\frac{t}{0,12}}$$

$$v(t) = [4 - 2 \cdot e^{-\frac{t}{0,12}}] u(t) \text{ V}$$

$$R_{\text{es}} = \frac{60 \cdot 60}{60 + 60} + 30 = 60 \text{ k}\Omega$$

2 durumda



$$\tau = RC = 60 \cdot 10^3 \cdot 2 \cdot 10^{-6} = 0,12 \text{ s}$$

$$i(\infty) = \frac{8}{120} = 0,066 \text{ mA}$$

$$v(\infty) = 0,066 \cdot 60 = 4 \text{ V}$$

$$v(0) = 4 + A = 2, \quad A = -2$$
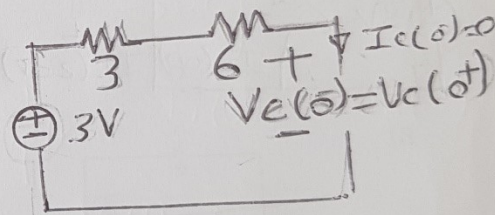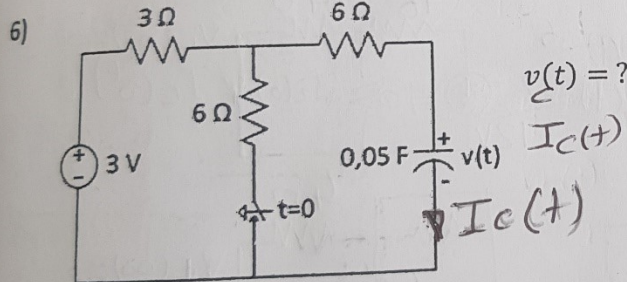
$$I_c(t) = C \frac{dV_c(t)}{dt} = 2 \times 10^{-6} \left[\left(-\frac{1}{0,12} \right) e^{-\frac{t}{0,12}} \right]$$



Çözüm:

$$v(0^-) = 3V = V_c(0^+)$$

$$v_{\infty} = A \cdot e^{-\frac{t}{RC}} = A \cdot e^{-\frac{t}{0,4}}$$

$$V_c(t) = A e^{-\frac{t}{RC}} + V_{c\infty}$$

$$v(t) = 2 + A \cdot e^{-2,5t}$$

$$v(0) = 2 + A = 3$$

$$A = 1$$

$$v(t) = [2 + e^{-2,5t}] u(t) \text{ V}$$

$$I_c(t) = C \cdot \frac{dV_c(t)}{dt} = 0,05 \cdot [-2,5 e^{-2,5t}]$$


$$\tau = R_{\text{es}}, C = 8 \times 0,05 = 0,4$$

$$R_{\text{es}} = \frac{3 \cdot 6}{9} + 6 = 8 \Omega$$

$$v_{\infty} = \frac{3}{9} \cdot 6 = 2V = V_c(\infty)$$

$$I_c(\infty) = 0$$

$$V_c(\infty) = V_{c\infty}$$

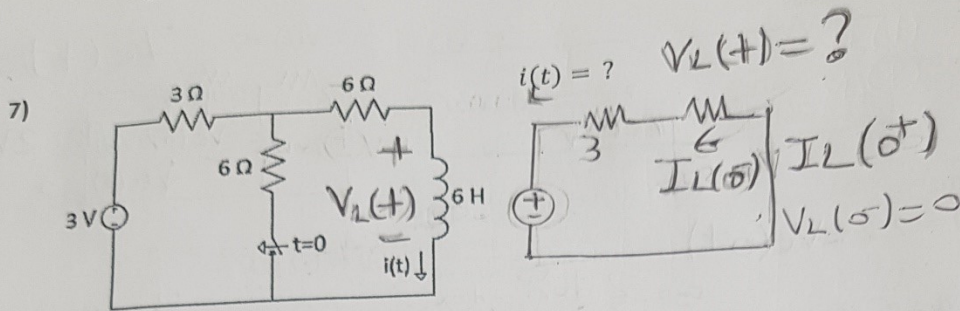

Çözüm:

$$i(0^-) = \frac{3}{3+6} = \frac{1}{3} \text{ A} = I_L(0^+)$$

$$Z = \frac{L}{R_{es}}$$

$$i_{öz} = A \cdot e^{-\frac{R}{L}t}$$

$$R_{es} = \frac{3 \cdot 6}{9} + 6 = 8 \Omega \quad r = \frac{R_{es}}{L} = \frac{8}{6} = 1,33 \left(\frac{1}{s}\right)$$

$$i_{öz} = A \cdot e^{-1,33 t}$$


$$i_{zor} = \frac{3}{3+3} \cdot \frac{1}{2} = 0,25 \text{ A}$$

$$I_L(t) = A \cdot e^{-\frac{t}{\tau}} + I_L(\infty)$$

$$i(0) = \frac{1}{3} = \frac{1}{4} + A$$

$$A = \frac{1}{12}$$


$$i(t) = 0,25 + A \cdot e^{-1,33 t}$$

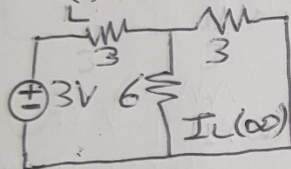


$$i(t) = \left[\frac{1}{4} + \frac{1}{12} \cdot e^{-1,33 t} \right] u(t) \text{ A}$$

$$I_L(t) = ?$$

$$V_L(t) = ?$$

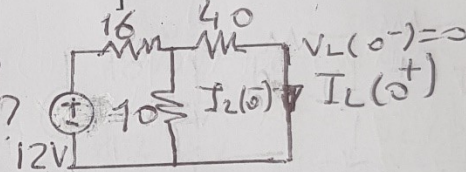

8)

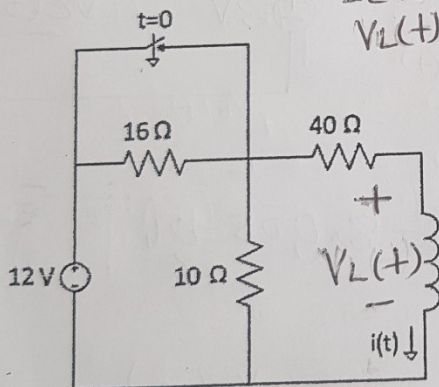

Çözüm:

$$i(0^-) = \frac{12}{16 + \frac{40 \cdot 10}{50}} \cdot \frac{1}{5} = 0,1 \text{ A} = I_L(0^+)$$

Zdurunda

$$i_{öz} = A \cdot e^{-\frac{R}{L}t}$$

$$r = \frac{R_{es}}{L} = \frac{40}{20} = 2 \frac{1}{s}$$

$$I_L(t) = A \cdot e^{-\frac{t}{\tau}} + I_L(\infty)$$

$$i_{zor} = \frac{12}{\frac{40 \cdot 10}{50}} \cdot \frac{1}{5} = 0,3 \text{ A}$$

$$Z = \frac{L}{R_{es}}$$


$$i(t) = A \cdot e^{-2t} + 0,3$$

$$i(0) = A + 0,3 = 0,1$$

$$A = -0,2$$

$$i(t) = [0,3 - 0,2 \cdot e^{-2t}] u(t) \text{ A}$$
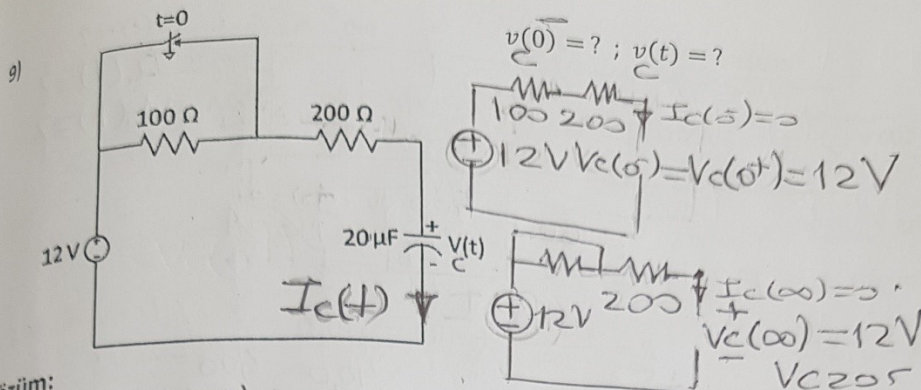
$$V_L(t) = L \cdot \frac{di(t)}{dt} = 20 \cdot [(-0,2)(-2) \cdot e^{-2t}]$$



Çözüm:

$$v(0^-) = 12V = V_C(0^+)$$

$$v_{\text{öz}} = A \cdot e^{-2500t} + V_C(\infty)$$

$$v(t) = A \cdot e^{-2500t} + 12$$


$$v(0^-) = A + 12 = 12 \quad A = 0$$

Öz çözüm için; $\frac{1}{R \cdot C} = \frac{10^6}{200 \cdot 20} = 2500 \frac{1}{s} = r$

2. durum $v_{\text{zor}} = 12V \quad \tau = \frac{L}{R_{\text{es}}}$

$$r = -\frac{1}{\tau}$$

10)

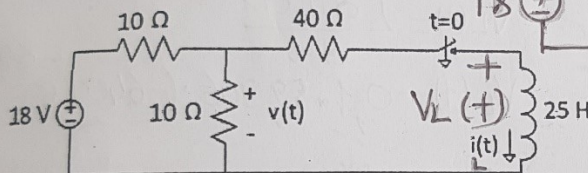

Çözüm:

$$v(0^-) = 9V$$

$$i_{\text{öz}} = A \cdot e^{-\frac{R}{L}t}$$

$$R = \frac{10 \cdot 10}{20} + 40 = 45\Omega \quad r = -\frac{R_{\text{es}}}{L} = -\frac{45}{25} = -1,8 \frac{1}{s}$$

$$i_{\text{öz}} = A \cdot e^{-1,8t}$$

$$I_L(\infty) = i_{\text{zor}} = \frac{18}{10 + \frac{10 \cdot 40}{50}} \cdot \frac{1}{40 + 10} \cdot 10 = 0,2A$$

$$I_L(t) = A \cdot e^{-\frac{t}{\tau}} + I_L(\infty)$$

$$i(t) = A \cdot e^{-1,8t} + 0,2$$

$$i(0) = A + 0,2 = 0$$

$$A = -0,2$$

$$i(t) = 0,2 - 0,2 \cdot e^{-1,8t}$$


$$V_L(t) = L \cdot \frac{di}{dt} = 25 \cdot 0,2 \cdot 1,8 \cdot e^{-1,8t} = 9 \cdot e^{-1,8t}$$

$$\frac{v}{10} + \frac{v-18}{10} + \frac{v-9 \cdot e^{-1,8t}}{40} = 0$$

$$9v - 72 - 9 \cdot e^{-1,8t} = 0$$

$$v(t) = [8 + e^{-1,8t}] u(t) \quad V$$

11)

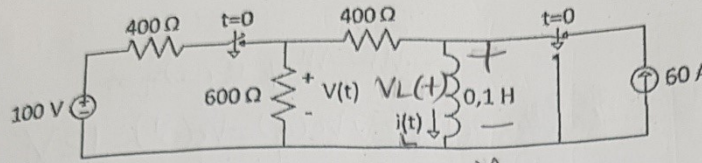

$$v(t) = ?$$

$$I_L(t) = ?$$

$$V_L(t) = ?$$

Çözüm:

$$i_L(0^-) = 60 \text{ A} = I_L(0^+) \quad v(0) = 0$$

$$i_{\text{öz}} = A \cdot e^{-\frac{R}{L}t}$$

$$R = \frac{400 \cdot 600}{1000} + 400 = 640 \Omega$$

$$\tau = \frac{L}{R} = \frac{0,1}{640} = 6400 = -\frac{1}{\tau}$$

$$i_{\text{öz}} = A \cdot e^{-6400t}$$

$$i_{\text{zor}} = \frac{100}{400 + \frac{600 \cdot 400}{1000}} \cdot \frac{6}{10} = 0,09375 \text{ A}$$

$$I_L(t) = A e^{-\frac{t}{\tau}} + I_L(\infty)$$

$$i(t) = A \cdot e^{-6400t} + 0,09375$$

$$i(0^+) = 60 = A + 0,09375$$

$$A = 59,906$$


$$i(t) = 0,09375 + 59,906 \cdot e^{-6400t}$$

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$V_L(t) = 0,1 \cdot 59,906 \cdot (-6400) e^{-6400t}$$

$$v(t) = 37,5 + [400 \cdot 59,9 - 6400 \cdot 59,9 \cdot 0,1] \cdot e^{-6400t} \text{ V}$$

12)

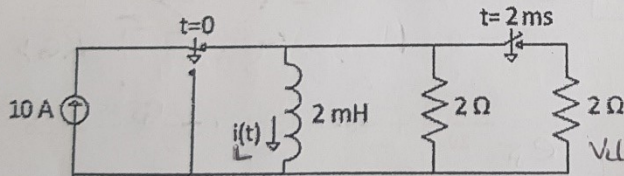

$$I_L(t) = ?$$

$$V(t) = ?$$

$$\text{Çözüm: } i_L(0^-) = 10 \text{ A} = I_L(0^+)$$

$$0^+ \leq t \leq 2 \text{ ms}$$

$$i(t) = 10 \cdot e^{-\frac{2000}{2}t} = 10 \cdot e^{-1000t}$$

$$t = 2 \cdot 10^{-3} \text{ s}$$

$$i(2 \text{ ms}) = 10 \cdot e^{-2} = 3,68 \text{ A}$$

bu 2ms deki



$$I_L(0^-) = I_L(0^+)$$

$$i(t) = 3,68 \cdot e^{-\frac{10^3}{2}(t - 2 \cdot 10^{-3})} \text{ A}$$

$$2 \text{ ms Sonra: } I_L(\infty) = 0$$

$$(t \geq 2 \text{ ms})$$

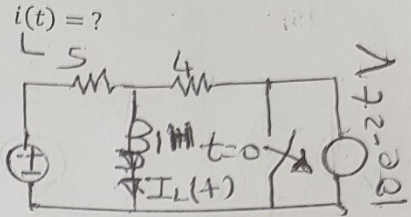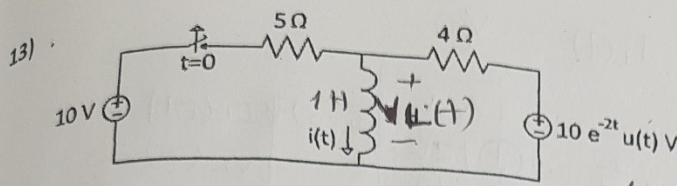halkası devre dışı
kaynak yok olduğu
selfin üzerindeki
akım halavur (2ms)




Çözüm:

$$i(0^-) = \frac{10}{5} = 2 \text{ A} = I_L(0^+) \quad i_{\text{öz}} = A \cdot e^{-\frac{4}{1}t} = A \cdot e^{-4t}$$

Devre denklemi; $t \geq 0^+$ için;
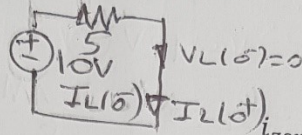
$$-10 \cdot e^{-2t} + 4i + \frac{di}{dt} = 0$$



$$-10 \cdot e^{-2t} + 4K \cdot e^{-2t} - 2K \cdot e^{-2t} = 0$$

$$2K = 10, K = 5$$


$$i_{\text{zor}} = 5 \cdot e^{-2t}$$

$$i(t) = 5 \cdot e^{-2t} + A \cdot e^{-4t}$$

$$i(0) = 2 = 5 + A$$

$$A = -3$$


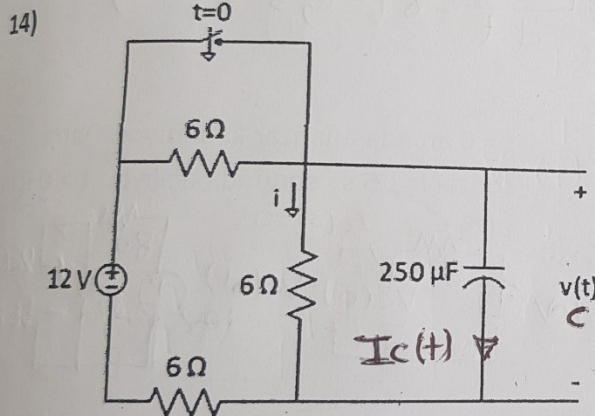
$$i(t) = [5 \cdot e^{-2t} - 3 \cdot e^{-4t}] u(t) \quad \text{A}$$



$$v(t) = ?$$

$$I_C(t) = ?$$

$$I_C(0^-) = 0$$

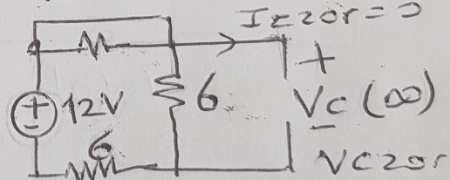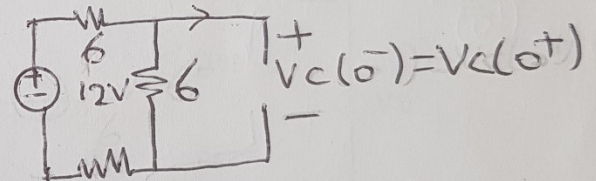

Çözüm:

$$i(0^-) = \frac{12}{18} \text{ A}$$

$$v(0^-) = \frac{12}{18} \cdot 6 = 4 \text{ V} = V_C(0^+)$$

$$v_{\text{öz}} = A \cdot e^{-\frac{t}{RC}}$$

$$R = \frac{6 \cdot 6}{12} = 3 \Omega \quad \tau = R \cdot C = 3 \cdot 10^{-6} \cdot 250 = 0,750 \cdot 10^{-3} \frac{1}{s}$$

$$v_{\text{öz}} = A \cdot e^{-1,333t}$$

$$i_{\text{zor}} = \frac{12}{12} = 1 \text{ A}$$

$$v_{\text{zor}} = 1 \cdot 6 = 6 \text{ V}$$

$$v(t) = A \cdot e^{-1,333t} + 6$$


$$v(0) = 4 = A + 6$$

$$A = -2$$

$$V_C(t) = A e^{-\frac{t}{\tau}} + V_C(\infty) \quad v(t) = [6 - 2 \cdot e^{-1,333t}] u(t) \text{ V}$$

$$I_C(t) = C \cdot \frac{dV_C(t)}{dt} = 250 \times 10^{-6} [(-2) \cdot (-1,333) \cdot e^{-1,333t}]$$

15)

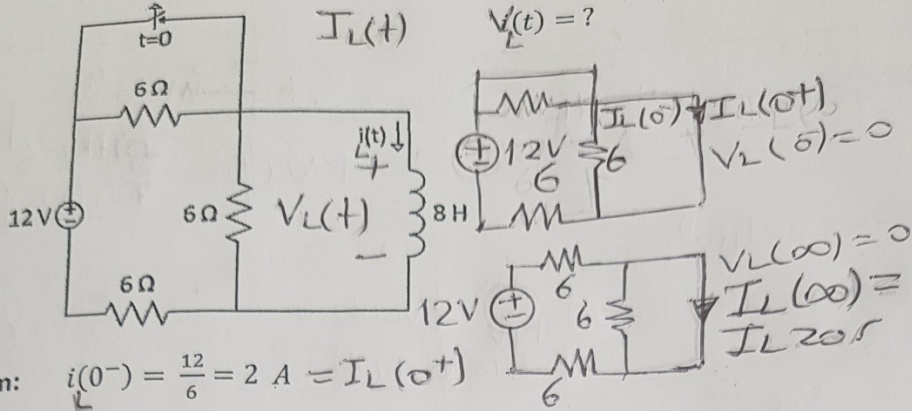

Çözüm: $i_L(0^-) = \frac{12}{6} = 2 \text{ A} = I_L(0^+)$

$$i_{\text{öz}} = A \cdot e^{-\frac{R}{L}t}$$

$$R = \frac{6 \cdot 12}{18} = 4 \Omega$$

$$\tau = \frac{L}{R} = \frac{8}{4} = 2 \text{ s}$$

$$i_{\text{öz}} = A \cdot e^{-0,5t}$$

$$i_{\text{zor}} = \frac{12}{12} = 1 \text{ A} = I_L(\infty)$$

$$i_L(t) = A \cdot e^{-0,5t} + 1$$


$$i_L(0) = 2 = A + 1$$

$$A = 1$$

$$i_L(t) = [e^{-0,5t} + 1] u(t) \text{ A}$$

$$V_L(t) = L \frac{di_L(t)}{dt} = 8(-0,5e^{-0,5t})$$



16)

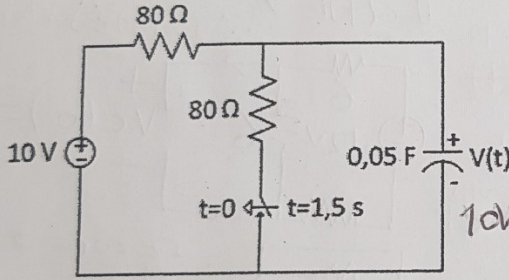

t = 0 anında anahtar kapanıyor. Daha

sonra t = 1,5 s sonunda açılıyor. t > 0 için

$$v(t) = ? \quad I_C(0) = 0$$

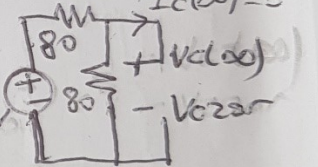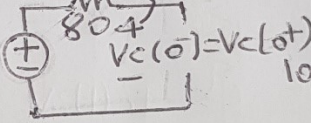

Çözüm: $v_C(0^-) = 10 \text{ V} = V_C(0^+)$

$$0 < t \leq 1,5 \text{ s}$$

$$v_{\text{öz}} = A e^{-\frac{t}{RC}}$$

$$R = \frac{80 \cdot 80}{160} = 40 \Omega$$

$$RC = 40 \cdot 0,05 = 2 \text{ s}$$

$$v_C(t) = A \cdot e^{-0,5t}$$

$$v_{\text{zor}} = \frac{10}{16} \cdot 8 = 5 \text{ V}$$

$$v_C(t) = A \cdot e^{-0,5t} + 5$$

$$v_C(0) = A + 5 = 10$$

$$A = 5$$

$$v_C(t) = 5 \cdot e^{-0,5t} + 5 \text{ V} \quad (0 < t \leq 1,5)$$

$$v_C(1,5) = 7,36 \text{ V}$$

$$t = 1,5 \text{ s}$$

$$v_{\text{öz}} = A \cdot e^{-\frac{t}{RC}}$$

$$RC = 80 \cdot 0,05 = 4 \text{ s}$$

$$v_{\text{zor}} = 10 \text{ V}$$

$$v_C(t) = 10 + A \cdot e^{-0,25t}$$

$$v_C(1,5) = 7,36 = A + 10$$


$$A = -2,64$$

$$v_C(t) = [10 - 2,64 \cdot e^{-0,25(t-1,5)}] u(t) \text{ V}$$


$$(t \geq 1,5 \text{ s})$$

1,5 s önceki

17)

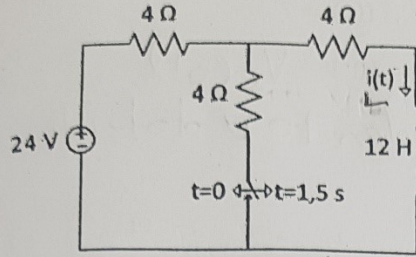

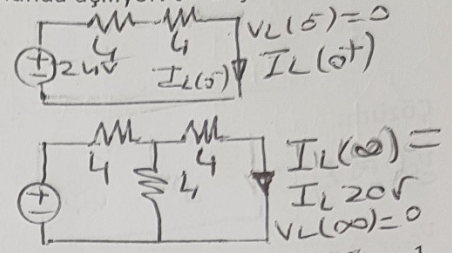$t = 0$ anında anahtar kapanıyor. Daha sonra $t = 1,5$ s sonunda açılıyor. $t > 0$ için $i(t) = ?$



Çözüm: $I_L(0^-) = I_L(0^+) = 3A$

$$i(0^-) = \frac{24}{8} = 3A = I_L(0^+) i(t) = A \cdot e^{-\frac{R}{L}t}$$

$$R = \frac{4 \cdot 4}{8} + 4 = 6\Omega \quad r = \frac{R_{es}}{L} = 0,5 \frac{1}{s}$$

$$i_{öz} = A \cdot e^{-0,5t}$$

$$i_{zor} = \frac{24}{4+2} \cdot \frac{4}{4+4} = 2A$$

$$i(t) = 2 + A \cdot e^{-0,5t}$$

$$i(0) = 2 + A = 3$$

$$A = 1$$

$$i(t) = 2 + e^{-0,5t} A$$

$$(0 < t < 1,5)$$

$$i(1,5) = 2 + e^{-0,75} = 2,472 A$$

$$t \geq 1,5 s$$

$$i_{öz} = A \cdot e^{-\frac{8}{12}t}$$

$$i_{zor} = \frac{24}{8} = 3A$$

$$i(t) = A \cdot e^{-0,667t} + 3$$


$$i(0) = A + 3 = 2,47$$

$$A = -0,53$$

$$i(t) = [3 - 0,53 \cdot e^{-0,667(t-1,5)}] u(t) A$$

$$(1,5 \geq t)$$

18)

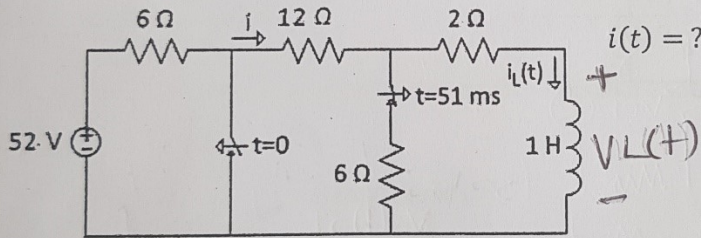

Çözüm:

$$t \leq 51 ms$$

$$i_L(0^-) = \frac{52}{6+12+\frac{6 \cdot 2}{8}} \cdot \frac{6}{8} = 2 A = I_L(0^+) \quad i_{Lzor} = 0 \quad \text{Kaynak yok}$$

$$i_{Löz} = A \cdot e^{-\frac{R}{L}t}$$

$$R_{es} = \frac{12 \cdot 6}{18} + 2 = 6\Omega$$

$$r = \frac{R_{es}}{L} = 6 \frac{1}{s}$$

$$i_L(t) = 2e^{-6t}$$

$$i(0^-) = 2 \cdot \frac{8}{6} = \frac{8}{3} A$$

$$i(t) = \frac{8}{3} \cdot e^{-6t}$$

$$\tau = -\frac{1}{r} \quad (0 \leq t \leq 51 ms)$$

$$t \geq 51 ms$$

$$i(51 ms) = \frac{8}{3} \cdot e^{-6 \cdot 51 \cdot 10^{-3}} = \frac{8}{3} \cdot \frac{1}{e^{0,306}} = 1,96 A$$

$$r = \frac{R_{es}}{L} = \frac{14}{1} \frac{1}{s}$$


$$i_{zor} = 0$$

$$i_L(t) = [1,96 \cdot e^{-14(t-0,051)}] u(t) A$$

$$R_{es} = (12+2) = 14 \quad (t > 51 ms)$$

$$\rightarrow I_L(0) = 2,666 \frac{6}{2+6} = 2$$

19)

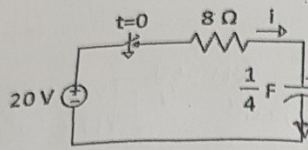

$$v_c(t) = ? , i(t) = ?$$

$$v_c(0^-) = 10 \text{ V} = v_c(0^+)$$

önceden 10 V doluydu

Çözüm:

$$v_{c_{öz}} = A \cdot e^{-\frac{t}{RC}}$$

$$RC = 8 \cdot \frac{1}{4} = 2 \text{ s}$$

$$v_{c_{öz}} = A \cdot e^{-0.5t}$$

$$v_{c_{zor}} = 20 \text{ V}$$

$$v_c(t) = A \cdot e^{-0.5t} + 20$$

$$v_c(0) = A + 20 = 10$$


$$A = -10$$

$$v_c(t) = 20 - 10 \cdot e^{-0.5t} \text{ V} \quad (t \geq 0)$$

$$i(t) = C \cdot \frac{dv_c}{dt}$$

$$i(t) = \frac{1}{4} \cdot 5 \cdot e^{-0.5t} = \frac{5}{4} \cdot e^{-0.5t} \text{ A} \quad (t \geq 0)$$

20)

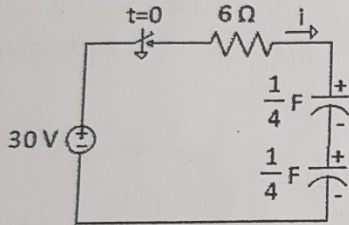

$$v_c(t) = ? , i(t) = ?$$

$$v_c(0^-) = 0 \text{ V} = v_c(0^+)$$

Çözüm:

$$C_e = \frac{C \cdot C}{2C} = \frac{\frac{1}{4} \cdot \frac{1}{4}}{\frac{2}{4}} = \frac{1}{8} \text{ F}$$

$$C_e \cdot R = \frac{6}{8} \text{ s}$$

$$v_{C_{eöz}} = A \cdot e^{-\frac{t}{RC_e}} = A \cdot e^{-\frac{8}{6}t}$$

$$v_{C_{e_{zor}}} = 30 \text{ V} \quad v_{C_e}(t) = 30 + A \cdot e^{-\frac{8}{6}t} \quad v_{C_e}(0) = 30 + A = 0 \quad A = -30$$

$$v_{C_e} = 30 - 30 \cdot e^{-\frac{8}{6}t} \text{ V} \quad v_c(t) = \frac{1}{2} v_{C_e} = 15 - 15 \cdot e^{-\frac{8}{6}t} \text{ V}$$

$$i(t) = C_e \cdot \frac{dv_{C_e}}{dt}$$

$$i(t) = \frac{1}{8} \cdot \left(30 \cdot \frac{8}{6} \right) \cdot e^{-\frac{8}{6}t} = 5 \cdot e^{-\frac{8}{6}t} \text{ A} \quad (t \geq 0)$$