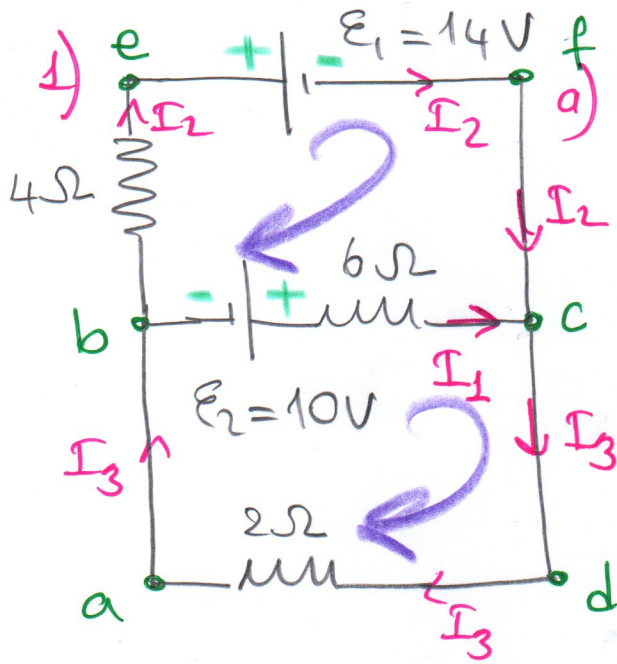


Exercises About DC Circuits

(1)



Find the currents I_1 , I_2 , and I_3 for the circuits

We have two closed loops in the circuits. So we can apply Kirchhoff's rules to obtain I_1 , I_2 , and I_3 currents.

To describe the loops, let's use letters shown in the figure. In this question, the directions of the currents flow are given.

So point c can be considered as a junction to write 1st Kirchhoff's rule:

$$\sum I_{in} = \sum I_{out} \Rightarrow I_1 + I_2 = I_3 \quad (1)$$

for the 2nd Kirchhoff's rule, let's consider the direction of circulation as clockwise!

for abcd a loop $\sum \Delta V = 0$

$$E_2 - I_1 \cdot 6 - I_3 \cdot 2 = 0 \rightarrow 10 - 6I_1 - 2I_3 = 0 \quad (2)$$

We leave the battery from its positive terminal. So that $E_2 > 0$

The direction of circulation and the directions of the I_1 and I_3 are the same. Due to this reason, the electric potential across these resistance must be negative!

for befc loop

(2)

$$-4I_2 - \mathcal{E}_2 + 6I_1 - \mathcal{E}_2 = 0 \rightarrow \boxed{6I_1 - 4I_2 = 24} \quad (3)$$

on the befc branch there is only I_2 current

By using Eqs. (1), (2), and (3) we can find the related electric currents.

$$6I_1 + 2(I_1 + I_2) = 10$$

$$6I_1 - 4I_2 = 24$$

$$I_1 = 2A$$

$$I_2 = -3A$$

$$I_3 = I_1 + I_2$$

$$I_3 = -1A$$

Please do not change the signs of the related currents for our following calculations!

We found negative values for the I_2 and I_3 currents. It means that I_2 and I_3 currents flow in the opposite direction to what we describe in the question.

b) find the electric potential difference of $V_b - V_c =$

$$V_b + \mathcal{E}_2 - 6I_1 = V_c \quad \text{from bc path}$$

$$V_b - V_c = 6I_1 - \mathcal{E}_2 = 6(2) - 10 = 2V$$

$$V_b - I_2 4 - \mathcal{E}_1 = V_c \quad \text{from befc path}$$

$$V_b - V_c = \mathcal{E}_1 + 4I_2 = 14 + 4(-3) = 2V$$

$$V_b + 2I_3 = V_c \quad \text{from badc path}$$

$$V_b - V_c = -2I_3 = -2(-1) = 2V$$


c) Find the powers supplied by the batteries and consumed by the resistors. ③

$$\left. \begin{aligned} P_{E_1} &= \mathcal{E}_1 I_2 = 14 \cdot 3 = 42 \text{ Watt} \\ P_{E_2} &= \mathcal{E}_2 I_1 = 10 \cdot 2 = 20 \text{ Watt} \end{aligned} \right\} P_{\text{supplied}} = 42 + 20 = 62 \text{ Watt}$$

$$\left. \begin{aligned} P_{R_1} &= I_1^2 6 = 2^2 \cdot 6 = 24 \text{ Watt} \\ P_{R_2} &= I_2^2 4 = (-3)^2 \cdot 4 = 36 \text{ Watt} \\ P_{R_3} &= I_3^2 2 = 1^2 \cdot 2 = 2 \text{ Watt} \end{aligned} \right\} P_{\text{consumed}} = 24 + 36 + 2 = 62 \text{ Watt}$$

2) An uncharged capacitor and resistor are connected in series to a battery as shown in the figure. If $\mathcal{E} = 12\text{V}$, $C = 5\mu\text{F}$ and $R = 8 \cdot 10^5 \Omega$, find

a) the time constant of the circuit

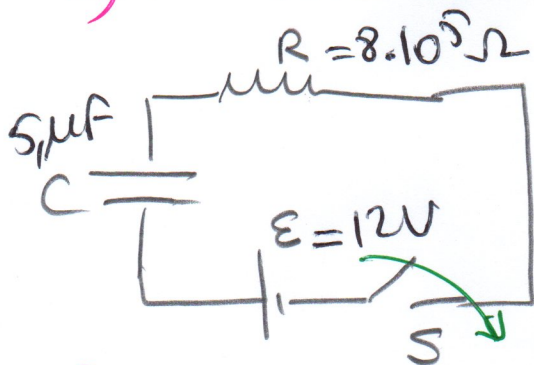

$$\begin{aligned} \text{Time constant} &= \tau = RC \\ \tau &= 8 \cdot 10^5 \cdot 5 \cdot 10^{-6} = 40 \cdot 10^{-1} \\ \tau &= 4 \text{ s} \end{aligned}$$

b) find the maximum charge on the capacitor. When the capacitor is fully charged, $I = 0$

$$\mathcal{E} - IR - \frac{q}{C} = 0$$

$$\mathcal{E} = \frac{Q_{\text{max}}}{C} \Rightarrow Q_{\text{max}} = \mathcal{E}C = 12 \cdot 5 \cdot 10^{-6} \\ Q_{\text{max}} = 60 \mu\text{C}$$

c) find the maximum current in the circuit. (4)

When $I = I_{\max}$ $q = 0$ ($\Delta V_C = 0$) (just after closing switch S)

$$\mathcal{E} - IR - \frac{q}{C} = 0$$

$$\mathcal{E} = I_{\max} R \rightarrow I_{\max} = \frac{\mathcal{E}}{R} = \frac{12}{8 \cdot 10^{-5}}$$

$$I_{\max} = 15 \cdot 10^{-6} \text{ A}$$

$$I_{\max} = 15 \mu\text{A}$$

d) find an expression for the charge and current as a function of time.

for charging process $q(t) = Q_{\max} [1 - e^{-t/RC}]$

$$q(t) = 60 \cdot 10^{-6} [1 - e^{-t/4}] \text{ (C)}$$

$$I = I_{\max} e^{-t/RC}$$

$$I = 15 \cdot 10^{-6} e^{-t/4} \text{ (A)}$$

e) find the ratio of the charge on the capacitor at $t = 18 \text{ s}$ to the final charge on it.

final charge at the end of charging process must be $Q_{\max}$.

$\frac{q(t=18 \text{ s})}{Q_{\max}} \rightarrow$ we will find this ratio.

$$q(t) = Q_{\max} [1 - e^{-t/\tau}]$$

when $t = 18 \text{ s}$, the 98.8% of the capacitor is charged!

$$\frac{q(t=18 \text{ s})}{Q_{\max}} = 1 - e^{-18/4} = 1 - 0.011 = \underline{\underline{0.988}}$$

(5)

3) A capacitor C discharges through a resistor R

a) after how many time constants does its charge fall to one-half its initial value?

$$q = q_{\max} e^{-t/RC} \quad \text{for discharging process}$$

$$\downarrow$$

$$\frac{q_{\max}}{2} = q_{\max} e^{-t/\tau}$$

$$\frac{1}{2} = e^{-t/\tau} \Rightarrow \ln\left(\frac{1}{2}\right) = -\frac{t}{\tau}$$

$$t = -\tau \ln\left(\frac{1}{2}\right) = \underbrace{0.69}_{-0.69} \tau$$

b) After how many time constants does the stored energy drop to half its initial energy?

At the beginning of the discharging process $U = U_{\max}$

$$U = U_{\max} = \frac{1}{2} \frac{q_{\max}^2}{C}$$

for any t during the discharging process q decreases.

$$U = \frac{1}{2} \frac{q(t)^2}{C} = \frac{1}{2} \frac{[q_{\max} e^{-t/\tau}]^2}{C}$$

$$U = \left(\frac{1}{2} \frac{q_{\max}^2}{C} \right) e^{-2t/\tau} = U_{\max} e^{-2t/\tau}$$

↑
the energy
stored on the capacitor
during discharging process

$$U = \frac{U_{\max}}{2} = U_{\max} e^{-2t/\tau}$$

$$\frac{1}{2} = e^{-2t/\tau}$$

$$t = -\frac{\tau}{2} \ln\left(\frac{1}{2}\right) = \underline{0.35\tau}$$

c) After how many time constants, does the current (6) in the RC circuit fall to one-half its initial current.

$$I = I_{\max} e^{-t/\tau}$$


$$\frac{I_{\max}}{2} = I_{\max} e^{-t/\tau}$$

$$\frac{1}{2} = e^{-t/\tau}$$

$$t = -\tau \ln\left(\frac{1}{2}\right)$$

$$t = 0.69\tau$$

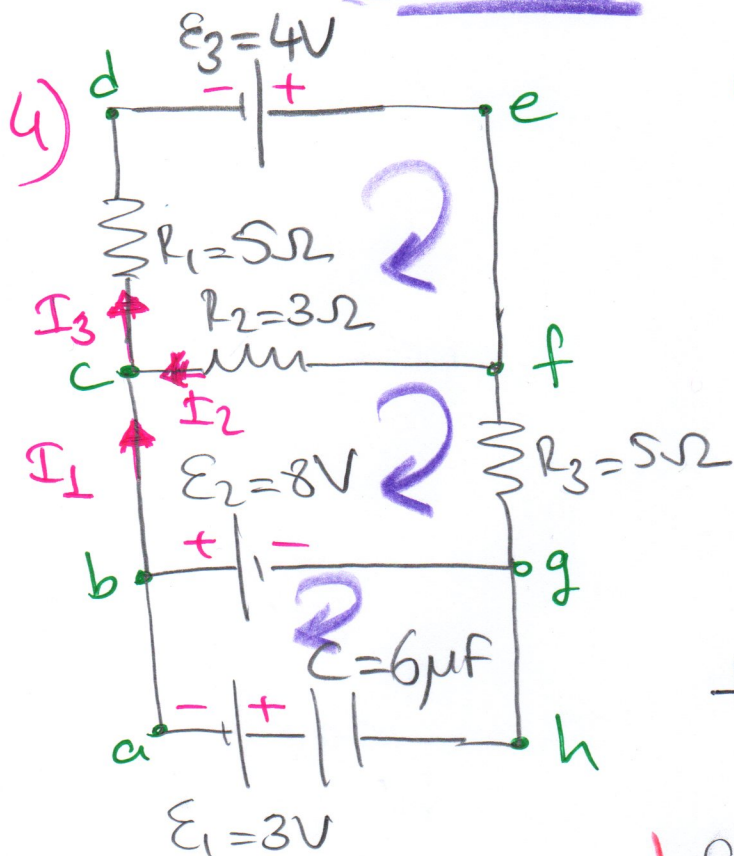When we want to find a particular time to decrease the current, we choose the absolute value of this equation. Because negative sign corresponds to the direction of the current!



a) find the steady currents of I_1 , I_2 , and I_3 when the circuit is running for a long time.

When the circuit is running for a long time, the capacitor is fully charged. So that there will be no current flowing through ah path.

$$\text{for ah branch } I = 0$$

for junction c $\sum I_{\text{in}} = \sum I_{\text{out}}$

$$I_1 + I_2 = I_3 \quad (1)$$

for bcfgb loop $\sum \Delta V = 0 \rightarrow +I_2 R_2 - I_1 R_3 + E_2 = 0$

$$3I_2 - 5I_1 = -8 \quad (2)$$

for cdefc loop $\Sigma \Delta V = -I_3 R_1 + \mathcal{E}_3 - I_2 R_2 = 0$ (7)

$$-5I_3 - 3I_2 = -4$$

$$5I_3 + 3I_2 = 4 \quad (3)$$

By using Eqs. (1), (2), and (3), we can find

$$I_1 = 1.38 \text{ A} \quad I_2 = -0.364 \text{ A} \quad I_3 = 1.02 \text{ A}$$

b) find the charge on the capacitor.

the charge on the capacitor can be calculated

by using $C = \frac{Q}{\Delta V_c} \Rightarrow Q = C \Delta V_c$

the electric potential difference between the capacitor's plate.

We can determine ΔV_c by writing 2nd Kirchhoff's rule for the closed loop of abgha.


for abgha loop $\Sigma \Delta V = 0$

$$-\mathcal{E}_2 + \Delta V_c - 3 = 0$$

$$\Delta V_c = 3 + 8 = 11 \text{ V}$$

$$Q = Q_{\text{max}} = 6 \cdot 10^{-6} \cdot 11 = 66 \mu\text{C}$$

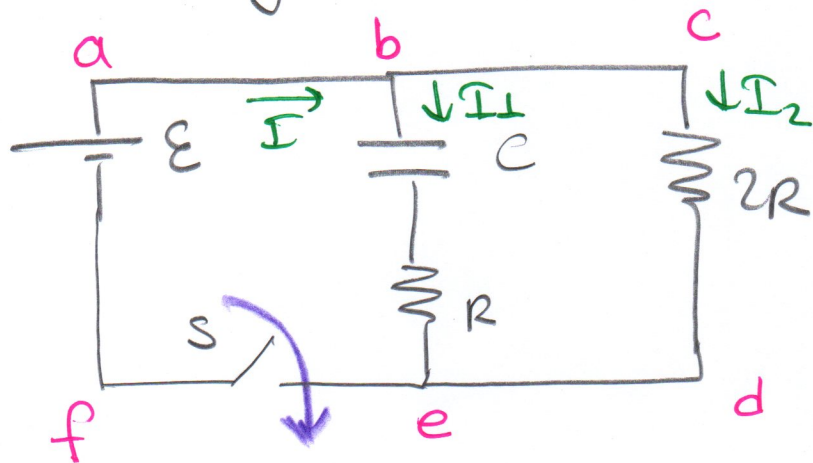5) In a circuit given below, the capacitor is uncharged. The switch S is closed at $t=0$.



a) Find an expression for current I as a function of time and draw $I=f(t)$ graph when the capacitor is charging.

As you know, when the switch S is closed, the battery is connected to the circuit so that the capacitor starts to charge. During this process,

for junction b $I = I_1 + I_2$


for $a c d f a$ loop $\sum \Delta V = -I_2 2R + \varepsilon = 0$

$$I_2 = \frac{\varepsilon}{2R}$$

We have already learned the charge in the electric current on the branch at which the capacitor is located :

$$I_1 = I_{\text{max}} e^{-t/\tau}$$

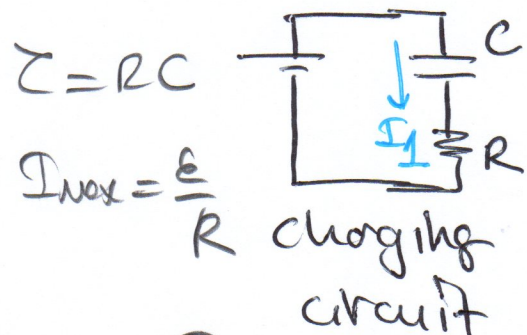
$$I_1 = \frac{\varepsilon}{R} e^{-t/RC}$$



Hence $I = I_1 + I_2 = \frac{\varepsilon}{R} e^{-t/RC} + \frac{\varepsilon}{2R}$

for $t=0$ $I = \frac{\varepsilon}{R} + \frac{\varepsilon}{2R} = \frac{3\varepsilon}{2R}$

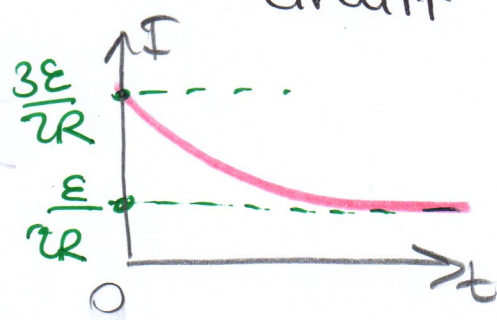
for $t \rightarrow \infty$ $I = \frac{\varepsilon}{2R}$



9

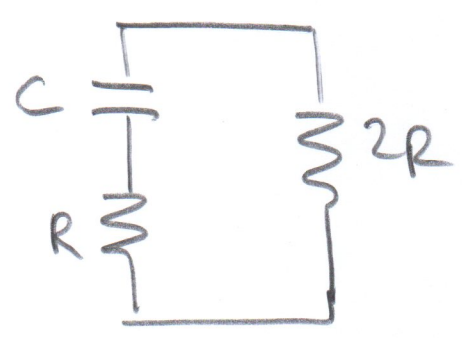b) After the circuit becomes a steady-state, the switch S is opened. Find the time required for the charge on the capacitor to fall one-half its initial value.

When the switch S is opened, the circuit becomes a **discharging circuit**. Let's draw the remaining circuit.



For the discharging circuit

$$\tau = R_{eq} C_{eq} = 3RC$$

$$R_{eq} = R + 2R = 3R$$

these resistors are connected in series!

for the discharging circuit

$$q(t) = Q_{max} e^{-t/\tau} = Q_{max} e^{-t/3RC}$$

for the question $q(t) = \frac{Q_{max}}{2}$

$$\frac{Q_{max}}{2} = Q_{max} e^{-t/3RC}$$

$$\frac{1}{2} = e^{-t/3RC}$$

$$\ln\left(\frac{1}{2}\right) = -\frac{t}{3RC} \Rightarrow t = -3RC \ln\left(\frac{1}{2}\right)$$


$$t = -3RC (-0.69)$$

$$t = 2.07 RC$$

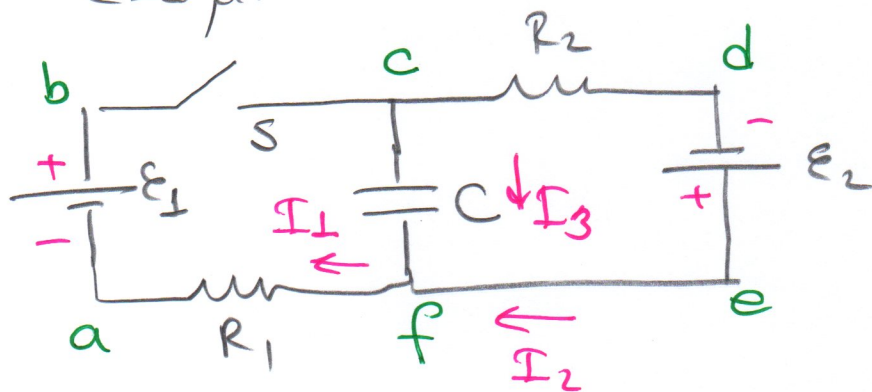6) Midterm Question!

The switch S in the circuit is initially open and the capacitor is uncharged.

In here, $\mathcal{E}_1 = 1V$, $\mathcal{E}_2 = 3V$, $R_1 = 0,2\Omega$, $R_2 = 0,3\Omega$, and $C = 5\mu F$



a) Find the currents in the circuit and the charge on the capacitor after a longtime while S is still open.

When S is opened for a long time there will be no current on each branch, and the capacitor is charged fully through $\mathcal{E}_2$ battery.

$I_1 = 0$ $\rightarrow$ since S is open

$I_3 = 0$ $\rightarrow$ the capacitor is fully charged.

$I_2 = 0$ $\rightarrow$ since the other currents are zero.


$$Q_{\max} = C \Delta V_c = C \Delta V_{cf} = C \Delta V_{de} = C \mathcal{E}_2$$

$$Q_{\max} = 5 \cdot 10^{-6} \cdot 3 = \underline{15 \mu C}$$

b) Now, the switch S is closed, Find the currents and the charge on the capacitor after a longtime after S is closed.

Again the capacitor is charged fully. ($I_3 = 0$)

So that $c f$ branch is open circuit.

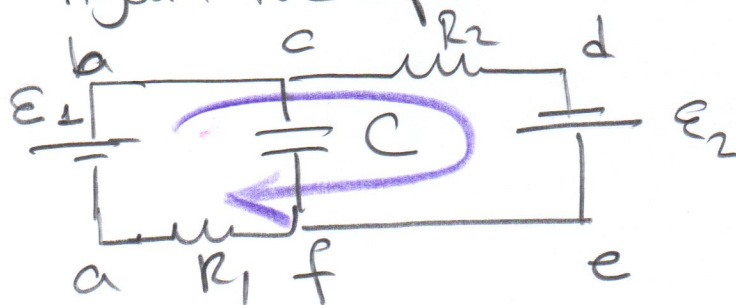

for $a b d e a$ loop

$$\mathcal{E}_1 + \mathcal{E}_2 - I(R_1 + R_2) = 0$$

$$I = \frac{\mathcal{E}_1 + \mathcal{E}_2}{R_1 + R_2} = \frac{1 + 3}{0,2 + 0,3} = \underline{\underline{8A}}$$

(11)

let's find ΔV_C to calculate the charge on the capacitor.

for abcfa loop $\mathcal{E}_1 + \Delta V_C - IR_1 = 0$

$$1 + \Delta V_C - 8 \cdot (0,2) = 0$$

$$\Delta V_C = 1,6 - 1 = 0,6V$$

or for edefc loop $-IR_2 + \mathcal{E}_2 + \Delta V_C = 0$

$$\Delta V_C = 8 \cdot 0,3 - 3$$

$$|\Delta V_C| = 0,6V$$

$$Q = C \Delta V_C = 5 \cdot 10^{-6} \cdot 0,6$$


$$Q = \underline{\underline{3\mu C}}$$

c) find powers supplied by the batteries and consumed across the resistors after switch S is closed for a long time.

$$\left. \begin{aligned} P_{R_1} &= I^2 R_1 = 8^2 \cdot 0,2 = 12,8W \\ P_{R_2} &= I^2 R_2 = 8^2 \cdot 0,3 = 19,2W \end{aligned} \right\} \Sigma P_{\text{consumed}} = \underline{\underline{32W}}$$

$$\left. \begin{aligned} P_{\mathcal{E}_1} &= I \mathcal{E}_1 = 8 \cdot 1 = 8W \\ P_{\mathcal{E}_2} &= I \mathcal{E}_2 = 8 \cdot 3 = 24W \end{aligned} \right\} \Sigma P_{\text{supplied}} = \underline{\underline{32W}}$$

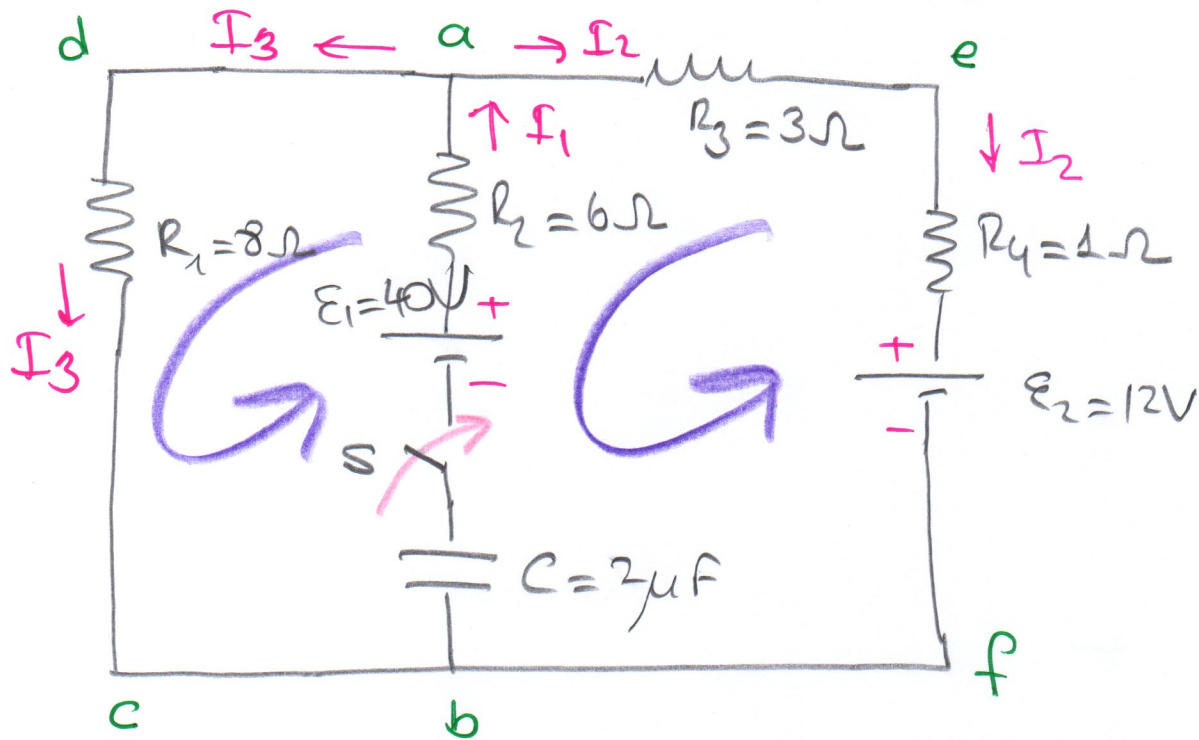7) Initially the capacitor is uncharged in the circuit. (12)
and switch S is closed at $t=0$.



a) find the currents of I_1 , I_2 , and I_3 just after the switch S is closed.

Just after the closing of the switch S , there will be no charge on the capacitor, hence $\Delta V_C = 0$

1st Kirchhoff's rule for junction a : $\sum I_{in} = \sum I_{out}$

$$\textcircled{1} \quad I_1 = I_2 + I_3$$

2nd Kirchhoff's rule

for $adcba$ loop $\sum \Delta V = 0$

$$-I_3 R_1 + E_1 - I_1 R_2 = 0$$

$$-8I_3 + 40 - 6I_1 = 0$$

$$6I_1 + 8I_3 = 40 \quad \textcircled{2}$$

for $abfea$ loop $\sum \Delta V = I_1 R_2 - E_1 + E_2 + I_2 (R_4 + R_3) = 0$


$$6I_1 + 4I_2 = 28 \quad \textcircled{3}$$

By using Eqs. (1), (2), and (3)

13

$$I_1 \approx 3.7A \quad I_2 \approx 2.2A \quad \text{and} \quad I_3 \approx 1.5A$$

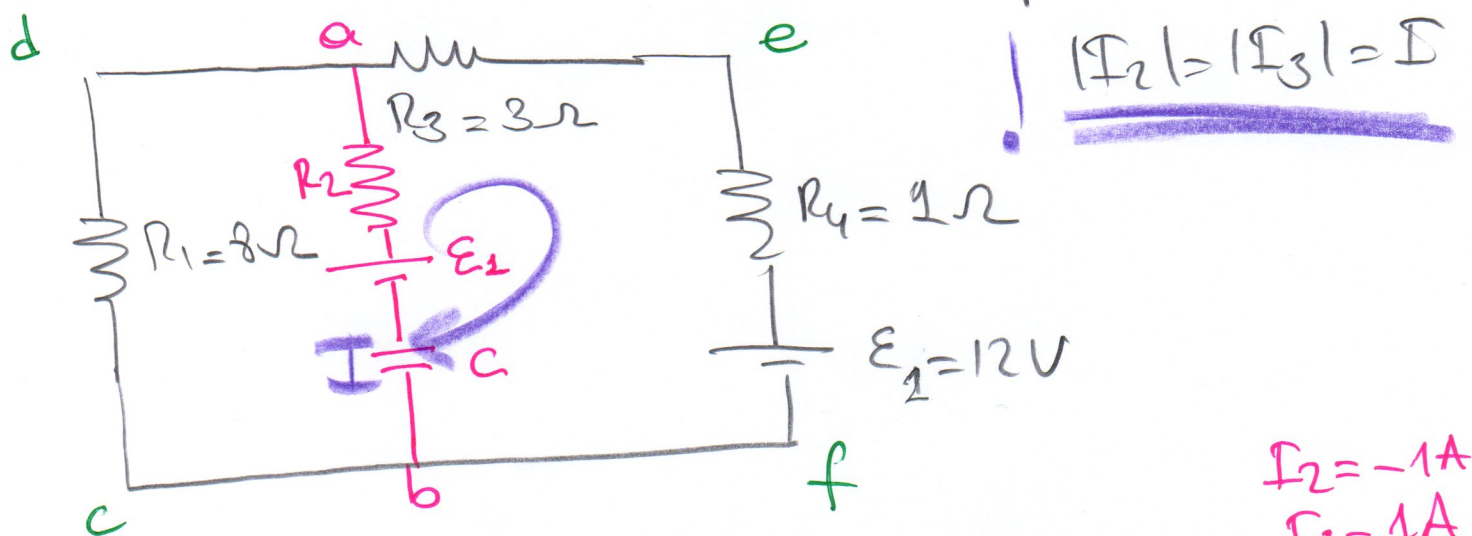- b) find the currents of I_1 , I_2 , and I_3 after for a long time after the switch S was closed.
 when the switch S was closed for a long time, since the capacitor is fully charged, there will be no current on the ab branch. Due to this reason;
 $I_1 = 0$ hence $I_1 = I_2 + I_3 \Rightarrow I_2 = -I_3$
 and the circuit becomes one loop circuit



for $cdefc$ closed loop $\sum \Delta V = 0$

$$-IR_1 - IR_3 - IR_4 - E_1 = 0$$

$$I(R_1 + R_3 + R_4) = E_1 \Rightarrow I = \frac{12}{8+3+1} = 1A$$

- c) find the electric potential difference between points a and b for a long time after switch S was closed for a long time.

$$V_a - E_1$$

By using a d c b path, I can write $V_a - V_b$. (14)

$$V_a + I R_1 = V_b \Rightarrow V_a - V_b = -I R_1 = -(-1) \cdot 8$$

$$V_a - V_b = 8(V)$$


By using a e f b path $V_a - I_2 R_3 - I_2 R_4 - \mathcal{E}_2 = V_b$

$$V_a - V_b = 12 + I_2 (R_3 + R_4) \\ = 12 + (-1) [3 + 1] = \underline{\underline{8V}}$$

At this moment we cannot use a b path for writing $V_a - V_b$, because we don't know the electric potential between the capacitor's plate

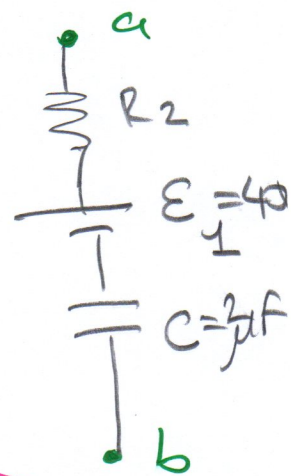d) find the charge on the capacitor after the switch S was closed for a long time.

$\Downarrow$
the capacitor is fully charged
there is no current on the a b
branch



$$V_a - \mathcal{E}_1 + \Delta V_C = V_b$$

$$\underline{V_a - V_b = \mathcal{E}_1 - \Delta V_C}$$

$$8 = 40 - \Delta V_C$$

$$\underline{\Delta V_C = 32V}$$


$$Q_{\max} = C \Delta V_C$$

$$\underline{Q_{\max} = 2 \cdot 10^{-6} \cdot 32 = 64 \mu C}$$

we found 8V in the part (c)

we don't write any electric potential difference for the R_2 resistor, since there is no current on the a b branch!

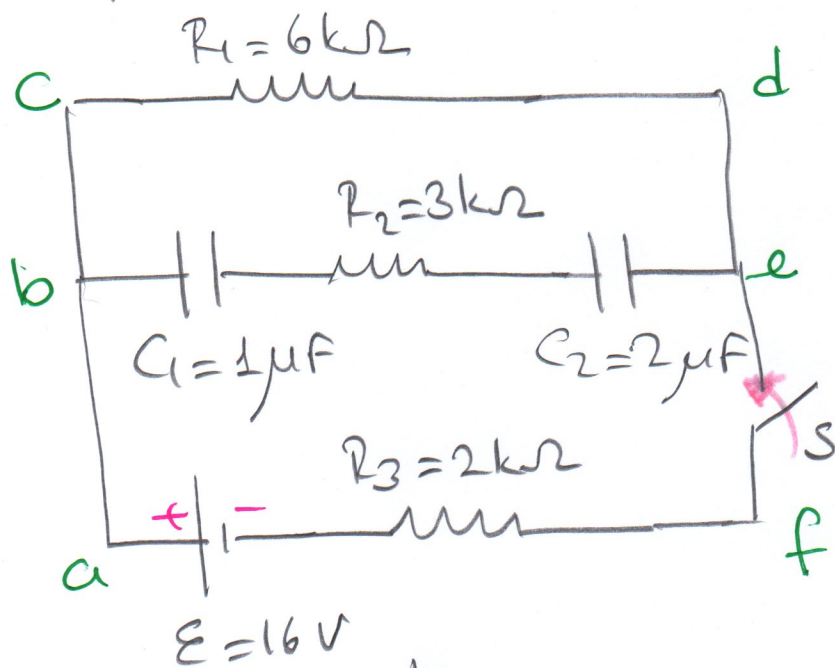
8) a) For the circuit given below find the electric currents across each resistors for a long time after switch S was closed. (15)



When the circuit is run for a long time after closing the switch S

capacitors are fully charged

no current flow on the be branch.

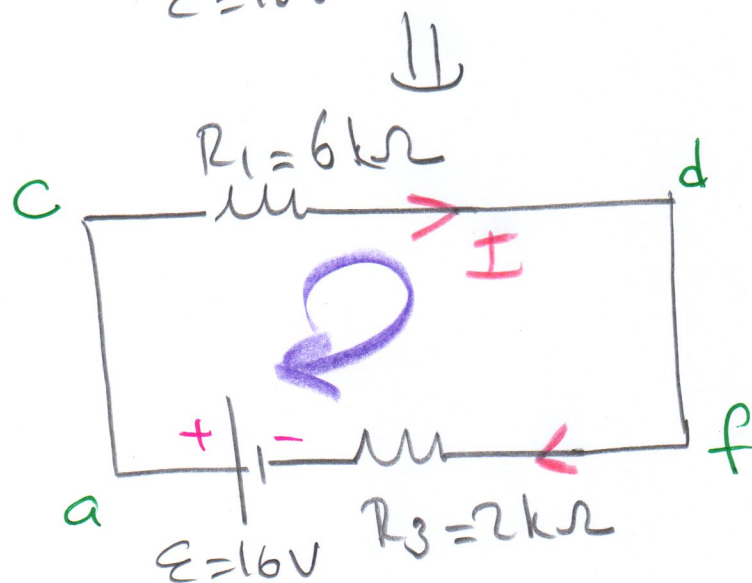

Hence, the circuit becomes one loop circuit

for acdfa closed loop

$$\sum \Delta V = -I(R_1 + R_3) + \varepsilon = 0$$

$$-I(6+2) \cdot 10^3 = -16$$

$$I = 2 \cdot 10^{-3} \text{ A}$$


$$I_{R_2} = 0, I_{R_1} = I_{R_3} = 2 \text{ mA}$$

$$I = 2 \text{ mA}$$

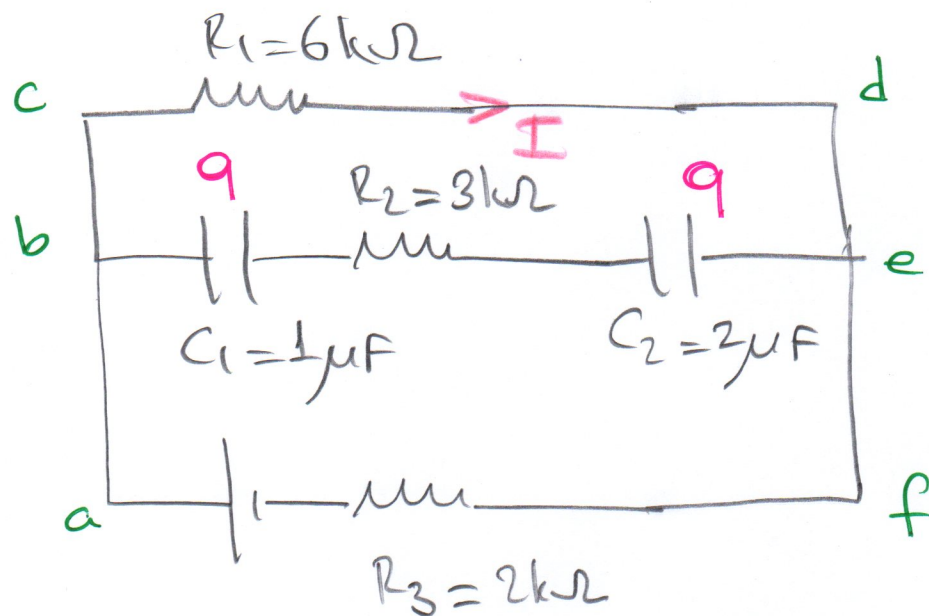b) find the each capacitor's charge and the power consumed on R_2 .

C_1 and C_2 capacitors are connected in series,

So their charges are the same $\Rightarrow q_1 = q_2 = q$



$$I_{be} = 0$$

for bcdeb loop $\sum \Delta V = 0$

$$-IR_1 + \Delta V_C + \Delta V_R = 0$$

$$-2 \cdot 10^{-3} \cdot 6 \cdot 10^3 + \frac{q}{C_2} + \frac{q}{C_1} = 0$$

$$-12 + q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = 0 \Rightarrow -12 + q \left[\frac{(1+2) \cdot 10^{-6}}{1 \cdot 2 \cdot 10^{-12}} \right] = 0$$

$$\frac{C_1 + C_2}{C_1 \cdot C_2}$$

$$12 = \frac{3q \cdot 10^{-6}}{2 \cdot 10^{-12}}$$


$$\frac{24}{3} 10^{-6} = q$$

$$q = 8 \cdot 10^{-6} \text{ C}$$

$$\underline{\underline{q = 8 \mu\text{C}}}$$

* $P_{R_2} = 0$; because there is no current flowing through R_2 resistor
 $(P = I^2 R)$

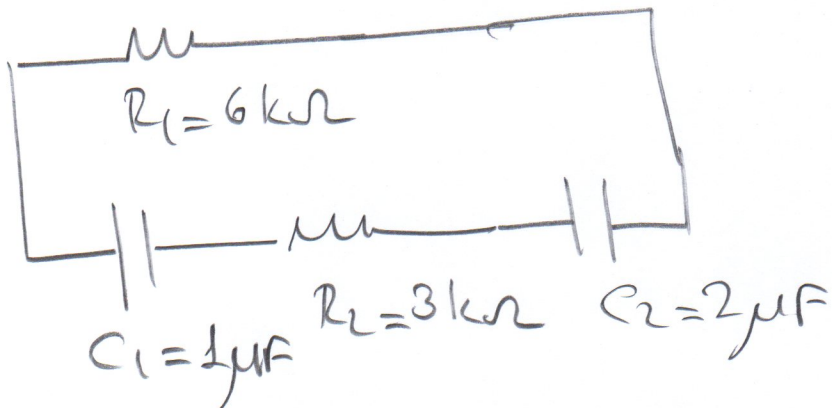- c) find the time constant of the discharging circuit when switch S is opened. (17)
- Let's draw the remaining circuit when the switch S is opened



$$\tau = R_{eq} C_{eq}$$

$$R_{eq} = R_1 + R_2$$

$$R_{eq} = (6+3) 10^3$$

$$R_{eq} = 9 \cdot 10^3 \Omega$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{1 \cdot 2}{1+2} = \frac{2}{3} \mu F = \frac{2}{3} \cdot 10^{-6} F$$

$$\tau = 9 \cdot 10^3 \cdot \frac{2}{3} \cdot 10^{-6} = 6 \cdot 10^{-3} (s) \quad \tau = 6 \text{ ms}$$

- d) After the switch S is opened, obtain an expression for the current on R_1 as a function of time.

For the discharging circuit $I = -I_{max} e^{-t/\tau}$

$$I_{max} = \frac{Q_{max}}{\tau} = \frac{8 \cdot 10^{-6}}{6 \cdot 10^{-3}} = \frac{4}{3} \cdot 10^{-3} (A)$$


$$I = \frac{4}{3} \cdot 10^{-3} e^{-t/6 \cdot 10^{-3}} = \frac{4}{3} \cdot 10^{-3} e^{-1000t/6} (A)$$

$$q = Q_{max} e^{-t/\tau}$$

$$I = \frac{dq}{dt} = -\frac{Q_{max}}{\tau} e^{-t/\tau} = -I_{max} \cdot e^{-t/\tau}$$

g) Initially the capacitor given in the figure is uncharged. The switch S is closed at $t=0$.

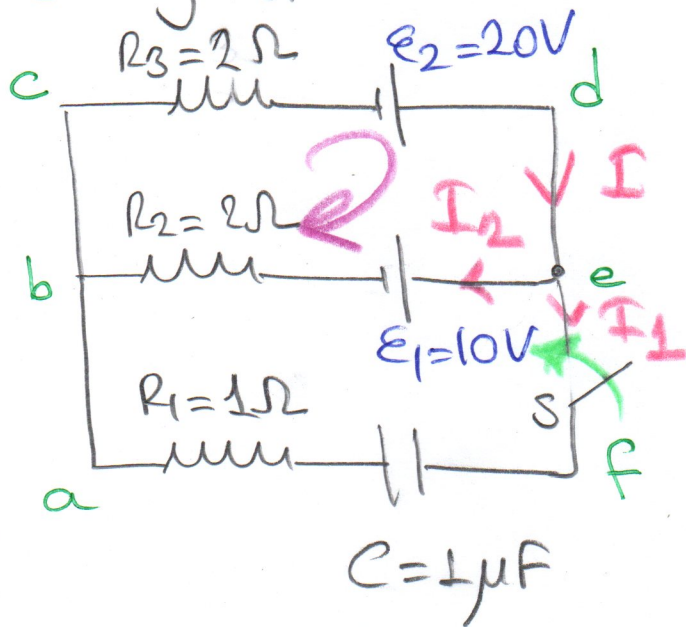a) Find I , I_1 , and I_2 when the circuit becomes steady state.



Steady state of the circuit corresponds to a fully charged capacitor. When the switch S is closed for a long time, the capacitor becomes fully charged and $I_1 = 0$

Junction Rule $\sum I_{in} = \sum I_{out}$ $I = \cancel{I_1} + I_2$ $I = I_2$

Loop Rule for bcdeb closed loop $\sum \Delta V = 0$

$$-IR_3 + E_2 - E_1 - I_2 R_2 = 0$$

$$\downarrow$$

$$I_2 = I$$

$$-I(R_2 + R_3) + E_2 - E_1 = 0$$

$$-I(2+2) + 20 - 10 = 0 \Rightarrow \underline{I = 2.5A}$$

$$\underline{I_1 = 0 \quad I_2 = 2.5A \quad I = 2.5A}$$

b) For the steady state find the charge on the capacitor and electrostatic potential energy stored in the capacitor.

For the closed abefa loop:

$$\sum \Delta V = 0$$

$$+I_2 R_2 + \mathcal{E}_1 + \Delta V_C = 0$$

$$\Delta V_{R_1} = 0 \quad (\text{because } I_1 = 0)$$

$$(2.5 \times 2) + 10 + \Delta V_C = 0$$

$$\Delta V_C = -15V \quad |\Delta V_C| = 15V$$

$$C = \frac{Q}{|\Delta V_C|} \Rightarrow Q = C |\Delta V_C| = 4 \cdot 10^{-6} \times 15 = 15 \mu C$$

$$U = \frac{Q^2}{2C} = \frac{(15 \cdot 10^{-6})^2}{2 \times 4 \cdot 10^{-6}} = 112.5 \cdot 10^{-6} \text{ Joule}$$

c) After closing switch S , find the I_1 current as a function of time while the capacitor is charging.

for the bcdeb closed loop $\sum \Delta V = 0$

$$-I R_3 + \mathcal{E}_2 - \mathcal{E}_1 - I_2 R_2 = 0$$

$$I = I_1 + I_2$$

$$(I_1 + I_2)$$

$$-(I_1 + I_2) \cdot 2 + 20 - 10 - I_2 \cdot 2 = 0$$

$$-2I_2 - 2I_1 - 2I_2 + 10 = 0$$

$$-4I_2 - 2I_1 = -10$$

$$4I_2 + 2I_1 = 10$$

$$2I_2 = 5 - I_1$$

for abefa closed loop $\sum \Delta V = 0$

$$+I_2 R_2 + \mathcal{E}_1 - \Delta V_C - I_1 R_1 = 0$$

$$\downarrow$$

$$(2I_2) + 10 - \Delta V_C - I_1 = 0$$

$$\downarrow$$

$$(5 - I_1) + 10 - \frac{q}{C} - I_1 = 0$$

$$15 - 2I_1 - \frac{q}{C} = 0 \Rightarrow I_1 = \frac{dq}{dt}$$

$$2I_1 + \frac{q}{C} = 15$$

$$2 \cdot \frac{dq}{dt} + \frac{q}{C} = 15$$

$$2 \frac{dq}{dt} = 15 - \frac{q}{C} = \frac{15C - q}{C}$$

$$\int_{q=0}^{q=q} \frac{dq}{15C - q} = \int_{t=0}^{t=t} \frac{dt}{2C}$$

$$15C - q = u$$

$$-dq = du$$

$$q=0 \quad u=15C$$

$$q=q \quad u=15C - q$$

$$\int_{15C}^{15C-q} \frac{(-du)}{u} = \frac{1}{2C} t \Rightarrow -\ln u \Big|_{15C}^{15C-q} = \frac{1}{2C} t$$

$$\ln\left(\frac{15C - q}{15C}\right) = -\frac{t}{2C}$$

(21)

$$\frac{15C - q}{15C} = e^{-t/2C}$$

$$15C - q = 15C e^{-t/2C}$$

$$q(t) = 15C (1 - e^{-t/2C})$$

$$I_1 = \frac{dq}{dt} = 15C \left(- \left(-\frac{1}{2C} \right) e^{-t/2C} \right)$$

$$I_1 = 7.5 e^{-t/2C}$$

$$\tau = 2C = 2 \times 1.10^{-6}$$

$$\tau = 2.10^{-6} (s)$$

$$\tau = 2 (\mu s)$$